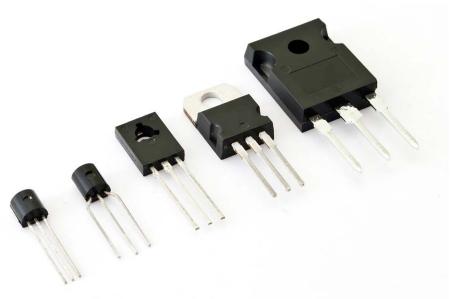


#### Last time: Field-effect transistors


- Introduction
- An overview of field-effect transistors
- Insulated-gate field-effect
- Junction-gate field-effect
- FET characteristics
- FET amplifiers
- Other FET applications
- FET circuit examples



#### **N-channel FET transistors**

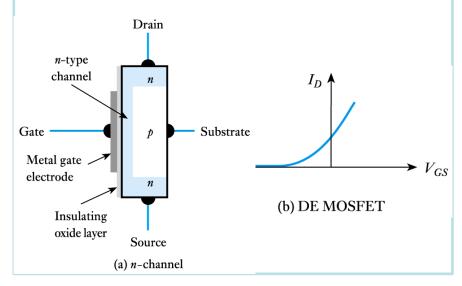
#### **DE-MOSFET**

The more  $V_{GG} < V_{SS} = 0V$  repels electrons from Gate deplete width of n-channel less current flows  $D \rightarrow S$ 


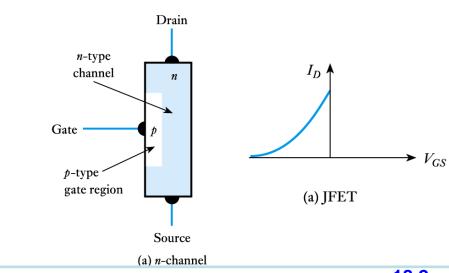
#### **JFET**


The more  $V_{GG} < V_{SS} = 0V$ increase the G-S reverse bias increase width of depletion layer less current flows  $D \rightarrow S$ 



#### **N-channel FET transistors**

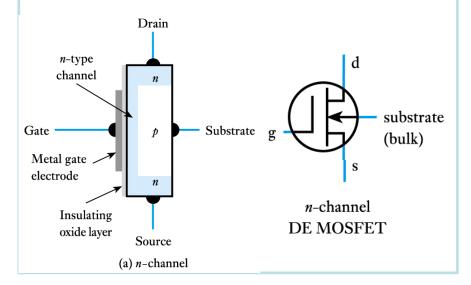
#### **DE-MOSFET**

The more  $V_{GG} < V_{SS} = 0V$  repels electrons from Gate deplete width of n-channel less current flows  $D \rightarrow S$ 




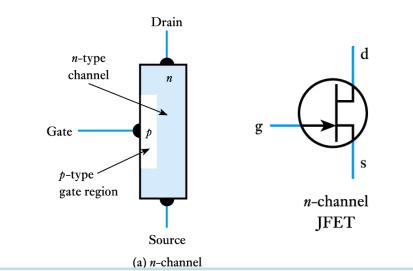
#### **JFET**

The more  $V_{GG} < V_{SS} = 0V$ increase the G-S reverse bias increase width of depletion layer less current flows  $D \rightarrow S$ 




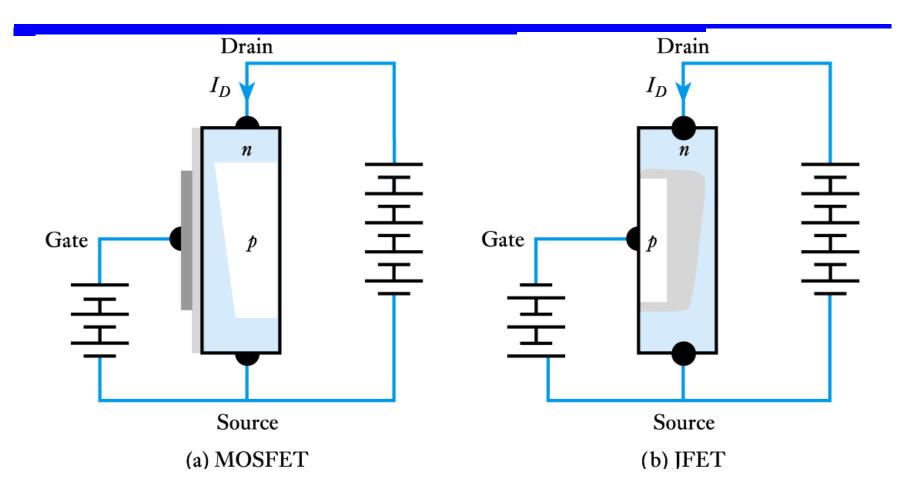Effectively get a bias set up between the potential on the drain and the gate. MOSFET  $V_D > V_G \rightarrow$  depleted channel,  $V_G > V_S \rightarrow$  enhanced channel JFET  $V_{GD} > V_{GS} \rightarrow$  larger reverse bias at drain end $\rightarrow$  larger depletion region Tapers and "pinches off" the channel at high  $V_{DS}$ .



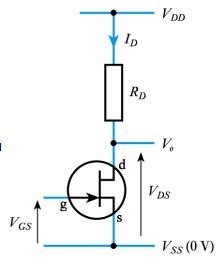


# FET output characteristics

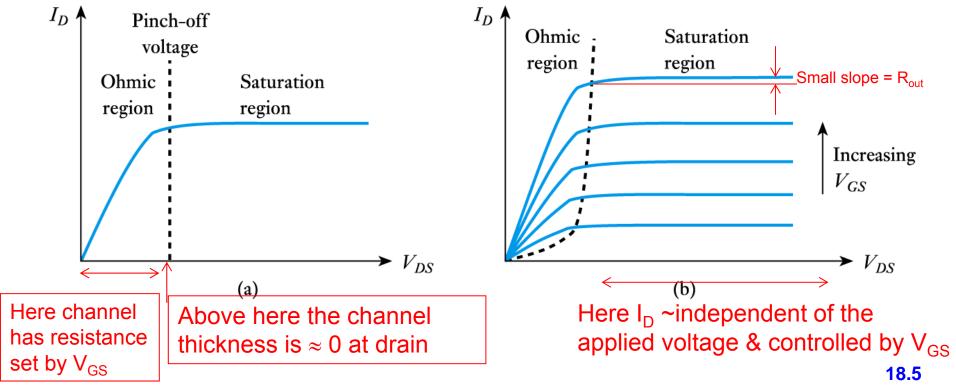

Neil Storey, Electronics: A Systems Approach, 5th Edition © Pearson Education Limited 2013


#### **Gain of device**

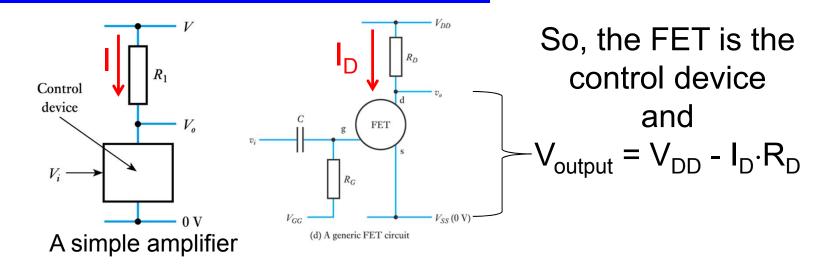

- When  $V_i = V_{GS}$  increases,  $I_D$  increases
- Then most of the voltage, V<sub>DD</sub>, drops across R<sub>D</sub>
  - Thus, Vo gets smaller
- Inverting amplifier
- $V_{GS}$  decreases  $\Rightarrow I_D$  decreases  $\Rightarrow V_o$  increases




# Equivalent circuit of a FET amplifier

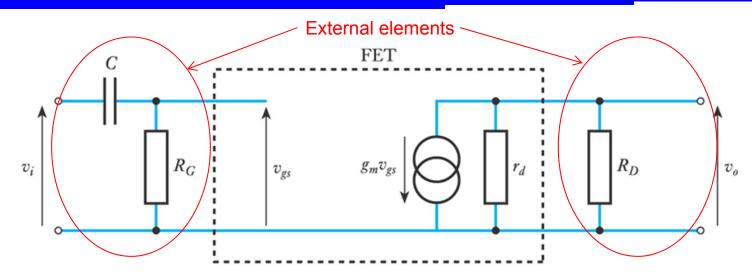

- This circuit can represent any of the FET amplifiers above (by choosing an appropriate value of  $R_G$ )
  - This is a small signal-equivalent circuit
  - Note that  $R_D$  goes to *ground*, since the supply voltage  $V_{DD}$  (and any DC voltage) is a virtual earth point for small signals (small signal  $\Rightarrow$  AC signals)
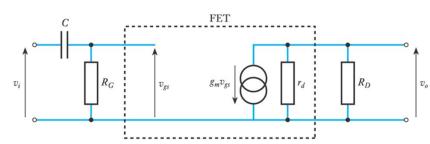
# **Small-signal voltage gain**

 From the equivalent circuit we can derive the small-signal voltage gain




$$\label{eq:vo} \text{V = I*R} \Rightarrow \qquad v_o = -g_m v_{gs} \big( r_d \, / / \, R_D \big) \\ = -g_m v_i \big( r_d \, / / \, R_D \big)$$
 therefore

$$\frac{v_O}{v_i} = -g_m(r_d /\!/ R_D)$$

Also

$$r_i \approx R_G$$
  $r_o \approx r_d // R_D$ 

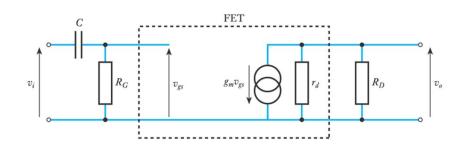- In many cases  $r_d >> R_D$ so  $r_d$  can often be ignored
- If this is the case



voltage gain = 
$$\frac{v_0}{v_i} \approx -g_m R_D$$

$$r_i \approx R_G$$

$$r_0 \approx R_D$$

# **Biasing considerations**

- The biasing arrangement determines the operation of the circuit
  - This is its quiescent state
- The quiescent output voltage v<sub>o(quies)</sub> is given by

$$V_{O(quies)} = V_{DD} - I_{D(quies)}R_{D}$$

 However, since the FET is not linear, determining the quiescent conditions is not straightforward


Normal operating operating range range 
$$I_D$$


Operating  $I_D$ 

Operating


$$\begin{aligned} V_{\text{output}} &= V_{\text{DS}} = V_{\text{DD}} - I_{\text{D}} \cdot R_{\text{D}} \\ & \text{When } I_{\text{D}} = 0 \quad \Rightarrow V_{\text{DS}} = V_{\text{DD}} \\ & \text{When } V_{\text{DS}} = 0 \Rightarrow V_{\text{DD}} = I_{\text{D}} \cdot R_{\text{D}} \end{aligned}$$
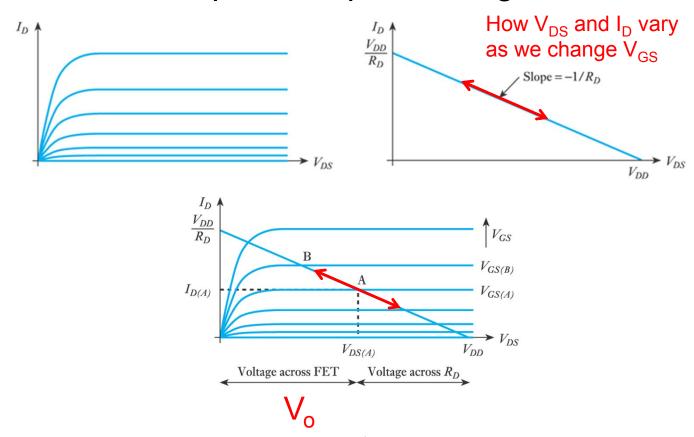
#### Bias to correct operation point using a load line




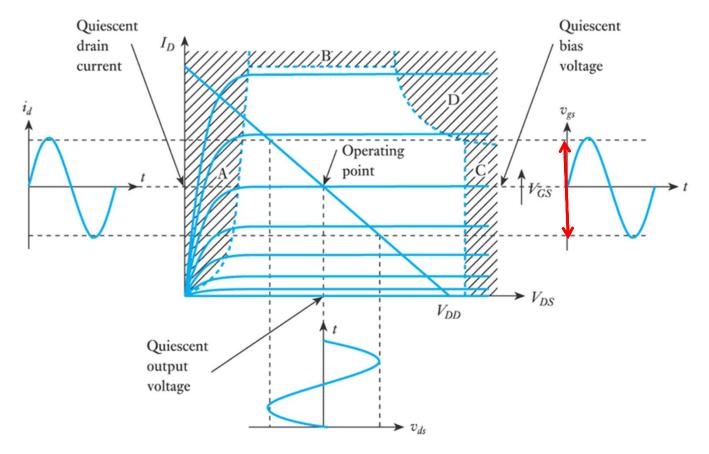


18.12

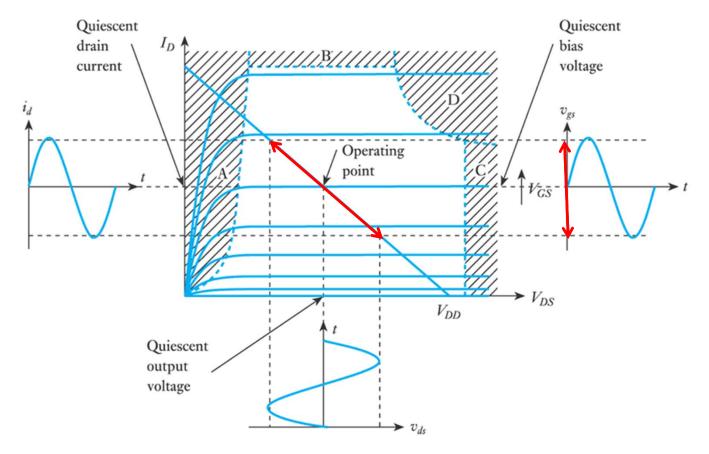

18.13

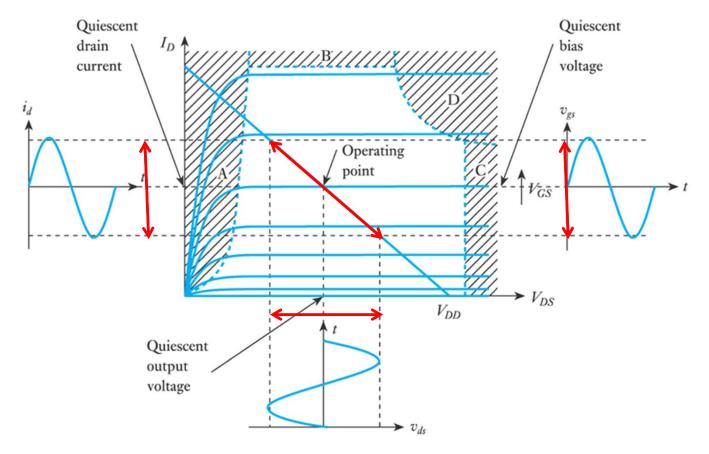


18.14

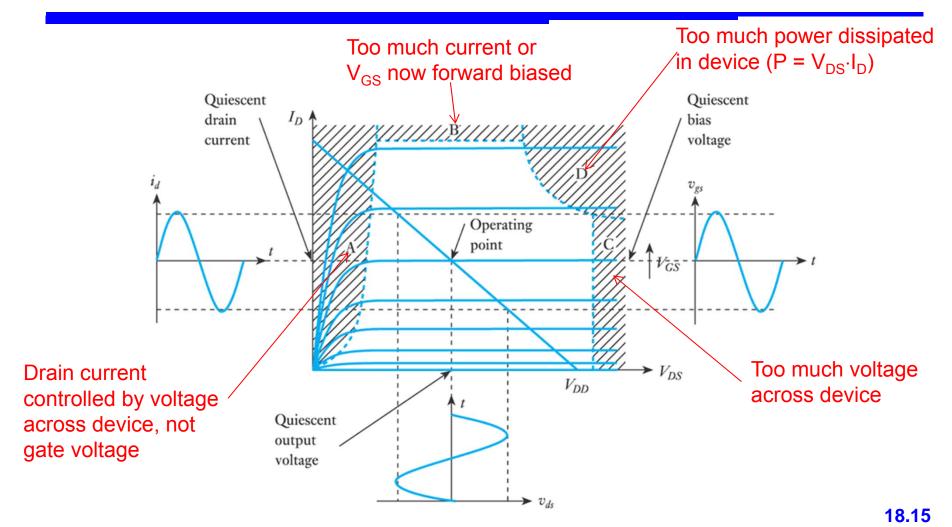

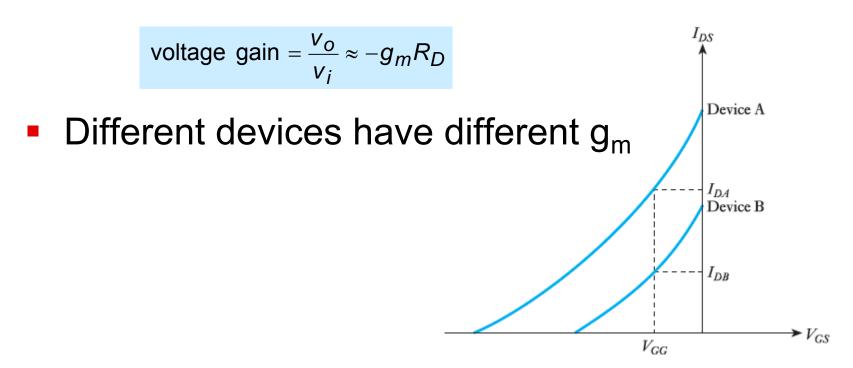
# **Device variability**

FETs, like all active devices, suffer from variability




Get a large spread in quiescent current between A and B

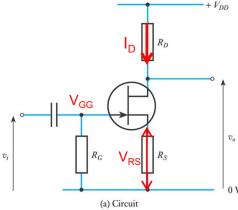
- The effects of device variability on the quiescent conditions of a circuit can be tackled using feedback
  - for example, the use of 'automatic' bias




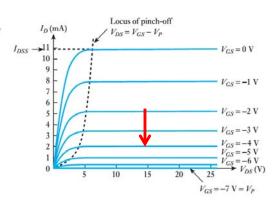 $I_D$  increases  $V_{RS} = I_D \cdot R_S$  increases  $V_{GG}$  the same so  $V_{GS}$  more negative So  $I_D$  decreases



- The effects of device variability on the quiescent conditions of a circuit can be tackled using feedback
  - for example, the use of 'automatic' bias
  - As we change V<sub>GS</sub> we move along the -1/R<sub>S</sub> line when we have feedback
  - Stable, but large loss in gain! (I<sub>D</sub> does not change as much for a change in V<sub>GS</sub>)
  - see Examples 18.3 and 18.4of the course text

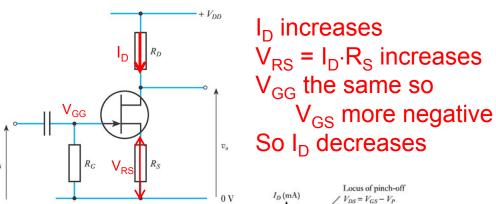


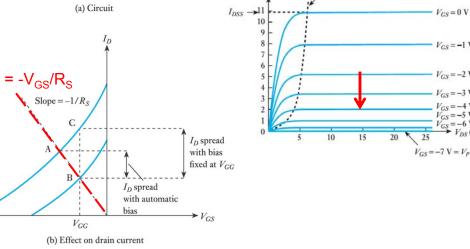


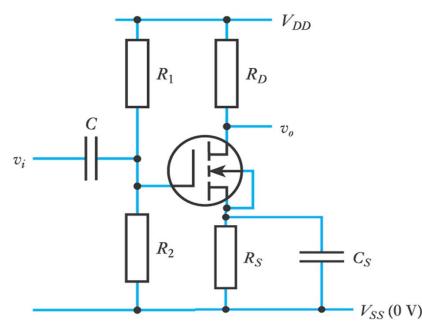
#### A negative feedback amplifier

 Feedback can be used not only to stabilise the biasing conditions of a circuit, but also its <u>(low)</u> voltage gain



voltage gain = 
$$\frac{v_o}{v_i} \approx -\frac{R_D}{R_S}$$


$$r_i \approx R_1 // R_2$$

$$r_0 \approx R_D$$

characteristics set by <u>stable passive components</u>
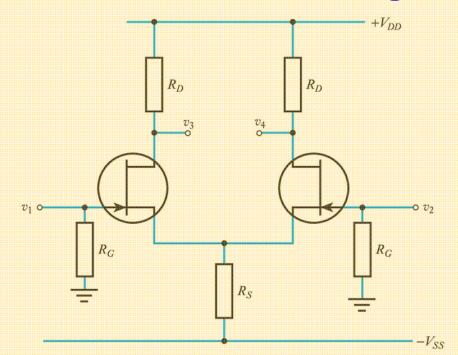
# Differential amplifiers (INFORMATION ONLY)

- A simple differential amplifier using JFETs
  - this is termed a long-tailed pair amplifier




voltage gain = 
$$\frac{v_0}{v_i} = \frac{v_3 - v_4}{v_1 - v_2} \approx -g_m R_D$$


Front end of a FET op-amp
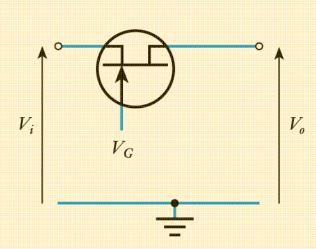
# Analogue/digital switch (INFORMATION ONLY)

A FET as an analogue switch or logical switch



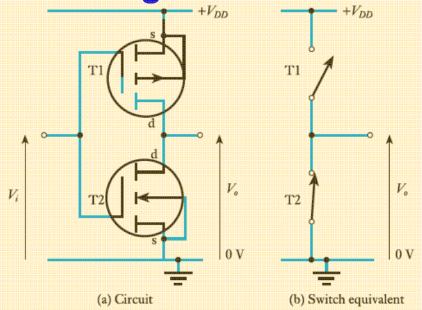 $V_G = 0$ , Device on &  $I_D$  large  $V_G << 0$ , Device off &  $I_D \approx 0$ 



 $V_i$  close to 0,  $T_2$  off,  $T_1$  on &  $V_o \approx V_{DD}$  $V_i$  close to  $V_{DD}$ ,  $T_2$  on,  $T_1$  off &  $V_o \approx 0$ 

**CMOS** logic





## **Further Study**

- The Further Study section at the end of Chapter 18 looks at the use of FETs as switches.
- The problem here is to design an amplifier in which the gain can be set to 1, 10 or 100 by pressing one of three pushbuttons.



 Use the techniques described earlier to produce this arrangement and then watch the video.

#### **Key points**


- FETs are widely used in both analogue and digital circuits
- They have high input resistance and small physical size
- There are two basic forms of FET: MOSFETs and JFETs
- MOSFETs may be divided into DE and Enhancement types
- In each case the gate voltage controls the current from the drain to the source
- The characteristics of the various forms of FET are similar except that they require different bias voltages
- FETs can be used in a range of amplifier configurations
- FETs can be also used to produce other circuit applications


# • Questions?


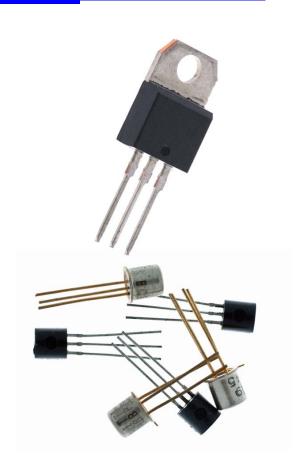
### **Bipolar junction transistors**


- Introduction
- An overview of bipolar transistors
- Bipolar transistor operation
- A simple amplifier
- Bipolar transistor characteristics
- Bipolar amplifier circuits
- Bipolar transistor applications
- Circuit examples



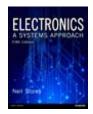
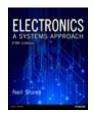
#### Introduction


- Bipolar transistors are one of the main 'building-blocks' in electronic systems
- They are used in both analogue and digital circuits
- They incorporate two pn junctions and are sometimes known as bipolar junction transistors or BJTs
- Here will refer to them simply as bipolar transistors




#### 19.2
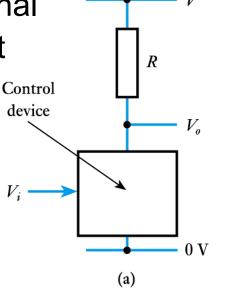
# An overview of bipolar transistors


- While control in a FET is due to an electric field, control in a bipolar transistor is generally considered to be due to an electric current
  - Current into one terminal determines the current between two others
  - As with a FET, a
     bipolar transistor
     can be used as a
     'control device'



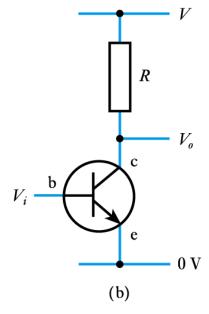
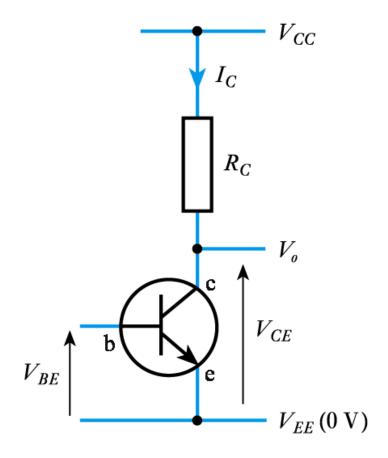
#### Notation


- bipolar transistors are 3 terminal devices
  - collector (c)
  - base (b)
  - emitter (e)
- the base is the control input
- diagram illustrates the notation used for labelling voltages and currents



# Why 2-types of transistors


	Field Effect Transistor (FET)	Bipolar Junction Transistor (BJT)
1	Low voltage gain	High voltage gain
2	High current gain	Low current gain
3	Very high input impedance	Low input impedance
4	High output impedance	Low output impedance
5	Low noise generation	Medium noise generation
6	Fast switching time	Medium switching time
7	Easily damaged by static	Robust
8	Some require an input to turn it "OFF"	Requires zero input to turn it "OFF"
9	Voltage controlled device	Current controlled device
10	Exhibits the properties of a Resistor	
11	More expensive than bipolar	Cheap
12	Difficult to bias	Easy to bias

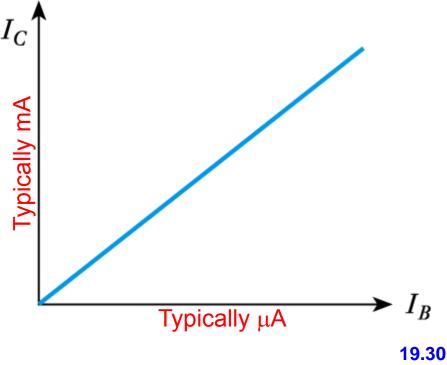
- Relationship between the collector current and the base current in a bipolar transistor
  - characteristic is approximately linear
  - magnitude of collector current is generally many times that of the base current
  - the device provides current gain




#### Construction


two polarities: ₀npn and pnp

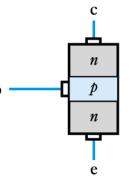


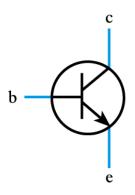


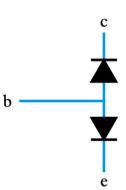


(a) An npn transistor

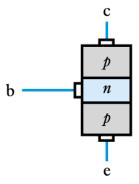

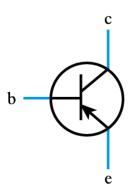

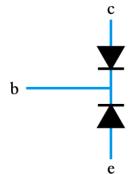


(b) An pnp transistor

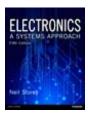
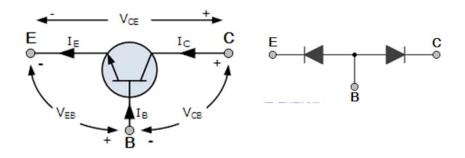
#### **Bipolar transistor operation**


- We will consider npn transistors
  - pnp devices are similar but with different polarities of voltage and currents
  - when using npn transistors
    - collector is normally more positive than the emitter
    - V<sub>CF</sub> might be a few volts
    - device resembles two back-to-back diodes but has very different characteristics
    - with the base open-circuit negligible current flows from the collector to the emitter



- Now consider what happens when a positive voltage is applied to the base (with respect to the emitter)
  - This forward biases the base-emitter junction
  - The base region is lightly doped and very thin
  - Because it is lightly doped, the current produced is mainly electrons flowing from the emitter to the base
  - Because the base region is thin, most of the electrons entering the base get swept across the base-collector junction (by E field there) into the collector
  - This produces a collector current (I in opposite direction of electron motion) that is much larger than the base current this gives current amplification


# NPN ⇒ Not Pointing iN Negative-Positive-Negative = on

#### Transistor action

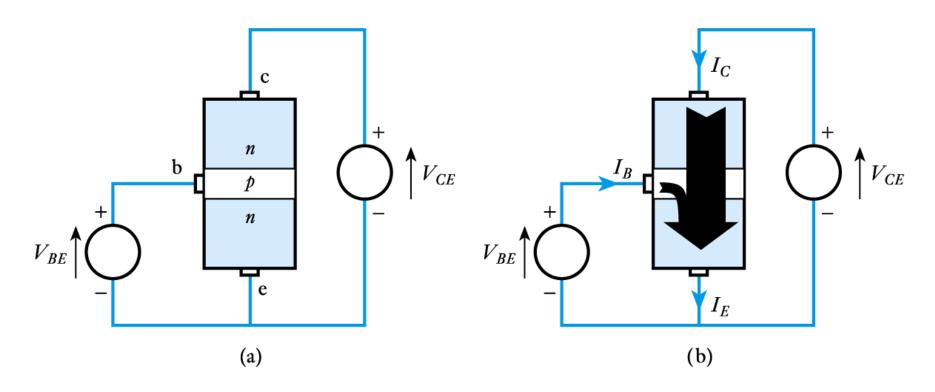




# Set the way-back machine, Sherman

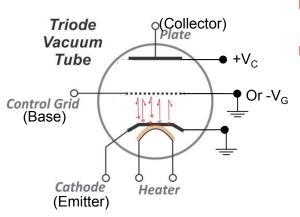
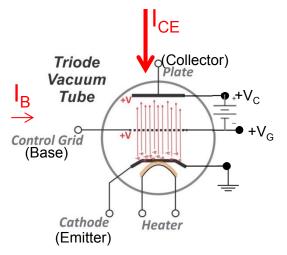
#### A NPN transistor!


- Off state,
  - Electrons emitted but shielded from +V<sub>C</sub> by grid that is at ground or slightly negative –V<sub>G</sub>
  - Only a few make it to collector



#### On state

- Emitted electrons accelerate towards grid at +V<sub>G</sub>
- Most pass through the grid (a few electrons collected)
- Remainder see +V<sub>C</sub> (>V<sub>G</sub>), and accelerate towards it
- Large number of electrons collected at collector.
- Small Base current, large Collector→Emitter current 19.35
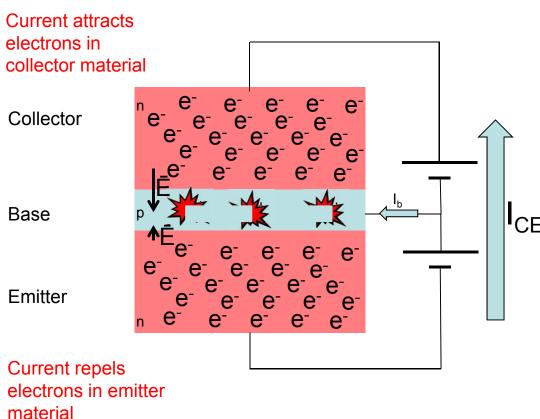
#### **NPN** transistor in "on" bias state



- Bias creates current flow from emitter to collector
- Electrons in collector recombine with holes from battery
- Electrons in emitter get repelled and pushed into base by electrons from battery
- Very few recombine in base. The few that do, create the small base current
- Most get pushed into the depletion region of the base-collector
- There they accelerate through the electric field into the collector
- Get large, continuous I<sub>CF</sub> current


# Is it a current or voltage device? Answer: Yes


- How do I increase I<sub>B</sub>?
- Increase the forward bias (I<sub>B</sub> = I<sub>BS</sub>·e<sup>40·V<sub>BE</sub></sup>)
  - Where I<sub>RS</sub> is a constant for the device
  - This lowers the base-emitter pn-barrier
  - This also makes the depletion region smaller
- More electrons are pushed through barrier
- I<sub>C</sub> increases proportionately with I<sub>B</sub>


Behaviour can be described by the current gain,  $h_{fe}$  or by the transconductance,  $g_m$  of the device

The AC gain of the device  $i_c = h_{fe} \cdot i_b$  (  $I \Rightarrow DC$ ,  $i \Rightarrow AC$ , or  $\triangle I$ )

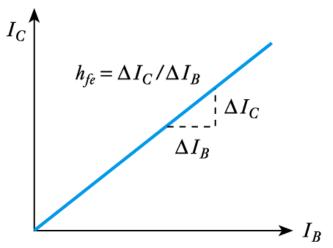Looks like a diode since  $I_C$  is  $\approx$  linear with  $I_B$ ! Note  $g_m$  depends on where device is operated  $(I_C \text{ and } I_E)$ 



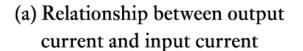

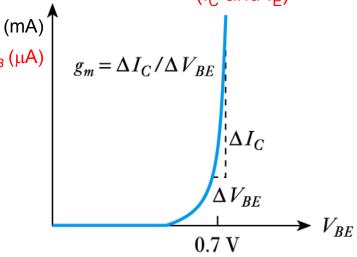

(b) Relationship between output current and input voltage






Video 19A

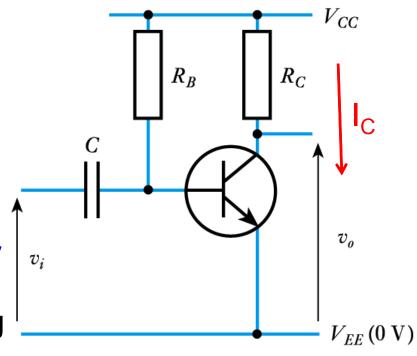
19.4

- A simple amplifier  $(\pm u_i)$
- The circuit shows a simple amplifier
  - R<sub>B</sub> is used to 'bias' the transistor by injecting an appropriate base current
  - Forward biases B-E
  - C is a coupling capacitor and is used to couple the AC signal while preventing external circuits from affecting the bias



Base more +, increase  $I_C$  and more drop across  $R_C \Rightarrow u_0$  decreases (inverting)

This is an AC-coupled amplifier

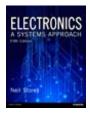


## **Bipolar transistor characteristics**

19.5

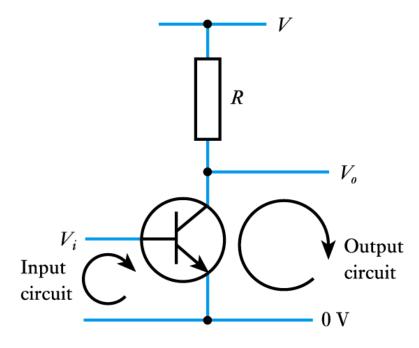
#### Transistor configurations

- Transistors can be used in a number of configurations
- Most common is as shown
- Emitter terminal is common to input and output circuits
- This is a common-emitter configuration
- We will look at the characteristics of the device in this configuration



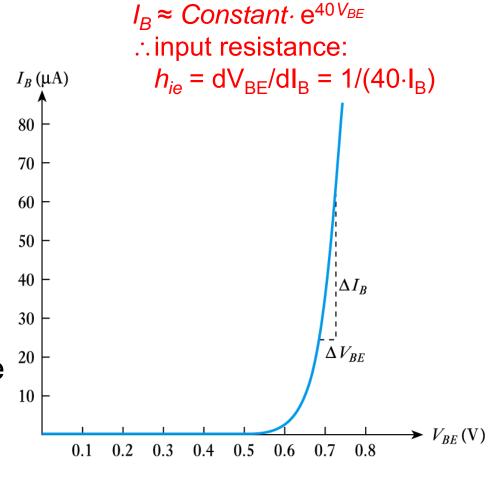
## Input characteristics

- The input takes the form of a forwardbiased pn junction
- The input
   characteristics are
   therefore similar to
   those of a
   semiconductor diode


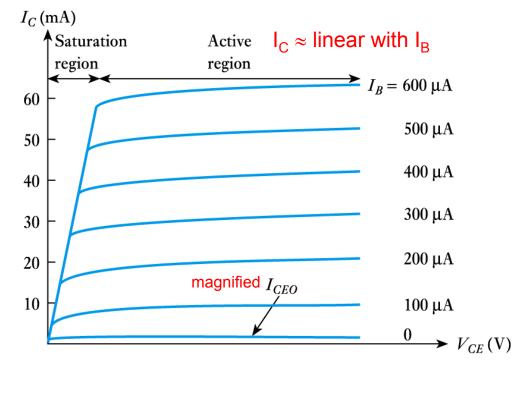
### Output characteristics

- region near to the origin is the saturation region
- this is normally avoided in linear circuits
- slope of lines
   represents the
   output resistance
   (r<sub>o</sub>)





#### Transfer characteristics

- can be described by either the current gain or by the transconductance
- DC current gain  $h_{FE}$  or  $\beta$  is given by  $I_C/I_B$
- AC current gain  $h_{fe}$  is given by  $i_c/i_b$
- transconductance  $g_m$  (=dI<sub>C</sub>/dV<sub>BE</sub>) is given approximately by  $g_m \approx 40 \cdot I_C \approx 40 \cdot I_E$  siemens (Since  $I_C \approx Constant \cdot e^{40V_{BE}}$ )

- the units of  $g_m$  are those of admittance
- therefore  $1/g_m$  has the units of resistance
- the quantity  $1/g_m$  is termed the **emitter** resistance  $r_e$
- therefore  $r_e = \frac{1}{g_m} \approx \frac{1}{40I_C} \approx \frac{1}{40I_E} \Omega$

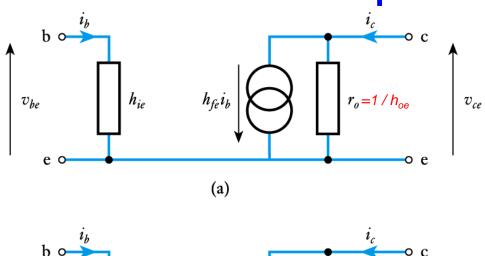Simple equivalent circuits for a bipolar transistor




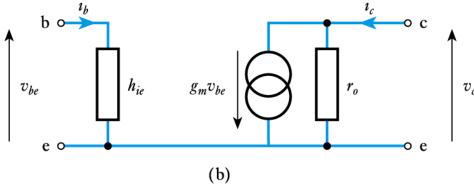


## V<sub>CE</sub> affects the base bias Called the Early effect
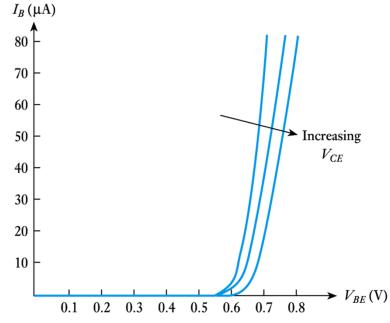
### Limitations of the simple models

- While the simple models shown above give a reasonable representation of the behaviour of devices they do not show the effects of the output voltage on the input (as shown here)
- This can be modelled by the reverse transfer ratio  $h_{re}$





# The hybrid-parameter model

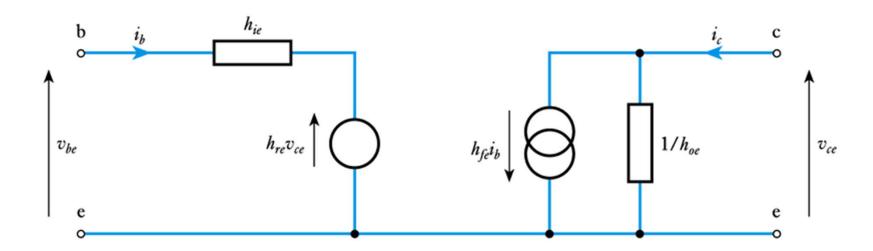

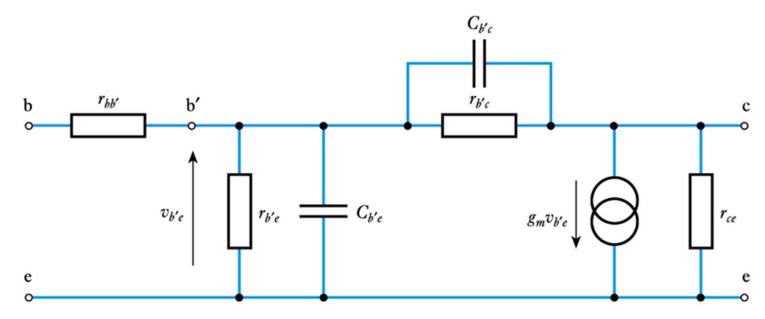
## The hybrid-π model

- gives a better representation at high frequencies



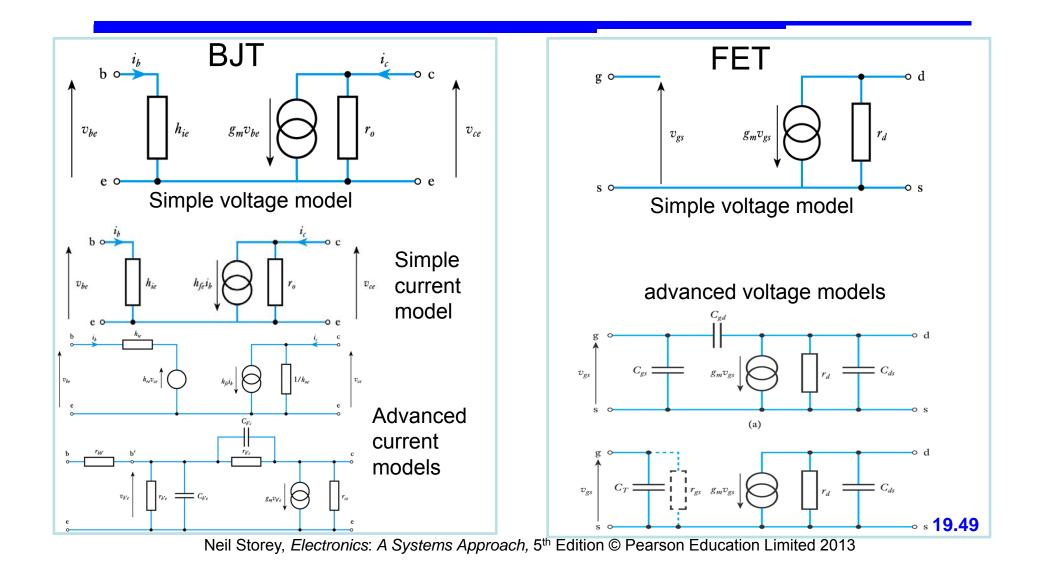

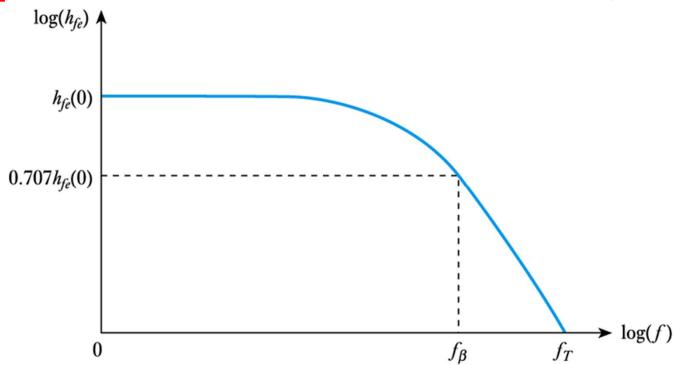 Bipolar transistors at high frequencies due to capacitance and resistance between be, bc and ce



# BJT parameters for common emitter configuration (subscript <sub>e</sub>)

# Input<sub>i</sub> Output<sub>o</sub> Forward<sub>f</sub> Reverse<sub>r</sub>

h <sub>FE</sub>	DC gain	$I_{C}/I_{B}$	
$h_{fe}$	AC gain	$i_{\rm c}/i_{\rm b}$	h <sub>FE</sub> ≈h <sub>fe</sub> (mostly)
$\mathbf{g}_{m}$	Transconductance	$\Delta I_{\rm C} / \Delta V_{\rm BE} = i_{\rm c} / v_{\rm be}$	$\sim 40 \cdot I_C \approx 40 \cdot I_E$
h <sub>ie</sub>	Small signal input resistance	$\Delta V_{BE} / \Delta I_{B} = v_{be} / i_{b}$	$\sim$ 1 / (40·I <sub>B</sub> ) $\Omega \approx h_{fe}$ / (40·I <sub>C</sub> )
h <sub>oe</sub>	Output admittance (1/r <sub>o</sub> )	$\Delta I_{\rm C} / \Delta V_{\rm CE} = i_{\rm c} / v_{\rm ce}$	
	where $r_0$ = Slope in the active region		
r <sub>e</sub>	Emitter resistance	$\Delta V_{BE} / \Delta I_{C} = v_{be} / i_{c} = 1/g_{m}$	$\approx v_{\rm be} / i_{\rm e}$ that is, $h_{\rm ie} = h_{\rm fe} \cdot r_{\rm e}$
h <sub>re</sub>	Early effect (V <sub>CE</sub> affects bias V <sub>BE</sub> )	$\Delta V_{CE} / \Delta V_{BE}$	

$$h_{FE} = \frac{I_C}{I_B}$$

$$I_E = I_C + I_B = (h_{FE} + 1) \cdot I_B$$

$$but because h_{FE} >> 1,$$

$$I_E \approx h_{FE} \cdot I_B = I_C$$

$$I_B = I_{BS} \cdot e^{40 \cdot V_{BE}}$$
 where  $I_{BS}$  is constant
$$I_C = h_{FE} \cdot I_B = h_{FE} \cdot I_{BS} \cdot e^{40 \cdot V_{BE}}$$

$$g_m = \frac{\Delta I_C}{\Delta V_{BE}} = \frac{dI_C}{dV_{BE}} = 40 \cdot h_{FE} \cdot I_{BS} \cdot e^{40 \cdot V_{BE}}$$

$$g_m = \frac{40 \cdot I_C}{\Delta V_{BE}} \approx 40 \cdot I_E$$

# **BJT** parameters for common emitter configuration (subscript <sub>e</sub>)



# **Key points**

- Bipolar transistors are widely used in both analogue and digital circuits
- They can be considered as either voltage-controlled or current-controlled devices
- Their characteristics may be described by their gain or by their transconductance
- Many amplifier circuits use transistors in a common-emitter configuration where the input is applied to the base and the output is taken from the collector



# **Nest time: Bipolar junction transistors**

- Introduction
- An overview of bipolar transistors
- Bipolar transistor operation
- A simple amplifier
- Bipolar transistor characteristics
- Bipolar amplifier circuits
- Bipolar transistor applications
- Circuit examples

