

Department of Physics

Examination paper for TFY4185 Measurement Technique/ Måleteknikk			
Academic contact during examination: Patrick Es	вру		
Phone: +47 41 38 65 78			
Examination date: 2 December 2015			
Examination time (from-to): 09:00 - 13:00			
Permitted examination support material:			
Single or Bi-lingual dictionary permitted All calculators permitted 1 side of an A5 sheet with printed or handwritten formulas perm	nitted		
Other information:			
Language: English			
Number of pages:			
Number of pages enclosed:			
		Checked by:	
	Date	Signature	

BJT parameters for common emitter configuration (subscript) other subscripts: Input, Output Forward, Reverse,

h _{FE}	DC gain	I_{C}/I_{B}	
h_{fe}	AC gain	$i_{\rm c}/i_{\rm b}$	h _{FE} ≈h _{fe} (mostly)
g _m	Transconductance	$\Delta I_{\rm C} / \Delta V_{\rm BE} = i_{\rm c} / v_{\rm be}$	$\sim 40 \cdot I_C \approx 40 \cdot I_E$
h _{ie}	Small signal input resistance	$\Delta V_{BE} / \Delta I_{B} = v_{be} / i_{b}$	\sim 1 / (40·I _B) $\Omega \approx h_{fe}$ / (40·I _C)
h _{oe}	Output admittance (1/r _o)	$\Delta I_{\rm C} / \Delta V_{\rm CE} = i_{\rm c} / v_{\rm ce}$	
	where r_0 = Slope in the active region		
r _e	Emitter resistance	$\Delta V_{BE} / \Delta I_{C} = v_{be} / i_{c} = 1/g_{m}$	$\approx v_{\rm be} / i_{\rm e}$ that is, $h_{\rm ie} = h_{\rm fe} \cdot r_{\rm e}$
h _{re}	Early effect (V _{CE} affects bias V _{BE})	$\Delta V_{CE} / \Delta V_{BE}$	

$$h_{FE} = \frac{I_C}{I_B}$$
 $I_E = I_C + I_B = (h_{FE} + 1) \cdot I_B$
but because $h_{FE} >> 1$,
 $I_E \approx h_{FE} \cdot I_B = I_C$

$$h_{FE} = \frac{I_C}{I_B}$$

$$I_E = I_C + I_B = (h_{FE} + 1) \cdot I_B$$
but because $h_{FE} >> 1$,
$$I_E \approx h_{FE} \cdot I_B = I_C$$

$$I_B = I_{BS} \cdot e^{40 \cdot V_{BE}} \quad \text{where } I_{BS} \text{ is constant}$$

$$I_C = h_{FE} \cdot I_B = h_{FE} \cdot I_{BS} \cdot e^{40 \cdot V_{BE}}$$

$$g_m = \frac{\Delta I_C}{\Delta V_{BE}} = \frac{dI_C}{dV_{BE}} = 40 \cdot h_{FE} \cdot I_{BS} \cdot e^{40 \cdot V_{BE}}$$

$$g_m = \frac{\Delta I_C}{\Delta V_{BE}} = 40 \cdot I_C \approx 40 \cdot I_E$$