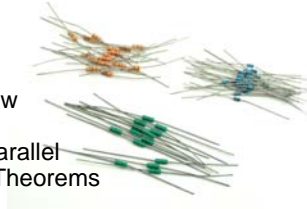


Resistance and DC Circuits



Chapter 3

- Introduction
- Current and Charge
- Voltage Sources
- Current Sources
- Resistance and Ohm's Law
- Kirchhoff's Laws
- Resistors in Series and Parallel
- Thévenin's and Norton's Theorems
- Superposition
- Nodal Analysis
- Mesh Analysis
- Solving Simultaneous Circuit Equations
- Choice of Techniques

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.1

Introduction



3.1

- Many circuits can be analysed, and in some cases designed, using little more than Ohm's law
- However, in some cases we need some additional techniques and these are discussed in this lecture.
- We begin by reviewing some of the basic elements that we use to describe our circuits

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.2

Current and Charge



3.2

- An electric **current** is a flow of electric **charge**
- At an atomic level a current is a flow of **electrons**
 - each electron has a charge of 1.6×10^{-19} coulombs
 - conventional current flows in the opposite direction
- Rearranging above expression gives

$$I = \frac{dQ}{dt}$$

$$Q = \int I dt$$

- For constant current

$$Q = I \times t$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.3

Voltage Sources




3.3

- A voltage source produces an **electromotive force (e.m.f.)** which causes a current to flow within a circuit
 - unit of e.m.f. is the **volt**
 - a volt is the potential difference between two points when a joule of energy is used to move one coulomb of charge from one point to the other
- Real voltage sources, such as batteries have resistance associated with them
 - in analysing circuits we use **ideal voltage sources**
 - we also use **controlled** or **dependent voltage sources**

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.4


Voltage sources

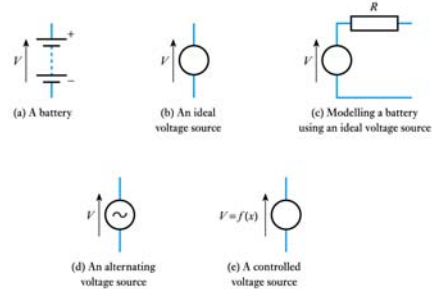Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.5

Current Sources

- We also sometimes use the concept of an **ideal current source**
 - unrealisable, but useful in circuit analysis
 - can be a fixed current source, or a **controlled** or **dependent current source**
 - while an ideal voltage source has *zero* output resistance, an ideal current source has *infinite* output resistance

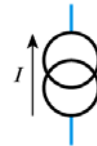Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.6

Resistance and Ohm's Law

Ohm's law

$$V \propto I$$

- constant of proportionality is the resistance R
- hence

$$V = IR \quad I = \frac{V}{R} \quad R = \frac{V}{I}$$

- current through a resistor causes power dissipation

$$P = IV \quad P = \frac{V^2}{R} \quad P = I^2 R$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.7

Kirchhoff's Laws

Node

- a point in a circuit where two or more circuit components are joined

Loop


- any closed path that passes through no node more than once

Mesh

- a loop that contains no other loop

Examples:

- A, B, C, D, E and F are *nodes*
- the paths ABEFA, BCDEB and ABCDEFA are *loops*
- ABEFA and BCDEB are *meshes*

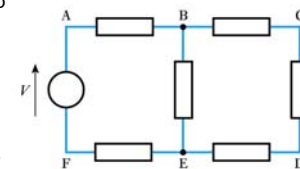
Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.8

Current Law

At any instant, the algebraic sum of all the currents flowing into any node in a circuit is zero

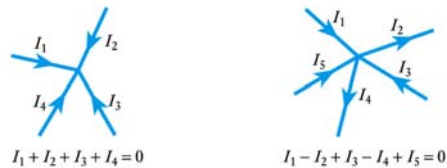- if currents flowing *into* the node are positive, currents flowing *out of* the node are negative, then $\sum I = 0$




Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.9

Voltage Law

At any instant the algebraic sum of all the voltages around any loop in a circuit is zero

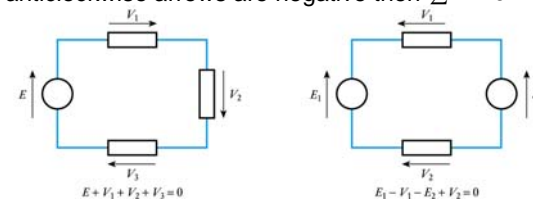
- if clockwise voltage arrows are positive and anticlockwise arrows are negative then $\sum V = 0$



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.10

In General: Single Loop Voltage Law

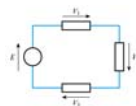

- The current $i(t)$ is:

$$i(t) = \frac{\sum V_{Si}}{\sum R_j} = \frac{\text{sum of voltage sources}}{\text{sum of resistances}} = \frac{E}{\sum R_j}$$

- This approach works for any single loop circuit with voltage sources and resistors.
- Resistors in series can be replaced by:


$$R_{\text{series}} = R_1 + R_2 + \dots + R_N = \sum R_j$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

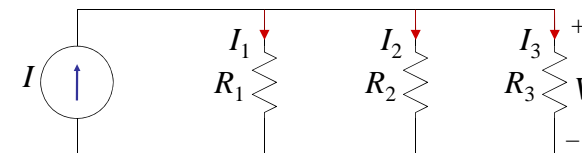3.11

Resistors in Parallel-Current Law

Same voltage across all the elements (have the same node)- the elements are in **parallel**



How do we find I_1 , I_2 , and I_3 ?


Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.12

Apply KCL at the Top Node

$$I = I_1 + I_2 + I_3$$

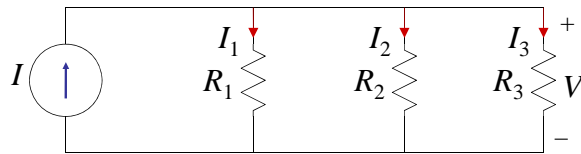But Ohm's Law: $I_1 = \frac{V}{R_1}$ $I_2 = \frac{V}{R_2}$ $I_3 = \frac{V}{R_3}$



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.13

Solve for V

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$V = \frac{I}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \quad \text{Ohm's Law: } R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$


Definition: **Parallel** - the elements share the same two end nodes (Voltage is the same across all the elements)

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

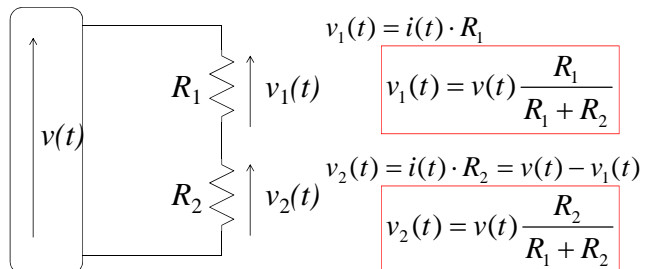3.14

Voltage Division

Two resistors **in series** with a voltage $v(t)$ across them
KVL: $v(t) - v_1(t) - v_2(t) = 0$ Ohm's Law: $i(t) = v(t)/(R_1 + R_2)$



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.15

In General: Voltage Division

Consider N resistors **in series**:

$$V_{R_i}(t) = \frac{R_i}{\sum R_j} \sum V_{S_k}(t)$$


Source voltage(s) are divided between the resistors in direct proportion to their resistances

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

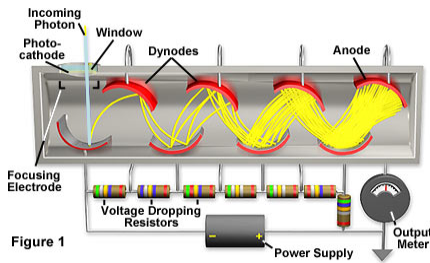3.16

Application of Voltage Divider

- Photomultiplier Tube
 - ~3000 V Potential Difference in 10-14 steps
 - Gain of 10^6 with low noise



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.17

Thévenin's and Norton's Theorems



■ Thévenin's Theorem

As far as its appearance from outside is concerned, any two terminal network of resistors and energy sources can be replaced by a series combination of an ideal voltage source V and a resistor R , where V is the open-circuit voltage of the network and R is the voltage that would be measured between the output terminals if the energy sources were removed and replaced by their internal resistance

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.18


Thevenin's Theorem 2

- Any linear circuit with sources (dependent and/or independent) and resistors **can be replaced by an equivalent circuit containing a single voltage source and a single resistor.**
- Thevenin's theorem implies that we can replace arbitrarily complicated networks with simple networks for purposes of analysis.
- If we have a single "load" resistor which is subject to change, we simplify circuit to a simple Thevenin equivalent with a single resistor and can recalculate easily for many different loads

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.19

A Realistic Source Model

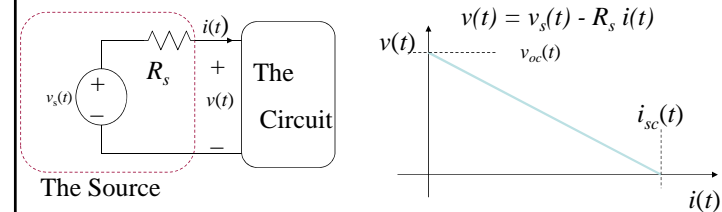


- Since the **open circuit voltage** and the **short circuit current** determine where the I-V line crosses both axes, they completely define the line.
- Any circuit that has the same I-V characteristics is an equivalent circuit.

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

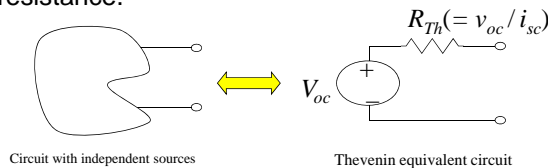3.20

Implications

- We use Thevenin's theorem to justify the concept of input and output resistance for amplifier circuits.
- We model transducers as equivalent sources and resistances.
- We model stereo speakers as an equivalent resistance.



Circuit with independent sources Thevenin equivalent circuit

3.21

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

Norton's Theorem

As far as its appearance from outside is concerned, any two terminal network of resistors and energy sources can be replaced by a parallel combination of an ideal current source I and a resistor R , where I is the short-circuit current of the network and R is the voltage that would be measured between the output terminals if the energy sources were removed and replaced by their internal resistance

3.22

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013


Norton's Theory 2

- Any Thevenin equivalent circuit is in turn equivalent to a current source in parallel with a resistor [source transformation].
- A current source in parallel with a resistor is called a Norton equivalent circuit.
- Finding a Norton equivalent circuit requires essentially the same process as finding a Thevenin equivalent circuit.

3.23

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

Source Transformation

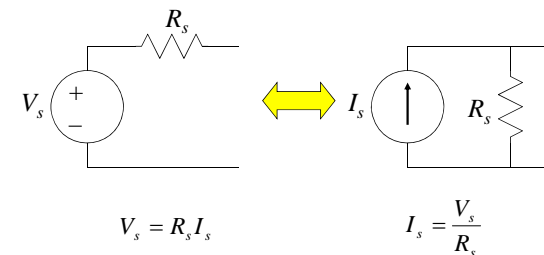

3.24

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

Any arrangement of resistors, voltage sources or current sources

Thévenin equivalent circuit

Norton equivalent circuit

- from the Thévenin equivalent circuit $I_{SC} = \frac{V_{OC}}{R}$
- hence for *either* circuit $R = \frac{V_{OC}}{I_{SC}}$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.25

▪ **Example** – see **Example 3.3** from course text

Determine Thévenin and Norton equivalent circuits of the following circuit

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.26

Example (continued)

- if nothing is connected across the output no current will flow in R_2 so there will be no voltage drop across it. Hence V_o is determined by the voltage source and the potential divider formed by R_1 and R_3 . Hence $V_{OC} = \frac{30}{2} = 15 \text{ V}$
- if the output is shorted to ground, R_2 is in parallel with R_3 and the current taken from the source is $30\text{V}/15 \text{ k}\Omega = 2 \text{ mA}$. This will divide equally between R_2 and R_3 so the output current, and so $I_{SC} = 1 \text{ mA}$
- the resistance in the equivalent circuit is therefore given by $R = \frac{V_{OC}}{I_{SC}} = \frac{15 \text{ V}}{1 \text{ mA}} = 15 \text{ k}\Omega$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.27

Example (continued)

– hence equivalent circuits are:

Thévenin equivalent circuit

Norton equivalent circuit

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.28

Superposition



3.9

Principle of superposition

In any linear network of resistors, voltage sources and current sources, each voltage and current in the circuit is equal to the algebraic sum of the voltages or currents that would be present if each source were to be considered separately. When determining the effects of a single source the remaining sources are replaced by their internal resistance

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.29


How to Apply Superposition

- To find the contribution due to an individual independent source, zero out the other independent sources in the circuit.
 - Voltage source \Rightarrow short circuit.
 - Current source \Rightarrow open circuit.
- Solve the resulting circuit using your favorite technique(s).

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013


3.30

The Summing Circuit

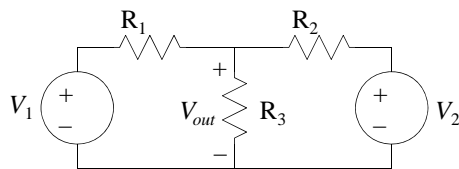Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.31

Superposition

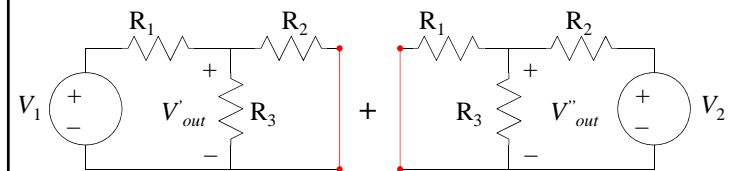

$$I' = V_1 / (R_1 + R_{2//3})$$

$$V'_{out} = I' R_{2//3}$$

Where

$$R_{2//3} = R_2 R_3 / (R_2 + R_3)$$

$$I'' = V_2 / (R_2 + R_{1//3})$$

$$V''_{out} = I'' R_{1//3}$$

Where

$$R_{1//3} = R_1 R_3 / (R_1 + R_3)$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.32

Use of Superposition

$$V_{out} = V_{out} + V'_{out}$$

$$\text{If } R_1=R_2=R_3=1\text{k}\Omega$$

then

$$V_{out} = V_1 / 3$$

$$V'_{out} = V_2 / 3$$

$$V_{out} = V_{out} + V'_{out} = V_1/3 + V_2/3$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.33

Summary and next time

- Nomenclature and symbols
- Circuit analysis using:
 - Ohms Law
 - Kirchoff's voltage law
 - Kirchoff's current law
- Further analysis using Thevenin and Norton theorems
- Superposition
- **Next time**
 - Further example of Superposition, Thevenin and Norton theorems
 - Mesh and Nodal analysis
 - AC circuits

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

3.34