

## Last time: Operational amplifiers



Chapter 16

- Introduction
- An ideal operational amplifier
- Basic operational amplifier circuits
- Some other useful circuits
- Real operational amplifiers
- Selecting component values
- Effects of feedback on op-amp circuits

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


16.1

## An ideal operational amplifier



16.2

- An *ideal* op-amp would be an ideal voltage amplifier and would have:  $A_v = \infty$ ,  $R_i = \infty$  and  $R_o = 0$

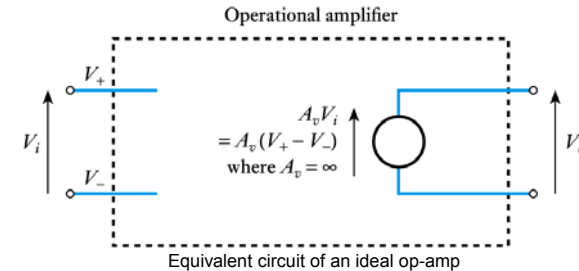Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

16.2

## To analyse basic operational amplifier circuits

### Two Basic Rules

1) An Op-Amp will do whatever is necessary with its output to **adjust the voltage at its inverting input** so that it is equal to the voltage at its non-inverting input. I.e. make the voltage difference between its inputs equal to zero. ( $V_+ = V_-$ )

2) Op-Amp inputs draw no current (reality 0.2nA to fA). (For an ideal op-amp  $I_{in} = 0$ )


Horowitz, Paul and Hill, Winfred, *The Art of Electronics*, Cambridge University Press, 1980

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

16.3

## Basic operational amplifier circuits

### A non-inverting amplifier

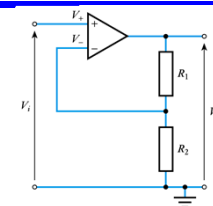

Since the gain is assumed infinite, if  $V_o$  is finite there is no difference in input voltages (Rule 1).

Hence:  $V_- = V_+ = V_i$

Since the input resistance of the op-amp is  $\infty$  no current flows into it from the feedback loop (Rule 2)

$$V_- = V_o \frac{R_2}{R_1 + R_2}$$

and hence, since  $V_- = V_+ = V_i$

$$V_i = V_o \frac{R_2}{R_1 + R_2} \quad \text{and}$$

$$G = \frac{V_o}{V_i} = \frac{R_1 + R_2}{R_2}$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

16.4

ELECTRONICS  
16.3.2

▪ **An inverting amplifier**

Since the gain is assumed infinite, if  $V_o$  is finite the input voltage must be zero. Hence

$$V_- = V_+ = 0 \quad (\text{Rule 1})$$

Since the input resistance of the op-amp is  $\infty$  its input current must be zero. Hence (applying KCL)

$$I_1 + I_2 - I_{in-} = 0 \quad \text{But as } I_{in-} = 0 \quad (\text{Rule 2}) \Rightarrow I_1 = -I_2$$

Now

$$I_1 = \frac{V_o - V_-}{R_1} = \frac{V_o - 0}{R_1} = \frac{V_o}{R_1} \quad I_2 = \frac{V_i - V_-}{R_2} = \frac{V_i - 0}{R_2} = \frac{V_i}{R_2}$$

$$I_1 = -I_2 \Rightarrow \frac{V_o}{R_1} = -\frac{V_i}{R_2} \Rightarrow G = \frac{V_o}{V_i} = -\frac{R_1}{R_2}$$

16.5

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

ELECTRONICS  
16.4.3

▪ **A differential amplifier (or subtractor)**

$V_+$  has changed from the previous analysis (where it was 0). Now:  $V_+ = V_1 \cdot R_1 / (R_1 + R_2)$  which must  $= V_-$ .

the algebra from before with  $V_i = V_2$ , and  $V_- = V_+$  as above, yields:

$$V_o = (V_1 - V_2) \frac{R_1}{R_2}$$


16.6

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

ELECTRONICS  
Chapter 16

**Last time: Operational amplifiers**

- Introduction
- An ideal operational amplifier
- Basic operational amplifier circuits
- Some other useful circuits
- Real operational amplifiers
- Selecting component values
- Effects of feedback on op-amp circuits



16.7

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

ELECTRONICS  
16.4

**Some other useful circuits**

- In addition to simple amplifiers, op-amps can also be used in a range of other circuit
- The next few slides show a few examples of op-amp circuits for a range of purposes
- The analysis of these circuits is similar to that of the non-inverting and inverting amplifiers but (in most cases) this is *not* included here (clues to analysis are)
- For more details of these circuits see the relevant section of the course text (as shown on the slides)

16.8

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

ELECTRONICS  
16.4.2

▪ **A current to voltage converter**

$KCL \rightarrow I_i + I_R - I_{in-} = 0$   
 $\text{Rule 2} \rightarrow I_{in-} = 0$   
 $\text{Ohms law} \rightarrow I_R = V_o / R$

$V_o = -I_i R$

16.9

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

ELECTRONICS  
16.4.4

▪ **An inverting summing amplifier**

$\text{Virtual Ground, KCL: } I_1 + I_2 + I_3 - I_{in-} = 0$   
 $\text{Rule 2: } I_{in-} = 0$

$V_o = -(V_1 + V_2) \frac{R_1}{R_2}$

16.10

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

ELECTRONICS  
16.4.5

▪ **An integrator**

$\text{Since } I_c + I_R = 0 \text{ (Rule 2)} \\ I_c = -V_i / R$   
 $\text{Since } V_- = V_+ = 0 \text{ (Rule 1)} \\ V_o = V_c$

$v_c(t) = \frac{1}{C} \int_0^t i_c(t') dt'$

$V_o = -\frac{1}{RC} \int_0^t V_i dt$

16.11

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

ELECTRONICS  
16.4.6

▪ **A differentiator**

$\text{Since } I_c + I_R = 0 \text{ (Rule 2)} \\ I_c = -V_o / R$   
 $\text{Since } V_- = V_+ = 0 \text{ (Rule 1)} \\ V_i = V_c$

$i_c(t) = C \frac{dv_c(t)}{dt}$

$V_o = -RC \frac{dV_i}{dt}$

16.12

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

ELECTRONICS  
16.4.7

■ **Active filters**

(a) A low-pass filter      (b) A high-pass filter  
(c) A band-pass filter      (d) A band-stop filter

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

16.13

### Real vs. Ideal Op-Amps

Parameter	Ideal Op Amp	Typical Op Amp	741
Differential voltage gain $A_d$	$\infty$	$10^5 - 10^9$	$2 \times 10^5$
Common mode voltage gain $A_{cm}$	0	0.2-60	6.3-63
Gain bandwidth product $f_c = G \cdot f$	$\infty$	1-20 MHz	1.5 MHz
Input resistance $R$	$\infty$	$10^6 \Omega$ (bipolar) $10^9 - 10^{12} \Omega$ (FET)	300 k $\Omega$ -2M $\Omega$
Output resistance $R$	0	100-1000 $\Omega$	75 $\Omega$

Simpson, Robert E., *Introductory Electronics for Scientists and Engineers*, 2nd Ed., Allyn and Bacon, 1987

Typically give Common Mode Rejection Ratio (CMRR) =  $A_d/A_{cm}$   
For the 741 op amp this about 3200-32000 (70 to 90 dB)  
Close enough to ideal that we can analyse circuits assuming ideal op-amps

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

16.14

ELECTRONICS  
16.6

### Selecting component values

- Our analysis assumed the use of an ideal op-amp
- When using real components we need to ensure that our assumptions are valid
- In general this will be true if we:
  - limit the *gain of our circuit*,  $G$ , to *much less* than the *open-loop gain of our op-amp*,  $A$
  - choose external resistors that are *small* compared with the *input* resistance of the op-amp
  - choose external resistors that are *large* compared with the *output* resistance of the op-amp.
- Generally we use resistors in the range 1 to 100 k $\Omega$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

16.15

ELECTRONICS  
16.7

### Effects of feedback on op-amp circuits

- Effects of feedback on the gain**
  - negative feedback *reduces* gain from  $A$  to  $A/(1 + AB)$
  - in return for this loss of gain we get consistency, provided that the open-loop gain is much greater than the closed-loop gain (that is,  $A \gg 1/B$ )
  - using negative feedback, standard cookbook circuits can be used – greatly simplifying the design
  - these can be analysed without a detailed knowledge of the op-amp itself

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


16.16



Video 16C
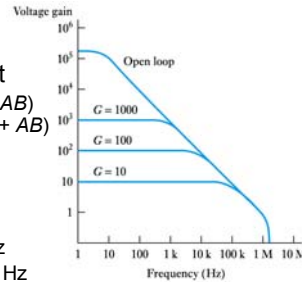
### Effects of feedback on frequency response

- as the gain is *reduced* the bandwidth is *increased*
- gain  $\times$  bandwidth  $\approx$  constant
  - since gain is *reduced* by  $(1 + AB)$  bandwidth is *increased* by  $(1 + AB)$
- for a 741,
  - gain  $\times$  bandwidth  $\approx 10^6$ 
    - if gain = 1000 BW  $\approx$  1000 Hz
    - if gain = 100 BW  $\approx$  10,000 Hz




16.17

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


Video 16D
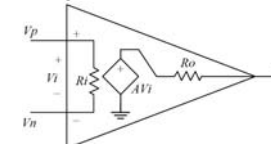
### Effects of feedback on input and output resistance

- input/output resistance can be increased or decreased depending on how feedback is used
  - in each case the resistance is changed by a factor of  $(1 + AB)$
- Looking towards  $R_{in}$  from the source, or  $R_{out}$  from the load parallel path to ground lowers effective impedance series path to ground raises effective impedance




16.18

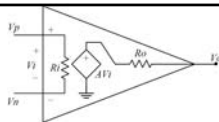Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

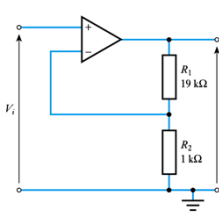
### Example (see Example 16.5 in the course text)

- determine the input and output resistance of the following circuit assuming op-amp is a 741




Open-loop gain ( $A$ ) of a 741 is  $2 \times 10^5$   
 Closed-loop gain ( $1/B$ ) is 20,  $B = 1/20 = 0.05$   
 $(1 + AB) = (1 + 2 \times 10^5 \times 0.05) = 10^4$   
 Feedback senses output *voltage* therefore it *reduces* output resistance of op-amp ( $75 \Omega$ ) by  $10^4$  to give  $7.5 \text{ m}\Omega$   
 Feedback subtracts a *voltage* from the input, therefore it *increases* the input resistance of the op-amp ( $2 \text{ M}\Omega$ ) by  $10^4$  to give  $20 \text{ G}\Omega$

16.19

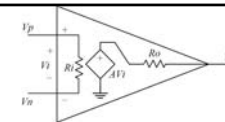Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013
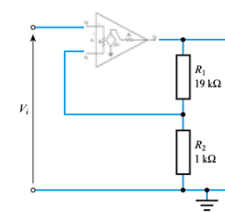
### Example (see Example 16.5 in the course text)


- determine the input and output resistance of the following circuit assuming op-amp is a 741



Open-loop gain ( $A$ ) of a 741 is  $2 \times 10^5$   
 Closed-loop gain ( $1/B$ ) is 20,  $B = 1/20 = 0.05$   
 $(1 + AB) = (1 + 2 \times 10^5 \times 0.05) = 10^4$   
 Feedback senses output *voltage* therefore it *reduces* output resistance of op-amp ( $75 \Omega$ ) by  $10^4$  to give  $7.5 \text{ m}\Omega$   
 Feedback subtracts a *voltage* from the input, therefore it *increases* the input resistance of the op-amp ( $2 \text{ M}\Omega$ ) by  $10^4$  to give  $20 \text{ G}\Omega$

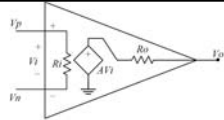
16.20

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013



▪ **Example** (see **Example 16.6** in the course text)

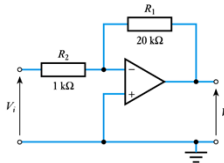
- determine the input and output resistance of the following circuit assuming op-amp is a 741



Open-loop gain ( $A$ ) of a 741 is  $2 \times 10^5$   
 Closed-loop gain ( $1/B$ ) is 20,  $B = 1/20 = 0.05$   
 $(1 + AB) = (1 + 2 \times 10^5 \times 0.05) = 10^4$   
 Feedback senses output **voltage** therefore, it **reduces** output resistance of op-amp ( $75 \Omega$ ) by  $10^4$  to give  $7.5 \text{ m}\Omega$   
 Feedback subtracts a **current** from the input, therefore it **decreases** the input resistance. In this case the input sees  $R_2$  to a virtual earth, therefore the input resistance is  $1 \text{ k}\Omega$


Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

16.21

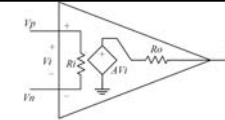

▪ **Example** (see **Example 16.6** in the course text)

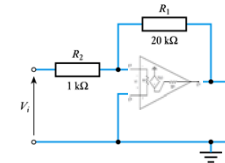- determine the input and output resistance of the following circuit assuming op-amp is a 741



Open-loop gain ( $A$ ) of a 741 is  $2 \times 10^5$   
 Closed-loop gain ( $1/B$ ) is 20,  $B = 1/20 = 0.05$   
 $(1 + AB) = (1 + 2 \times 10^5 \times 0.05) = 10^4$   
 Feedback senses output **voltage** therefore, it **reduces** output resistance of op-amp ( $75 \Omega$ ) by  $10^4$  to give  $7.5 \text{ m}\Omega$   
 Feedback subtracts a **current** from the input, therefore it **decreases** the input resistance. In this case the input sees  $R_2$  to a virtual earth, therefore the input resistance is  $1 \text{ k}\Omega$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

16.22

## Further Study



Video 16E Further Study

- The **Further Study** section at the end of Chapter 16 looks at the identification of op-amp circuits.
- Normally our task is to design a circuit to perform a given task. However, it is also useful to be able to look at a circuit and see what it does!
- Look at the circuits given in the text and see if you can work out their function. Then look at the video to see if you are correct.



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


16.23

## Key points

- Operational amplifiers are among the most widely used building blocks in electronic circuits
- An *ideal* operational amplifier would have infinite voltage gain, infinite input resistance and zero output resistance
- Designers often make use of cookbook circuits
- Real op-amps have several non-ideal characteristics. However, if we choose components appropriately this should not affect the operation of our circuits
- Feedback allows us to increase bandwidth by trading gain against bandwidth
- Feedback also allows us to alter other circuit characteristics

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

16.24




Chapter 17

## Semiconductors and diodes


---

- Introduction
- Electrical properties of solids
- Semiconductors
- *pn* Junctions
- Diodes
- Semiconductor diodes
- Special-purpose diodes
- Diode circuits.



17.25

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013



17.1

## Introduction

---

- So far we have taken a '**black-box**' view of active components (such as op-amps)
- It is now time to look 'inside the box'
  - we will start by looking at diodes and semiconductors
  - then progress to transistors
  - later, we will look at more detailed aspects of circuit design

17.26


Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

## Quantum Mechanical Electronic energy levels in atoms

- The electrons have discrete energy levels
- Form a continuum band at high quantum number


(Like the steps in a ladder, but with uneven distance between the steps.)

Energy ↑

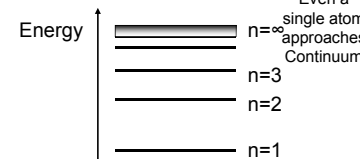

Even a single atom approaches Continuum


**Bohr's atom model**

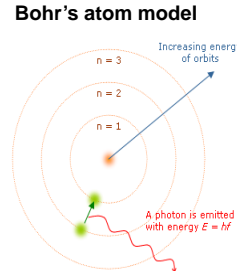

27

## Electronic energy levels in solids, N atoms

ELECTRON ENERGY

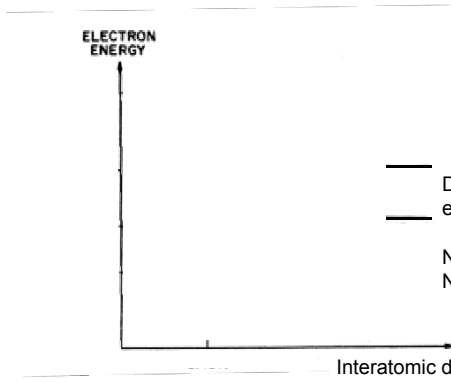


Interatomic distance

Discrete energy levels

N isolated atoms  
N = 10<sup>23</sup>/cm<sup>3</sup>


28
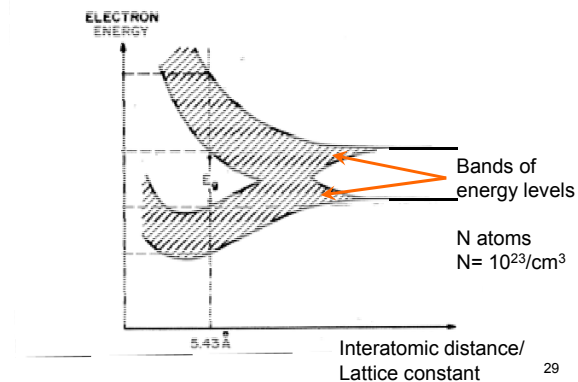
## Electronic energy levels in solids, N atoms



29
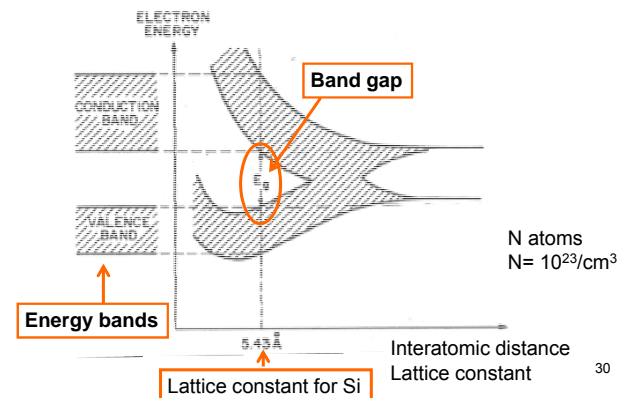
## Electronic energy levels in solids, N atoms



30


The "band diagram" tells you which energy levels are available, not if they are occupied by electrons or not....

If the levels are occupied or not, depends on the number of electrons available; i.e. on the type of atom....

(...and on the external energy available)

31

## Energy Level Diagrams

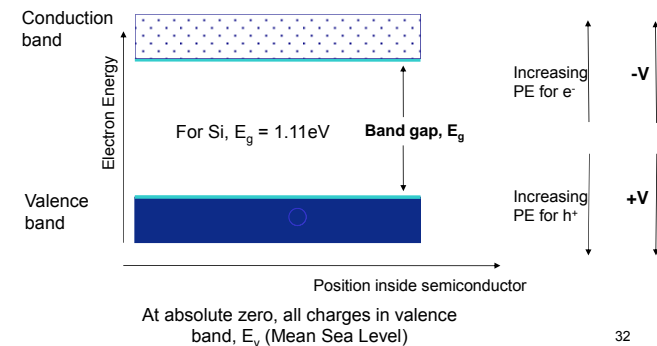

32



### The Fermi distribution and the Fermi level

- The probability that an electronic state with energy  $E$  is occupied by an electron is given by the Fermi-Dirac distribution function (also called the Fermi distribution)

$$f(E) = \frac{1}{1 + e^{(E-E_F)/kT}}$$

where  $k$  is the Boltzmann constant,  $T$  the absolute temperature and  $E_F$  the Fermi level.


The Fermi level is the energy at which the probability of occupation by an electron is exactly one half.

$$f(E_F) = 0.5$$

33
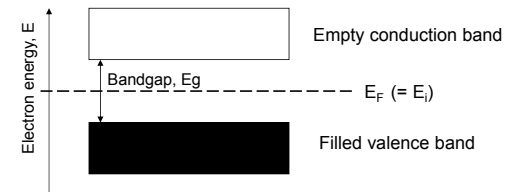
### Fermi level in undoped semiconductors

- In an undoped semiconductor in thermal equilibrium at zero Kelvin, all electronic states with energy up till the top of the valence band (the valence band edge) are occupied (filled), and all electronic states above the bottom of the conduction band are empty




- There is 100% probability of finding an electron in the valence band and 0% probability to find an electron in the conduction band, so the Fermi level (the energy of 50% probability) is in the middle of the bandgap.

34

### Band separation and electronic properties

#### Insulators

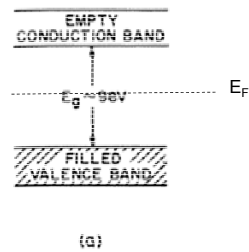


35

### Band separation and electronic properties


#### Insulators

#### Undoped Semiconductors

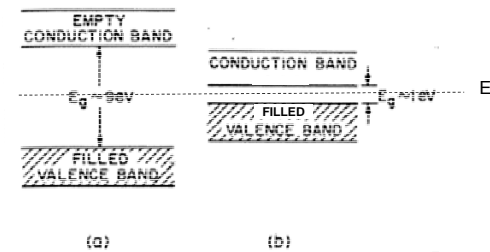


36
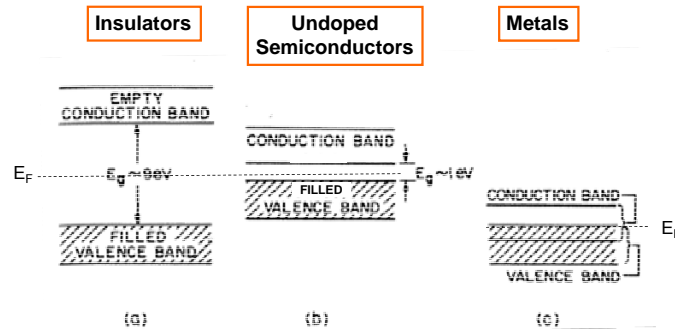
## Band separation and electronic properties



37
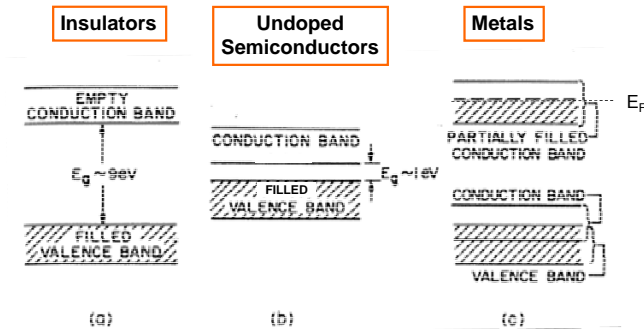
## Band separation and electronic properties



38

## Electrical properties of solids



17.2

- **Conductors**

- e.g. copper or aluminium
- have a cloud of free electrons (at all temperatures above absolute zero). If an electric field is applied electrons will flow causing an electric current

- **Insulators**

- e.g. polythene
- electrons are tightly bound to atoms, so, only a few can break free to conduct electricity

17.39

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

- **Semiconductors**

- e.g. silicon or germanium
- at very low temperatures these have the properties of insulators
- as the material warms up some electrons break free and can move about, and it takes on the properties of a conductor – albeit a poor one
- however, semiconductors have several properties that make them distinct from conductors and insulators

17.40

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

## Semiconductors



17.3

### ■ Pure semiconductors


- thermal vibration results in some bonds being broken, generating **free electrons** which move about
- these leave behind **holes** which accept electrons from adjacent atoms and therefore, also move about
- electrons are **negative charge carriers**
- holes are **positive charge carriers**
- At room temperatures there are few charge carriers
  - *pure* semiconductors are poor conductors
  - this is **intrinsic conduction**

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.41

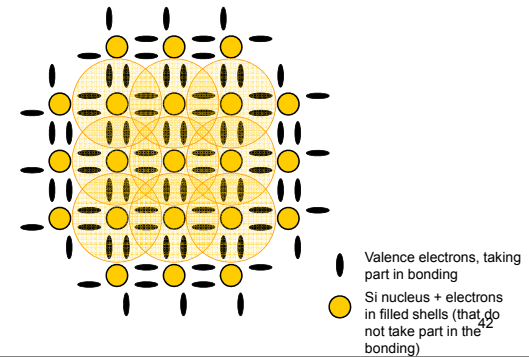
## Pure Silicon

The outermost shell of Si, the so called valence shell, can hold 8 electrons. Each Si atom has only 4 valence electrons (electrons in the outermost shell). Each Si atom then shares 4 valence electrons with its nearest neighbours, so that it has 8 in total (and has filled the outer shell).



## Pure silicone: thermal effect-partially conducts

- The effect of thermal vibration on the structure of silicon-occasional electron-hole pairs generated
- Want to enhance this effect by adding impurities in a process called “doping”

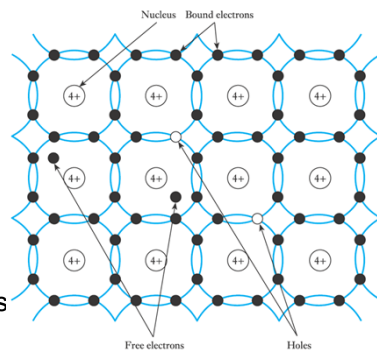Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.43

## Doping of semiconductors

### ■ Doping


- the addition of small amounts of impurities drastically affects its properties
- some materials form an excess of *electrons* and produce an ***n*-type semiconductor**
- some materials form an excess of *holes* and produce a ***p*-type semiconductor**
- both *n*-type and *p*-type materials have much greater conductivity than pure semiconductors
- this is **extrinsic conduction**

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.44
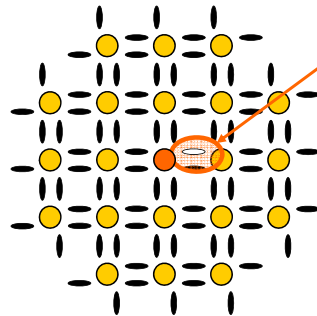
### P-doping

Replace one silicon atom with an atom that has only three valence electrons (i.e. boron) (and also one less proton in the core).




A hole, that can be filled by nearby electrons. When that happens the dopant is ionized, and negatively charged.

Note the Si atom that donated the electron now lacks one, so it has a positive charge, making the whole material neutral

The p-dopant can accept electrons from the silicon atoms, and are called acceptors.

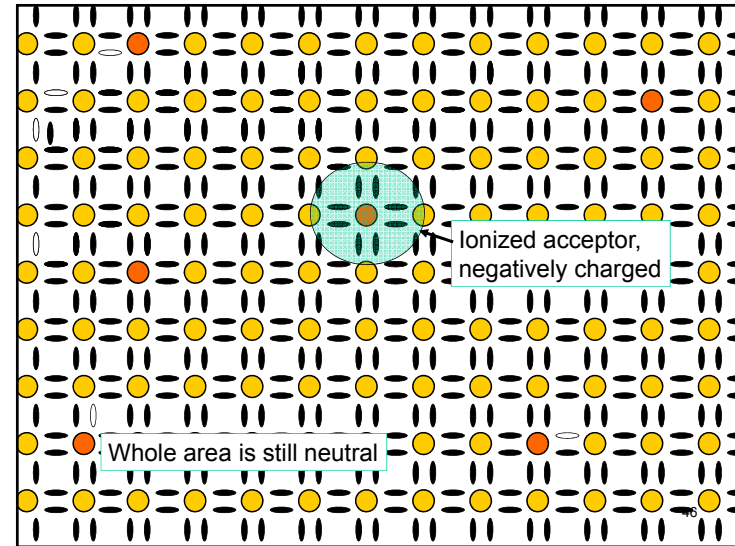● Binding electrons, keeping the material together  
● Si nucleus + electrons in filled shells (that do not take part in the bonding)




Ionized acceptor, negatively charged

Whole area is still neutral
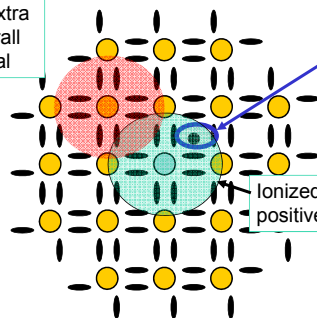
### N-doping

Replace one silicon atom with an atom that has five valence electrons (i.e. phosphorus) (and also one proton more in the core).

This Si has an extra electron, so overall material is neutral




An excess (free) electron not participating in the bonding process

Ionized donor, positively charged

● Binding electrons, keeping the material together  
● Si nucleus + electrons in filled shells (that do not take part in the bonding)  
● Conduction electrons

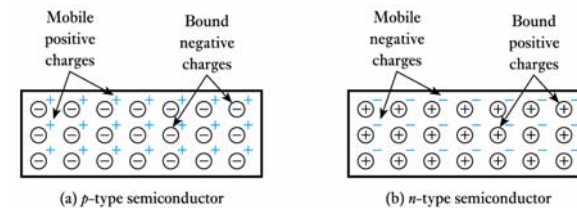- The dominant charge carriers in a doped semiconductor (e.g. electrons in *n*-type material) are called **majority charge carriers**. The other type are **minority charge carriers**
- The overall doped material is electrically neutral



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.48

**pn-junction**

To create an built-in electric field : join a p-type and an n-type semiconductor, to create a pn-junction.

Here shown before ionization of the dopants; in the ionization process the free carriers will be (thermally) released to the surrounding semiconductor.

What happens when the p- and n-type materials are brought together?

49

At the junction electrons diffuse from the n-type to the p-type semiconductor, where they recombine with available holes. This creates a depletion of free charges.

An opposing electric field builds up due to the charge associated with the ionized donor and acceptor atoms.

This electric field stops the diffusion. But any thermal electrons generated more towards n-type

50


## pn Junctions

- When *p*-type and *n*-type materials are joined, this forms a **pn junction**
  - the majority charge carriers on each side diffuse across the junction where they combine with (and remove) the charge carriers of the opposite polarity
  - hence, around the junction there are few free charge carriers and we have a **depletion layer** (also called a **space-charge layer**)

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.51

- The diffusion of positive charge in one direction and negative charge in the other produces a charge imbalance
  - this results in an **Electric Field** and **potential barrier** across the junction

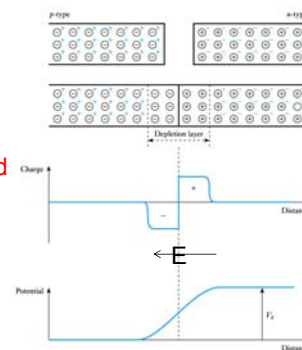Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.52

### Potential barrier


- the barrier opposes the flow of *majority* charge carriers and only a small number have enough energy to surmount it
  - This generates a *small diffusion current*
- the barrier encourages the flow of *minority* carriers and any that come close to it will be swept over
  - This generates a small *drift current*
- for an isolated junction these two currents must balance each other and the net current is zero

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.53
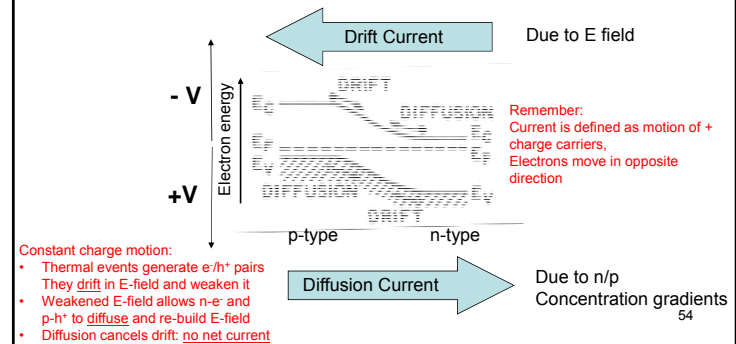
## Currents at Equilibrium

- The Drift and Diffusion currents are = and opposite:  $J_t = J_{\text{drift}} - J_{\text{diffusion}} = 0$



## Biassing the pn Junction


### Forward bias

- if the *p*-type side is made *positive* with respect to the *n*-type side the height of the barrier is reduced
- more majority charge carriers have sufficient energy to surmount it
- the diffusion current therefore increases while the drift current remains the same
- there is thus a net current flow across the junction which increases with the applied voltage

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.55

## Biassing of the p-n junction

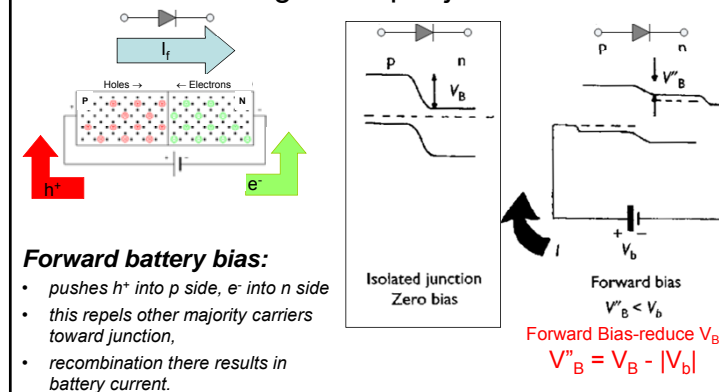

bb


### Reverse bias

- if the *p*-type side is made *negative* with respect to the *n*-type side the height of the barrier is increased
- the number of majority charge carriers that have sufficient energy to surmount it rapidly decreases
- the diffusion current therefore vanishes while the drift current remains the same
- thus the only current is a small leakage current caused by the (approximately constant) drift current
- the leakage current is usually negligible (a few nA)

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.57


### Biasing of the p-n junction

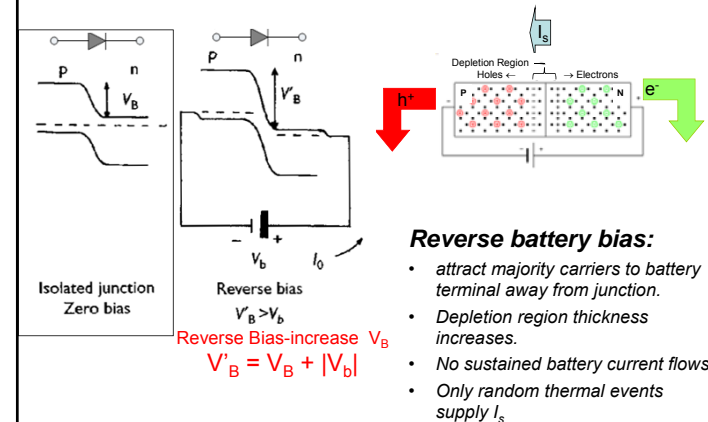

58

### Currents in a pn junction

Diffusion or forward current  $\rightarrow$   
Drift or thermal current  $\leftarrow$

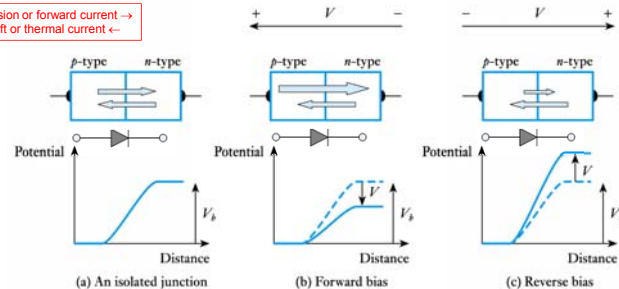Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.59

### Forward and reverse currents

- *pn* junction current is given approximately by

$$I = I_s \left( \exp \frac{eV}{\eta kT} - 1 \right)$$

- where  $I$  is the current,  $e$  is the electronic charge,  $V$  is the applied voltage,  $k$  is Boltzmann's constant,  $T$  is the absolute temperature and  $\eta$  (Greek letter *eta*) is a constant in the range 1 to 2 determined by the junction material
- for most purposes we can assume  $\eta = 1$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.60

- Thus,

$$I \approx I_s \left( \exp \frac{eV}{kT} - 1 \right)$$

at room temperature  $e/kT \sim 40 \text{ V}^{-1}$

- If  $V > +0.1 \text{ V}$ ,

$$I \approx I_s \left( \exp \frac{eV}{kT} \right) = I_s (\exp 40V)$$

- If  $V < -0.1 \text{ V}$ ,

$$I \approx I_s (0 - 1) = -I_s$$

–  $I_s$  is the **reverse saturation current**


That is, our drift or thermal current,  $I_s$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.61
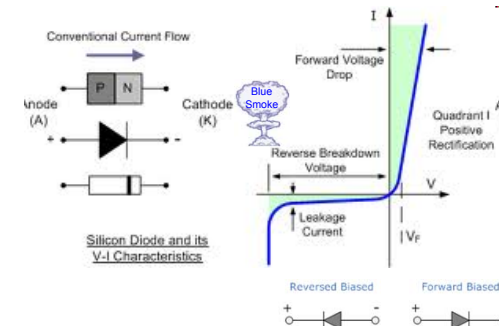
## External currents across a pn-junction


- The diode passes current in one direction.




62
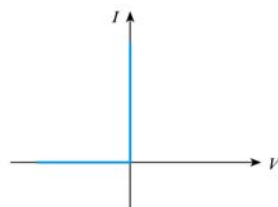
## Diodes

- An **ideal diode** passes electricity in one direction but not in the other



(a) I–V characteristic

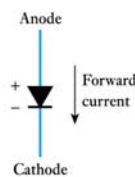


(b) Diode circuit symbol

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

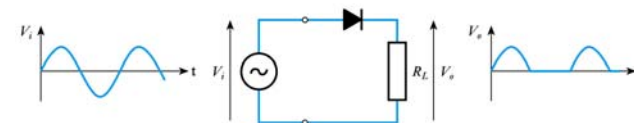17.63

- One application of diodes is in **rectification**
  - the example below shows a **half-wave rectifier**



- In practice, no real diode has ideal characteristics but semiconductor **pn junctions** make good diodes

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.64




## Semiconductor diodes



17.6

### Forward and reverse currents

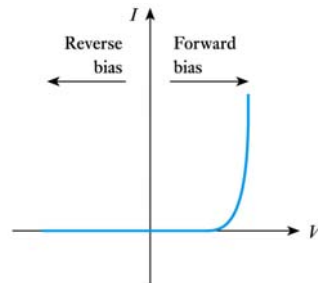Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.65


### Silicon diodes

- generally have a turn-on voltage of about 0.5 V
- generally have a conduction voltage of about 0.7 V
- have a breakdown voltage that depends on their construction
  - perhaps 75 V for a **small-signal diode**
  - perhaps 400 V for a **power device**
- have a maximum current that depends on their construction
  - perhaps 100 mA for a **small-signal diode**
  - perhaps many amps for a **power device**

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.66


### Turn-on and breakdown voltages for a silicon device

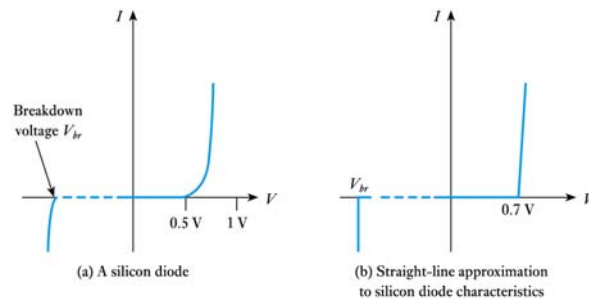Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.67

## Diode equivalent circuits


- Sometimes we represent a diode by an equivalent circuit. Models have different levels of sophistication

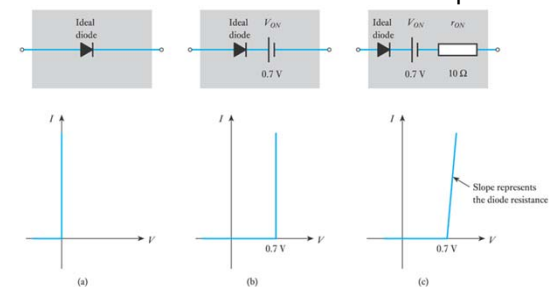Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.68
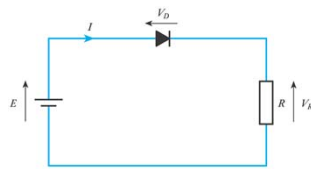
## Diode circuit analysis

- The non-linear behaviour of diodes makes analysis difficult – consider this simple circuit



Applying Kirchhoff's voltage law

$$E = V_D + V_R$$

$$= V_D + IR$$

From the diode equation


$$I = I_s (\exp 40 V_D)$$

To find  $I$  we need to solve these two simultaneous equations

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

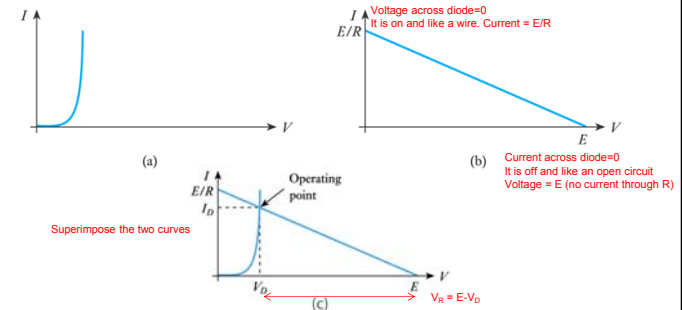17.69


- One approach is through the use of a **load line**



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

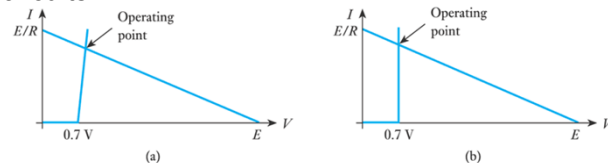17.70


- Load lines can also be used with equivalent circuits...



...however, this is rarely done, since if an equivalent circuit is used, the circuit can normally be analysed directly, without resorting to a graphical method

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.71

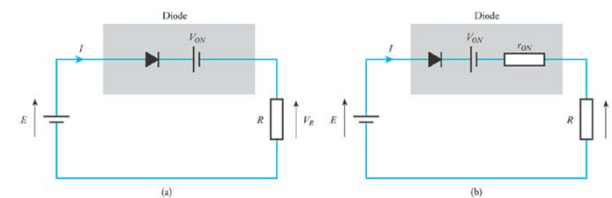

$$I = \frac{E - V_{ON}}{R}$$

$$I = \frac{E - V_{ON}}{R + r_{ON}}$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.72

### Effects of temperature

- Earlier we noted that

$$I \approx I_s \left( \exp \frac{eV}{kT} - 1 \right)$$

- for a given  $I$ , the voltage is inversely proportional to  $T$
- for a silicon diode,  $V$  decreases by about 2 mV per °C
- the diode current is also affected by the reverse saturation current, which increases with temperature
- $I_s$  increases by about 7% per °C

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.73

### Reverse breakdown

- Can be caused by two mechanisms:
- Zener breakdown**
  - in devices with heavily doped  $p$ - and  $n$ -type regions the transition from one to the other is very abrupt
  - this produces a very high field strength across the junction that can pull electrons from their covalent bonds.
  - produces a large reverse current
  - breakdown voltage is largely constant
  - Zener breakdown normally occurs below 5 V

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.74

### Avalanche breakdown

- occurs in diodes with more lightly doped materials
- field strength across junction is insufficient to pull electrons from their atoms, but is sufficient to accelerate the electrons within the depletion layer
- they lose energy by colliding with atoms
- if they have sufficient energy they can liberate other electrons, leading to an avalanche effect
- usually occurs at voltages above 5 V

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.75

### Special-purpose diodes


Too much current will  
kill diode



17.7
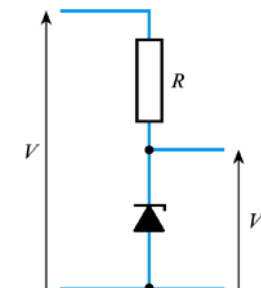
#### Zener diodes

- uses the relatively constant reverse breakdown voltage to produce a voltage reference
- breakdown voltage is called the **Zener voltage,  $V_Z$**
- output voltage of circuit shown is equal to  $V_Z$  despite variations in input voltage  $V$
- a resistor is used to **limit the current** in the diode



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.76

### ▪ Schottky diodes


- formed by the junction between a layer of metal (e.g. aluminium) and a semiconductor
- action relies only on majority charge carriers
- much faster in operation than a *pn* junction diode
  - Don't have to wait for recombination of minority carriers
- has a low forward voltage drop of about 0.25 V
- used in the design of high-speed logic gates

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.77


### ▪ Tunnel diodes

- high doping levels produce a very thin depletion layer which permits 'tunnelling' of charge carriers
- results in a characteristic with a **negative resistance** region
- used in high-frequency oscillators, where they can be used to 'cancel out' resistance in passive components

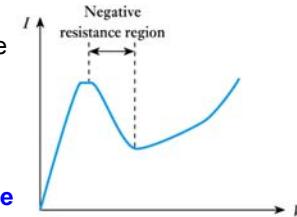Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.78

Extra Large  
depletion region

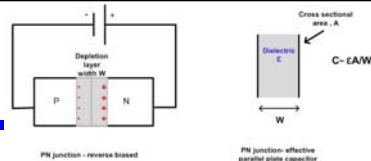

### ▪ Varactor diodes

- a reversed-biased diode **looks like** two conducting regions separated by a **large** insulating depletion region
- this structure resembles a capacitor
- variations in the reverse-bias voltage change the width of the depletion layer and hence the capacitance
- this produces a **voltage-dependent capacitor**
- these are used in applications such as **automatic tuning circuits**

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.79

## Diode circuits




Video 17A



17.8

### ▪ Half-wave rectifier


- peak output voltage is equal to the peak input voltage minus the conduction voltage of the diode
- reservoir capacitor used to produce a steadier output

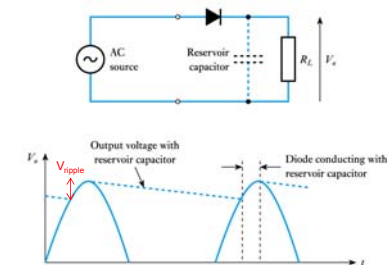Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.80
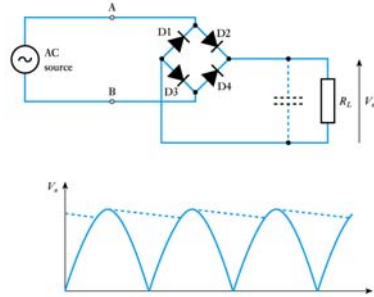
### Full-wave rectifier

- use of a diode bridge reduces the time for which the capacitor has to maintain the output voltage and thus reduce the ripple voltage




Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.81
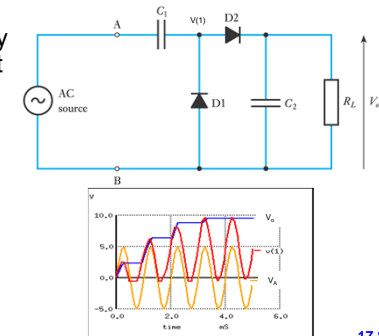
### Voltage doubler

- charges  $C_2$  to nearly twice the peak input voltage
- several stages can be cascaded to produce very high voltages
- ideal in applications requiring high voltages at low currents



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.82




Video 17B
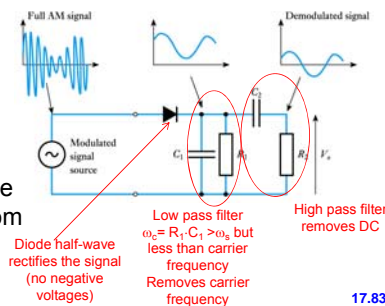
### Signal rectifier

Signal is the low frequency part  
Carrier is the high frequency part

- used to demodulate full amplitude modulated signals (**full-AM**)
- also known as an **envelope detector**
- found in a wide range of radio receivers from crystal sets to superheterodynes




Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.83
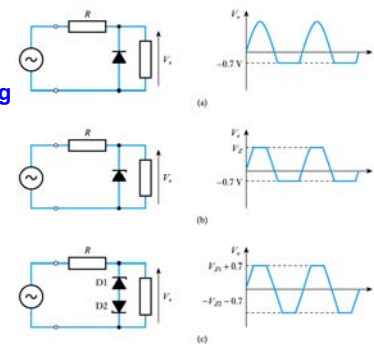
### Signal clamping

- a simple form of **signal conditioning**
- circuits limit the excursion of the voltage waveform
- can use a combination of signal and Zener diodes




Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.84
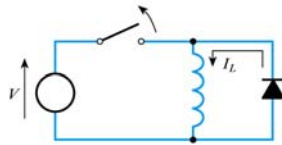
### Catch diode

- used when switching inductive loads
- the large back e.m.f. can cause problems such as arcing in switches
- **catch diodes** provide a low impedance path across the inductor to dissipate the stored energy
- the applied voltage reverse-biases the diode, which therefore has no effect
- when the voltage is removed the back e.m.f. forward biases the diode which then conducts



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.85

### Further Study



Video 17C Further Study

- The **Further Study** section at the end of Chapter 17 is concerned with the design of a mains power supply.
- The supply is to drive an appliance that requires a fairly constant input of 12V and takes a current that varies from 100 to 200 mA.
- Design such a unit and then look at the video.



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.86

### Key points

- Diodes allow current to flow in only one direction
- At low temperatures semiconductors act like insulators
- At higher temperatures they begin to conduct
- Doping of semiconductors leads to the production of *p*-type and *n*-type materials
- A junction between *p*-type and *n*-type semiconductors has the properties of a diode
- Silicon semiconductor diodes approximate the behaviour of ideal diodes but have a conduction voltage of about 0.7 V
- There are also a wide range of special purpose diodes
- Diodes are used in a range of applications

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

17.87