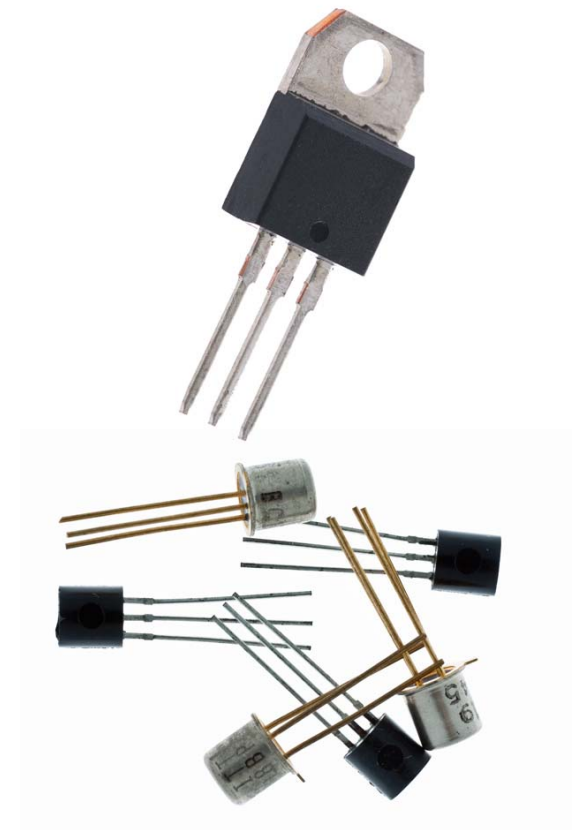


# Bipolar junction transistors

- Introduction
- An overview of bipolar transistors
- Bipolar transistor operation
- A simple amplifier
- Bipolar transistor characteristics
- Bipolar amplifier circuits
- Bipolar transistor applications
- Circuit examples




# BJT parameters for common emitter configuration (subscript <sub>e</sub>)

## ■ Input<sub>i</sub>      Output<sub>o</sub>      Forward<sub>f</sub>      Reverse<sub>r</sub>

$h_{FE}$	DC gain	$I_C / I_B$	
$h_{fe}$	AC gain	$i_c / i_b$	$h_{FE} \approx h_{fe}$ (mostly)
$g_m$	Transconductance	$\Delta I_C / \Delta V_{BE} = i_c / v_{be}$	$\sim 40 \cdot I_C \approx 40 \cdot I_E$
$h_{ie}$	Small signal input resistance	$\Delta V_{BE} / \Delta I_B = v_{be} / i_b$	$\sim 1 / (40 \cdot I_B) \Omega \approx h_{fe} / (40 \cdot I_C)$
$h_{oe}$	Output admittance ( $1/r_o$ ) where $r_o$ = Slope in the active region	$\Delta I_C / \Delta V_{CE} = i_c / v_{ce}$	
$r_e$	Emitter resistance	$\Delta V_{BE} / \Delta I_C = v_{be} / i_c = 1/g_m$	$\approx v_{be} / i_e$ that is, $h_{ie} = h_{fe} \cdot r_e$
$h_{re}$	Early effect ( $V_{CE}$ affects bias $V_{BE}$ )	$\Delta V_{CE} / \Delta V_{BE}$	

$h_{FE} = \frac{I_C}{I_B}$ $I_E = I_C + I_B = (h_{FE} + 1) \cdot I_B$ <p>but because <math>h_{FE} \gg 1</math>,</p> $I_E \approx h_{FE} \cdot I_B = I_C$	$I_B = I_{BS} \cdot e^{40 \cdot V_{BE}} \quad \text{where } I_{BS} \text{ is constant}$ $I_C = h_{FE} \cdot I_B = h_{FE} \cdot I_{BS} \cdot e^{40 \cdot V_{BE}}$ $g_m = \frac{\Delta I_C}{\Delta V_{BE}} = \frac{dI_C}{dV_{BE}} = 40 \cdot h_{FE} \cdot I_{BS} \cdot e^{40 \cdot V_{BE}}$ $g_m = \quad \quad \quad = 40 \cdot I_C \approx 40 \cdot I_E$
--	---
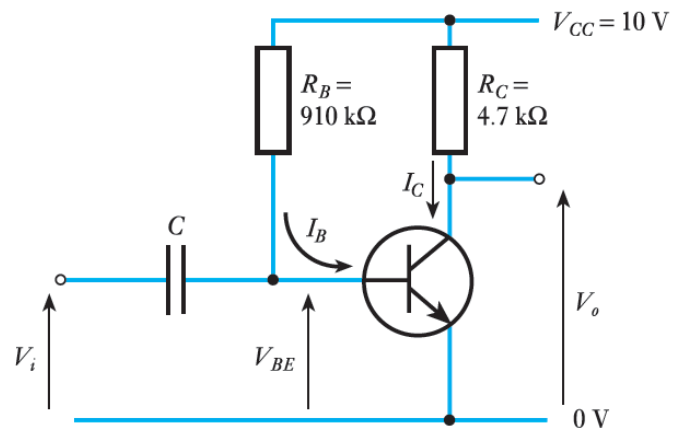
# Last time: bipolar transistor-no feedback




DC-large signal

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} :$$

$$I_C = h_{FE} I_B$$

$$V_o = V_{CC} - I_C R_C$$

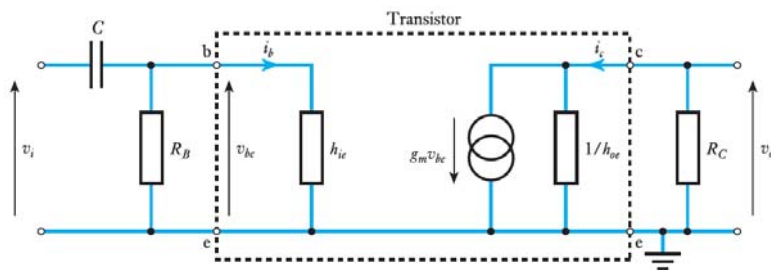

AC-small signal

$$\frac{v_o}{v_i} = -g_m \cdot \frac{R_C}{h_{oe} \cdot R_C + 1} \quad R_C \ll \frac{1}{h_{oe}} \Rightarrow \frac{v_o}{v_i} \approx -g_m \cdot R_C$$


$$r_i = \frac{h_{ie}}{\frac{h_{ie}}{R_B} + 1}$$

$$R_B \gg h_{ie} \Rightarrow r_i \approx h_{ie}$$


$$r_o = \frac{R_C}{h_{oe} \cdot R_C + 1}$$

$$R_C \ll \frac{1}{h_{oe}} \Rightarrow r_o = R_C$$

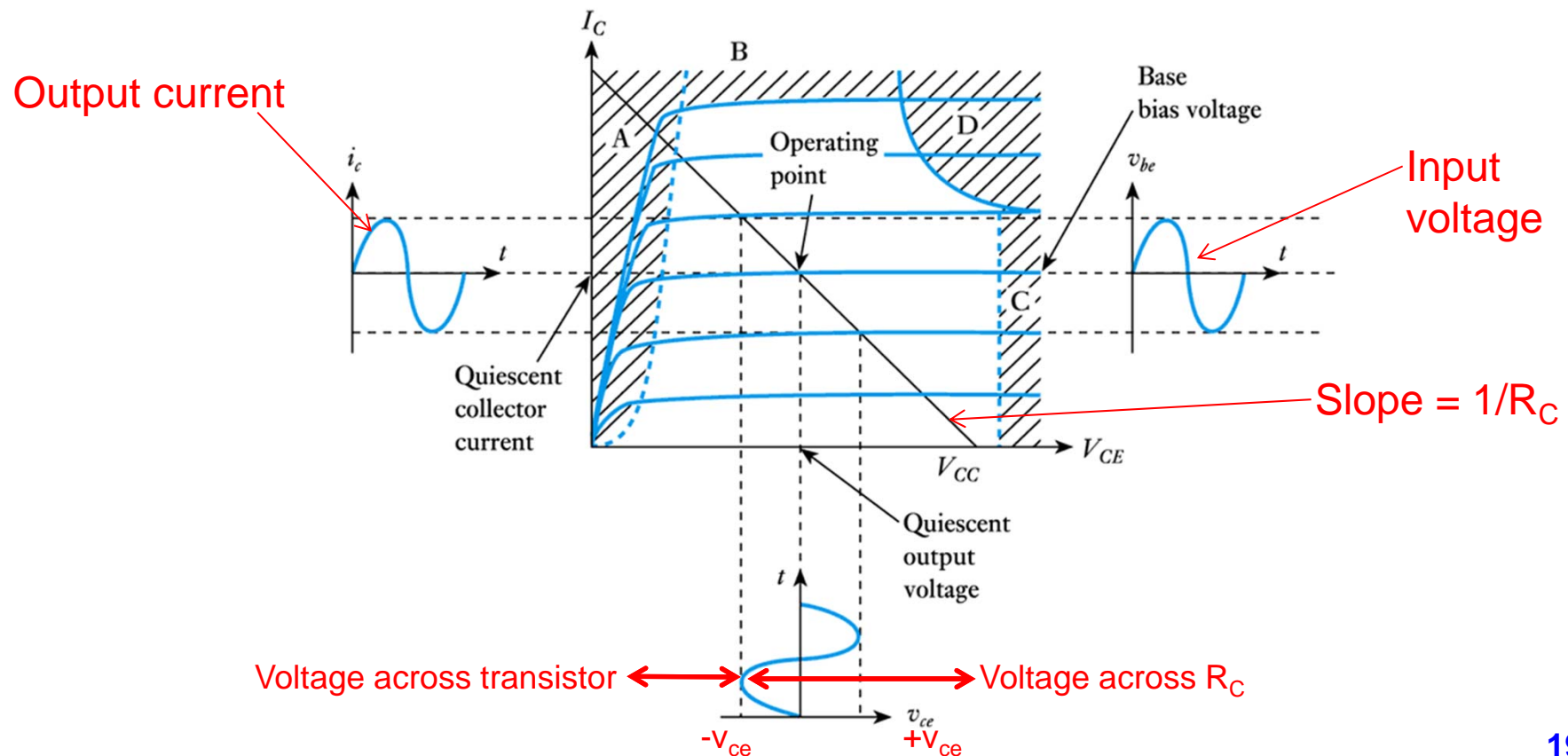- Choice of operating point in a simple amplifier



# Problems with this circuit

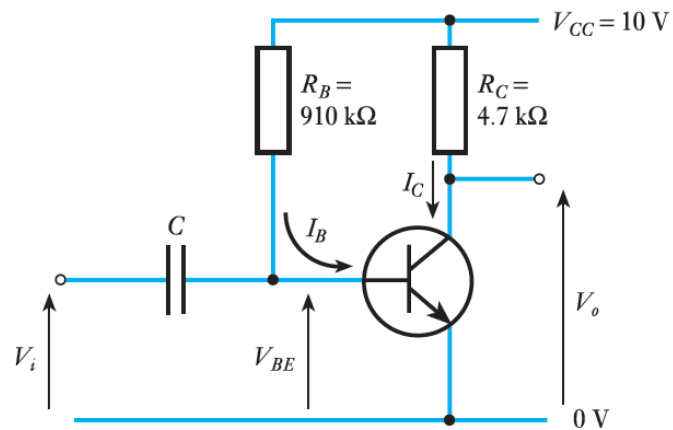

AC gains depend on:


Properties of transistor

And since  $g_m \approx 40 \cdot I_C$ ,

$V_o/V_i \approx -40 \cdot V_{RC}$

the signal gain changes with DC operating point

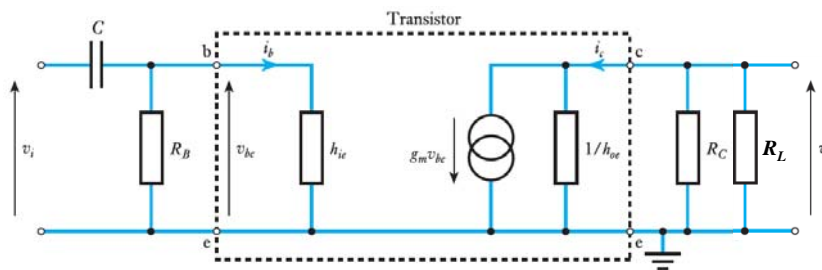$R_L$  interacts with  $R_C$  to change gain



## AC-small signal

$$\frac{v_o}{v_i} = -g_m \cdot \frac{R_C}{h_{oe} \cdot R_C + 1}$$

$$R_C \ll \frac{1}{h_{oe}} \Rightarrow \frac{v_o}{v_i} \approx -g_m \cdot R_C$$

$$r_i = \frac{h_{ie}}{\frac{h_{ie}}{R_B} + 1}$$


$$R_B \gg h_{ie} \Rightarrow r_i \approx h_{ie}$$

$$r_o = \frac{R_C}{h_{oe} \cdot R_C + 1}$$

$$R_C \ll \frac{1}{h_{oe}} \Rightarrow r_o = R_C$$

19.5

# Problems with this circuit

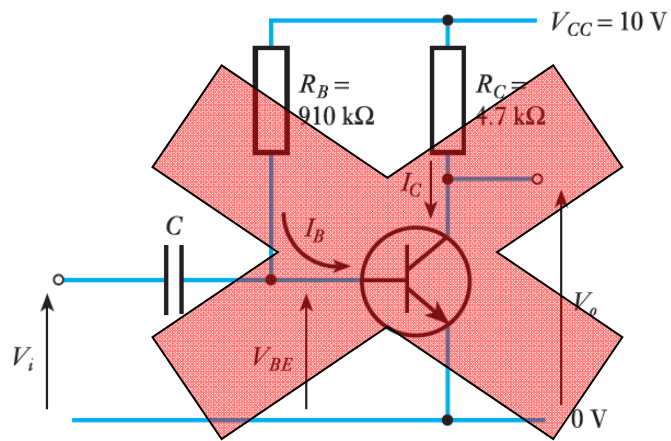

AC gains depend on:


Properties of transistor

And since  $g_m \approx 40 \cdot I_C$ ,

$v_o/v_i \approx -40 \cdot V_{RC}$

the signal gain changes with DC operating point

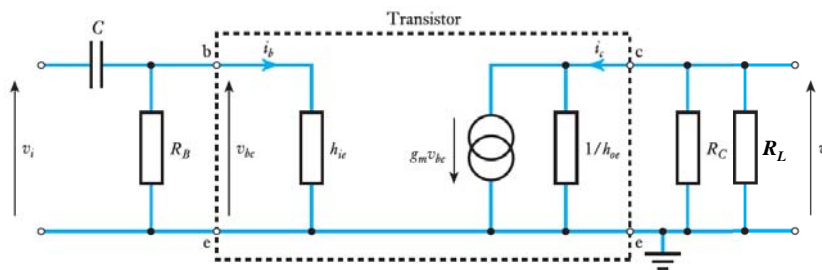$R_L$  interacts with  $R_C$  to change gain



## AC-small signal

$$\frac{v_o}{v_i} = -g_m \cdot \frac{R_C}{h_{oe} \cdot R_C + 1}$$

$$R_C \ll \frac{1}{h_{oe}} \Rightarrow \frac{v_o}{v_i} \approx -g_m \cdot R_C$$

$$r_i = \frac{h_{ie}}{\frac{h_{ie}}{R_B} + 1}$$

$$R_B \gg h_{ie} \Rightarrow r_i \approx h_{ie}$$

$$r_o = \frac{R_C}{h_{oe} \cdot R_C + 1}$$

$$R_C \ll \frac{1}{h_{oe}} \Rightarrow r_o = R_C$$



19.6



Video 19C
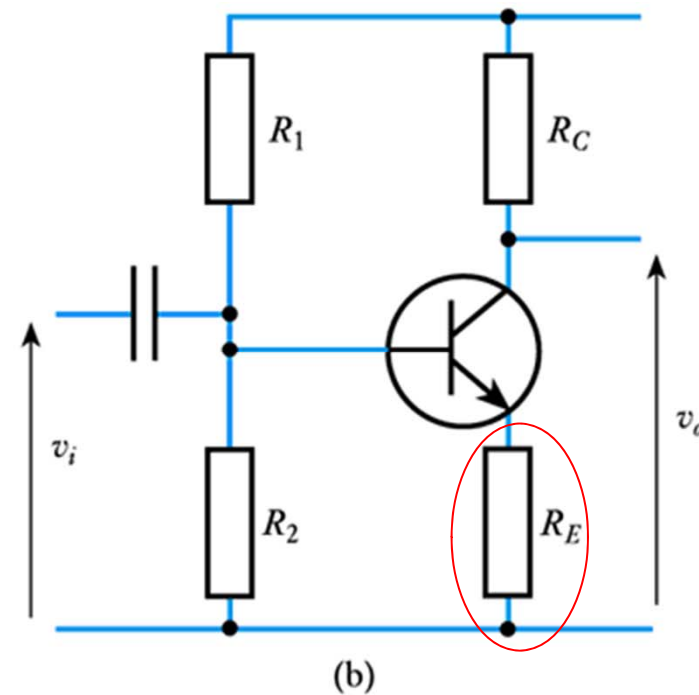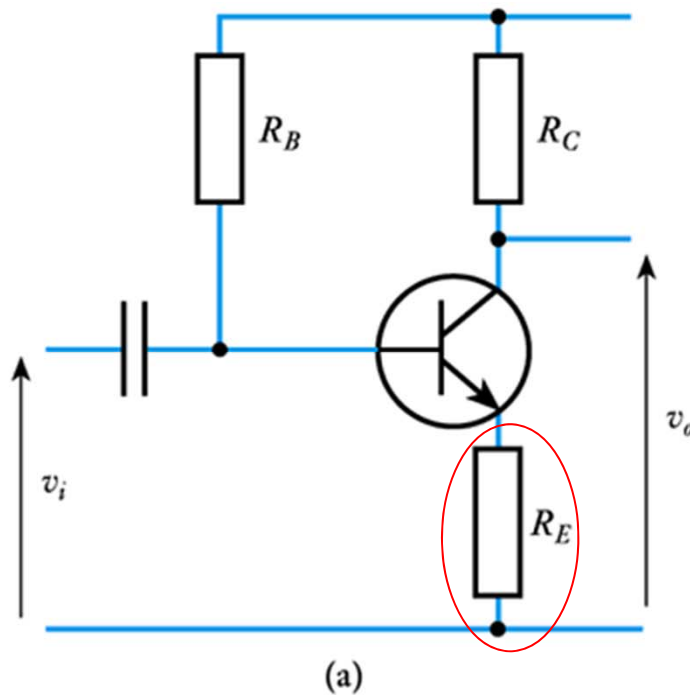
## The use of feedback


- Feedback can be used to overcome the effects of device variability. Consider the following circuits




19.7
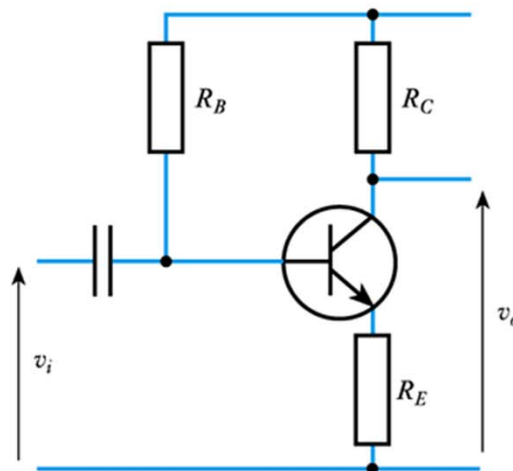
## How does this work?

- As  $v_i \approx v_b$  rises,  $v_{be}$  forward bias increases and more  $i_b$  flows
- This causes more current,  $i_c$ , to flow
- This increases the voltage at the top of  $R_E$  (*catches up to  $v_i$* )
- And this reduces the  $v_{be}$  forward bias
- Voltage at the top of  $R_E$  tracks  $v_b \approx v_i$ , and reduces gain



(a)

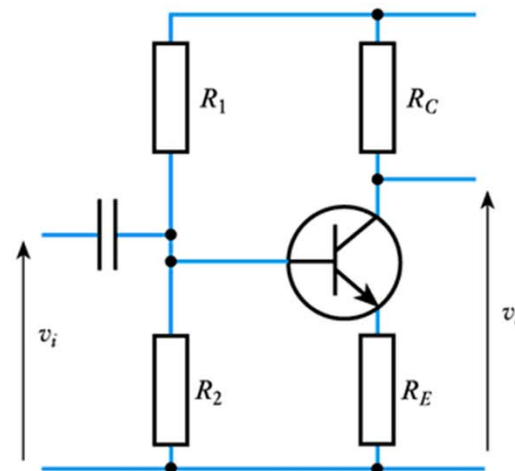


(b)



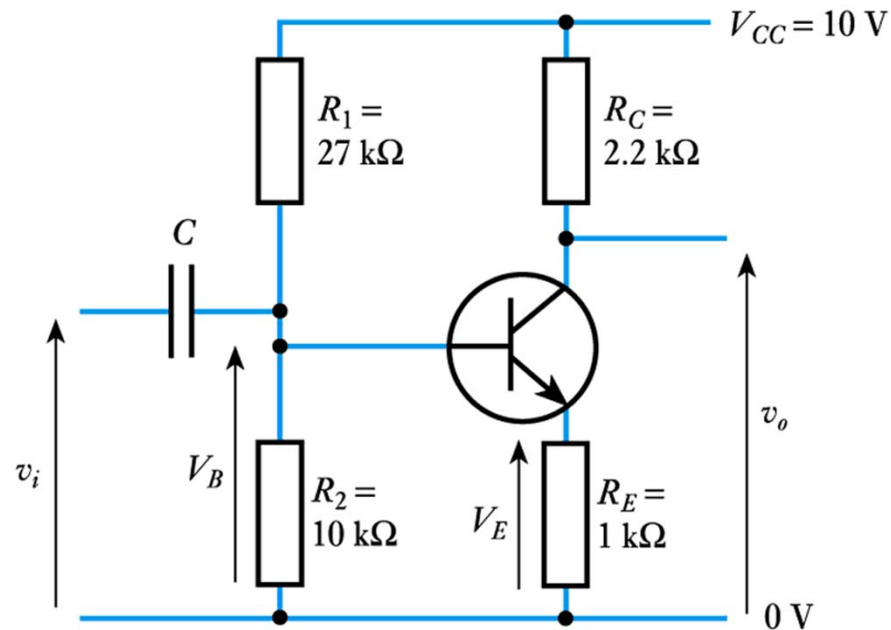
# Analysis of amplifier with feedback

- See **Example 19.3** from course text  
Determine the quiescent voltages and currents in the following circuit
- See **Example 19.4** from course text  
Determine the small-signal behaviour of the following circuit



# Results: Bipolar transistor-with feedback

## DC-large signal

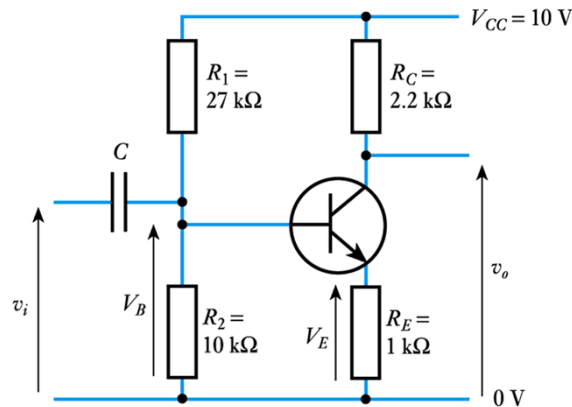

$$V_B \approx V_{CC} \frac{R_2}{R_1 + R_2}$$

$$V_E = V_B - V_{BE}$$

$$V_{BE} \approx \text{constant} \approx 0.7\text{V}$$

$$I_B \ll I_C \approx I_E$$


$$I_E \approx I_C = \frac{V_E}{R_E}$$

$$V_o = V_{CC} - I_C R_C$$

Gain,  $r_i$  and  $r_o$  only depend on passive components

## AC-small signal

Note  $R_1 // R_2$  in series with C

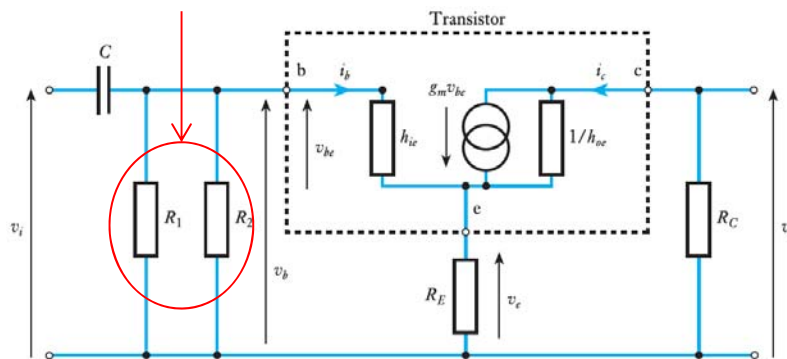

$$\frac{v_o}{v_i} = - \frac{R_C}{R_E + \frac{1}{g_m}}$$

$$r_b = h_{ie} + (h_{fe} + 1) R_E$$

$$r_i = R_1 \parallel R_2 \parallel r_b$$

$$r_o = R_C \parallel \left( \frac{1}{h_{oe}} + R_E \right)$$

$$R_E \gg \frac{1}{g_m}$$

$$h_{fe} \cdot R_E \gg h_{ie} \gg 1 \Rightarrow r_b \approx h_{fe} \cdot R_E$$

$$r_b \gg R_1 \approx R_2 \Rightarrow r_i \approx \frac{R_1 \cdot R_2}{R_1 + R_2}$$


$$R_C \ll \frac{1}{h_{oe}} + R_E \Rightarrow r_o \approx R_C$$


19.10

Reduces the amount of AC negative feedback while maintaining DC feedback.  
This increases the small-signal gain of the circuit but does not affect the DC feedback,  
This provides stability to the bias conditions of the circuit
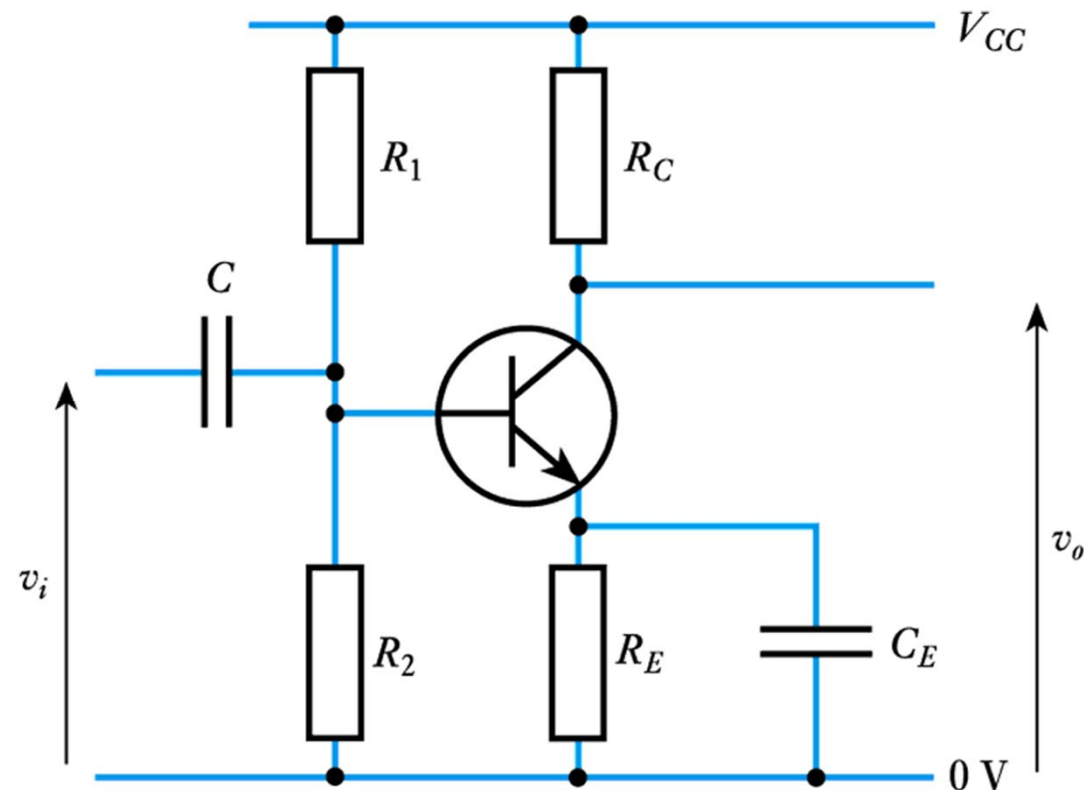
## Use of a decoupling capacitor


- A decoupling capacitor removes small-signal feedback



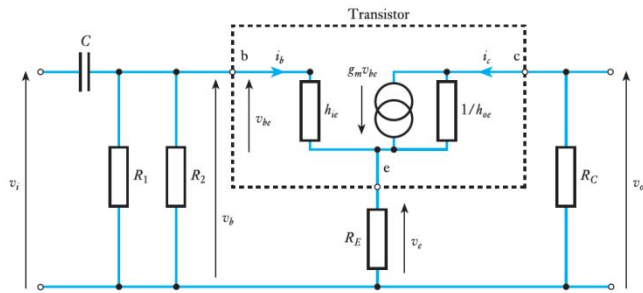

Small signal equivalent circuit  
without coupling capacitor

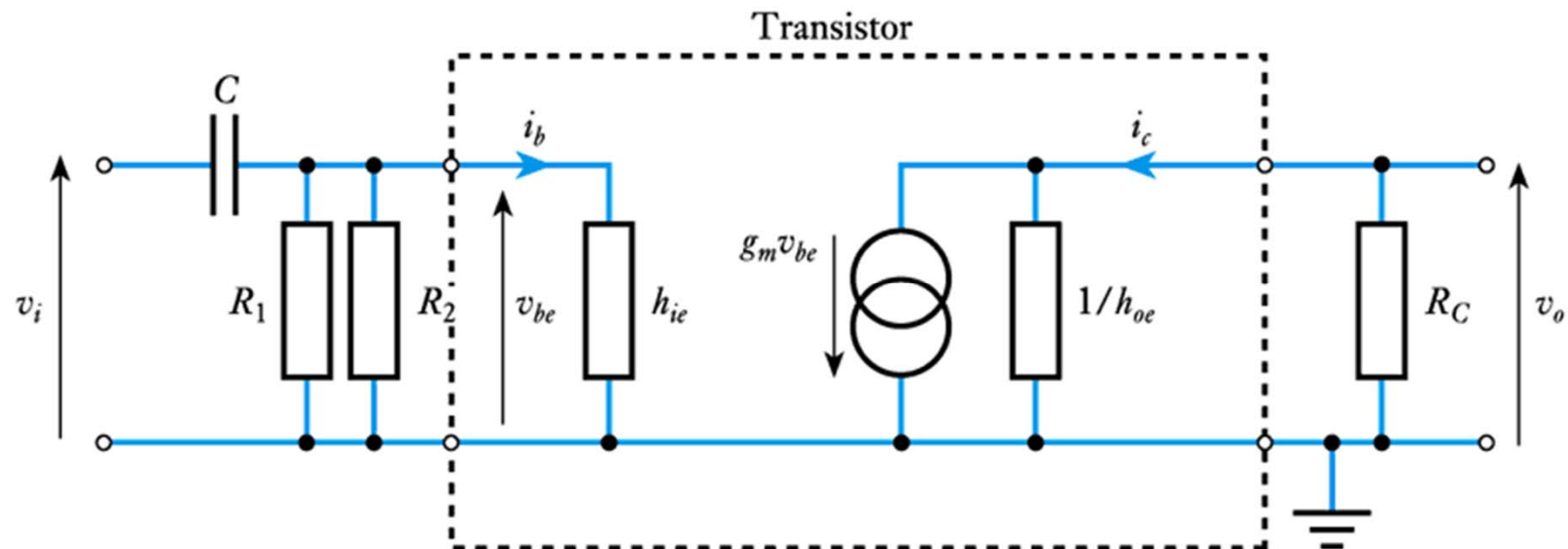- Small-signal equivalent circuit of an amplifier using a decoupling capacitor (Shorts out  $R_E$  in signal band)




Remember  $r_e = 1/g_m$  and gain was  $g_m \cdot R_c$

- A comparison of the frequency responses of various amplifiers

- for simplicity, the figure shows the responses of amplifiers that are *not* fitted with coupling capacitors

With an ac coupling capacitor

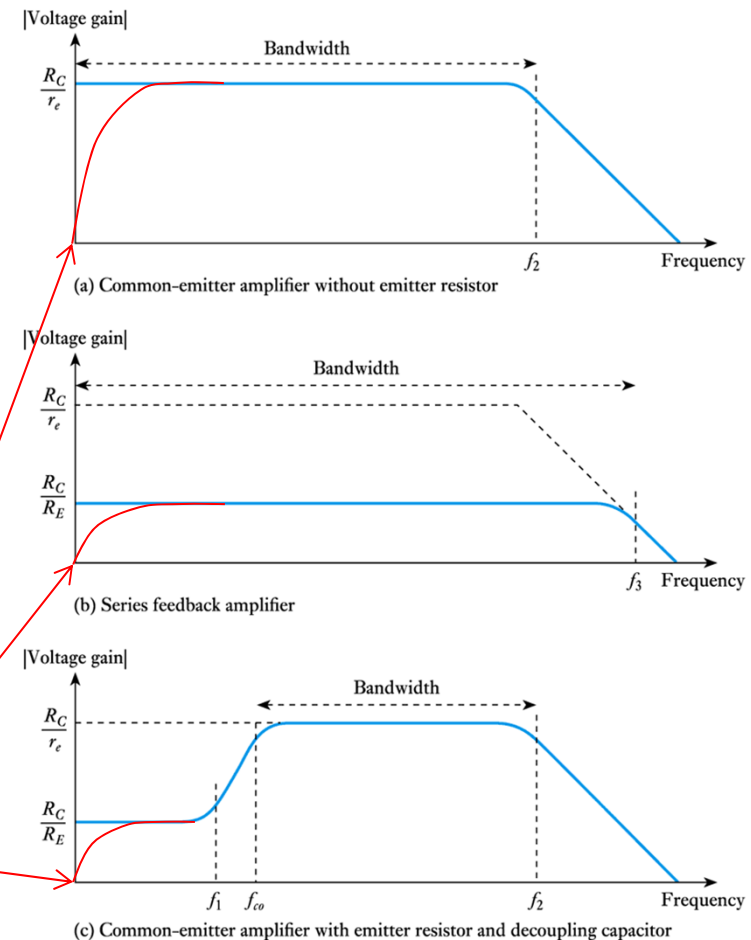


# Summary

---

- DC and small-signal (AC) gains no feedback
  - Gain depends on characteristics of specific transistor
- DC and small-signal gains with negative feedback
  - Small-gain but depends on stable passive resistors
- Decoupling capacitor
  - Claw back some of the lost gain within the signal band



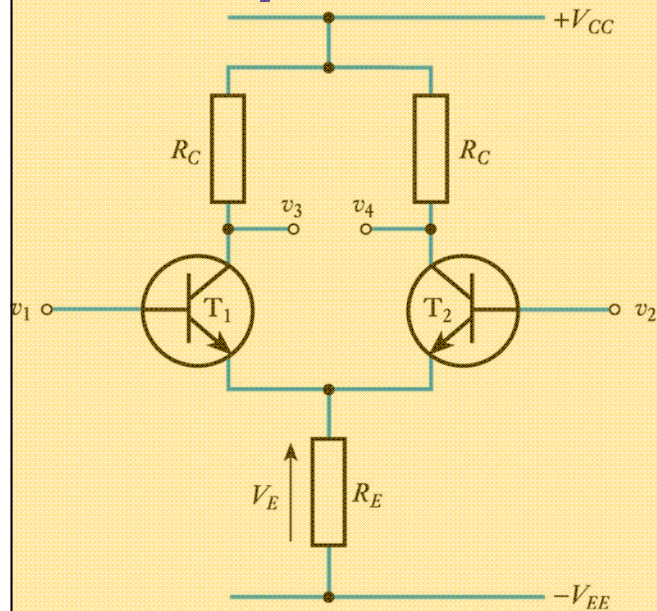
## ■ Bipolar transistors as differential amplifiers



$$\text{voltage gain} = \frac{v_o}{v_i} = \frac{v_3 - v_4}{v_1 - v_2} \approx -g_m R_C$$

$$\text{CMRR} \approx g_m R_E$$

Compare


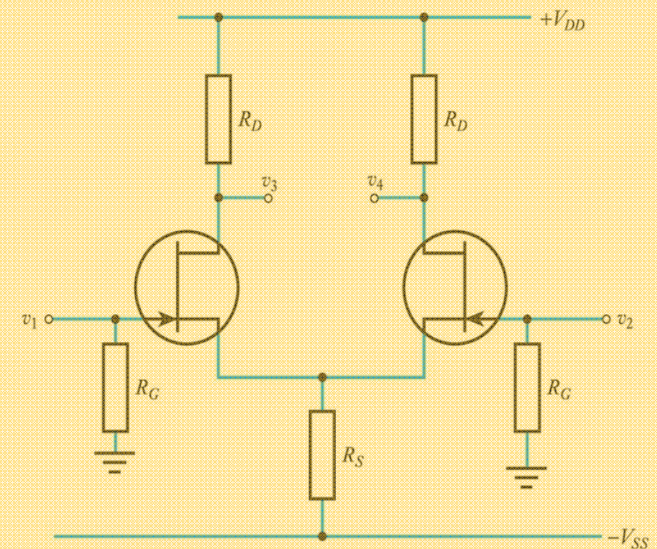


$$\text{voltage gain} = \frac{v_o}{v_i} = \frac{v_3 - v_4}{v_1 - v_2} \approx -g_m R_D$$

$$\text{CMRR} \approx g_m R_S$$




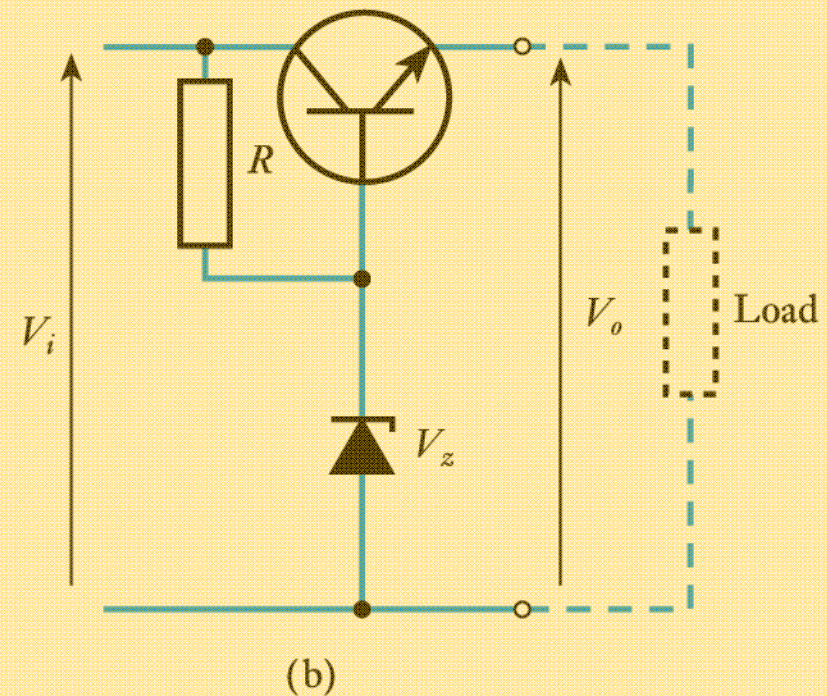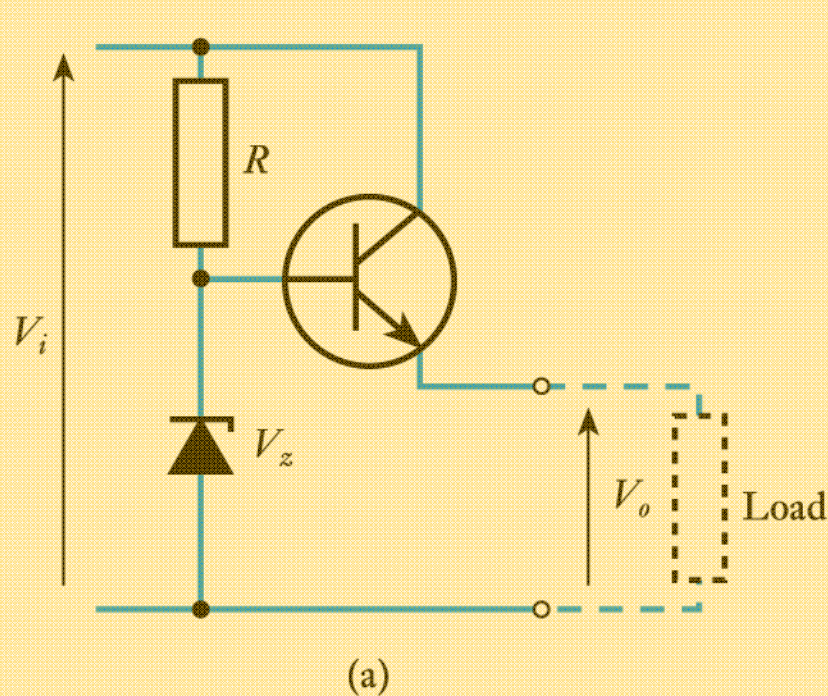- **A voltage regulator** (keeps constant voltage  $V_o$ , since  $V_B$  is constant, by adjusting the current through the load)





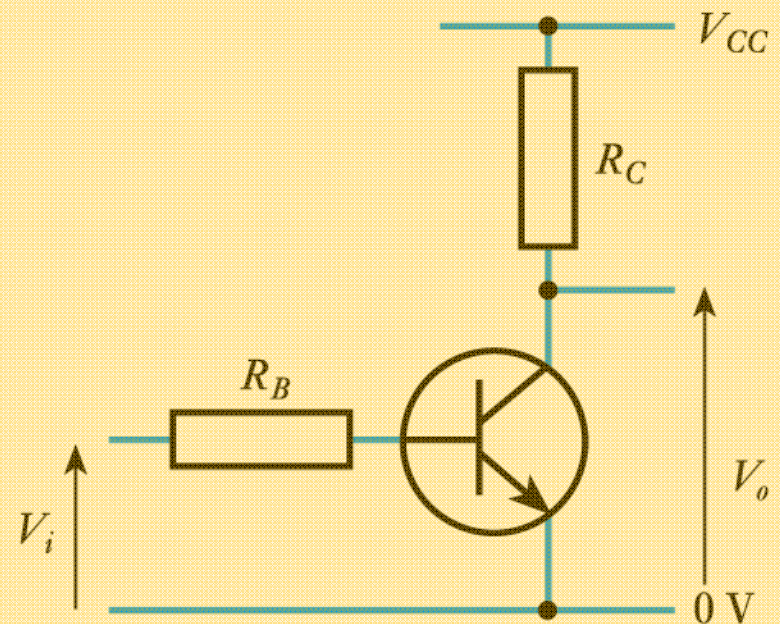- **A logical switch**
- $V_i$  low, transistor off
  - $V_o$  is at  $V_{CC}$
  - can source current to load
- $V_i$  high, transistor on
  - $V_o$  is drawn to ground
  - Can sink current from load
- Basis of TTL logic  
(transistor-transistor logic)






Video 19E Further Study
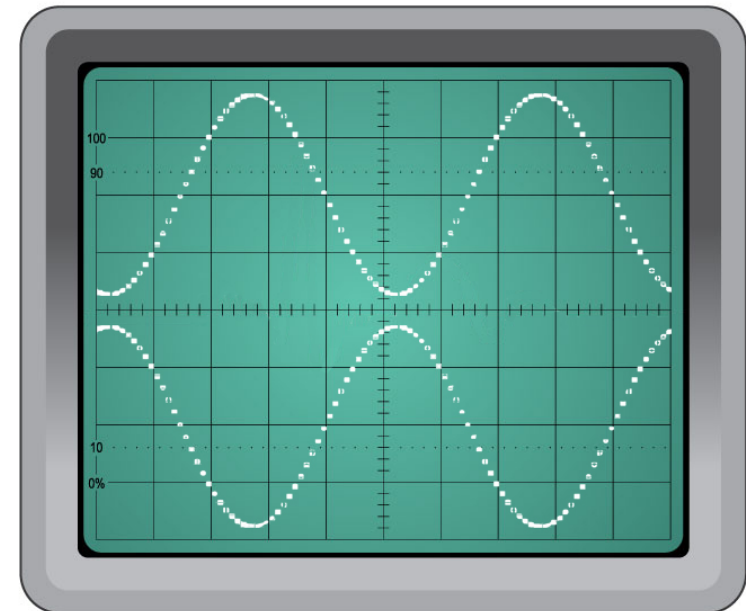
## Further Study

- The Further Study section at the end of Chapter 19 looks at the design of a phase splitter.
- We considered a simple circuit earlier, but this suffers from the fact that its two outputs have very different output resistances.
- Design an arrangement to overcome this problem and then compare it with that shown in the video.



19.18

## Key points


---

- Bipolar transistors are widely used in both analogue and digital circuits
- They can be considered as either voltage-controlled or current-controlled devices
- Their characteristics may be described by their gain or by their transconductance
- Feedback can be used to overcome problems of variability
- Many amplifier circuits use transistors in a common-emitter configuration where the input is applied to the base and the output is taken from the collector
- Common-collector circuits make good buffer amplifiers
- Bipolar transistors are used in a wide range of applications


## FET vs. BJT

- Device characteristics mean  $FET-R_i \gg BJT-R_i$ 
  - No current flow into FET gate, small  $I_B$  in BJT
- Current output  $\propto V_{gs}$  or  $V_{be}$


– FET

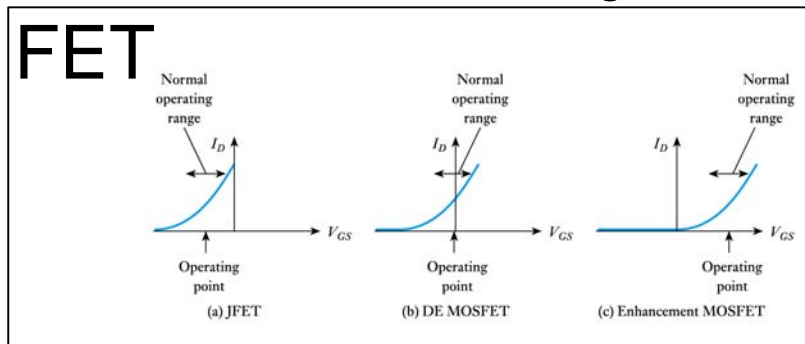

BJT

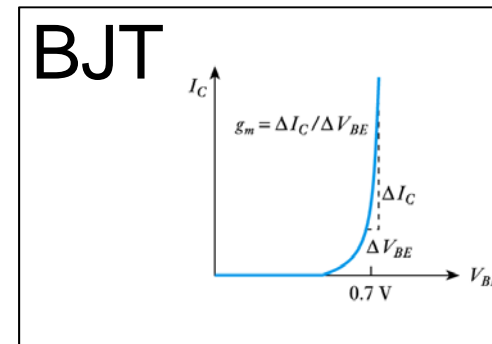

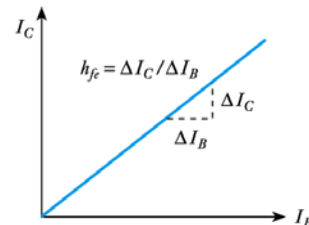- But Base current in BJT  $I_B \approx \text{constant} \cdot e^{40 \cdot V_{BE}}$ 
  - So BJT looks like a linear current amp
  - makes biasing easy





# Comparison of FET and Bipolar

---


	Field Effect Transistor (FET)	Bipolar Junction Transistor (BJT)
1	Low voltage gain	High voltage gain
2	High current gain	Low current gain
3	Very high input impedance	Low input impedance
4	High output impedance	Low output impedance
5	Low noise generation	Medium noise generation
6	Fast switching time	Medium switching time
7	Easily damaged by static	Robust
8	Some require an input to turn it "OFF"	Requires zero input to turn it "OFF"
9	Voltage controlled device	Current controlled device
10	Exhibits the properties of a Resistor	
11	More expensive than bipolar	Cheap
12	Difficult to bias	Easy to bias

# Noise and Electromagnetic Compatibility



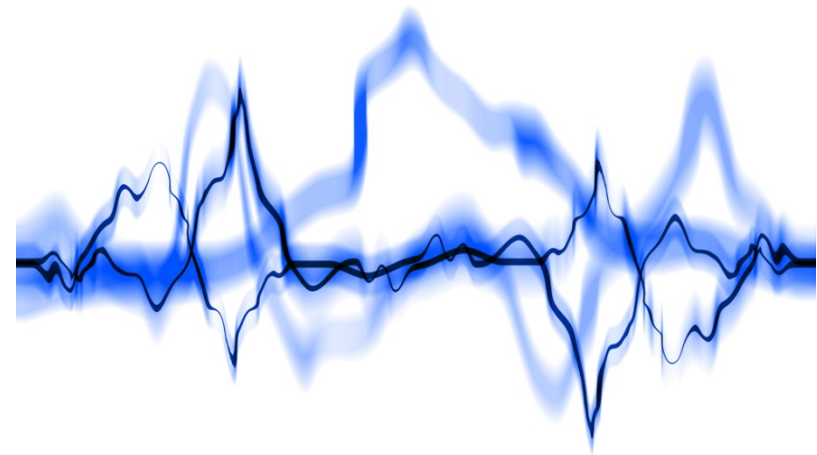
## Chapter 22

- Introduction
- Noise sources
- Representing noise sources within equivalent circuits
- Noise in bipolar transistors
- Noise in FETs
- Signal-to-noise ratio
- Noise Figure
- Designing for low-noise applications
- Electromagnetic compatibility
- Designing for EMC



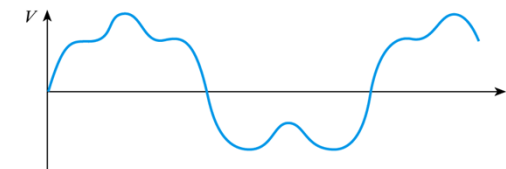
# Introduction


- All systems add noise to the signals that pass through them
- Noise is **random** and not repeatable
- Noise can often be removed from digital signals but this is often impossible with analogue signals




(a) Original analogue signal

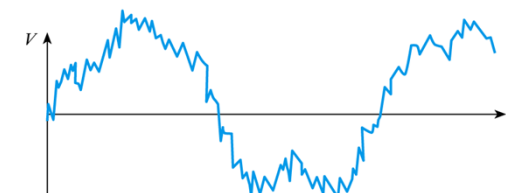

(b) Analogue signal with noise

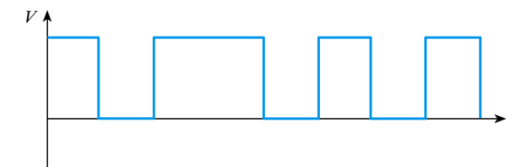

(c) Original digital signal

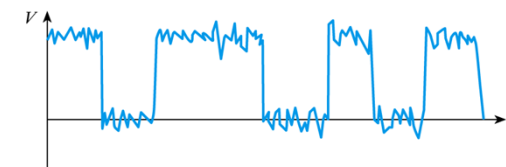

(d) Digital signal with noise



Video 22A



22.2


## Noise sources

### ■ Thermal noise


- all components that have resistance,  $R$ , and temperature,  $T$ , produce thermal noise in the voltage across the resistor

$$V_{n(\text{rms})} = (4k \cdot T \cdot R \cdot B)^{1/2}$$

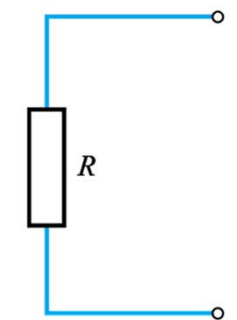- thermal noise is both **white** and **Gaussian** over our measurement bandwidth,  $B$ .
- a ‘noisy’ resistor can be modelled by an ideal noiseless resistor in series with a voltage generator



(a) A ‘noisy’ resistor

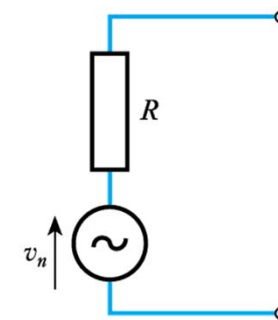

(b) Equivalent circuit

19.24



This current noise will appear, for example, in the currents flowing across pn-junctions  
If that junction is part of a high-gain transistor amplifier, the noise will also be amplified

---


## ■ Shot noise

- the current flowing in a circuit is made up of a large number of individual charge carriers
- with large currents, the averaging effect gives the impression of a continuous and constant stream
- for smaller currents the granular nature of the current is more apparent
- the statistical nature of the flow gives rise to a noise current, the magnitude of which is given by

$$I_{n(\text{rms})} = (2eBI)^{1/2}$$

- shot noise is both white and Gaussian

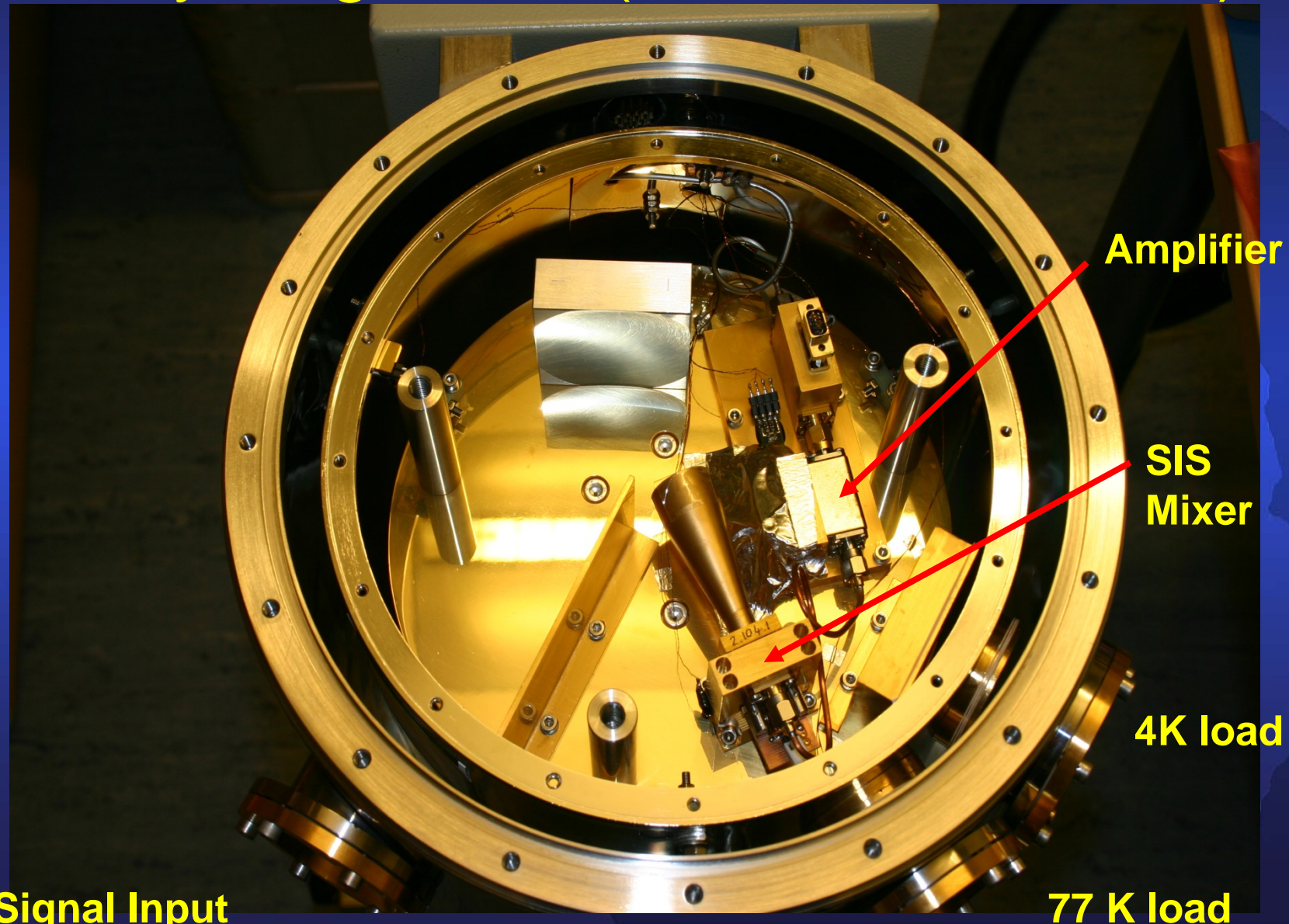One way to beat thermal noise: cool everything to 4 K (250 GHz detector)



---

## ■ 1/f noise

- produced by a number of noise sources
- power spectrum is inversely proportional to frequency (falls as 3dB/octave)
- this form of noise is called ‘pink’ noise (more noise at low frequency)
- one form of 1/f noise is **flicker noise** which is caused by the random variations in the diffusion of charge carriers within devices
- other forms include the current-dependent fluctuations of resistance exhibited by all real resistors


---

## ■ Interference


- can take many forms
- can enter the system at any stage
- common noise sources include radio transmitters, AC power cables, lightning, switching transients, mechanical vibrations (particularly in mechanical sensors), ambient light (particularly in optical sensors)
- interference will be discussed in more detail when we look at electromagnetic compatibility

# Representing noise in equivalent circuits 22.3

- An output network with noise

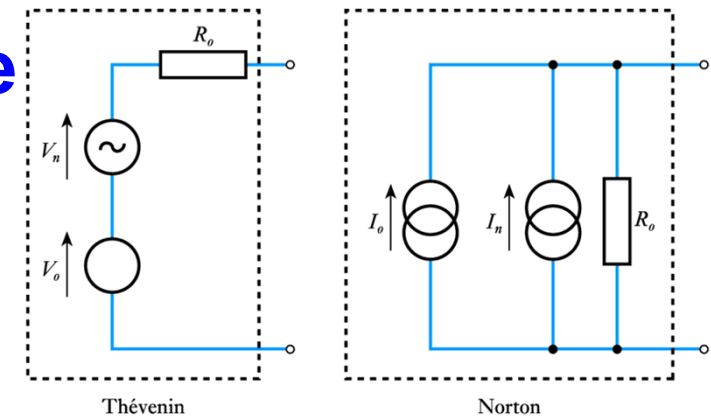


- An Op-amp with noise

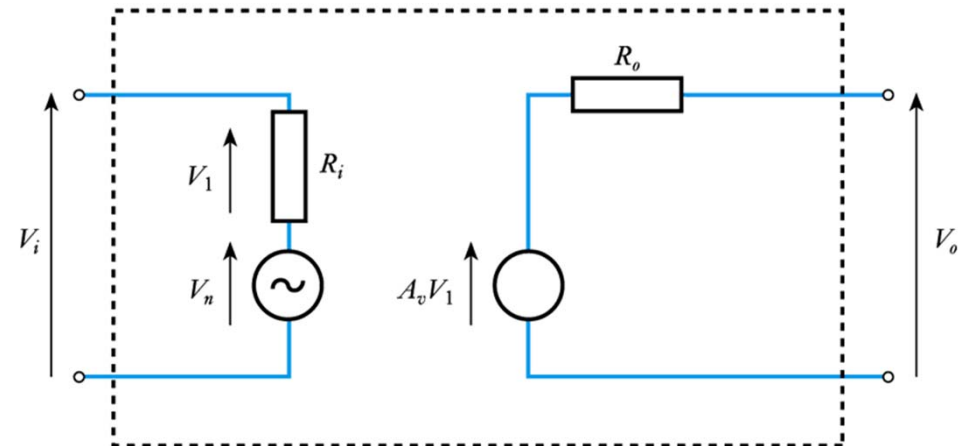
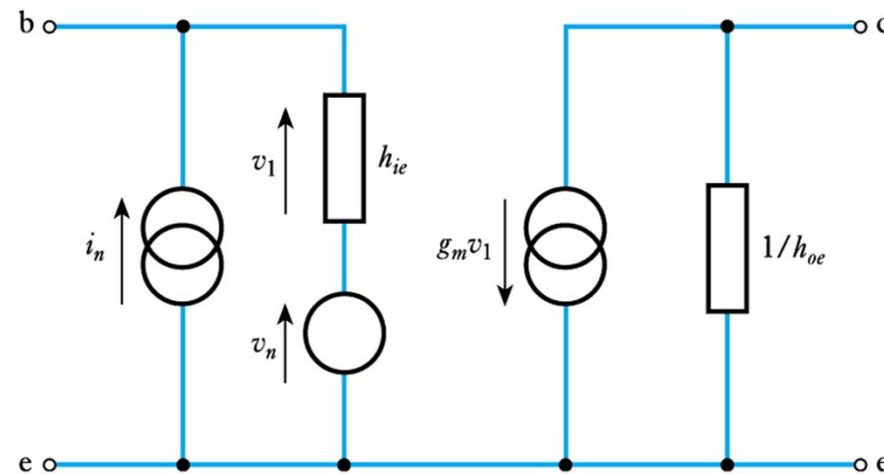
# Noise in bipolar transistors

- Caused by a number of mechanisms
  - thermal noise (produced by resistances in the materials)
  - shot noise (produced by the currents across the junctions)
  - flicker noise (caused by fluctuations in the diffusion process) This is largest at low frequencies ( $1/f$ )





22.5

## Noise in FETs

---

- **Caused by a number of mechanisms**
  - noise in FETs is normally dominated by **flicker noise** (particularly at low frequencies) and by **thermal noise** resulting from the resistance of the channel
  - shot noise is normally insignificant, as in MOSFETs there is no junction, and in JFETs the only currents across the gate junction are those caused by leakage

19.31





22.6

# Signal-to-noise ratio

- **A measure of signal quality**
  - from earlier we know that
$$\text{S/N ratio} = 20 \log_{10} \left( \frac{V_s}{V_n} \right) \text{ dB}$$
  - in many cases noise is made up of different components, because of their random nature they cannot simply be added
  - instead we must add squares of the rms voltages (which are related to the noise power) then take the square root to obtain the rms voltage of the combination

$V_s$  and  $V_n$  are rms values  
Usually quote  $\text{max-S/N} \propto \text{max}(V_s)$

$$V_n = \sqrt{V_{n1}^2 + V_{n2}^2}$$

19.32



# Noise figure

- **A measure of circuit performance**

- S/N ratio can be used to indicate the quality of a signal, but not to describe how well an amplifier, or other circuit, performs regarding noise
- (Noise of source + all amplifier noise sources) / (noise of source)
- this can be done using the noise figure

$$NF = 10 \log_{10} \frac{\text{noise output power from amplifier}}{\text{noise output power from noiseless amplifier}}$$

$$NF = 20 \log_{10} \frac{\text{rms noise output voltage from amplifier}}{\text{rms noise output voltage from noiseless amplifier}}$$

19.33



22.8

# Designing for low-noise applications

## ■ A number of issues are of importance

- often it is the noise of the **first stage** that dominates the performance of the entire system
- the **source resistance** is important: **optimum**
- bipolar transistors can produce good low-noise circuits with source resistances from a few hundred ohms to few hundred kilohms
- FETs can produce good low-noise circuits with source resistances from a few tens of kilohms up to several hundred megohms
- Low  $R_S \Rightarrow$  bi-polar; High  $R_S \Rightarrow$  FET

$$R_s = \sqrt{\frac{V_n^2}{I_n^2}}$$

19.34

So far we have looked at self-generated noise. What about pick-up noise

## Electromagnetic compatibility



Video 22B




22.9

- Examples of EMC problems



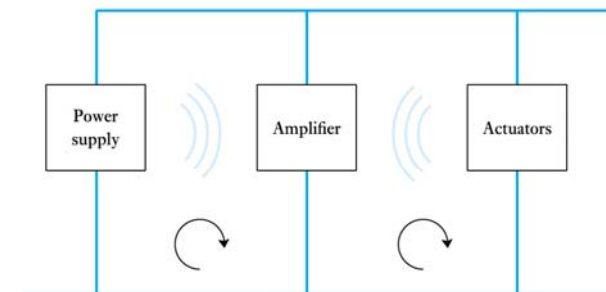(a) An external noise source causes problems



(b) One part of a system interferes with another



(c) A system interferes with the operation of other equipment

19.35

# Electromagnetic compatibility






Video 22B




22.9

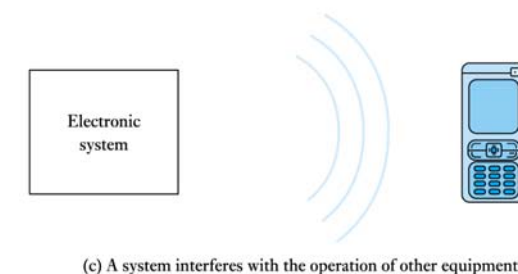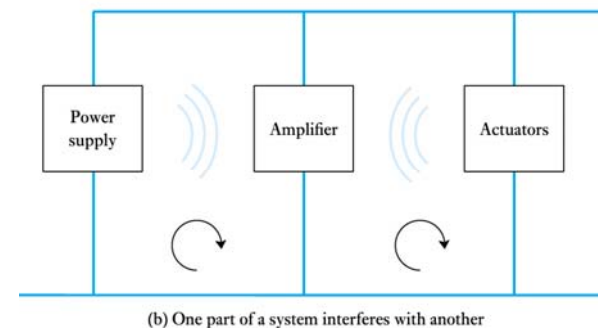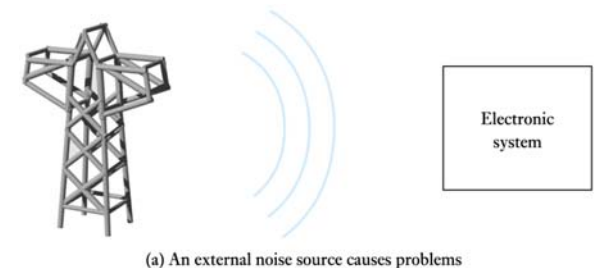- Examples of EMC problems
- Generally, noise at  $f < 30$  MHz is conducted (“in wire”)
- Noise at  $f > 30$  MHz, or transients can be radiated
- Current loops  $\Rightarrow$  magnetic dipole radiation




19.36
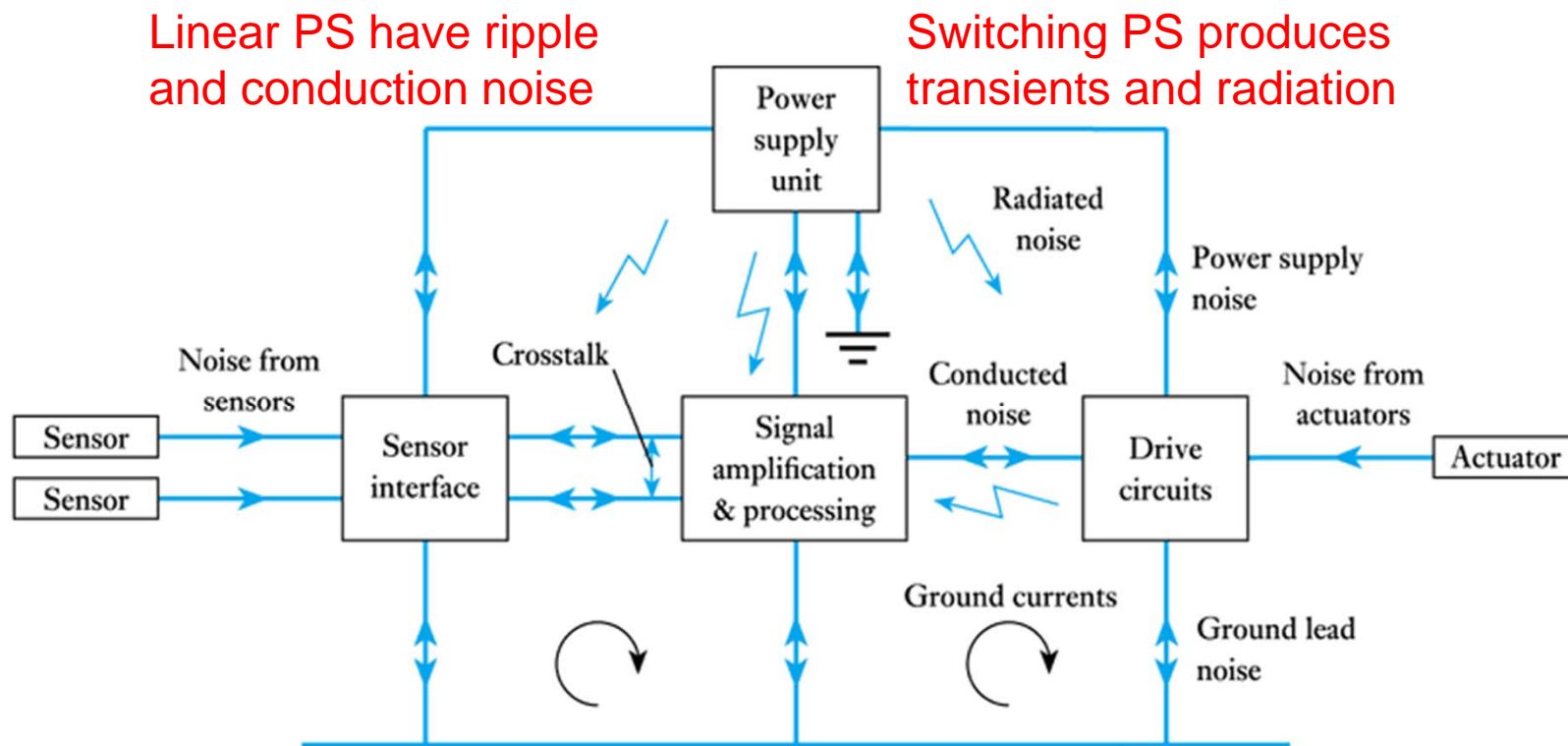
## ■ Electromagnetic coupling between stages





# Designing for EMC

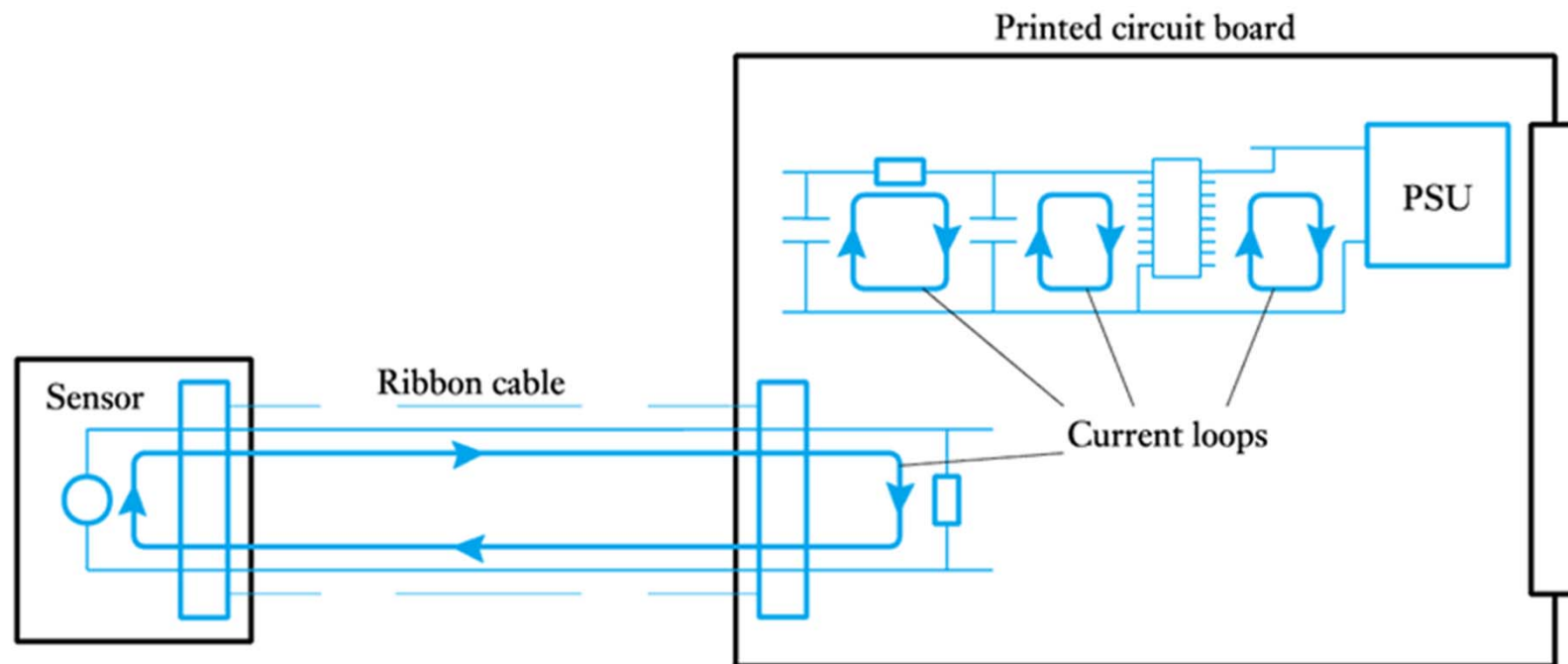
- Examples of current loops within circuits



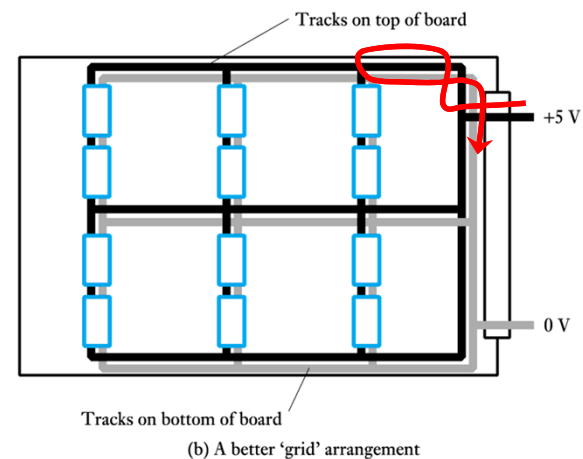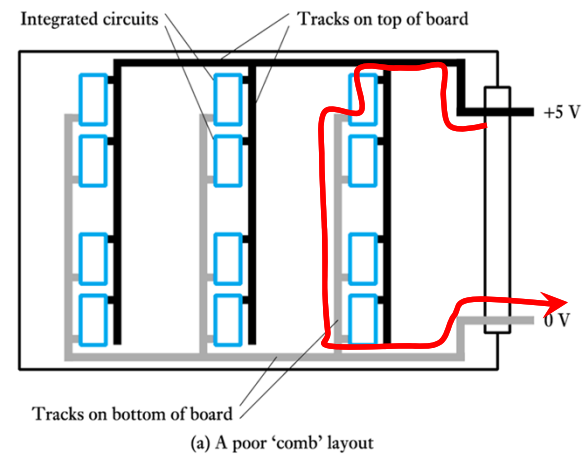- Examples of power supply routing methods
- 2-Rail technique can allow large current loops to form
- Better to use grid
- Use rounded corners to reduce field strength
- Extend to power plane and ground plane in multi level boards




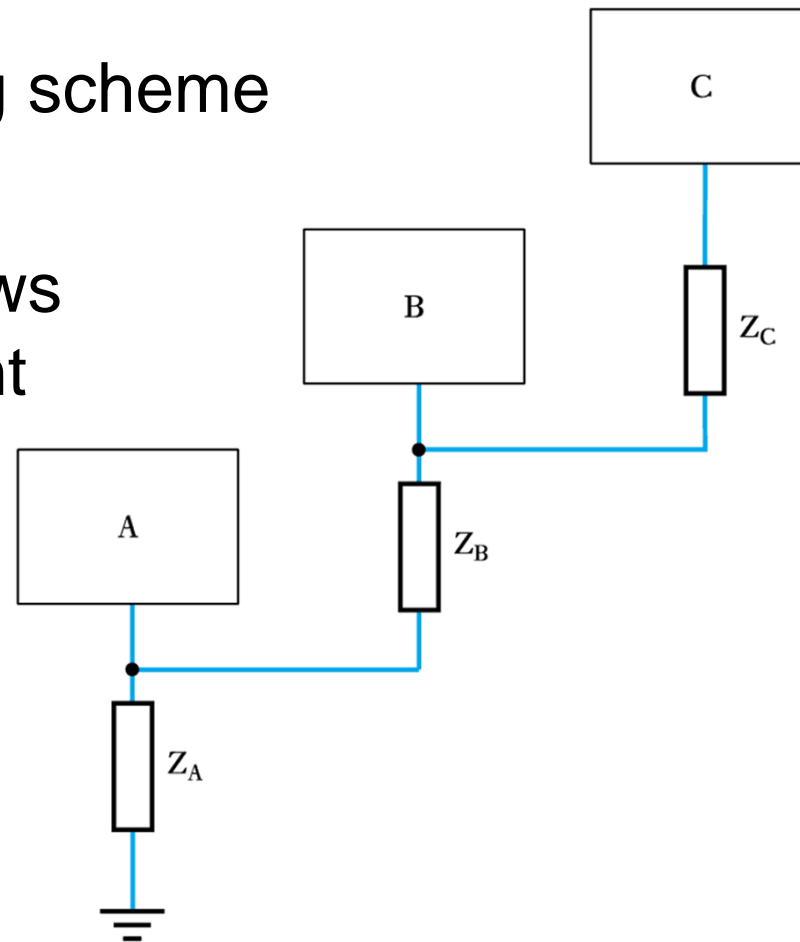- A simple series grounding scheme
- If module B suddenly draws power, large return current will raise the potential of the ground point in A





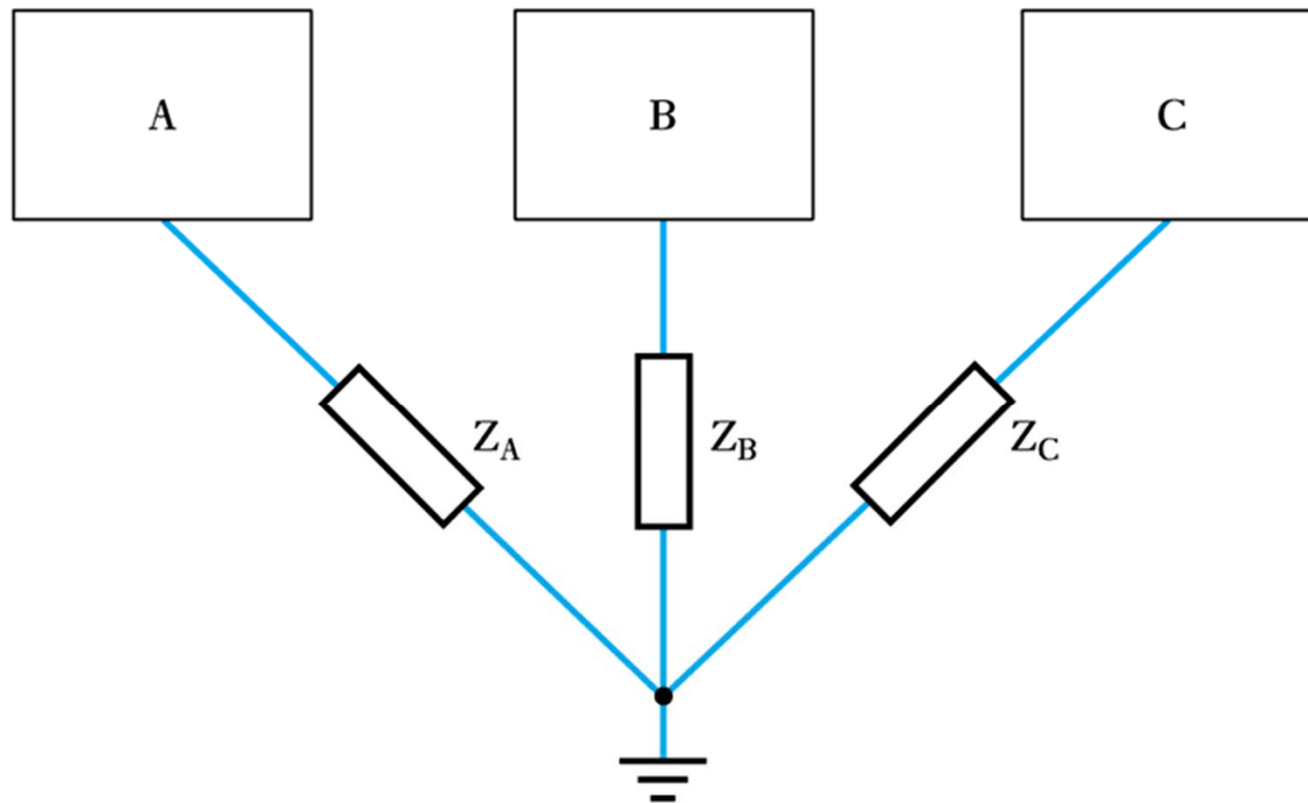- A single-point grounding scheme uncouples modules




---

- System partitioning to reduce EMC problems


Less sensitive to noise  
But better at producing it!  
Clock signals & switching

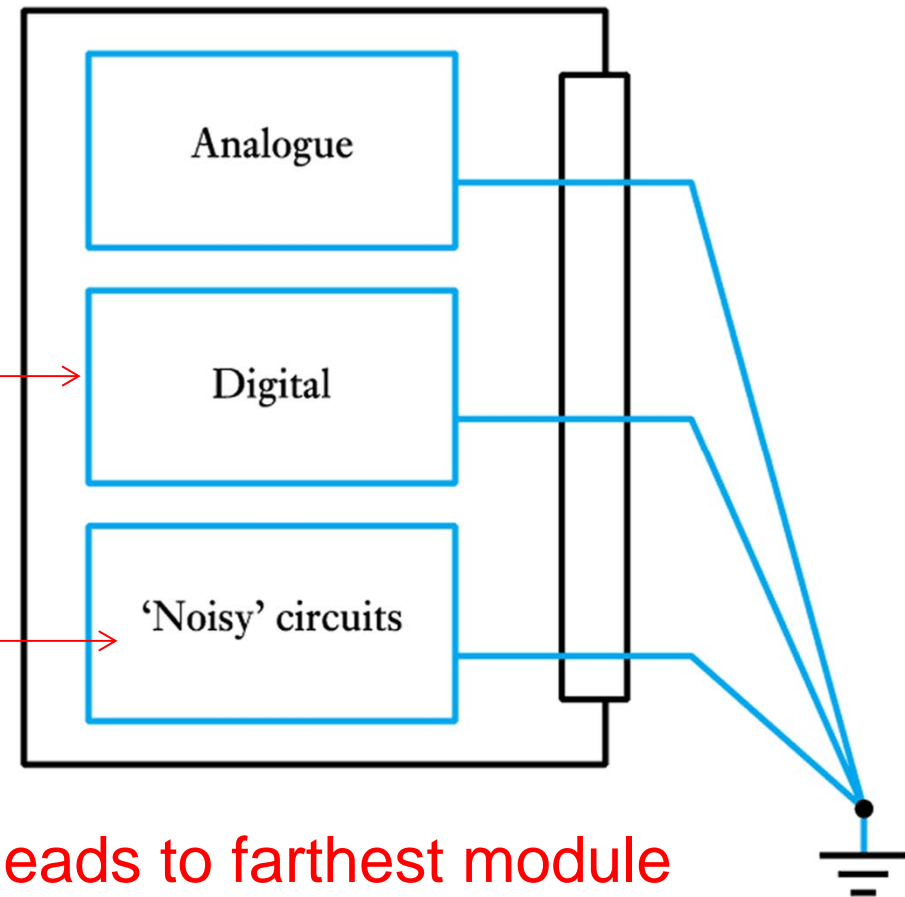E.g. power supplies,  
oscillators, relays etc.




But can create long ground leads to farthest module

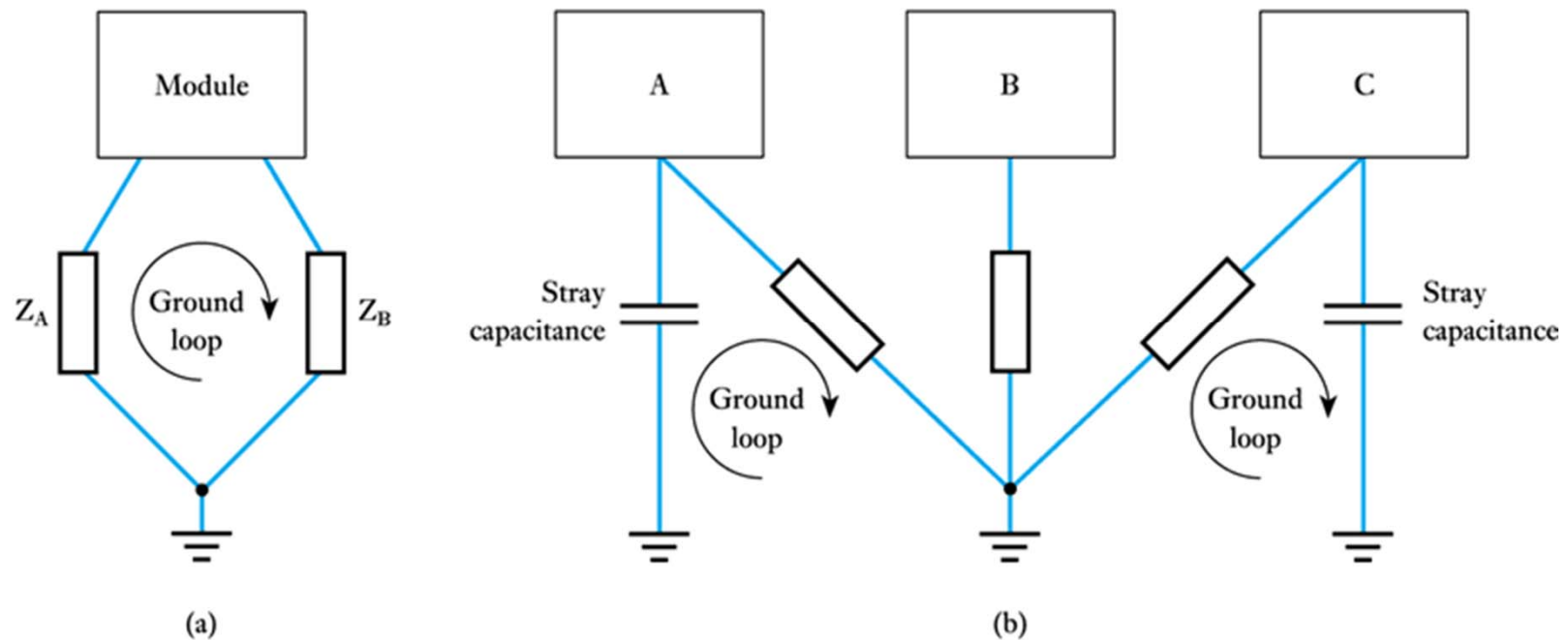- Multiple paths to ground create Ground loops
- Stray capacitance at high frequency ( $> 1$  MHz) can create loops where you least expect them




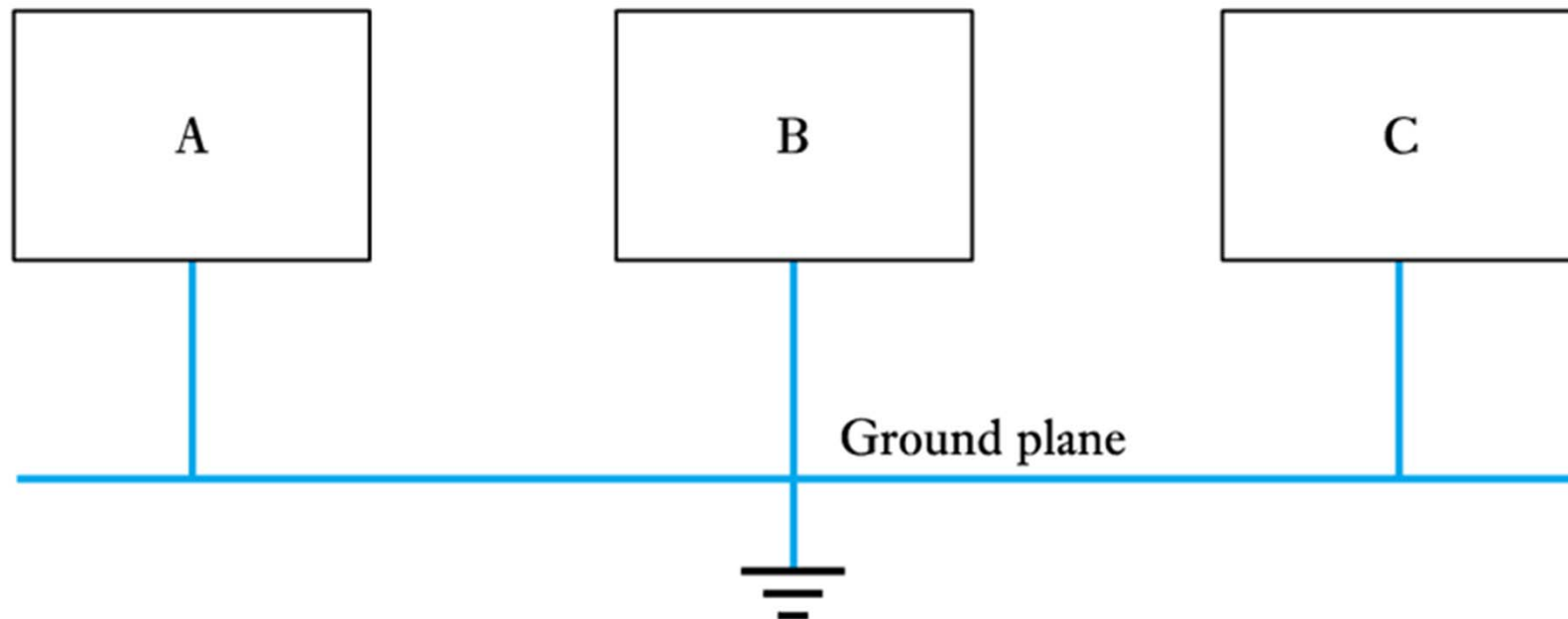- A multipoint grounding scheme (good at high frequencies or modules where you don't know how they are grounded internally)



- Cable-screening techniques

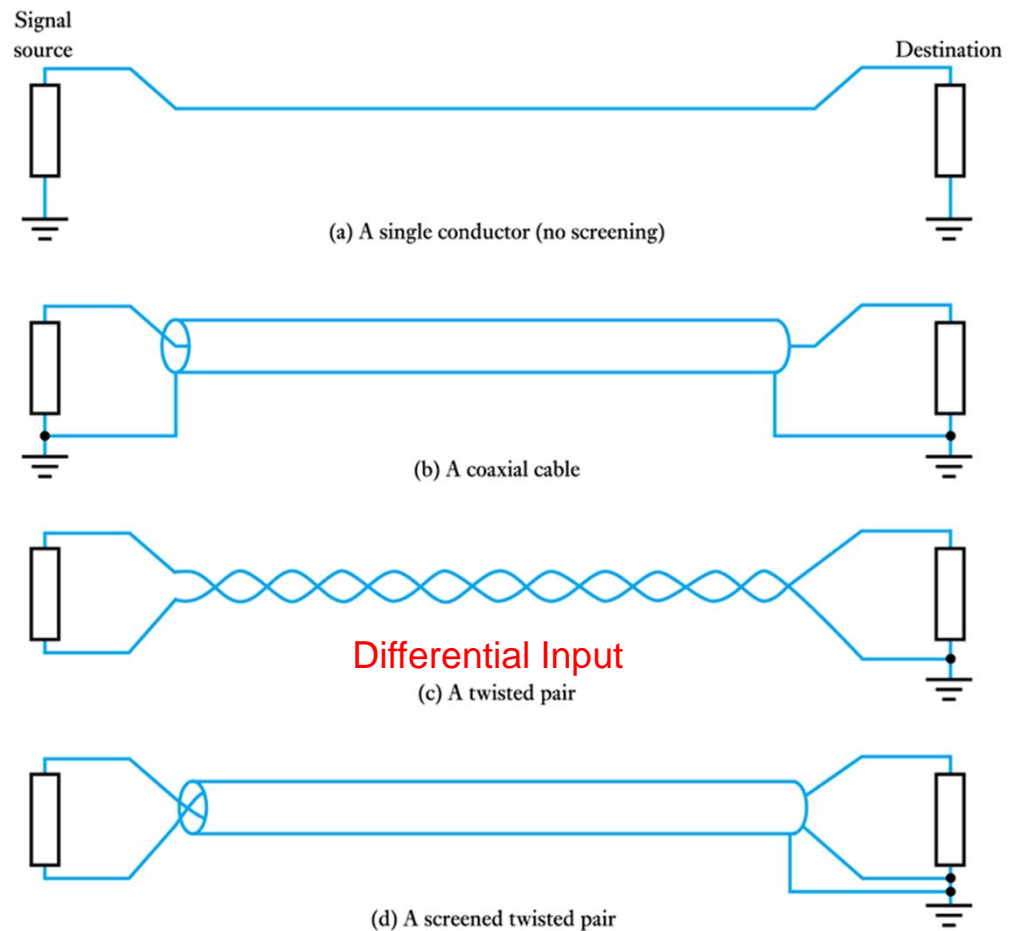- Can have separate Signal and Chassis grounds, tied at a single point.





Video 22C Further Study

## Further Study

---

- The Further Study section at the end of Chapter 22 considers the implications of EMC for safety critical systems, such as those found within cars.
- Identify some of the safety-related systems within a modern car and consider how EMC related factors could affect their operation. Then, watch the video for a discussion of some of the issues involved.



## Key points

---

- Noise in electronic circuits can be of various forms, including thermal noise, shot noise,  $1/f$  noise and interference
- Both bipolar transistors and FETs suffer from noise
- Electromagnetic compatibility (EMC) is concerned with the ability of a system to operate in the presence of interference and to not interfere with other equipment (or itself)
- Circuit layout plays a major role in determining EMC performance