



## Last time: Sequential logic

---

- Introduction
- Bistables
- Monostables or one-shots
- Astables
- Timers
- Memory registers
- Shift registers
- Counters



# Introduction



Video 25A




25.1

- Sequential logic is built with combinational logic elements
- Combines the characteristics of combinational logic with **memory**
- When constructing sequential logic circuits our building blocks are often some form of **multivibrator**
  - A term used to describe a range of circuits
    - these have two outputs that are the inverse of each other
    - the output are labelled  $Q$  and  $\bar{Q}$
    - three basic forms:
      - **Bistables (flip-flops or latches)**
      - **Monstables (one-shots)**
      - **Astables (digital oscillators)**

**25.2**
 
## Monostables or one-shots

- Monostables are another form of multivibrator
  - while **bistables** have two stable output states that we can switch between
  - **monostables** have one stable & one metastable states
    - when in its stable state  $Q = 0$
    - when an appropriate signal is applied to the trigger input ( $T$ ) the circuit enters its metastable state with  $Q = 1$
    - after a set period of time (determined by circuit components) it reverts to its stable state
    - it is therefore a **pulse generator**



Circuit symbol

Initially in stable state:

T low and Q low  $\Rightarrow$  !Q high

No current flows across R

(both sides of C at same voltage,  $\Delta V_c = 0$ )

$V_1$  floats high keeping Q low

## ■ A simple monostable

Then trigger to metastable:

T goes high briefly  $\Rightarrow$  !Q goes low


Capacitor initially has no charge  
and so no voltage across it

So  $V_1$  drops to 0  $\Rightarrow$  Q goes high, keeping !Q low


Current flows through R,  
charging the capacitor

$V_1$  increases until Q goes low

System returns to stable state


 


(a) Logic circuit

 

 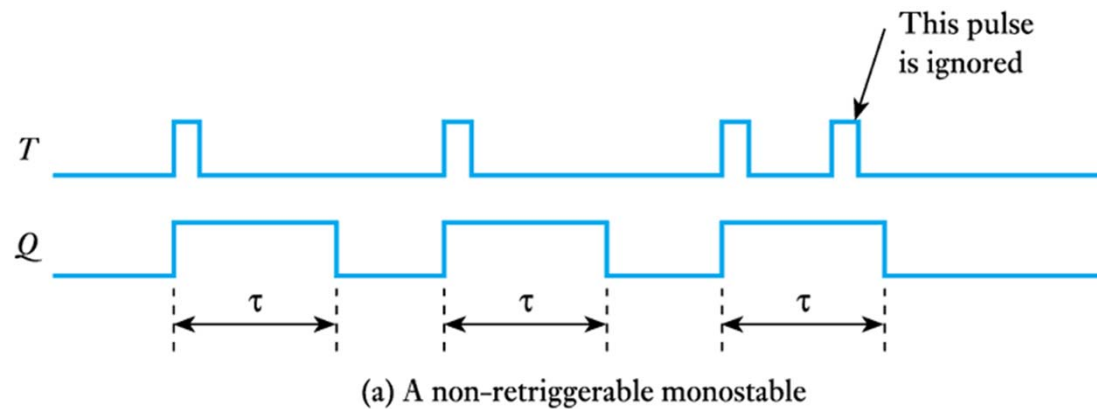(b) Waveform diagram

- Monostables can be **retriggerable** or **non-retriggerable**




# Astables


---

- The last member of the multivibrator family is the **astable**
  - this has two metastable states
  - has the function of a **digital oscillator**
  - circuit spends a fixed period in each state (determined by circuit components)
  - if the period in each state is set to be equal, this will produce a square waveform

- A simple astable arrangement

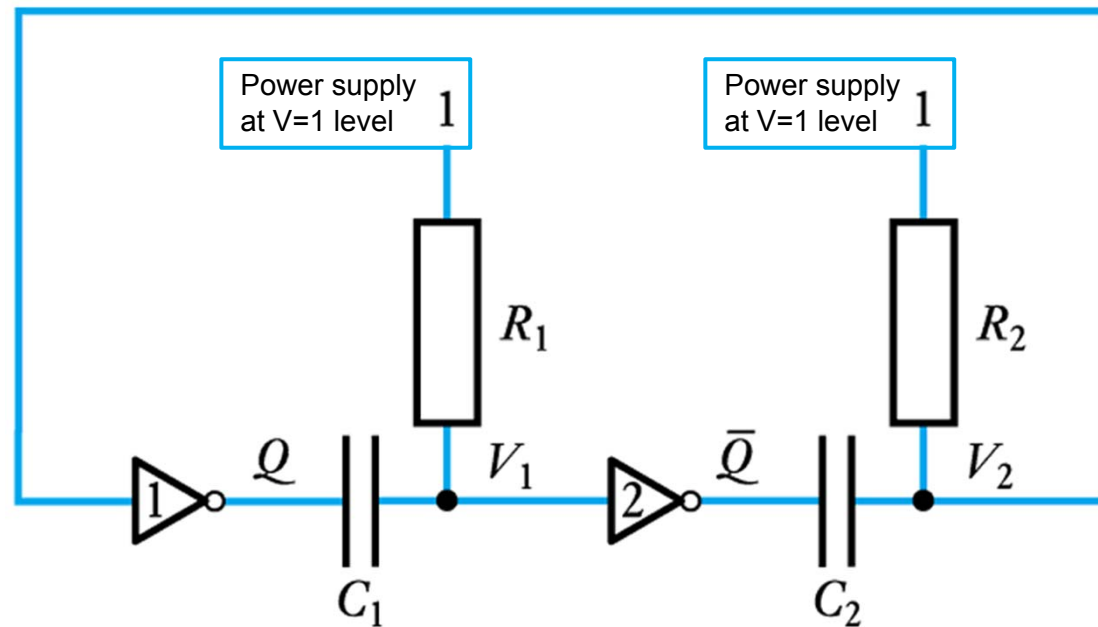

 
## ■ Waveforms of the simple astable circuit



25.8



 


## ■ Waveforms of the simple astable circuit.


(2)  $V_2$  hits trigger point,  
switches  $Q \rightarrow V_1$  Low  
but charging  
sets  $\bar{Q}$  high

(3)  $V_1$  hits trigger point  
switches  $\bar{Q}$  low  $\rightarrow V_2$  Low  
but charging  
sets  $Q$  high

 (1)  $\bar{Q}$  low  $\rightarrow V_2$  Low  
but charging  
keeps  $Q$  high



 How do I get the signal out to the world?




## ■ Waveforms of the simple astable circuit.


(2)  $V_2$  hits trigger point,  
switches  $Q \rightarrow V_1$  Low  
but charging  
sets  $\bar{Q}$  high

(3)  $V_1$  hits trigger point  
switches  $\bar{Q} \rightarrow V_2$  Low  
but charging  
sets  $Q$  high

 (1)  $\bar{Q}$  low  $\rightarrow V_2$  Low  
but charging  
keeps  $Q$  high



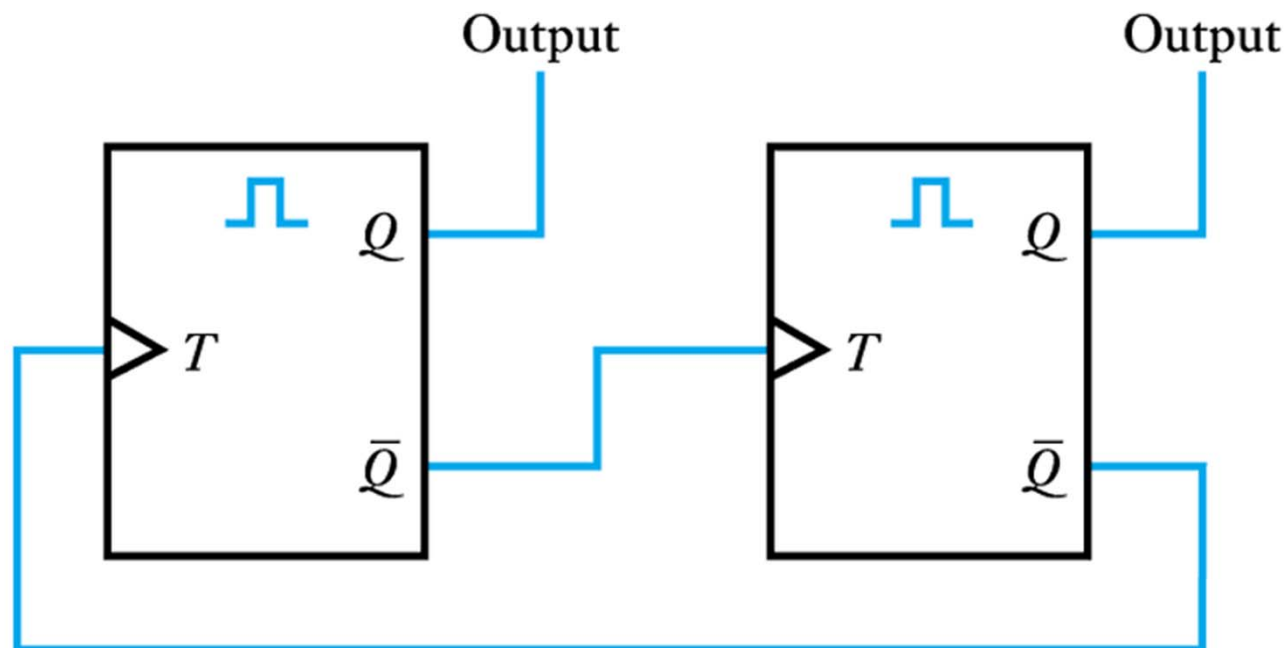- 
- An astable formed by two monostables





25.5


# Timers

---


- The **integrated circuit timer** can produce a range of functions
  - including those of a monostable or astable
  - various devices
  - one of the most popular is the **555 timer**
  - can be configured using just a couple of external passive components
  - internal construction largely unimportant – all required information on using the device is in its data sheet

 **25.12**


- A simplified circuit diagram of the **555 timer** is shown here
  - It consists basically of a flip-flop, two comparators, a switching transistor and a resistive network.



 - The diagram here shows the 555 configured as a monostable.
  - It can be seen that only a couple of external components are needed.



 - Here the 555 is shown configured as an astable
  - Again very few additional components are required.



# Sequential Logic or Multivibrators

## Logic with memory!

---

- **Bistables**  $\Rightarrow$  two stable output states
  - $Q=1$  ( $\bar{Q}=0$ ) and  $Q=0$  ( $\bar{Q}=1$ )
  - Switch between the two with external signals
- **Monostables**  $\Rightarrow$  one stable & one metastable states
  - External trigger switches from stable to metastable state
  - After a time (determined by circuit) return to stable state
- **Astable**  $\Rightarrow$  this has two metastable states
  - Self switches between the two states with time constant determined by circuit components
  - digital oscillator or timer circuit



---

- Questions?



# Today: Sequential logic uses


---

- Introduction
- Bistables
- Monostables or one-shots
- Astables
- Timers
- Memory registers
- Shift registers
- Counters



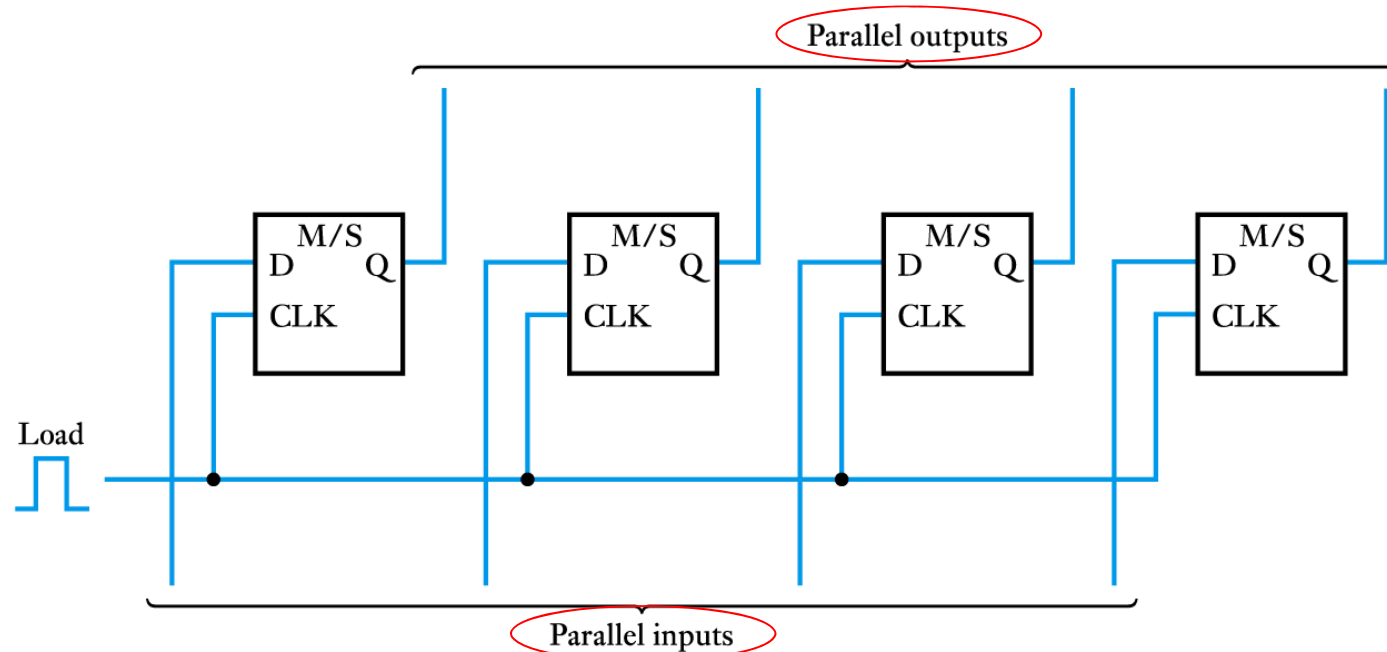
# Memory Registers

- Combining a number of bistables we can construct a **memory register**
  - several forms of bistable can be used, for example:



 - Often we are not concerned with the internal construction of the register
  - they are a standard integrated component



# Shift Registers




Video 25B




25.7

- The operation of a shift register

 



(a) Parallel to serial conversion

 

(b) Serial to parallel conversion

25.21

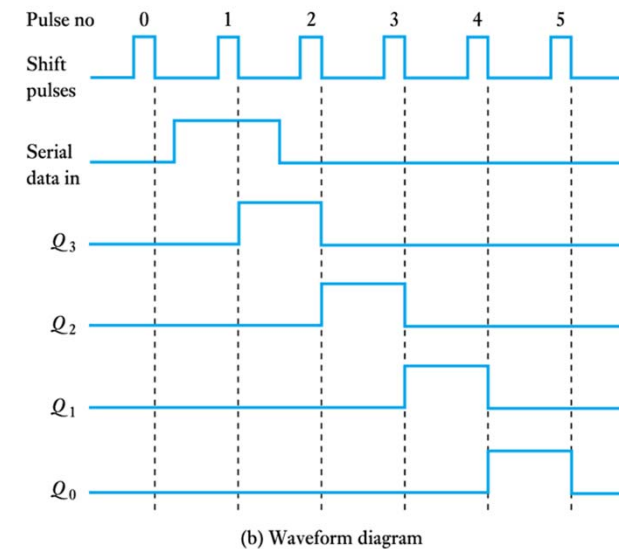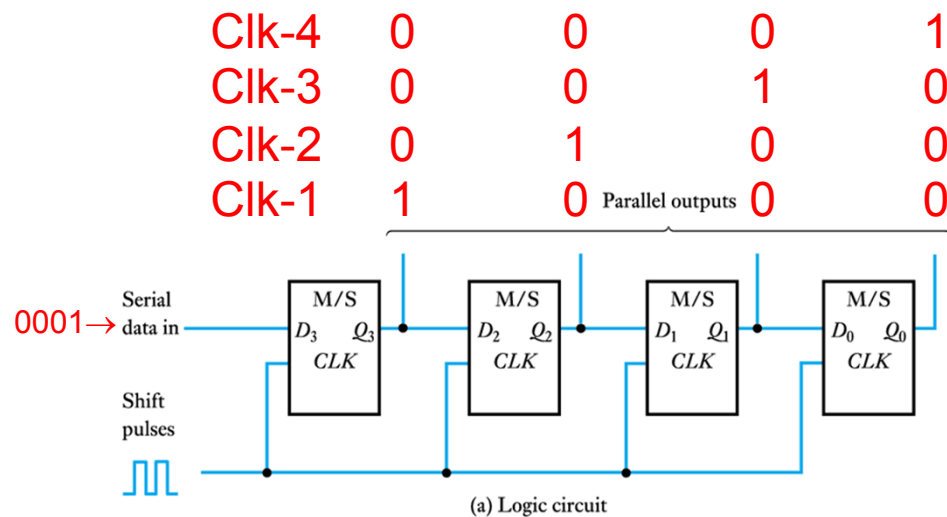
## ■ A simple serial to parallel shift register




Every 4 Clk cycles we need to tell the reader to read the word

Need to change a memory register (parallel in-parallel out)  
 where the D's are independent inputs  
 To a shift register (parallel in-serial out)  
 where D is from the Q output of previous stage
 
## ■ A 4-bit parallel load shift register-



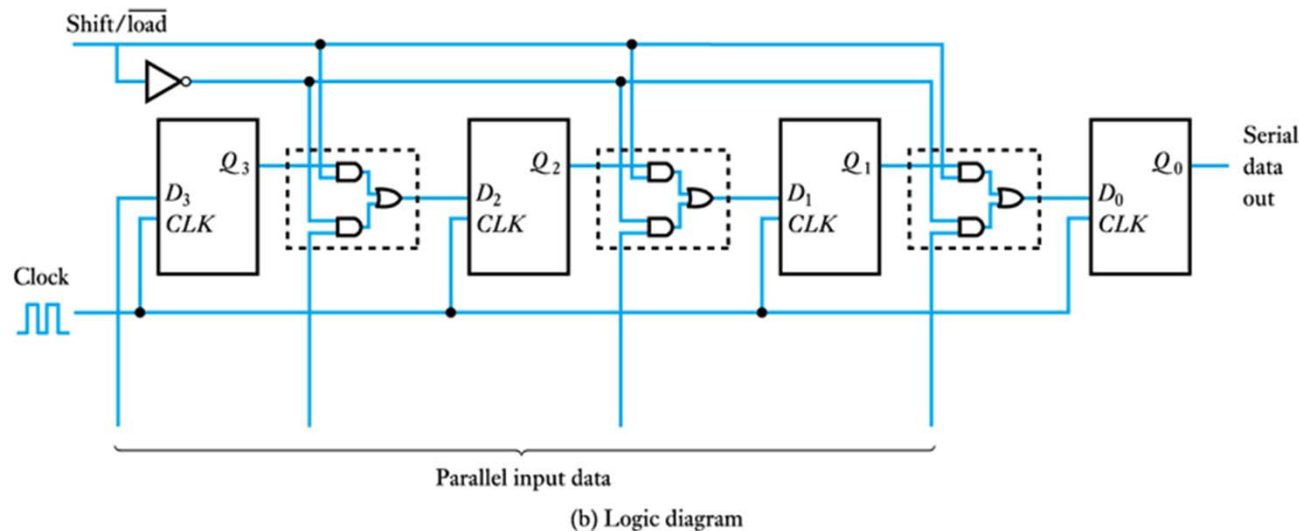Select=1  $\Rightarrow$  X = A  
 Select=0  $\Rightarrow$  X = B



Select=0  $\Rightarrow$  Each D  
 connected to  
 an input line  
**MEMORY REGISTER**


Select=1  $\Rightarrow$  Each D  
 connected to  
 previous stage's  
 output, Q  
**SHIFT REGISTER**

25.23

- A design example - see **Example 25.3** in course text
 
## Application of a shift register

- shift registers are widely used in communications systems





# Counters




Video 25C



25.8
 
## ■ Ripple counters


- can be constructed using several forms of bistable
- consider the following arrangement
- with  $J = K = 1$  each bistable toggles on the falling edge of its clock input



25.25

Remember our 4-bit serial to parallel converter  
Wanted to tell reader to read on every 4<sup>th</sup> clock fall  $\Rightarrow Q_1$

---

 


- Each stage toggles at half the frequency of the previous one
  - acts as a frequency divider
  - divides frequency by  $2^n$  (where  $n$  is the number of stages)

- A design example - see **Example 25.4** in course text
 
## Clock generator for a digital watch

- 15-stage counter divides signal from a crystal oscillator by 32,768 to produce a 1 Hz signal to drive stepper motor or digital display




- Consider the pattern on the outputs of the counter shown earlier – displayed on the right
- the outputs count in binary from 0 to  $2^n-1$  and then repeat
  - the circuit acts as a **modulo- $2^n$  counter**
  - since the counting process propagates from one bistable to the next this is called a **ripple counter**
  - circuit shown is a **4-bit** or **modulo-16** (or **mod-16**) ripple counter

Number of clock pulses	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1
16	0	0	0	0
17	0	0	0	1
18	0	0	1	0
19	0	0	1	1
20	0	1	0	0

Reset when you detect the counter has reached a binary value.  
Mod10 $\Rightarrow 10_{10}=1010$ , so first occasion one see bit 1 and 3 go high, reset

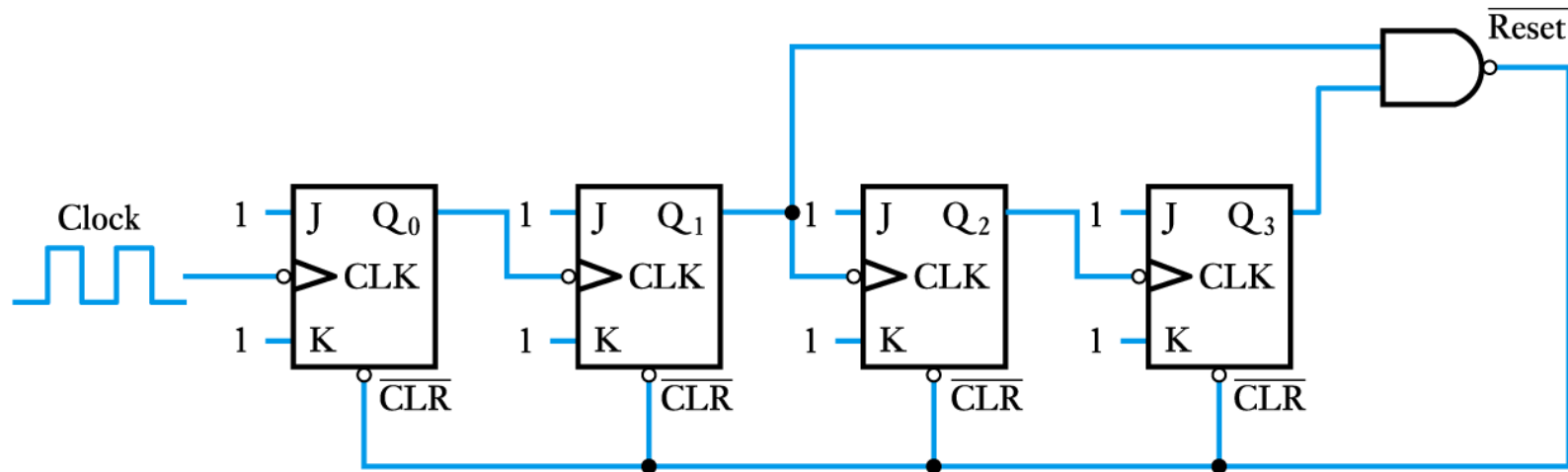
## ■ **Modulo- $N$ counters**

- by using an appropriate number of stages the earlier counter can count modulo any power of 2
- to count to any other base we add reset circuitry
- e.g. the modulo-10 or decade counter shown here




25.29

 
## ■ Waveform diagram for the decade counter



## ■ A ripple down counters

 

(a) Logic diagram

 


(b) Waveform diagram

- The output sequence of the ripple-down counter

Number of clock pulses	$Q_3$	$Q_2$	$Q_1$	$Q_0$	Count
0	0	0	0	0	0
1	1	1	1	1	15
2	1	1	1	0	14
3	1	1	0	1	13
4	1	1	0	0	12
5	1	0	1	1	11
6	1	0	1	0	10
7	1	0	0	1	9
8	1	0	0	0	8
9	0	1	1	1	7
10	0	1	1	0	6
11	0	1	0	1	5
12	0	1	0	0	4
13	0	0	1	1	3
14	0	0	1	0	2
15	0	0	0	1	1
16	0	0	0	0	0
17	1	1	1	1	15
18	1	1	1	0	14
19	1	1	0	1	13
20	1	1	0	0	12



## ■ An up/down counter

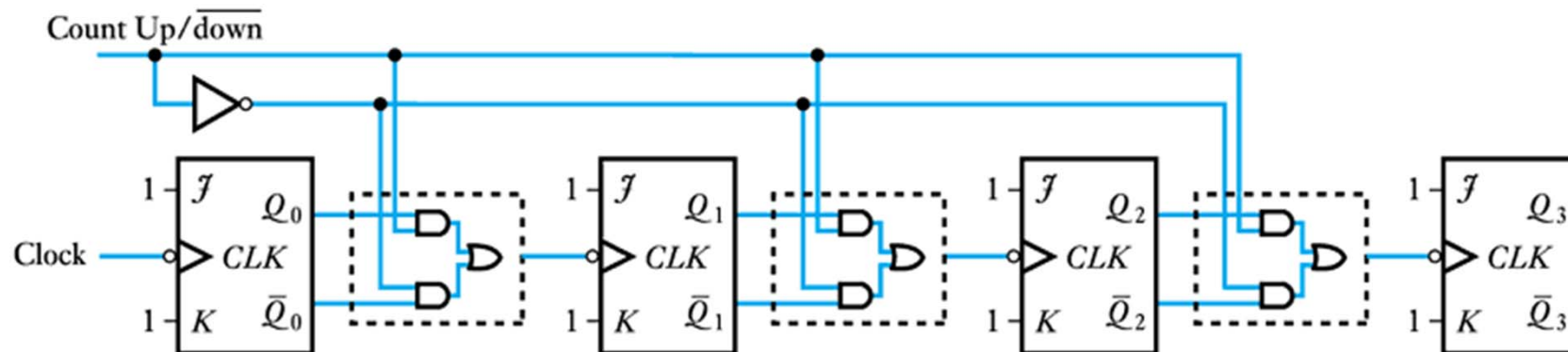


---

## ■ Propagation delay in ripple counters

- while ripple counters are very simple they suffer from problems at high speed
- since the output of one flip-flop is triggered by the change of the previous device, delays produced by each flip-flop are summed along the chain
- the time for a single device to respond is termed its **propagation delay time**  $t_{PD}$
- an  $n$ -bit counter will take  $n \times t_{PD}$  to respond
- if read before this time the result will be garbled
 
## Counters (contd.)

- With a ripple counter, what we really have at each transition is a slight delay from clock fall to output  $Q_n$  change:
- But each output  $Q_n$  change is the clock to the next stage, which adds its own delay from this clock fall to its output  $Q_{n+1}$ !



So since each output feeds that delay into next clock:  
Final bit has the delay of  $gate_0$ ,  $gate_1$ ,  $gate_2$  and  $gate_3$


25.35

---

## ■ Synchronous counters


- these overcome the propagation delay in ripple counters by connecting all the flip-flops to the same clock signal
- thus each stage changes state at the same time
- additional circuitry is used to determine which stages change state on each clock pulse
- faster than ripple counters but more complex
- available in many forms including up, down, up/down and modulo- $N$  counters

## ■ A synchronous four-stage counter

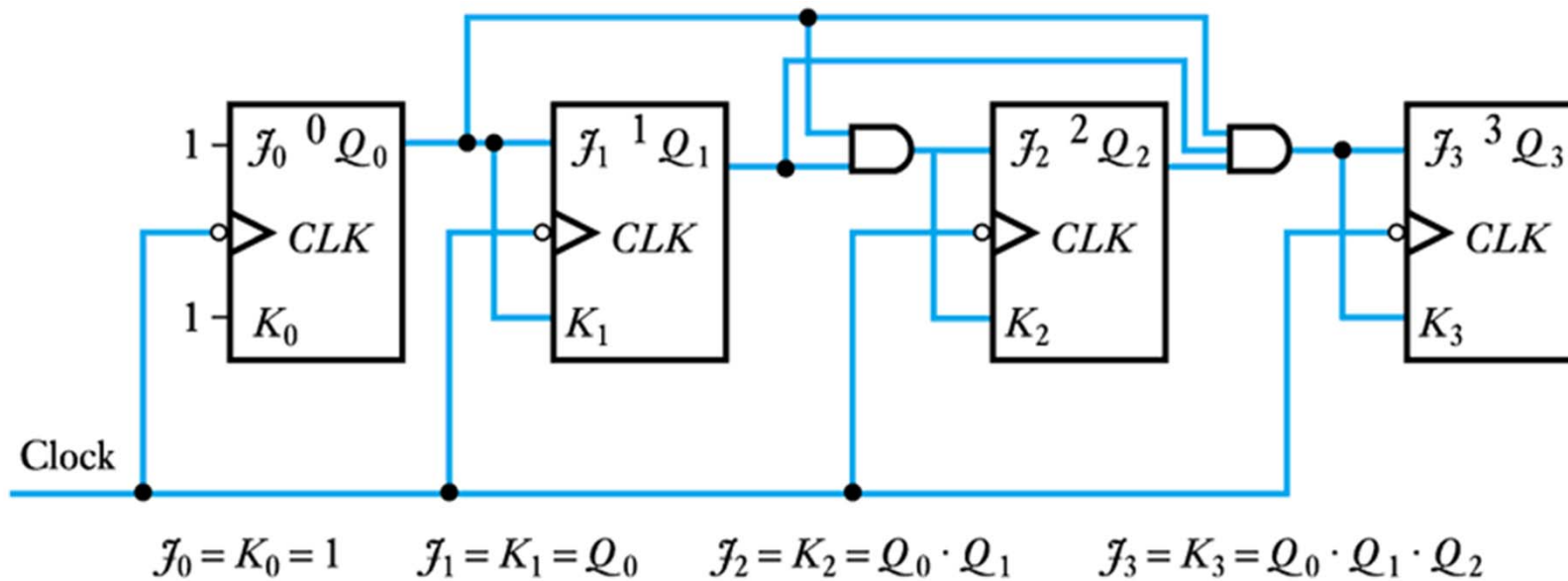


---

- A cascadable 4-bit synchronous counter

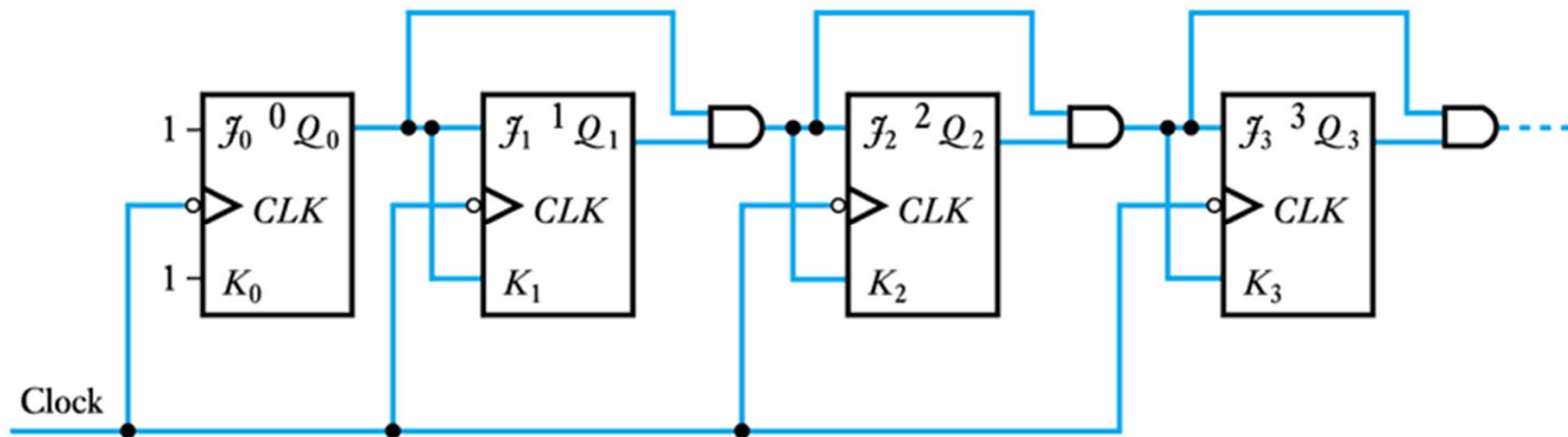
 
## ■ Integrated circuit counters

- while we can build counters from flip-flops, we more often use dedicated ICs
- these are available in numerous forms, such as binary, decade, BCD, up, down and up/down
- they are normally designed to simplify cascading





25.9

# Design of Sequential Logic Circuits

---

- Sequential systems may be **synchronous** or **asynchronous**
  - the design stages involved are similar, although synchronous design is slightly easier
  - the major elements of synchronous design are
    - identification of the system states
    - a state transition diagram
    - a state transition table
    - state reduction
    - state assignment
    - generation of an excitation table
    - circuit design
    - investigation of unused states

25.40





Video 25D Further Study

## Further Study

---

- The **Further Study** section at the end of Chapter 25 looks at the design of a digital stopwatch.
- The watch has a display showing seconds and minutes, and three pushbuttons.
- Apply the techniques described in this lecture to design such a watch, then compare your design with that given in the video.



25.41

## Key points

---

- Sequential logic circuits have the characteristic of memory
- Among the most important groups of sequential components are the various forms of multivibrator
  - bistables
  - monostables
  - astables
- The most widely used form is the bistable which includes
  - latches, edge-triggered flip-flops and master/slave devices
- Registers form the basis of various memories
- Counters are widely used in a range of applications
- Monostables and astables perform a range of functions