

This time

- Review Power in AC circuits (Chapter 7)
- Frequency Characteristics of AC Circuits (Chapter 8)

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013


7.1

Definitions: Sine Waves



Video 2A 2.2

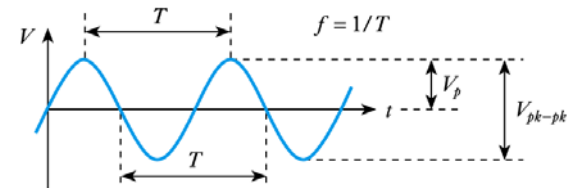- The instantaneous voltage and current v , and i .
– For example: $v(t) = V_p \sin(\omega \cdot t + \phi)$
- Where V_p and I_p are the Peak Voltage and Current
- And $V_{pk-pk} = 2 \cdot V_p$



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.2

r.m.s. value of a sine wave

- the instantaneous power (p) in a resistor is given by

$$p = \frac{v^2}{R}$$

- therefore the average power is given by

$$P_{av} = \frac{[\text{average (or mean) of } v^2]}{R} = \frac{\overline{v^2}}{R}$$

- where $\overline{v^2}$ is the **mean-square voltage**

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.3

- While the mean-square voltage is useful, more often we use the square root of this quantity, namely the root-mean-square voltage V_{rms}

$$\text{– where } V_{rms} = \sqrt{\overline{v^2}}$$

$$\text{– we can also define } I_{rms} = \sqrt{\overline{i^2}}$$

- it is relatively easy to show that (see text for analysis)

$$V_{rms} = \frac{1}{\sqrt{2}} \times V_p = 0.707 \times V_p$$

$$I_{rms} = \frac{1}{\sqrt{2}} \times I_p = 0.707 \times I_p$$

Text writes V_{rms} and I_{rms} as V and I

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.4

- r.m.s. values are useful because their relationship to average power is similar to the corresponding DC values

$$P_{av} = V_{rms} \cdot I_{rms} = VI = \frac{V_p}{\sqrt{2}} \cdot \frac{I_p}{\sqrt{2}}$$

$$P_{av} = \frac{V_{rms}^2}{R} = \frac{V^2}{R} = \frac{V_p^2}{2R}$$

$$P_{av} = I_{rms}^2 R$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.5

Power in Resistive Components



7.2

- Suppose a voltage $v = V_p \sin \omega t$ is applied across a resistance R . The resultant current i will be

$$i = \frac{v}{R} = \frac{V_p \sin \omega t}{R} = I_p \sin \omega t$$

- The result power p will be:

$$p = vi = V_p I_p (\sin^2 \omega t) = V_p I_p \left(\frac{1 - \cos 2\omega t}{2} \right)$$


$$\begin{aligned} \text{and Average Power } P &= \frac{1}{2} V_p I_p \\ &= \frac{V_p}{\sqrt{2}} \times \frac{I_p}{\sqrt{2}} \\ &= VI \end{aligned}$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.6

Positive power \Rightarrow power delivered to the circuit

- Relationship between v , i and p in a resistor

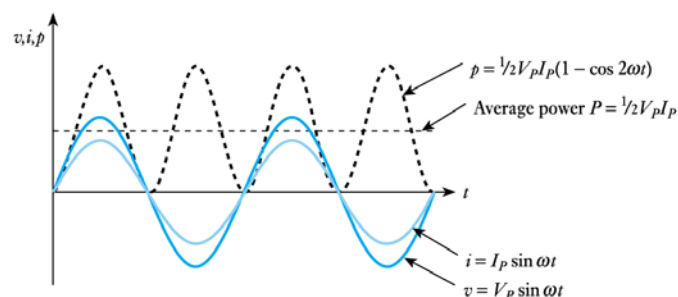Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.7

Power in Capacitors



7.3

- From our discussion of capacitors we know that the current leads the voltage by 90°. Therefore, if a voltage $v = V_p \sin \omega t$ is applied across a capacitance C , the current will be given by $i = I_p \cos \omega t$

- Then

$$\begin{aligned} p &= vi \\ &= V_p \sin \omega t \times I_p \cos \omega t \\ &= V_p I_p (\sin \omega t \times \cos \omega t) \\ &= V_p I_p \left(\frac{\sin 2\omega t}{2} \right) \end{aligned}$$


- The average power is zero

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

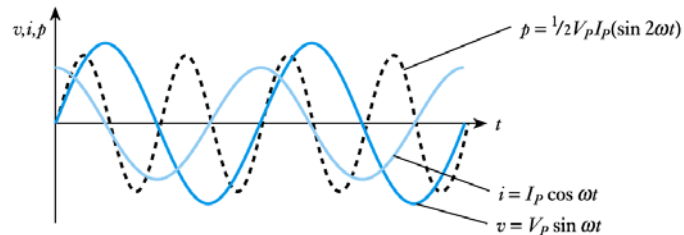7.8

Positive power \Rightarrow power delivered to the circuit
 Negative power \Rightarrow power the circuit delivers back


Relationship between v , i and p in a capacitor



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

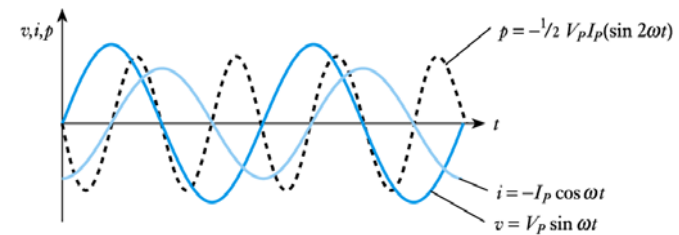7.9

Relationship between v , i and p in an inductor



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.10

Trig relation:
 $\{\cos x - \cos(y)\} = -2 \cdot \sin\left(\frac{x+y}{2}\right) \cdot \sin\left(\frac{x-y}{2}\right)$

Circuit with Resistance and Reactance

- When a sinusoidal voltage $v = V_p \sin \omega t$ is applied across a circuit with resistance *and* reactance, the current will be of the general form $i = I_p \sin(\omega t - \phi)$
- Therefore, the instantaneous power, p is given by

$$\begin{aligned} p &= vi \\ &= V_p \sin \omega t \times I_p \sin(\omega t - \phi) \\ &= \frac{1}{2} V_p I_p \{\cos \phi - \cos(2\omega t - \phi)\} \\ p &= \frac{1}{2} V_p I_p \cos \phi - \frac{1}{2} V_p I_p \cos(2\omega t - \phi) \end{aligned}$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.11

$$p = \frac{1}{2} V_p I_p \cos \phi - \frac{1}{2} V_p I_p \cos(2\omega t - \phi)$$

- The expression for p has two components
- The second part oscillates at 2ω and has an average value of zero over a complete cycle
 - this is the power that is stored in the reactive elements and then returned to the circuit within each cycle
- The first part represents the power dissipated in resistive components. **Average power dissipation** is

$$P = \frac{1}{2} V_p I_p (\cos \phi) = \frac{V_p}{\sqrt{2}} \times \frac{I_p}{\sqrt{2}} (\cos \phi) = VI \cos \phi$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.12

- The average power dissipation given by

$$P = \frac{1}{2} V_P I_P (\cos \phi) = VI \cos \phi$$

is termed the **active power** in the circuit and is measured in watts (W)

- The product of the r.m.s. voltage and current VI is termed the **apparent power**, **S**. To avoid confusion this is given the units of volt amperes (VA)

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.13

- From the above discussion it is clear that

$$P = VI \cos \phi \\ = S \cos \phi$$

- In other words, the active power is the apparent power times the cosine of the phase angle.
- This cosine is referred to as the **power factor**

$$\frac{\text{Active power (in watts)}}{\text{Apparent power (in volt amperes)}} = \text{Power factor}$$

$$\text{Power factor} = \frac{P}{S} = \cos \phi$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.14

Active and Reactive Power




7.6

- When a circuit has resistive and reactive parts, the resultant power has 2 parts:
 - The first is *dissipated* in the resistive element. This is the **active power**, **P**
 - The second is *stored and returned* by the reactive element. This is the **reactive power**, **Q**, which has units of **volt amperes reactive** or **var**
- While reactive power is not dissipated it does have an effect on the system
 - for example, it increases the current that must be supplied and increases losses with cables

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

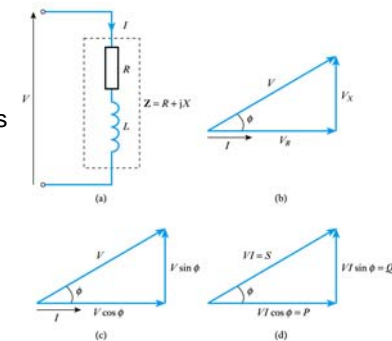7.15

- Consider an RL circuit
 - the relationship between the various forms of power can be illustrated using a power triangle



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.16

- Therefore

Active Power	$P = VI \cos \phi$	watts
--------------	--------------------	-------

Reactive Power	$Q = VI \sin \phi$	var
----------------	--------------------	-----

Apparent Power	$S = VI$	VA
----------------	----------	----

$$S^2 = P^2 + Q^2$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.17

Power Factor Correction



7.7

- Power factor (Active/Apparent power) is particularly important in high-power applications
- Inductive loads have a *lagging* power factor
- Capacitive loads have a *leading* power factor
- Many high-power devices are inductive
 - a typical AC motor has a power factor of 0.9 lagging
 - the total load on the national grid is 0.8-0.9 lagging
 - this leads to major inefficiencies
 - power companies therefore penalize industrial users who introduce a poor power factor

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.18

- The problem of poor power factor is tackled by adding additional components to bring the power factor back closer to unity
 - a capacitor of an appropriate size in parallel with a lagging load can 'cancel out' the inductive element
 - this is **power factor correction**
 - a capacitor can also be used in series but this is less common (since this alters the load voltage)
 - for examples of power factor correction see **Examples 7.2 and 7.3** in the course text

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.19

Three-Phase Systems




7.8

- So far, our discussion of AC systems has been restricted to **single-phase** arrangement
 - as in conventional domestic supplies
- In high-power industrial applications we often use **three-phase** arrangements
 - these have three supplies, differing in phase by 120°
 - phases are labeled **red**, **yellow** and **blue** (R, Y & B)

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

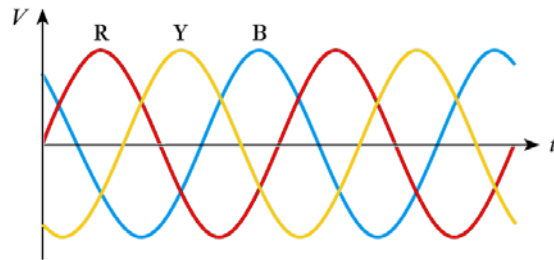7.20


- Relationship between the phases in a three-phase arrangement



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

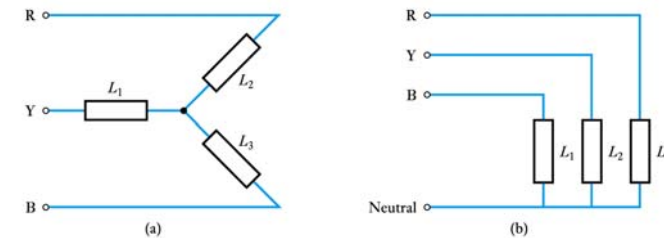7.21

- Three-phase arrangements may use either 3 or 4 conductors



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.22

Power Measurement



7.9

- When using AC, *power* is determined not only by the r.m.s. values of the **voltage** and **current**, but also by the **phase angle** (which determines the **power factor**)
 - consequently, you cannot determine the power from independent measurements of current and voltage
- In **single-phase systems** power is normally measured using an **electrodynamic wattmeter**
 - measures power directly using a single meter which effectively multiplies instantaneous current and voltage

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.23


- In **three-phase systems** we need to sum the power taken from the various phases
 - in three-wire arrangements we can deduce the total power from measurements using 2 wattmeters
 - in a four-wire system it may be necessary to use 3 wattmeters
 - in balanced systems (systems that take equal power from each phase) a single wattmeter can be used, its reading being multiplied by 3 to get the total power

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

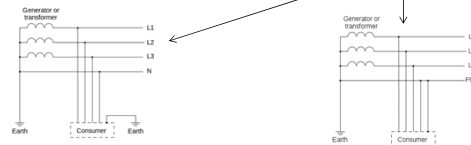
7.24

Who cares?

- In Europe, the standard is TT or TN-C earthing



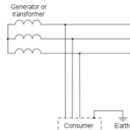- In Norway (and perhaps Albania) it is IT earthing
Buy equipment with TT or TN-C
You will need an additional transformer to run it in Norway



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.25

Further Study



Video 7B Further Study

- The Further Study section at the end of Chapter 7 is concerned with power factor correction for a high-power motor.
- Your task is to calculate the size of capacitor needed to achieve a specific power factor.
- Do the sums and then watch the video.



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.26

Key Points

- In resistive circuits the average power is equal to VI , where V and I are r.m.s. values
- In a capacitor the current *leads* the voltage by 90° and the average power is zero
- In an inductor the current *lags* the voltage by 90° and the average power is zero
- In circuits with both resistive and reactive elements, the average power is $VI \cos \phi$
- The term $\cos \phi$ is called the power factor
- Power factor correction is important in high-power systems
- High-power systems often use three-phase arrangements

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.27

Frequency Characteristics of AC Circuits



Chapter 8

- Introduction
- Two-port Networks
- The Decibel (dB)
- Frequency Response
- A High-Pass RC Network
- A Low-Pass RC Network
- A Low-Pass RL Network
- A High-Pass RL Network
- A Comparison of RC and RL Networks
- Bode Diagrams
- Combining the Effects of Several Stages
- RLC Circuits and Resonance
- Filters
- Stray Capacitance and Inductance



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.28


Introduction

- Having now looked at the AC behaviour of simple components, we can consider their effects on the frequency characteristics of simple circuits
- While the properties of a pure *resistance* are not affected by the frequency of the signal concerned, this is not true of *reactive* components
- We will start with a few basic concepts and then look at the characteristics of simple combinations of resistors, capacitors and inductors

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

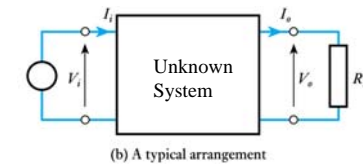7.29

- We then define voltages and currents at the input and output



- Then

$$\text{voltage gain } (A_v) = \frac{V_o}{V_i}$$

$$\text{current gain } (A_i) = \frac{I_o}{I_i}$$

$$\text{power gain } (A_p) = \frac{P_o}{P_i}$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.30

The Decibel (dB)

- The power gain of modern electronic amplifiers is often very high, gains of 10^6 or 10^7 being common
- With such large numbers it is often convenient to use a logarithmic expression for gain
- This is often done using **decibels**
- The decibel is a dimensionless figure for power gain

$$\text{Power gain (dB)} = 10 \log_{10} \frac{P_2}{P_1}$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013


7.31

- Sample gains expressed in dBs

Power gain	Decibels (dBs)
100	20
10	10
1	0

Power gain	Decibels (dBs)
0.5	-3
0.1	-10
0.01	-20

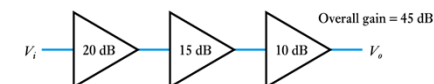- Using dBs simplifies calculation in cascaded circuits



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.32

- Power gain is related to voltage gain

$$\text{Power gain (dB)} = 10 \log_{10} \frac{P_2}{P_1} = 10 \log_{10} \frac{V_2^2 / R_2}{V_1^2 / R_1}$$

- If $R_1 = R_2$

$$\text{Power gain (dB)} = 10 \log_{10} \frac{V_2^2}{V_1^2} = 20 \log_{10} \frac{V_2}{V_1}$$

$$\text{Power gain (dB)} = 20 \log_{10}(\text{Voltage gain})$$

- This expression is **almost always** used even when $R_1 \neq R_2$
– see **Example 8.4** in the course text

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.33

Frequency response




8.4

- Since the characteristics of reactive components change with frequency, the behaviour of circuits using these components will also change
- The way in which the gain of a circuit changes with frequency is termed its **frequency response**
- These variations take the form of variations in the **magnitude** of the gain and in the **phase response**

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.34

Impedance vs. Frequency

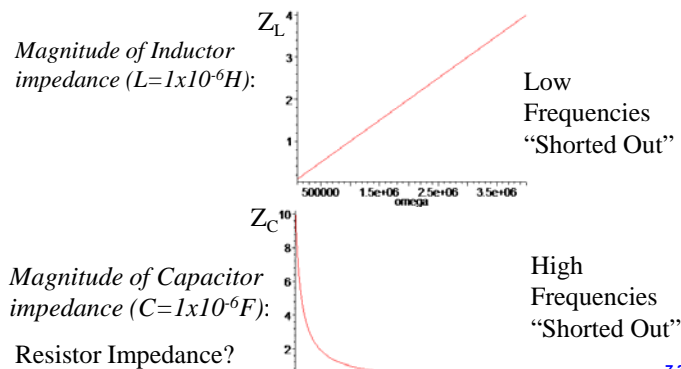


Neil Storey, *Electronics: A Sy.*

Limited 2013

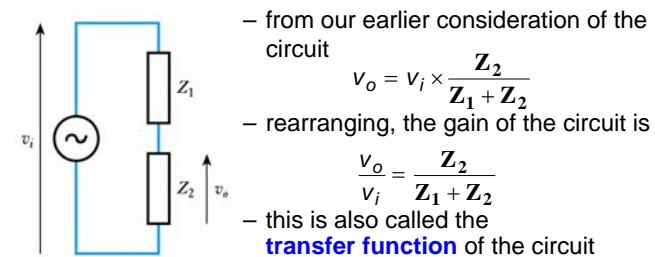7.35

- We will start by considering very simple circuits
- Consider the potential divider shown here




Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

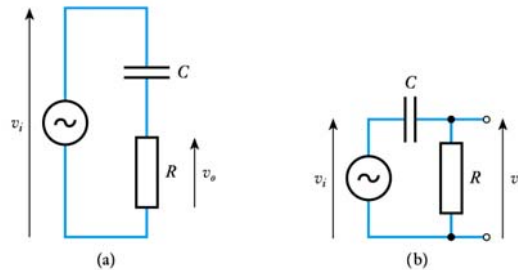7.36

A High-Pass RC Network



- Consider the following circuit
 - which is shown re-drawn in a more usual form




Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

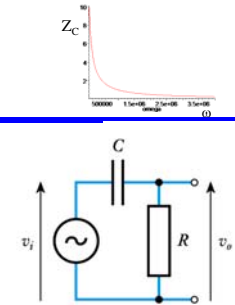7.37

- Clearly the transfer function is

$$\frac{v_o}{v_i} = \frac{Z_R}{Z_R + Z_C} = \frac{R}{R - j\frac{1}{\omega C}} = \frac{1}{1 - j\frac{1}{\omega CR}}$$



- At high frequencies
 - ω is large, voltage gain ≈ 1
(capacitor looks like a wire \Rightarrow nearly all the voltage drops across resistor)
- At low frequencies
 - ω is small, voltage gain $\rightarrow 0$
(capacitor looks like a huge resistor \Rightarrow hardly any voltage drop across resistor)

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.38


- Since the denominator has real and imaginary parts, the *magnitude* of the voltage gain is

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1^2 + \left(\frac{1}{\omega CR}\right)^2}}$$

- When $1/(\omega CR) = 1$

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$$

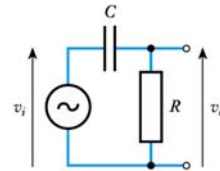- This is a halving of power, or a fall in gain of 3 dB



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.39

- The half power point is the **cut-off frequency** of the circuit
 - the angular frequency ω_c at which this occurs is given by

$$\frac{1}{\omega_c CR} = 1$$

$$\omega_c = \frac{1}{CR} = \frac{1}{T} \text{ rad/s}$$

- where T is the time constant of the CR network. Also

$$f_c = \frac{\omega_c}{2\pi} = \frac{1}{2\pi CR} \text{ Hz}$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.40

- Substituting $\omega = 2\pi f$ and $CR = 1/2\pi f_c$ in the earlier equation gives

$$\frac{v_o}{v_i} = \frac{1}{1 - j \frac{1}{\omega CR}} = \frac{1}{1 - j \frac{1}{(2\pi f) \left(\frac{1}{2\pi f_c} \right)}} = \frac{1}{1 - j \frac{f_c}{f}}$$

- This is the general form of the gain of the circuit
- It is clear that both the *magnitude* of the gain and the *phase angle* vary with frequency

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.41

- Consider the behaviour of the circuit at different frequencies:

- When $f \gg f_c$**

– $f_c/f \ll 1$, the voltage gain ≈ 1

- When $f = f_c$**

$$\frac{v_o}{v_i} = \frac{1}{1 - j \frac{f_c}{f}} = \frac{1}{1 - j} = \frac{1 \times (1 + j)}{(1 - j) \times (1 + j)} = \frac{(1 + j)}{2} = 0.5 + 0.5j$$

Output leads input by 45°

- When $f \ll f_c$**


$$\frac{v_o}{v_i} = \frac{1}{1 - j \frac{f_c}{f}} \approx \frac{1}{-j \frac{f_c}{f}} = j \frac{f}{f_c}$$

Output leads input by 90°

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

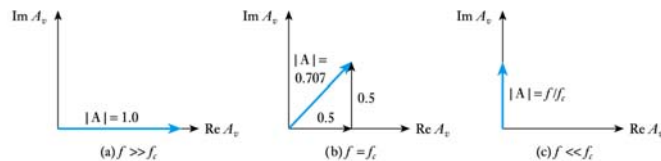7.42

- The behaviour in these three regions can be illustrated using phasor diagrams




- At *low* frequencies the gain is linearly related to frequency. $\frac{1}{2}$ the frequency $\Rightarrow \frac{1}{2}$ the voltage gain
Voltage gain falls at -6dB/octave (-20dB/decade)

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.43


- Frequency response of the high-pass network
 - the gain response has two *asymptotes* that meet at the cut-off frequency
 - figures of this form are called **Bode diagrams**

Phase shifts important in control systems

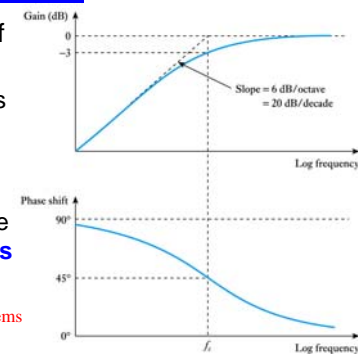Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013


7.44

A Low-Pass RC Network

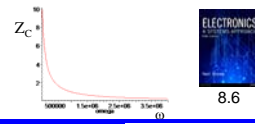

- Transposing the C and R gives
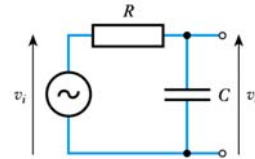
$$\frac{v_o}{v_i} = \frac{Z_C}{Z_R + Z_C} = \frac{-j\frac{1}{\omega C}}{R - j\frac{1}{\omega C}} = \frac{1}{1 + j\omega CR}$$




- At high frequencies
 - ω is large, voltage gain $\rightarrow 0$
(capacitor looks like a wire \Rightarrow nearly all the voltage drops across resistor)
- At low frequencies
 - ω is small, voltage gain ≈ 1
(capacitor looks like a huge resistor \Rightarrow hardly any voltage drop across resistor)

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.45

- A similar analysis to before gives

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1 + (\omega CR)^2}}$$

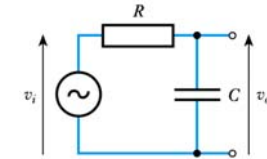

- Therefore when, when $\omega CR = 1$

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$$

- Which is the cut-off frequency

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.46

- Therefore
 - the angular frequency ω_c at which this occurs is given by

$$\omega_c CR = 1$$

$$\omega_c = \frac{1}{CR} = \frac{1}{T} \text{ rad/s}$$

- where T is the time constant of the CR network, and as before

$$f_c = \frac{\omega_c}{2\pi} = \frac{1}{2\pi CR} \text{ Hz}$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.47

- Substituting $\omega = 2\pi f$ and $CR = 1/2\pi f_c$ in the earlier equation gives

$$\frac{v_o}{v_i} = \frac{1}{1 + j\omega CR} = \frac{1}{1 + j\frac{\omega}{\omega_c}} = \frac{1}{1 + j\frac{f}{f_c}}$$

- This is similar, but not the same, as the transfer function for the high-pass network

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.48

- Consider the behaviour of this circuit at different frequencies:

- When $f < f_c$**

- $f/f_c \ll 1$, the voltage gain ≈ 1

- When $f = f_c$**

$$\frac{V_o}{V_i} = \frac{1}{1 + j\frac{f}{f_c}} = \frac{(1-j)(1+j)}{(1+j)} = \frac{(1-j)}{2} = 0.5 - 0.5j$$


- When $f \gg f_c$**

$$\frac{V_o}{V_i} = \frac{1}{1 + j\frac{f}{f_c}} \approx \frac{1}{j\frac{f}{f_c}} = -j\frac{f_c}{f}$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

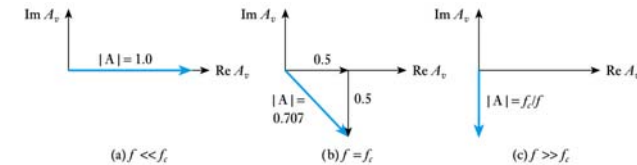7.49

- The behaviour in these three regions can again be illustrated using phasor diagrams



- At *high* frequencies the gain is linearly related to frequency. It falls at 6dB/octave (20dB/decade)


Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.50

- Frequency response of the low-pass network

- the gain response has two *asymptotes* that meet at the cut-off frequency

- you might like to compare this with the Bode Diagram for a high-pass network

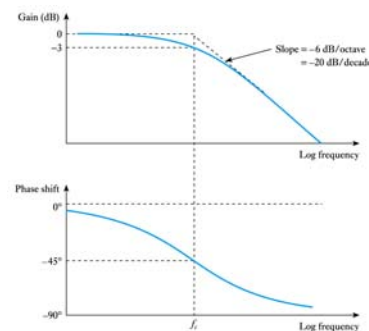Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.51

A Low-Pass RL Network

- Low-pass networks can also be produced using *RL* circuits



- these behave similarly to the corresponding *CR* circuit
- the voltage gain is

$$\frac{V_o}{V_i} = \frac{Z_R}{Z_R + Z_L} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega \frac{L}{R}}$$

- the cut-off frequency is


$$\omega_c = \frac{R}{L} = \frac{1}{T} \text{ rad/s} \quad f_c = \frac{\omega_c}{2\pi} = \frac{R}{2\pi L} \text{ Hz}$$

At Low frequencies
L looks like a wire
At High frequencies
L looks like a big resistor

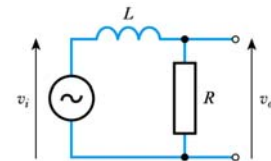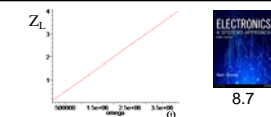Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.52

A High-Pass RL Network

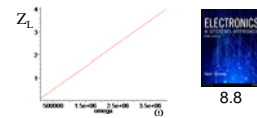

8.8

- High-pass networks can also be produced using RL circuits
 - these behave similarly to the corresponding CR circuit
 - the voltage gain is

$$\frac{v_o}{v_i} = \frac{Z_L}{Z_R + Z_L} = \frac{j\omega L}{R + j\omega L} = \frac{1}{1 + \frac{R}{j\omega L}} = \frac{1}{1 - j\frac{R}{\omega L}}$$

- the cut-off frequency is

$$\omega_c = \frac{R}{L} = \frac{1}{T} \text{ rad/s} \quad f_c = \frac{\omega_c}{2\pi} = \frac{R}{2\pi L} \text{ Hz}$$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013


7.53

A Comparison of RC and RL Networks



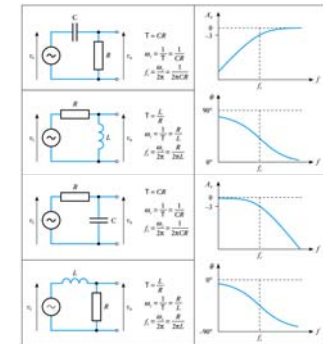8.9

- Circuits using RC and RL techniques have similar characteristics
 - see **Figure 8.12** in the course text



7.54


Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

Bode Diagrams




Video 8A 8.10

- Straight-line approximations

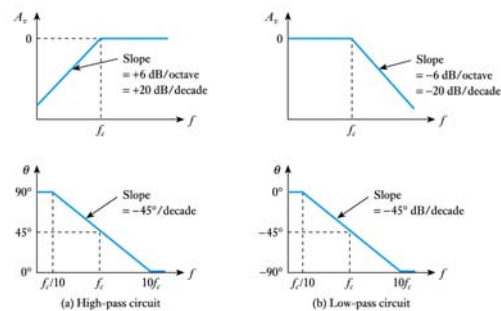Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.55

- Creating more detailed Bode diagrams

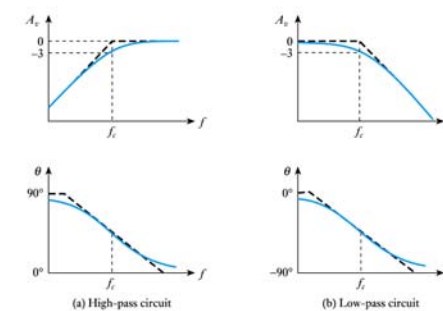


7.56

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

Combining the Effects of Several Stages 8.11

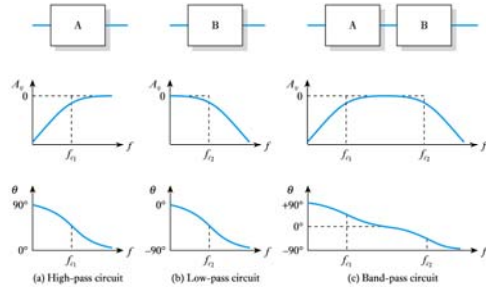
- The effects of several stages 'add' in bode diagrams



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

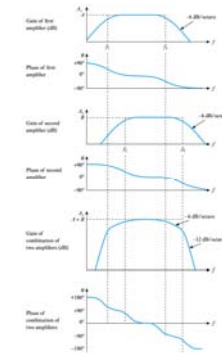7.57

- Multiple high- and low-pass elements may also be combined – this is illustrated in **Figure 8.16** in the course text



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

7.58