



## Last time:

# Digital systems-combinational logic











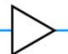


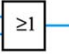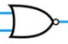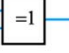

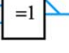
---

- Binary quantities and variables
- Logic gates
- Boolean algebra
- Combinational logic
- Boolean algebraic manipulation
- Algebraic simplification
- Karnaugh maps
- Propagation delay and hazards
- Number systems and binary arithmetic
- Examples of combinational logic design



# Combinational logic building blocks

- The symbols shown earlier for the various logic gates are the '**distinctive shape**' symbols
- Other symbols are also used such as those described in IEC 617 (shown under 'Alternative symbol' here)

Function	Symbol	Alternative symbol	Boolean expression	Truth table															
Buffer			$B = A$	<table><tr><th>A</th><th>B</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	A	B	0	0	1	1									
A	B																		
0	0																		
1	1																		
NOT			$B = \bar{A}$	<table><tr><th>A</th><th>B</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	B	0	1	1	0									
A	B																		
0	1																		
1	0																		
AND			$C = A \cdot B$	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	C	0	0	0	0	1	0	1	0	0	1	1	1
A	B	C																	
0	0	0																	
0	1	0																	
1	0	0																	
1	1	1																	
OR			$C = A + B$	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	C	0	0	0	0	1	1	1	0	1	1	1	1
A	B	C																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	
NAND			$C = \overline{A \cdot B}$	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	0	0	1	0	1	1	1	0	1	1	1	0
A	B	C																	
0	0	1																	
0	1	1																	
1	0	1																	
1	1	0																	
NOR			$C = \overline{A + B}$	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	0	0	1	0	1	0	1	0	0	1	1	0
A	B	C																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	0																	
Exclusive OR			$C = A \oplus B$	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	0	0	0	0	1	1	1	0	1	1	1	0
A	B	C																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	0																	
Exclusive NOR			$C = \overline{A \oplus B}$	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	C	0	0	1	0	1	0	1	0	0	1	1	1
A	B	C																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	1																	

25.2

---

- **Further design examples**

- The text contains further combinational logic design examples:
- **Example 24.28:** A 4-input multiplexer

## Key points

---

- Logic circuits are usually implemented using logic gates
- Circuits in which the output is determined solely by the current inputs are termed combinational logic circuits
- Logic functions can be described by truth tables or using Boolean algebraic notation
- Boolean expressions can often be simplified by algebraic manipulation, or using techniques such as Karnaugh maps
- Binary digits may be combined to form digital words that can be processed using binary arithmetic
- Several codes can be used to represent different forms of information



Video 24H Further Study

## Further Study

---


- The Further Study section at the end of Chapter 24 is concerned with the design of fault tolerant arrangements, such as those used within critical systems within aircraft.
- Your task is to design a simple ‘voting’ arrangement, that allows a system to continue working correctly even in the event of a fault.
- Try the design and then look at the video.




 
# Sequential logic

- Introduction
- Bistables
- Monostables or one-shots
- Astables
- Timers
- Memory registers
- Shift registers
- Counters



# Introduction



Video 25A




25.1

- Sequential logic is built with combinational logic elements
- Combines the characteristics of combinational logic with **memory**
- When constructing sequential logic circuits our building blocks are often some form of **multivibrator**
  - A term used to describe a range of circuits
    - these have two outputs that are the inverse of each other
    - the output are labelled  $Q$  and  $\bar{Q}$
    - three basic forms:
      - **Bistables (flip-flops or latches)**
      - **Monstables (one-shots)**
      - **Astables (digital oscillators)**

**25.7**

# Bistables

- A regenerative switching circuit

 

- This arrangement has two stable states
  - It will stay in whichever state it finds itself
- It is a form of bistable – though not a very useful one



S going high Sets Q to 1


R going high Re-sets Q to 0

Re-setting or setting several times does not affect Q

## ■ The S-R Latch

NOR

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

 

With R and S = 0

$\bar{Q} = 0, Q = 1 \rightarrow \bar{Q} = 0$  or

$\bar{Q} = 1, Q = 0 \rightarrow \bar{Q} = 1$

If  $S \uparrow 1$  briefly,  $\bar{Q} \downarrow 0$   
and Q switches to 1

- Replacing the inverters with NOR gates produces a more useful circuit
  - The circuit still has two stable states
  - But now the inputs can switch it between these states

S going high sets Q to 1

R going high re-sets Q to 0


Re-setting or setting several times does not affect Q

---

- **The S-R latch (SET-RESET latch)**


- More often drawn like this

 - when  $R = S = 0$ 
  - Circuit stays in current state
- when  $S = 1, R = 0$ 
  - Q is **SET** to 1 ( $\bar{Q} = 0$ )
- when  $S = 0, R = 1$ 
  - Q is **RESET** to 0 ( $\bar{Q} = 1$ )
- when  $S = 1, R = 1$ 
  - Both outputs at 0 – not allowed




Active Low {  $\bar{S}$  going low sets Q to 1  
 $\bar{R}$  going low re-sets Q to 0  
 Re-setting or setting several times does not affect Q

 - An S-R latch can also be produced using NAND gates
  - produces an **active-low circuit** ( $\bar{S}$  or  $\bar{R} = 0$  set/reset)



(a) An S–R latch using two NOR gates.

 

(b) An S–R latch using two NAND gates.


$R=S=0 \rightarrow$  Memory State  
 $R=0, S=0 \rightarrow 1$  sets  $Q=1$   
 $R=0 \rightarrow 1, S=0$  re-sets  $Q=0$   
 $R=S=1$  undetermined

$\bar{R} = \bar{S} = 1 \rightarrow$  Memory State  
 $\bar{R}=1, \bar{S}=1 \rightarrow 0$  sets  $Q=1$   
 $\bar{R}=1 \rightarrow 0, \bar{S}=1$  re-sets  $Q=0$   
 $\bar{R}=\bar{S}=0$  undetermined


25.11

---


- **S-R latch logic symbols**

 

(a) Active high inputs

 

(b) Active low inputs

 


S going high sets Q to 1

R going high re-sets Q to 0

Re-setting or setting several times does not affect Q

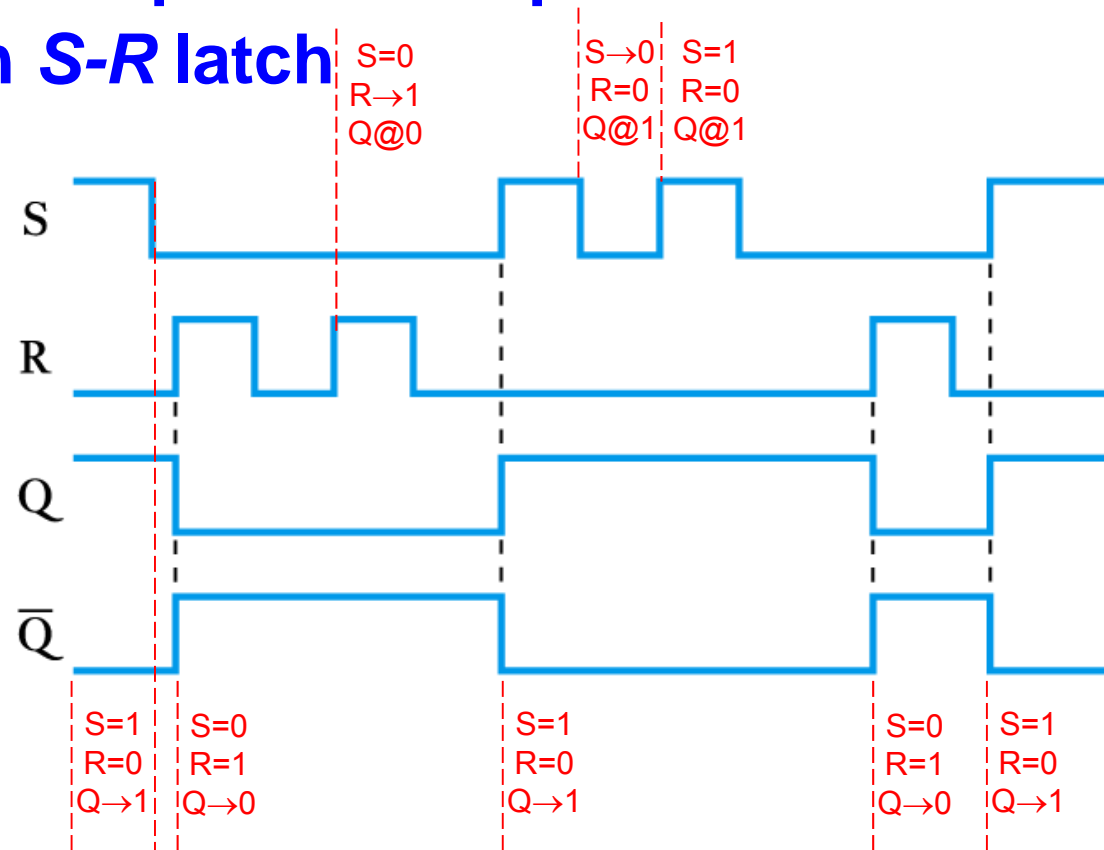- **Sample input and output waveforms for an S-R latch**




# So What?

- A design example - see **Example 25.1** in course text
 
## Use of an S-R latch in switch debouncing

- All mechanical switches suffer from switch bounce
- Switch makes and breaks contact several times




$\bar{S}$  going low sets  $Q$  to 1

$\bar{R}$  going low re-sets  $Q$  to 0

Re-setting or setting several times does not affect  $Q$


## ■ A design example (continued)

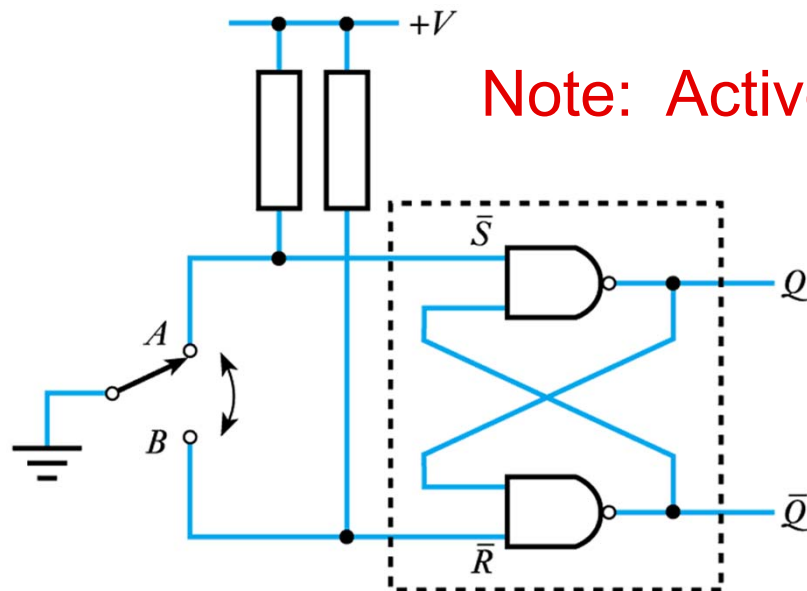- Problem can be tackled using an S-R bistable and a changeover switch (when  $A$  breaks contact, line goes low)



Note: Active Low Latch

Switch  $B \rightarrow A$

 


25.15

# Sometimes the lecture topics really happen!!

---

Top trace-at switch

Bottom-at output  
of the latch

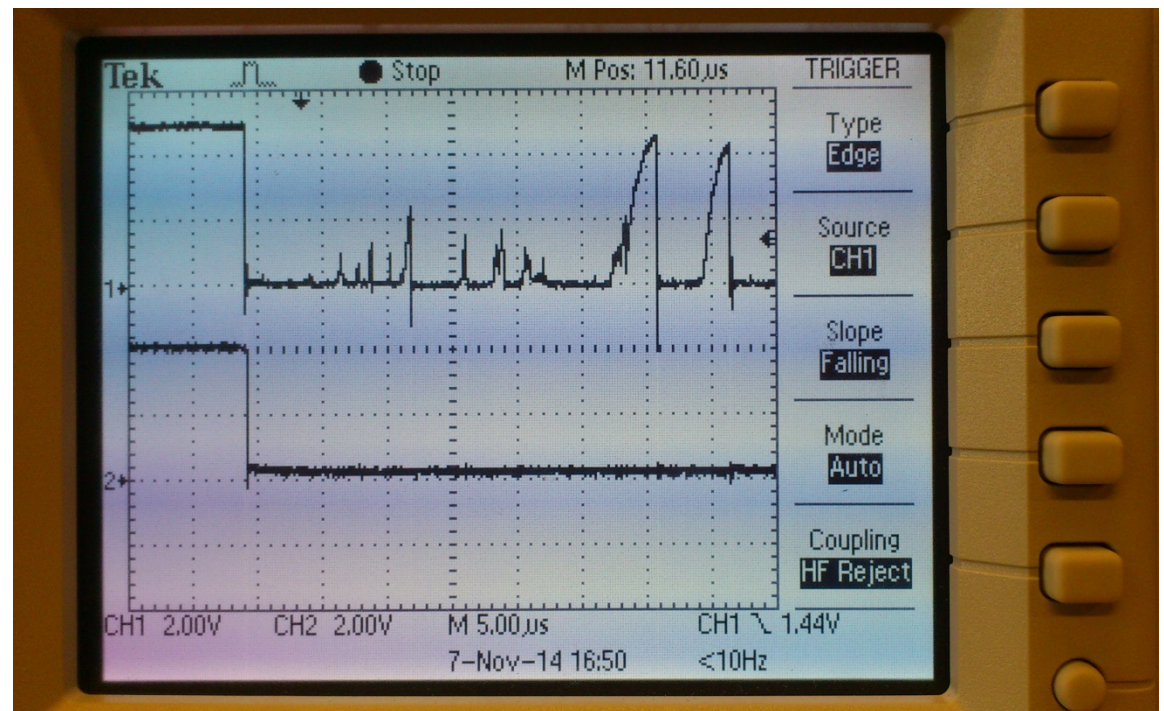

Picture by Lise Kvalø


25.16



- A design example - see **Example 25.2** in course text
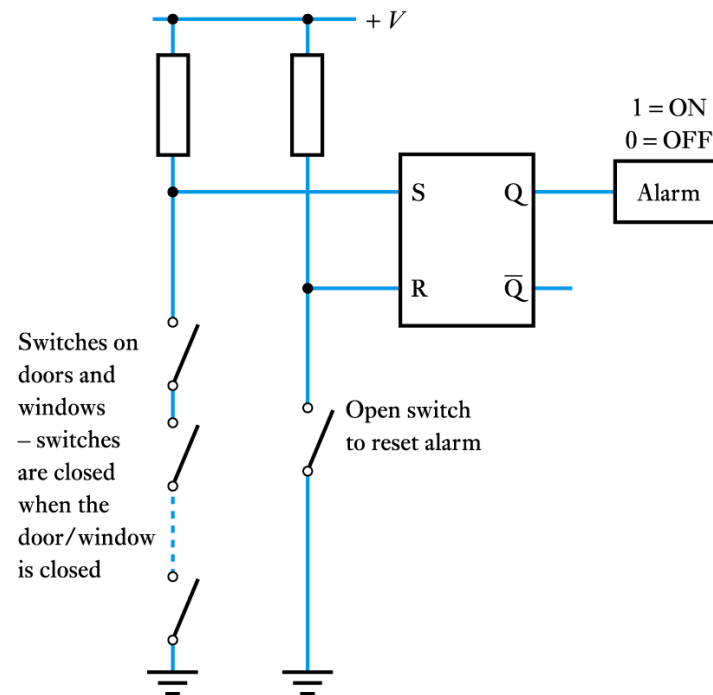
## A Burglar Alarm


- Close all doors and window (closing switches)
- open reset switch to initialise system
- opening any of the door/window switches will activate alarm.
- alarm will continue if switch is then closed
- alarm is silenced by opening reset switch



In the fine tradition of this course, let's look at variations on a theme!


- **The gated S-R latch.**

Note: Active Low Latch


 


Start with  $Q=0$ , and S, En and R all 0 → Memory state  
If R or S go High, but En stays low, Nothing happens!

 - 
- **Sample input and output waveforms for a gated  $S$ - $R$  latch**



  - The *D* latch-a particular type of enabled latch with one external input, *D*




---

- **Sample input and output waveforms for a  $D$  latch.**


Use to Latch (or hold) value of  $D$

 Use in a parallel group to Latch value of a word



25.21

## ■ Fundamental Storage Register

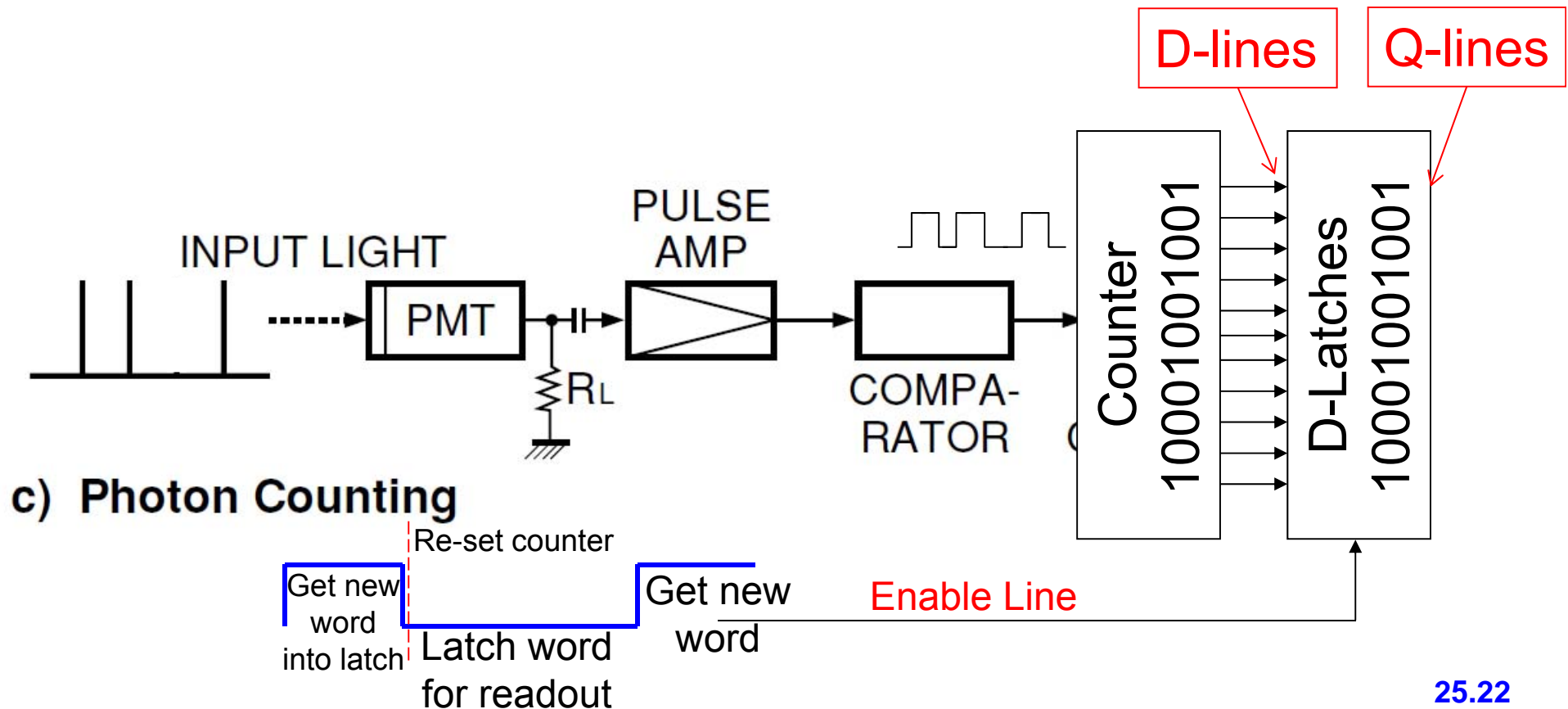


25.22

# So far, you now already know how to build:

 
## ■ Photo-tube—voltage divider

- Potential difference accelerates electrons




## ■ R-C high-pass filter

- Only the pulse passes

 

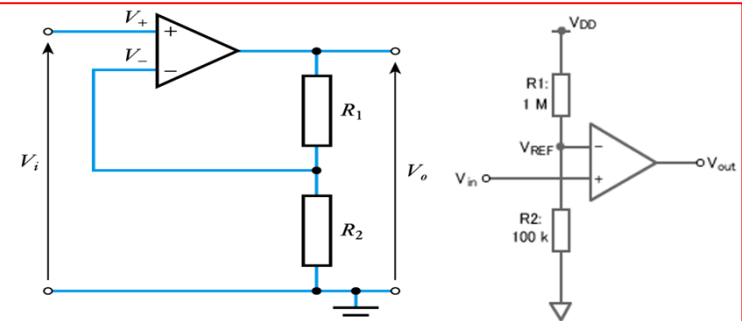
## ■ Pulse amplifier $G = \frac{V_o}{V_i} = \frac{R_1 + R_2}{R_2}$

and comparator ( $V_{out} = V_{DD}$   
when  $V_{in} > V_{ref}$ )



 
## ■ Edge-triggered devices

- It is often necessary to synchronise many devices
- This can be done using a **clock input**
  - such devices respond on a particular transition of the clock.
  - these are called **edge-triggered devices** or **flip-flops**
  - can have **positive-edge** or **negative-edge** triggered devices



(a) Positive edge-triggered

 


(b) Negative edge-triggered



---



- **The *D* flip-flop**

 - Symbol as in previous slide
- Behaviour of positive-edge triggered device as below
- *Q* becomes equal to *D* at the time of the trigger event


  
## ■ The J-K flip-flop


- Similar to S-R flip-flop but *toggles* when  $J = K = 1$




(a) Logic symbol

 (b) Sample input and output waveforms


- Use of a J-K flip-flop to reproduce other flip-flop functions (hence it is widely used due to its versatility)



(a) S-R flip-flop

 

(b) D flip-flop

 

(c) T flip-flop


When toggle  $T=1$   
Each clock pulse  
changes Q

25.27


Before, J&K set/reset output Q only at the moment of an appropriate transition of the clock signal (*CLK*).
 
## ■ Asynchronous inputs

- Some flip-flops have asynchronous inputs (that clear/reset independently of the clock)




(a) Logic symbol

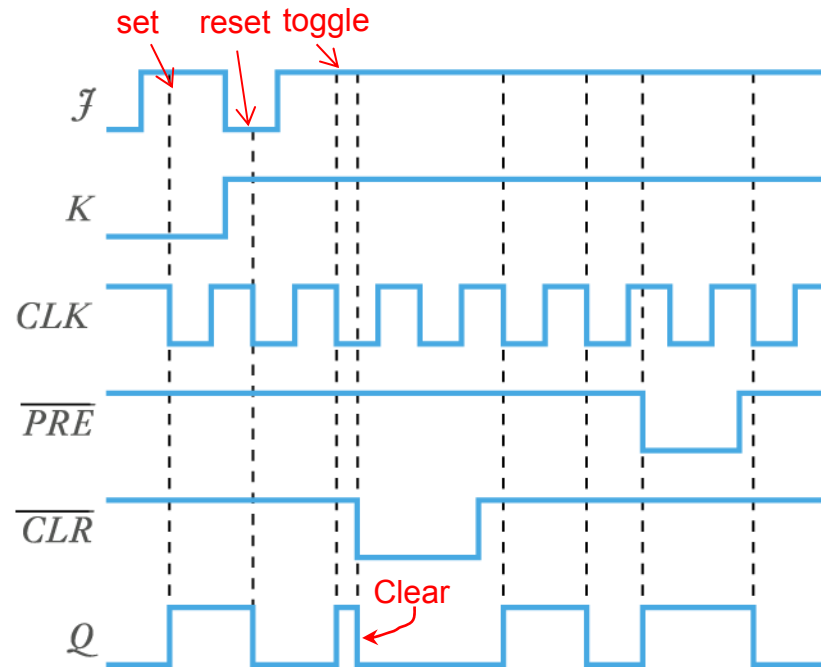

(b) Sample input and output waveforms
 
## ■ Propagation delays and races


- Real logic gates take a finite time to react
- Some circuits (as below) can suffer from **race hazards** where the operation of the circuit is uncertain
  - In this circuit the output depends on which device is fastest



25.29

 
## ■ Pulse-triggered or master/slave bistables

- These overcome race hazards by responding to the state of the inputs shortly *before* the clock trigger



CLK=1 determines what outputs should be, but outputs change only on CLK↓0

(a) Logic symbol

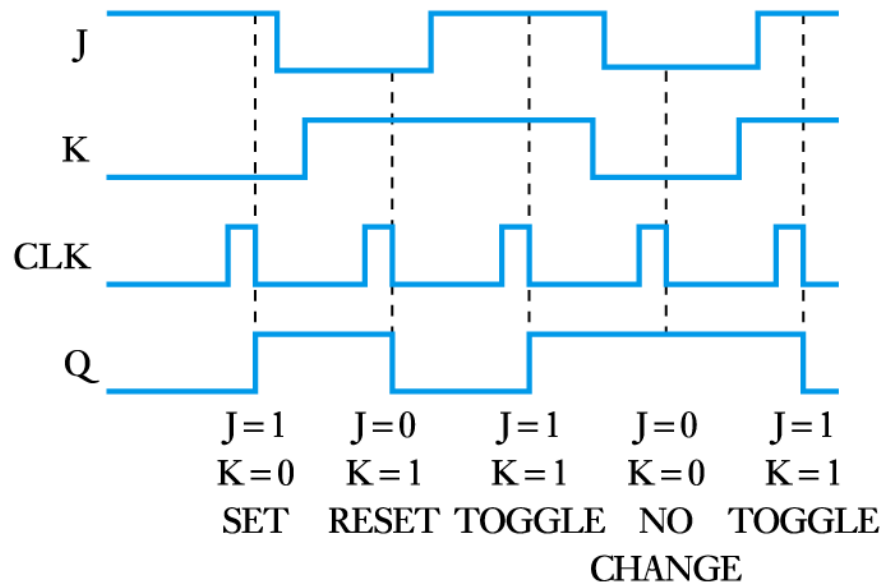

(b) Sample input and output waveforms

Disable S (it holds its output steady)

Enable M moment later


(it updates its outputs to match inputs)

Disable M (it holds its outputs steady)

Enable S moment later

(it updates its outputs to match M)

 
## ■ Circuit of a basic J-K master/slave flip-flop



Master-latch and inverter delays timed so slave is disabled shortly before the master is enabled, preventing race condition
 
## Monostables or one-shots


- Monostables are another form of multivibrator
  - while **bistables** have two stable output states
  - **monostables** have one stable & one metastable states
    - when in its stable state  $Q = 0$
    - when an appropriate signal is applied to the trigger input ( $T$ ) the circuit enters its metastable state with  $Q = 1$
    - after a set period of time (determined by circuit components) it reverts to its stable state
    - it is therefore a **pulse generator**




Circuit symbol



## ■ A simple monostable

 


(a) Logic circuit

 


 (b) Waveform diagram

- Monostables can be **retriggerable** or **non-retriggerable**



(a) A non-retriggerable monostable

 

(b) A retriggerable monostable



25.4

# Astables


---

- The last member of the multivibrator family is the **astable**
  - this has two metastable states
  - has the function of a **digital oscillator**
  - circuit spends a fixed period in each state (determined by circuit components)
  - if the period in each state is set to be equal, this will produce a square waveform


**25.35**

---


- A simple astable arrangement

 
 
## ■ Waveforms of the simple astable circuit



25.37

 



## ■ Waveforms of the simple astable circuit.

(2)  $V_2$  hits trigger point,  
switches  $Q$  low  $\rightarrow V_1$  Low  
but charging  
sets  $\bar{Q}$  high

(3)  $V_1$  hits trigger point  
switches  $\bar{Q}$  low  $\rightarrow V_2$  Low  
but charging  
sets  $Q$  high

 (1)  $\bar{Q}$  low  $\rightarrow V_2$  Low  
but charging  
keeps  $Q$  high



 


## ■ Waveforms of the simple astable circuit.


(2)  $V_2$  hits trigger point,  
switches  $Q$  low  $\rightarrow V_1$  Low  
but charging  
sets  $\bar{Q}$  high

(3)  $V_1$  hits trigger point  
switches  $\bar{Q}$  low  $\rightarrow V_2$  Low  
but charging  
sets  $Q$  high

 (1)  $\bar{Q}$  low  $\rightarrow V_2$  Low  
but charging  
keeps  $Q$  high



 - 
- An astable formed by two monostables







25.5


# Timers

---


- The **integrated circuit timer** can produce a range of functions
  - including those of a monostable or astable
  - various devices
  - one of the most popular is the **555 timer**
  - can be configured using just a couple of external passive components
  - internal construction largely unimportant – all required information on using the device is in its data sheet

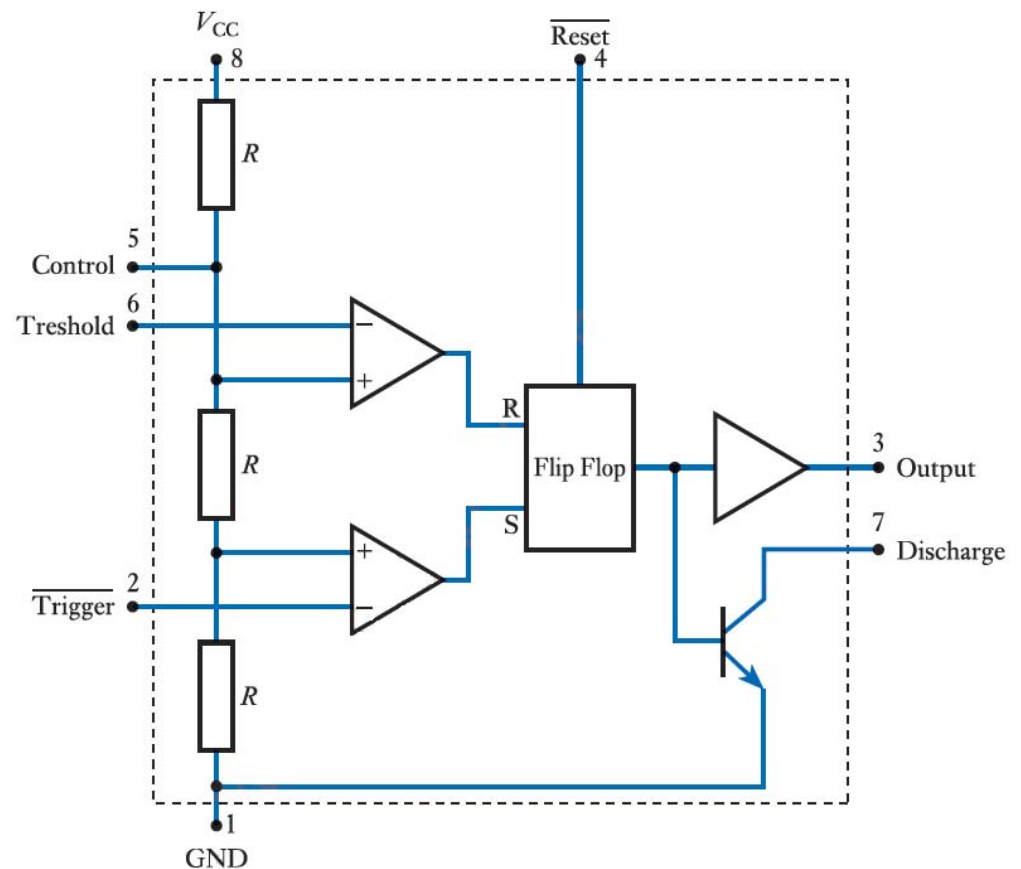**25.41**


- A simplified circuit diagram of the **555 timer** is shown here
  - It consists basically of a flip-flop, two comparators, a switching transistor and a resistive network.



 - The diagram here shows the 555 configured as a monostable.
  - It can be seen that only a couple of external components are needed.



 - Here the 555 is shown configured as an astable
  - Again very few additional components are required.



## Key points

---

- Sequential logic circuits have the characteristic of memory
- Among the most important groups of sequential components are the various forms of multivibrator
  - Bistables-flip flops and latches
  - Monostables-one shots
  - Astables-digital oscillators and timers