


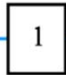
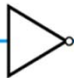
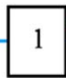




-
- Reference group report is on It's Learning
 - The reference group will be available at the end of lecture today to take any additional comments


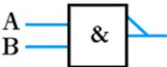

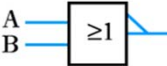

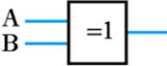

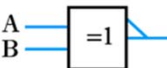
Last time: Digital systems

- Introduction
- Binary quantities and variables
- Logic gates
- Boolean algebra
- Combinational logic
- Boolean algebraic manipulation
- Algebraic simplification
- Karnaugh maps
- Automated methods of minimisation
- Propagation delay and hazards
- Number systems and binary arithmetic
- Numeric and alphabetic codes
- Examples of combinational logic design



Last time: Summary of combinational logic

Function	Symbol	Alternative symbol	Boolean expression	Truth table															
Buffer			$B = A$	<table><tr><th>A</th><th>B</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	A	B	0	0	1	1									
A	B																		
0	0																		
1	1																		
NOT			$B = \bar{A}$	<table><tr><th>A</th><th>B</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	B	0	1	1	0									
A	B																		
0	1																		
1	0																		
AND			$C = A \cdot B$	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	C	0	0	0	0	1	0	1	0	0	1	1	1
A	B	C																	
0	0	0																	
0	1	0																	
1	0	0																	
1	1	1																	
OR			$C = A + B$	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	C	0	0	0	0	1	1	1	0	1	1	1	1
A	B	C																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	

Function	Symbol	Alternative symbol	Boolean expression	Truth table															
NAND			$C = \overline{A \cdot B}$	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	0	0	1	0	1	1	1	0	1	1	1	0
A	B	C																	
0	0	1																	
0	1	1																	
1	0	1																	
1	1	0																	
NOR			$C = \overline{A + B}$	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	0	0	1	0	1	0	1	0	0	1	1	0
A	B	C																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	0																	
Exclusive OR			$C = A \oplus B$	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	0	0	0	0	1	1	1	0	1	1	1	0
A	B	C																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	0																	
Exclusive NOR			$C = \overline{A \oplus B}$	<table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	C	0	0	1	0	1	0	1	0	0	1	1	1
A	B	C																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	1																	

Boolean theorems

Boolean identities

AND function

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

$$A \cdot 0 = 0$$

$$0 \cdot A = 0$$

$$A \cdot 1 = A$$

$$1 \cdot A = A$$

$$A \cdot A = A$$

$$A \cdot \bar{A} = 0$$

OR function

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

$$A + 0 = A$$

$$0 + A = A$$

$$A + 1 = 1$$

$$1 + A = 1$$

$$A + A = A$$

$$A + \bar{A} = 1$$

NOT function

$$\bar{0} = 1$$

$$\bar{1} = 0$$

$$\bar{\bar{A}} = A$$

Boolean laws

Commutative law

$$AB = BA$$

$$A + B = B + A$$

Absorption law

$$A + AB = A$$

$$A(A + B) = A$$

Distributive law

$$A(B + C) = AB + AC$$

$$A + BC = (A + B)(A + C)$$

De Morgan's law

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

Associative law

$$A(BC) = (AB)C$$

$$A + (B + C) = (A + B) + C$$

Note also

$$A + \bar{A}B = A + B$$

$$A(\bar{A} + B) = AB$$

Note: Boolean expression are not unique

- Can express an exclusive-OR as:

*“The output is true if A OR B is true,
AND if A AND B are NOT true.”*

$$X = (A + B) \cdot (\overline{AB})$$

- Can also express an exclusive-OR as:

*“The output is true if A is true AND B is NOT true,
OR if A is NOT true AND B is true.”*

$$X = A\bar{B} + \bar{A}B$$

- Both give:

$$X = A \oplus B$$

■ Implementing a logic function from a truth table

Example – see **Example 24.6** in the course text

Implement the function of the following truth table

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

– first write down a Boolean expression for the output as the sum of the **minterms**


– then implement as before

– in this case

$$X = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C$$

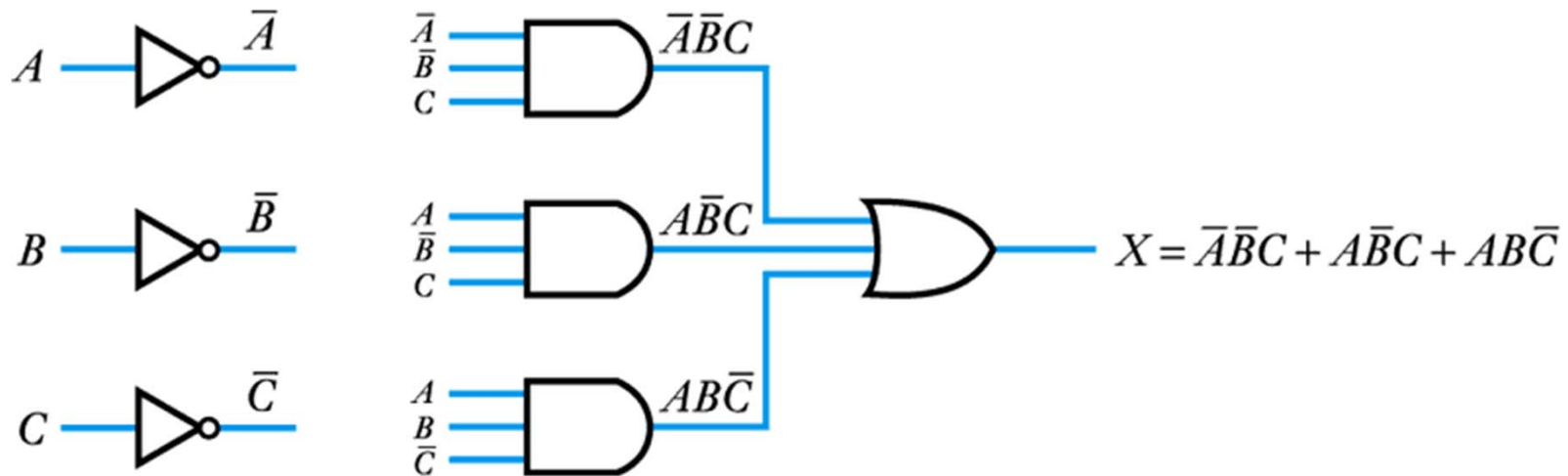
Example (continued)

- Complex logic diagrams are often made easier to understand by the use of labels, rather than showing complex interconnections – the earlier circuit becomes




Simplify the Boolean equation, simplify the circuit

- We can use Boolean laws to simplify expression and the circuit

$$\begin{aligned} X &= \bar{A}\bar{B}C + A\bar{B}C + AB\bar{C} \\ &= \bar{B}C(A + \bar{A}) + AB\bar{C} \\ &= \bar{B}C + AB\bar{C} \end{aligned}$$

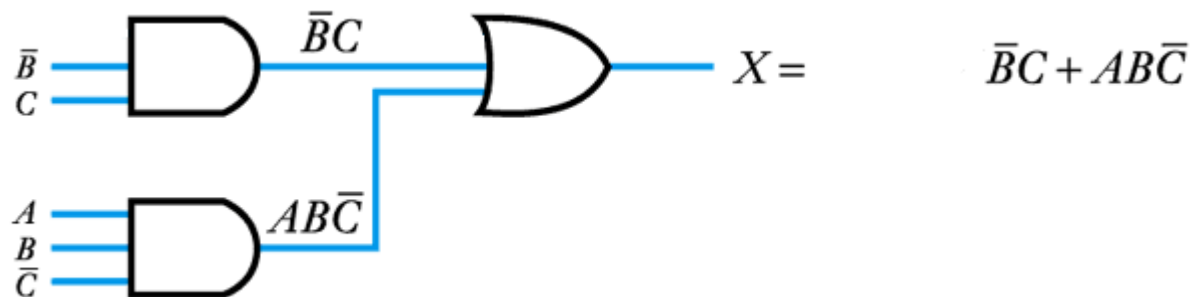- So a circuit with identical logical properties is:





- Questions?

Can use Boolean relationships to re-format so that only 1 type of gate (NAND) is used

- Using De Morgan's 1st Law: $\overline{A+B} = \bar{A} \bullet \bar{B}$ can be written

$$\overline{\overline{A+B}} = \overline{\bar{A} \bullet \bar{B}} = A+B$$

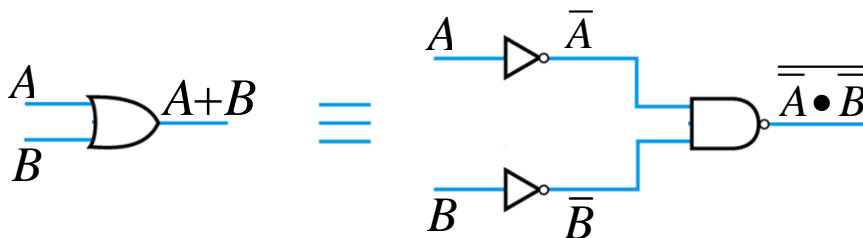- Hence: 

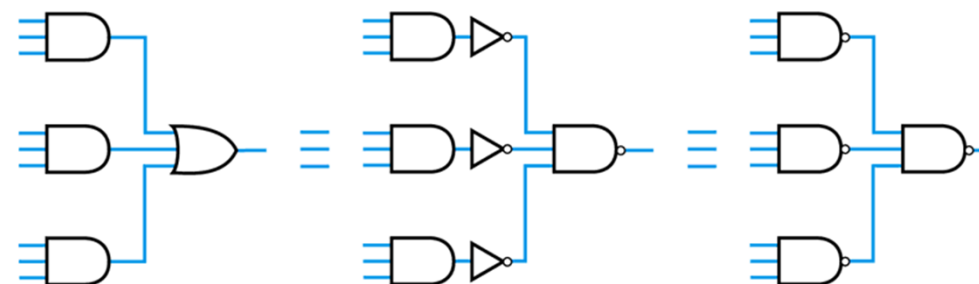
- So any multi-term 


Why?

Many logic arrays use only one type of gate, or multiple NANDs or NORs on one chip
For logic arrays user generally does not need to know as this is auto-implemented!

Similarly with NOR gates

- Using De Morgan's second: $\overline{A \bullet B} = \bar{A} + \bar{B}$ *can be written*
 $\overline{\overline{A \bullet B}} = A \bullet B = \overline{\bar{A} + \bar{B}}$

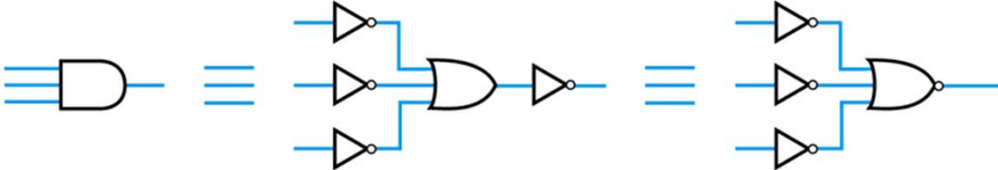- Hence: The diagram shows the equivalence between a NAND gate and a NOR gate with inverted inputs. On the left, a NAND gate is shown with three inputs. This is followed by an equivalence symbol (≡). In the middle, a NOR gate is shown with three inputs, each preceded by an inverter (triangle with a circle). This is followed by another equivalence symbol (≡). On the right, a single NAND gate is shown with three inputs, each preceded by an inverter.

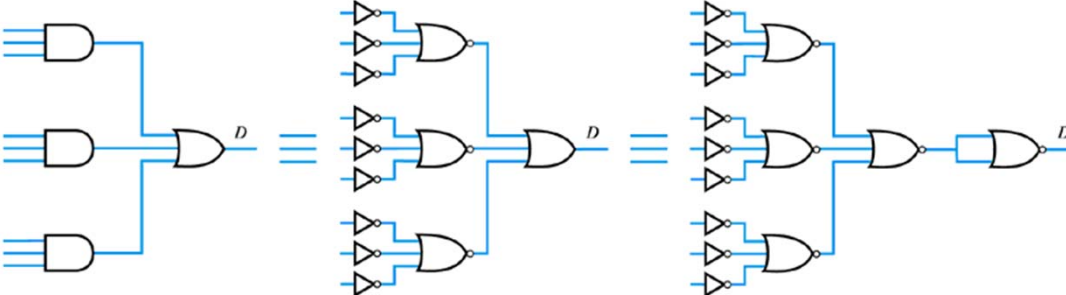- So: The diagram shows the equivalence between a multi-input NAND gate and a multi-input NOR gate with inverted inputs. On the left, a multi-input NAND gate is shown with three inputs. This is followed by an equivalence symbol (≡). In the middle, a multi-input NOR gate is shown with three inputs, each preceded by an inverter. This is followed by another equivalence symbol (≡). On the right, a single multi-input NAND gate is shown with three inputs, each preceded by an inverter.

How do we know what to simplify?



Video 24E



24.8

Karnaugh maps

- With algebraic simplification it is not obvious whether an optimum form has been obtained
- Karnaugh maps are a graphical approach
- They represent the information of a truth table within a two dimensional grid



<i>A</i>	<i>B</i>	<i>C</i>
0	0	0
0	1	0
1	0	1
1	1	0


(a) Truth table

		<i>A</i>	
		0	1
<i>B</i>	0	0	1
	1	0	0


(b) Karnaugh map

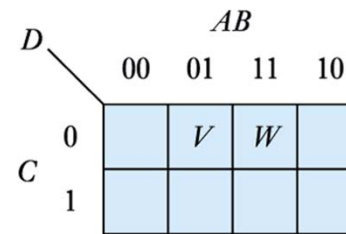24.12

- The diagram here shows maps for systems with three and four inputs



(a)

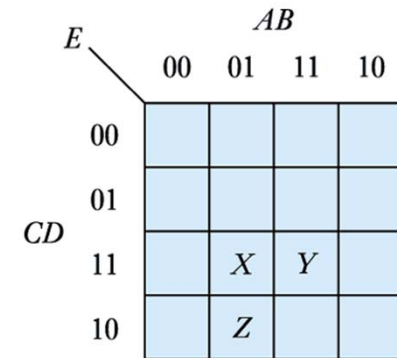

(b)


- Note the numbering of the grid – **Gray Code**
- Any adjacent cells (vertically or horizontally) differ by only one term
- For example

$$V = \overline{A}\overline{B}\overline{C}$$

$$W = A\overline{B}\overline{C}$$


■ Forming Gray code

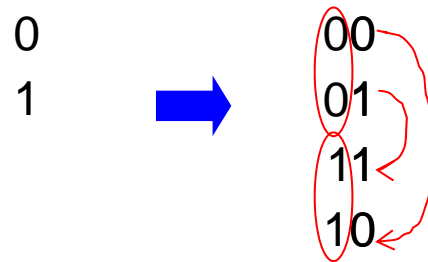- first write down the first two numbers (0 and 1)
- then repeat in reverse order with a 1 in front (add 0's to top half)
- then keep repeating in reverse order with a 1 in front



■ Forming Gray code

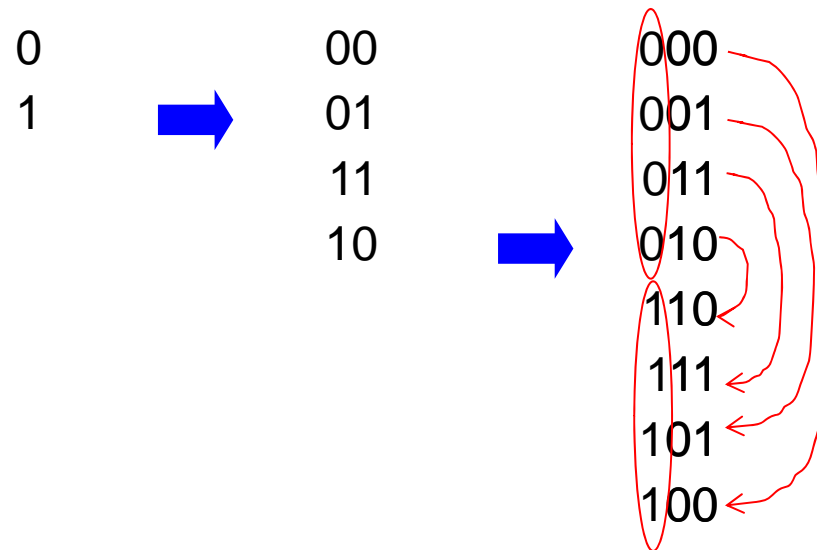- first write down the first two numbers (0 and 1)
- then repeat in reverse order with a 1 in front (add 0's to top half)
- then keep repeating in reverse order with a 1 in front



■ Forming Gray code

- first write down the first two numbers (0 and 1)
- then repeat in reverse order with a 1 in front (add 0's to top half)
- then keep repeating in reverse order with a 1 in front

0		00		000	
1	→	01		001	
		11		011	
		10	→	010	
				110	
				111	→ etc.
				101	
				100	

Consider the two truth tables

Can they be simplified?

ABCD	E
0000	0
0001	0
0010	0
0011	0
0100	0
0101	1
0110	0
0111	0
1000	0
1001	0
1010	0
1011	0
1100	0
1101	0
1110	0
1111	1

$$E = \overline{A}\overline{B}\overline{C}D + ABCD$$

ABCD	F
0000	0
0001	0
0010	0
0011	0
0100	0
0101	1
0110	0
0111	0
1000	0
1001	0
1010	0
1011	0
1100	0
1101	1
1110	0
1111	0

$$F = \overline{A}\overline{B}\overline{C}D + AB\overline{C}D$$

- Consider these maps
- We can extract the algebraic expressions, as in a truth table

		<i>AB</i>			
		00	01	11	10
<i>E</i>	00	0	0	0	0
	01	0	1	0	0
	11	0	0	1	0
	10	0	0	0	0

(a)

		<i>AB</i>			
		00	01	11	10
<i>F</i>	00	0	0	0	0
	01	0	1	1	0
	11	0	0	0	0
	10	0	0	0	0

(b)

$$E = \overline{A}\overline{B}\overline{C}D + A\overline{B}C\overline{D}$$



$$F = \overline{A}\overline{B}\overline{C}D + A\overline{B}C\overline{D}$$

$$= \overline{B}\overline{C}D(A + \overline{A})$$

$$= \overline{B}\overline{C}D$$

- When adjacent cells contain '1's they can *always* be combined, thus simplifying the expression

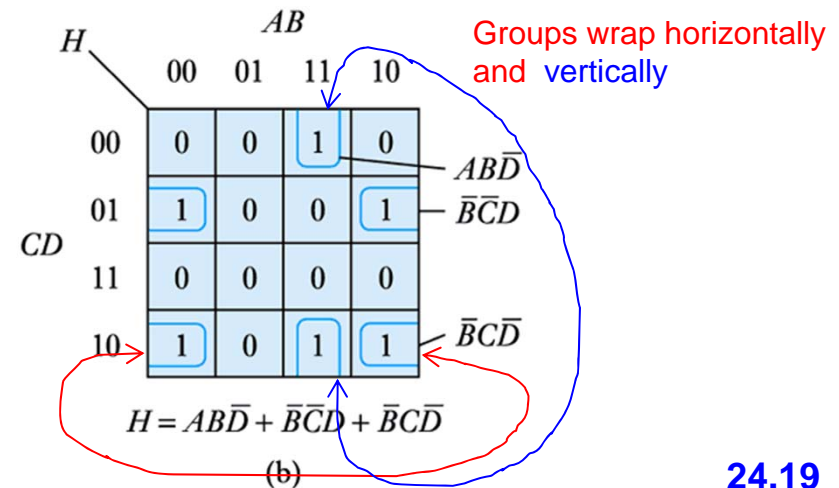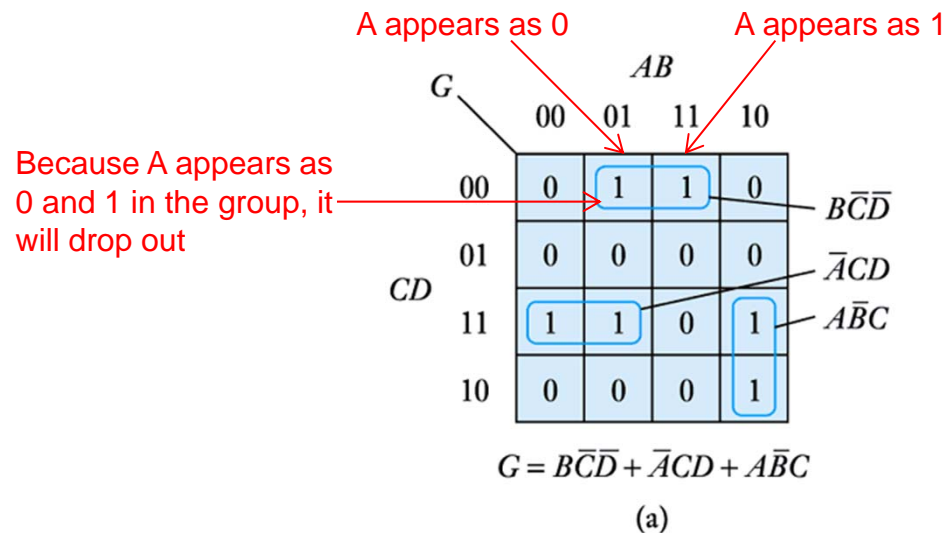- We group terms on the map by drawing a loop around them (size of 2^n , where n =number of input variables).
- The expression for this group is made up of the terms that are consistent for the cells within
- The expression for the function is the sum of the groups







24.9

Method of minimisation



- The largest possible groups of cells should be constructed first, each group containing 2^n elements (n = number of input variables)
- Progressively smaller groups should be added until every cell containing a '1' has been included at least once.
- Any redundant groups should then be removed, even if these are large groups, to avoid duplication.
- Karnaugh maps can be used fairly easily with up to six variables. Beyond that computer algorithms are generally used

24.20

- Allowable groups

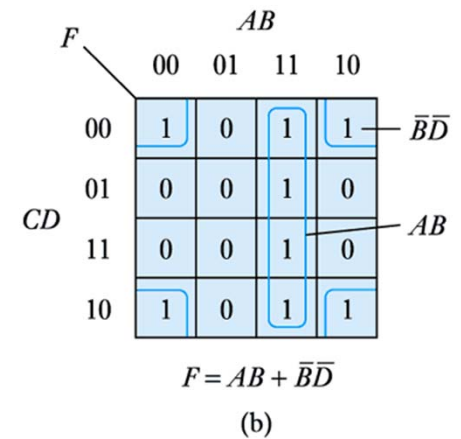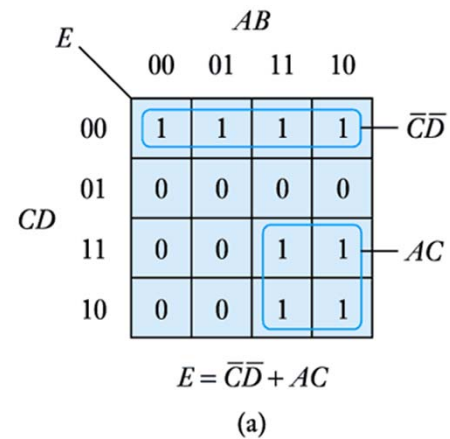


- Illegal groups

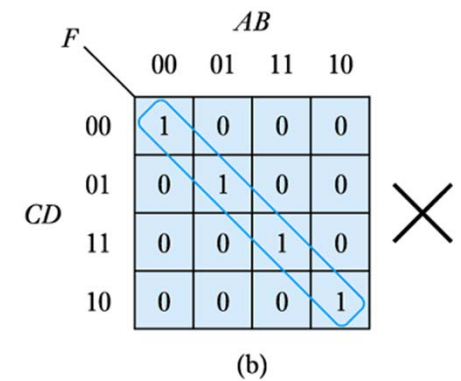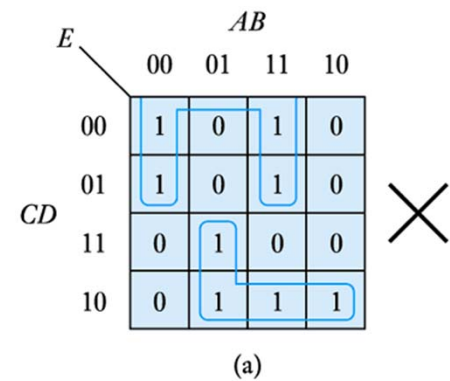

Propagation delay and hazards

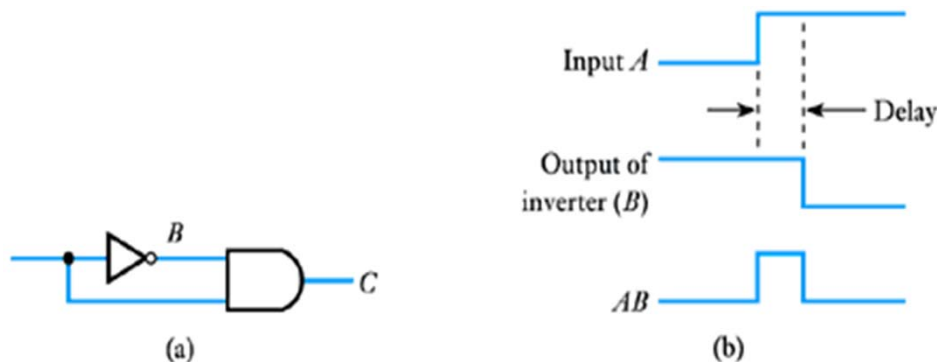- All physical logic gates take a finite time to respond to input signals and there is a delay between the time the input changes and when the output responds
- This is the **propagation time delay**
- This delay can cause problems. Consider this circuit



- The delay causes the output to differ from what we might expect
- This is an example of a **hazard** (can be identified and eliminated using a Karnaugh map)

24.22



24.11

Number systems and binary arithmetic

- Most number systems are order dependent

- **Decimal**

$$1234_{10} = (1 \times 10^3) + (2 \times 10^2) + (3 \times 10^1) + (4 \times 10^0)$$

- **Binary**

$$1101_2 = (1 \times 2^3) + (1 \times 2^2) + (0 \times 2^1) + (1 \times 2^0) = 13_{10}$$

- **Octal**

$$123_8 = (1 \times 8^2) + (2 \times 8^1) + (3 \times 8^0) = 83_{10}$$

- **Hexadecimal**

$$123_{16} = (1 \times 16^2) + (2 \times 16^1) + (3 \times 16^0) = 291_{10}$$

here we need 16 characters – 0,1,2,3,4,5,6,7,8,9,A,B,C,D,E,F


24.23



Video 24F

■ Binary arithmetic

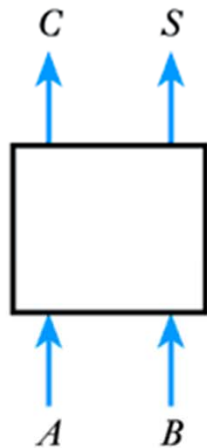- much simpler than decimal arithmetic
- can be performed by simple circuits, e.g. half adder




(a) Block diagram

Binary
Addition

	A	B	C	S
0 + 0 = 0	0	0	0	0
0 + 1 = 1	0	1	0	1
1 + 0 = 1	1	0	0	1
1 + 1 = 10	1	1	1	0

(b) Truth table

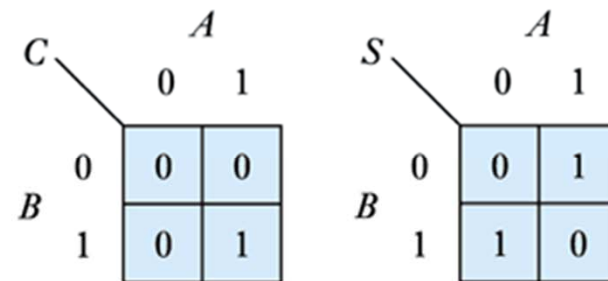


(c) Karnaugh maps

$$C = A \cdot B$$
$$S = \bar{A}B + A\bar{B} = A \oplus B$$


24.24

■ Implementation of a half adder

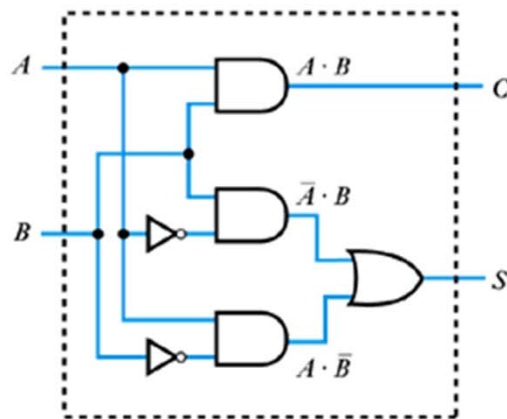


(a)
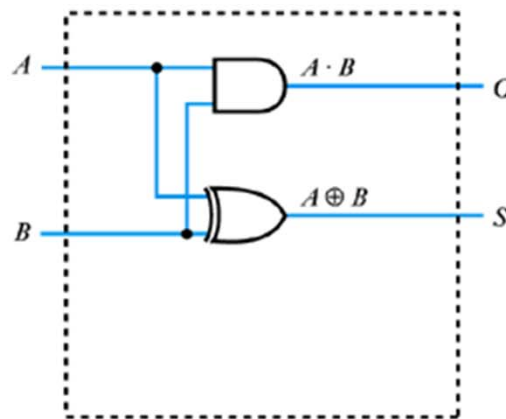
$$C = A \cdot B$$
$$S = \bar{A}B + A\bar{B}$$



(b)


$$C = A \cdot B$$
$$S = A \oplus B$$

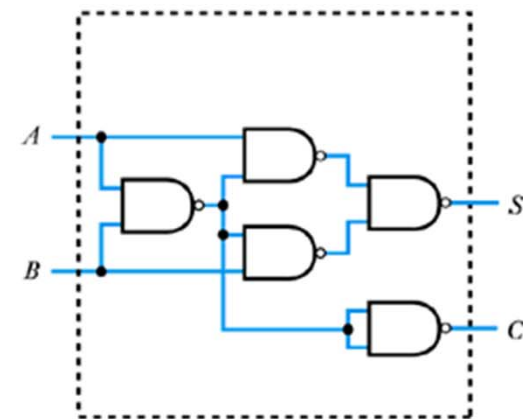

(c)


Or if you only have
NAND gates

■ Adding multiple-bit words

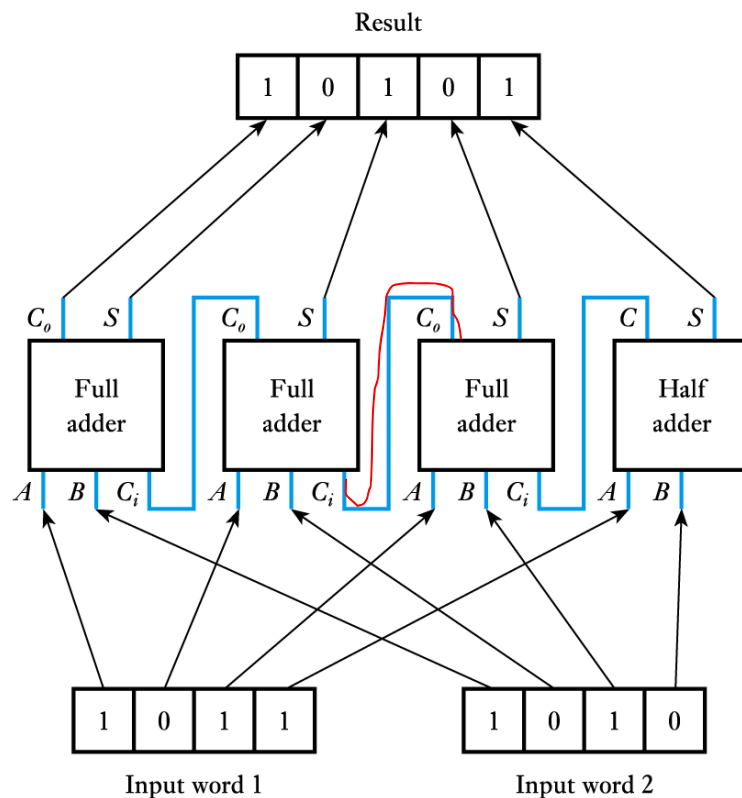

- A half adder can add two single bits
- To add multiple-bit words we also need a component that can also cope with a carry from the previous stage
- This is a **full adder**

■ A full adder

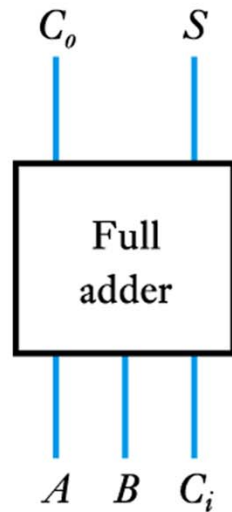

(a)

A	B	C_i	C_o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(b)

		AB			
	C_o	00	01	11	10
C_i	0	0	0	1	0
	1	0	1	1	1


		AB			
	S	00	01	11	10
C_i	0	0	1	0	1
	1	1	0	1	0

$$C_o = \bar{A}BC_i + A\bar{B}C_i + ABC_i + AB\bar{C}_i$$


$$C_o = AB + AC_i + BC_i$$

$$S = \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + AB\bar{C}_i + A\bar{B}C_i$$


■ Implementation of a full adder

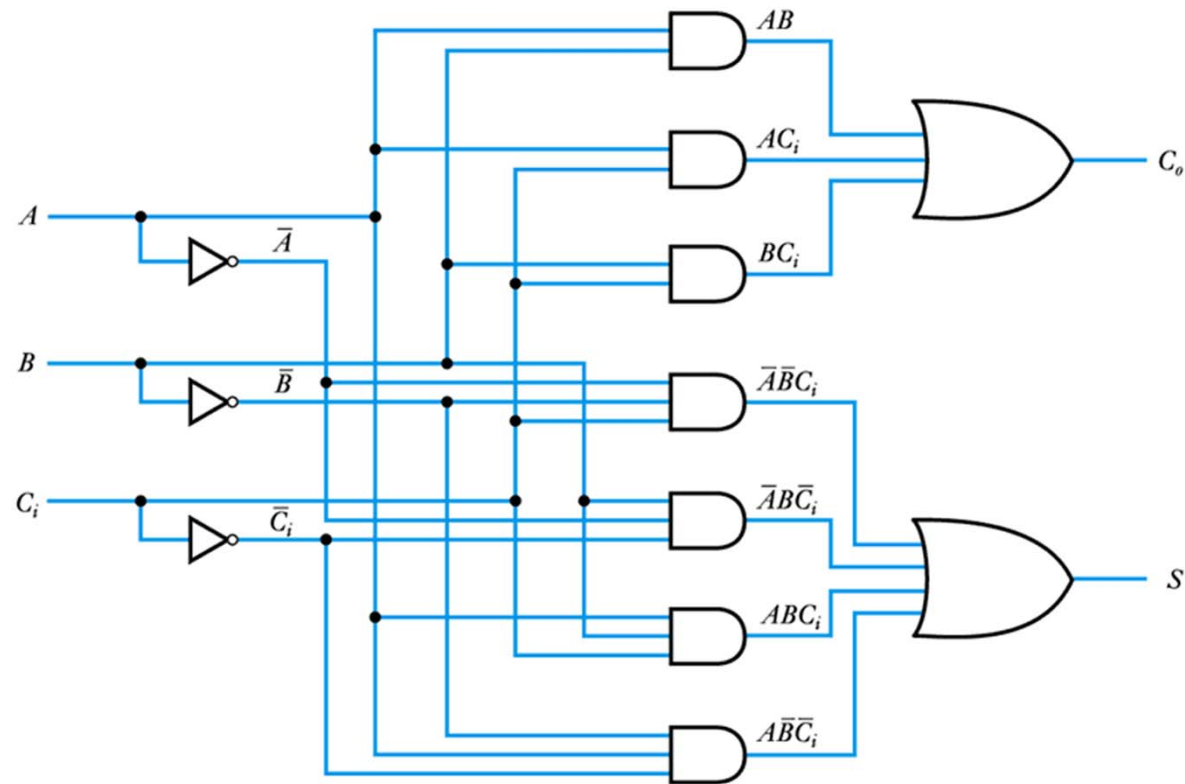

- A cascadable 4-bit adder

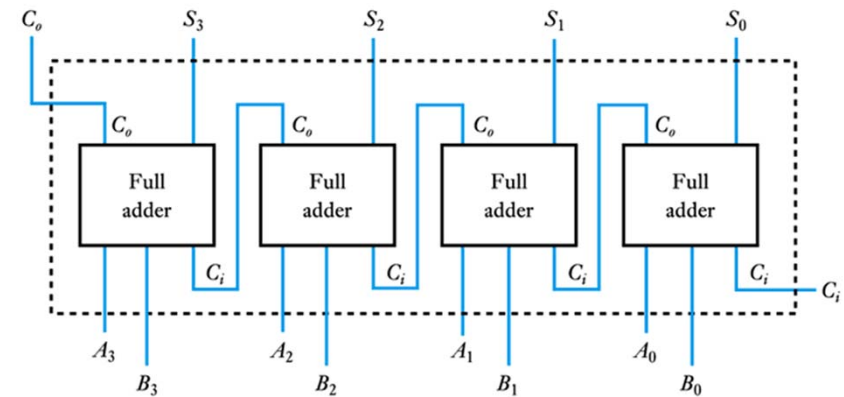

(a) A typical 4-bit adder

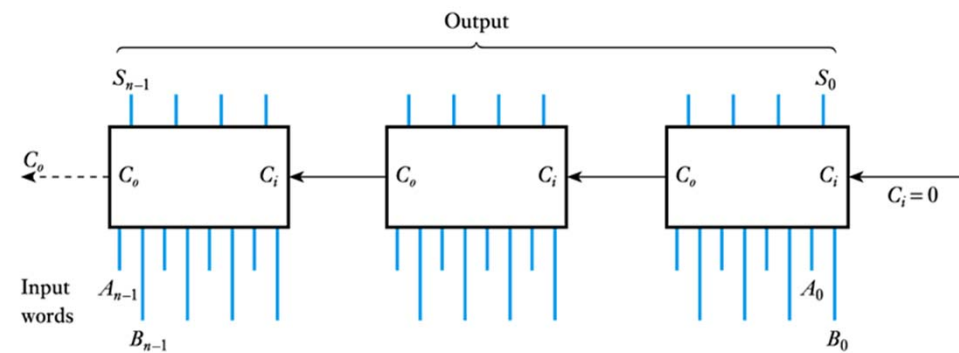

(b) Cascaded circuits


■ Binary subtraction

- A similar approach can be applied to subtraction
- A half subtractor has two outputs called:

D difference

B_o borrow output

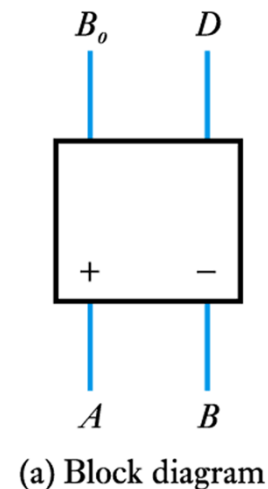
The inputs are also labelled
+ and – to show which is
subtracted from which



A	B	B_o	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

(b) Truth table

■ A 4-bit subtractor

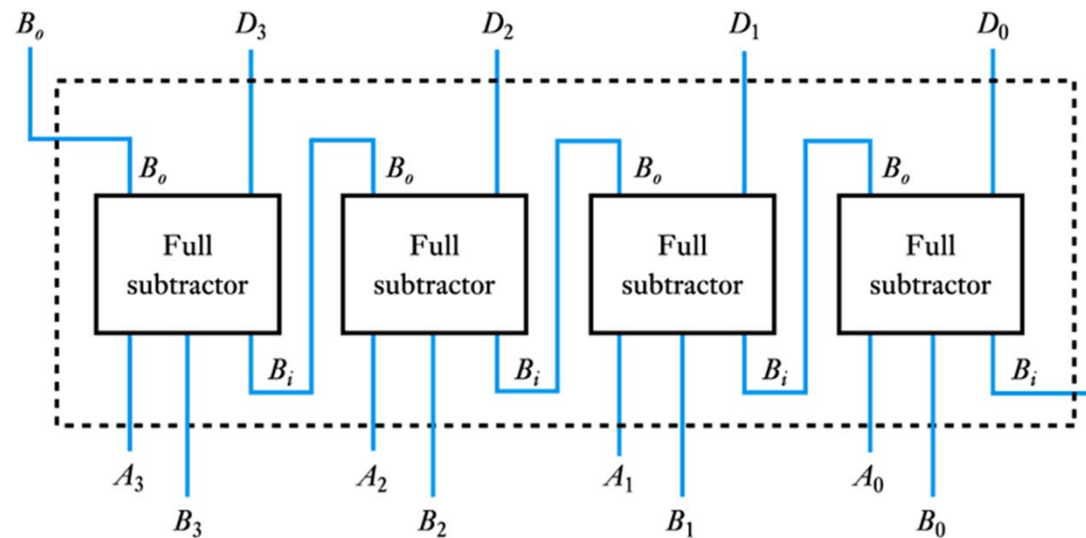

– These can be cascaded as with the adder circuits

■ Binary multiplication and division

- Although it is possible to construct circuits to perform multiplication and division using simple logic gates, it is fairly unusual as the complexity of the circuits makes them impractical
- It is more usual to use dedicated circuits containing large numbers of gates or to use a microprocessor
- We will look at such techniques in later lectures



Video 24G



24.12

Numeric and alphabetic codes

■ Binary code

- by far the most common way of representing numeric information
- has advantages of simplicity and efficiency of storage

Decimal	Binary
0	0
1	1
2	10
3	11
4	100
5	101
6	110
7	111
8	1000
9	1001
10	1010
11	1011
12	1100
etc.	etc.

24.33

■ Gray code

- used in Karnaugh maps
- also used in encoders and high-speed counters
- only one bit changes state between adjacent values
- allows counters/encoders to be read unambiguously

Decimal	Gray code
0	0000
1	0001
2	0011
3	0010
4	0110
5	0111
6	0101
7	0100
8	1100
9	1101
10	1111
11	1110
12	1010
13	1011
14	1001
15	1000

Examples of combinational logic design

- **Example** – see **Example 24.25** in the course text
- Design a circuit to convert 3-bit binary numbers into Gray code



– First we produce a Truth Table

dec	binary			Gray		
	A	B	C	X	Y	Z
0	0	0	0	0	0	0
1	0	0	1	0	0	1
2	0	1	0	0	1	1
3	0	1	1	0	1	0
4	1	0	0	1	1	0
5	1	0	1	1	1	1
6	1	1	0	1	0	1
7	1	1	1	1	0	0

- From the truth table we produce Karnaugh maps

		AB			
		00	01	11	10
C	X	0	0	1	1
	1	0	0	1	1

$X = A$


		AB			
		00	01	11	10
C	Y	0	1	0	1
	1	0	1	0	1

$Y = \bar{A}B + A\bar{B} = A \oplus B$

		AB			
		00	01	11	10
C	Z	0	1	1	0
	1	1	0	0	1

$Z = B\bar{C} + \bar{B}C = B \oplus C$

- and implement the circuit

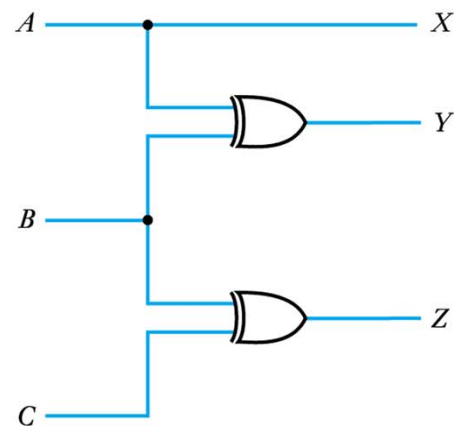

- **Further design examples**

- The text contains further combinational logic design examples:
- **Example 24.28:** A 4-input multiplexer



Video 24H Further Study

Further Study

- The Further Study section at the end of Chapter 24 is concerned with the design of fault tolerant arrangements, such as those used within critical systems within aircraft.
- Your task is to design a simple ‘voting’ arrangement, that allows a system to continue working correctly even in the event of a fault.
- Try the design and then look at the video.



24.38

Key points

- Logic circuits are usually implemented using logic gates
- Circuits in which the output is determined solely by the current inputs are termed combinational logic circuits
- Logic functions can be described by truth tables or using Boolean algebraic notation
- Boolean expressions can often be simplified by algebraic manipulation, or using techniques such as Karnaugh maps
- Binary digits may be combined to form digital words that can be processed using binary arithmetic
- Several codes can be used to represent different forms of information