







Video 18A



18.6

FET amplifiers-ac amplifier

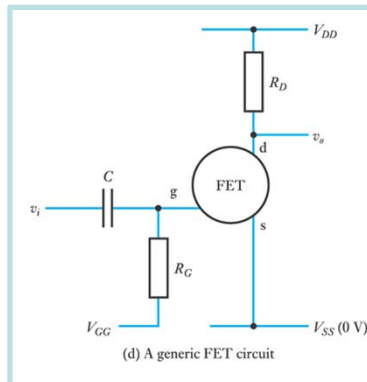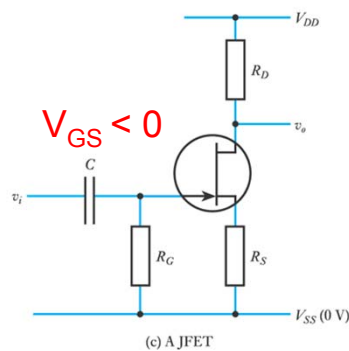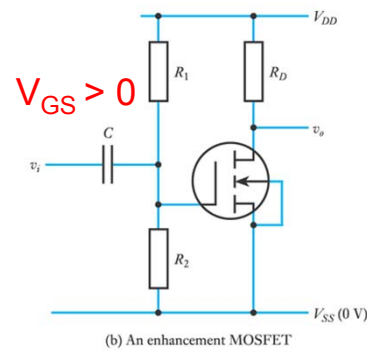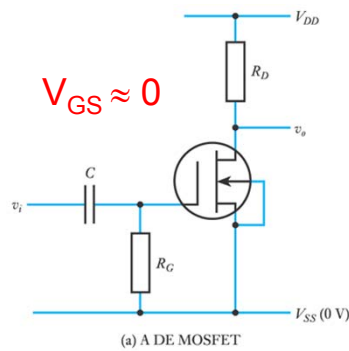

Equivalent



Circuit

Where


Transconductance

$$g_m = di_D/dV_{GS}$$

$$= i_D/v_{GS}$$

and the small letters refer to

only the AC part (e.g. $v_{DD}=0$)

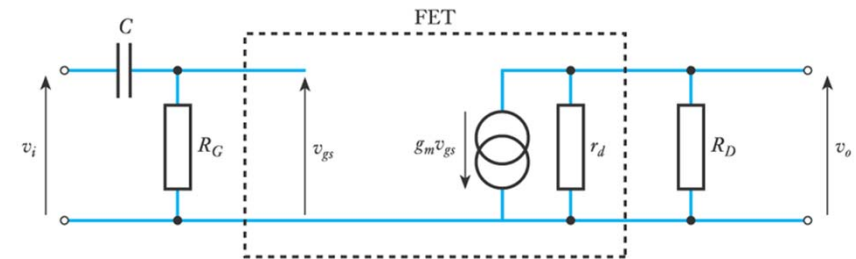

$$\text{voltage gain} = \frac{v_o}{v_i} \approx -g_m R_D$$

$$r_i \approx R_G \quad \text{can be made very big}$$

$$r_o \approx R_D \quad \text{all for } r_d \gg R_D$$


18.1



Video 18C

A negative feedback amplifier

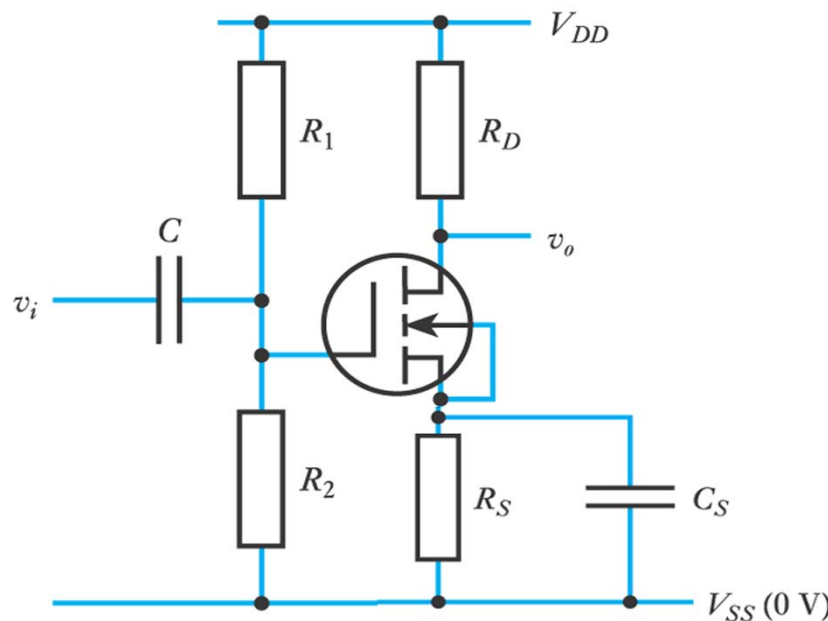- Feedback can be used not only to stabilise the biasing conditions of a circuit, but also its **(low)** voltage gain



$$\text{voltage gain} = \frac{v_o}{v_i} \approx -\frac{R_D}{R_S}$$

$$r_i \approx R_1 \parallel R_2$$

$$r_o \approx R_D$$

– characteristics set by **stable passive components**



18.2


- Introduction
- An overview of bipolar transistors
- Bipolar transistor operation
- A simple amplifier
- Bipolar transistor characteristics
- Bipolar amplifier circuits
- Bipolar transistor applications
- Circuit examples




An overview of bipolar transistors

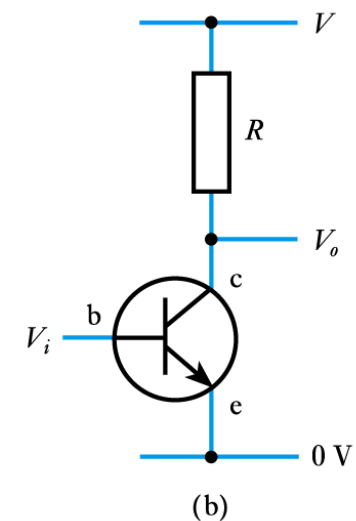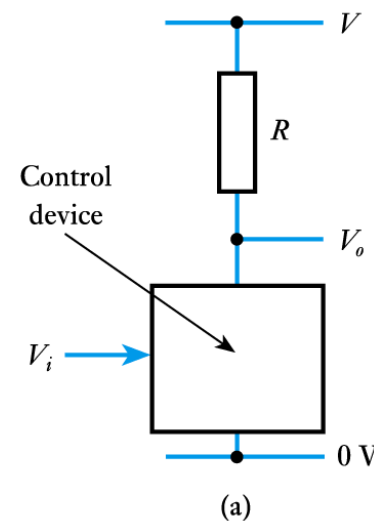- FET is a single pn-junction
 - control is due to an electric *field or potential* at gate,
- Bipolar transistor has two pn-junctions
 - control is considered to be due to a *current* at the base
 - Current into one terminal determines the current between two others
 - As with a FET, a bipolar transistor can be used as a 'control device'



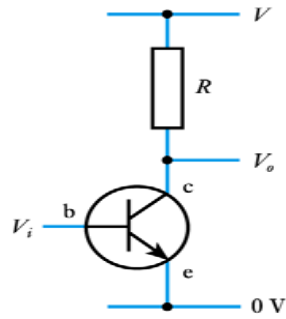



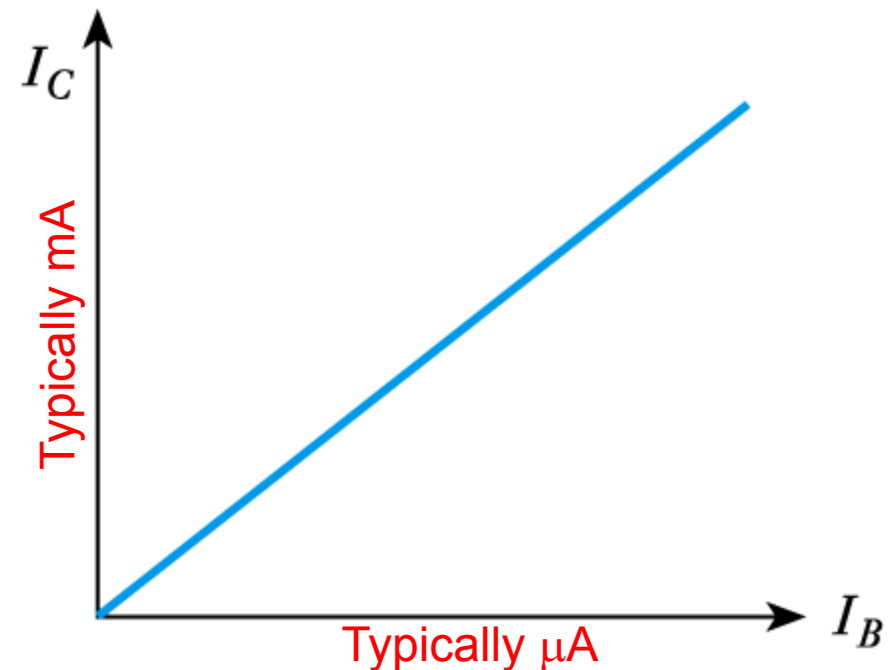
- Relationship between the collector current and the base current in a bipolar transistor
 - approximately linear
 - Collector current generally \gg base current
 - the device provides **current gain**






18.5

■ Construction

- two polarities:
npn and *pnp*

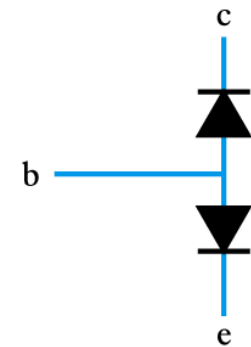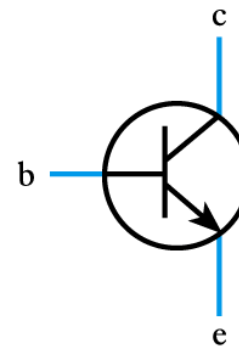
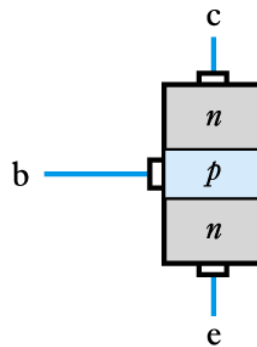


(a) An *npn* transistor

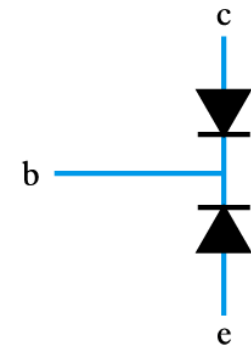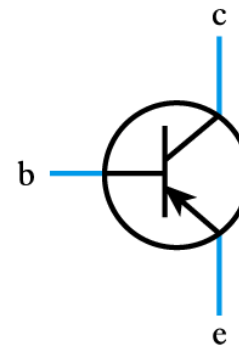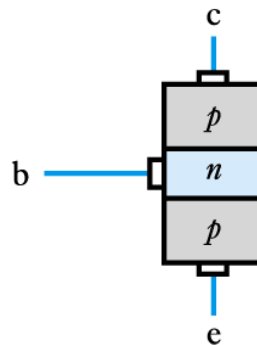



(b) An *pnp* transistor

Bipolar transistor operation

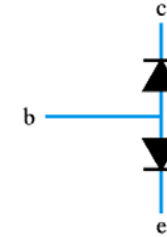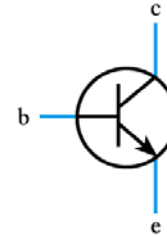

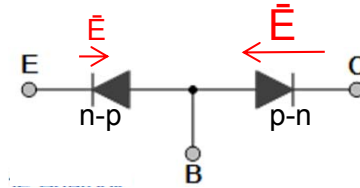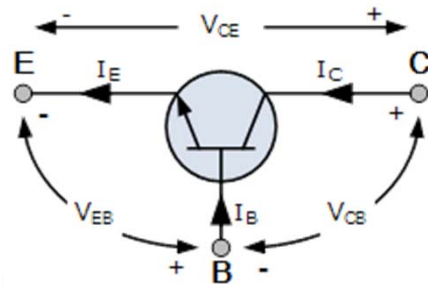19.3


- We will consider *npn* transistors
 - *pnp* devices are similar but with different polarities of voltage and currents
 - when using *npn* transistors
 - collector is normally more positive than the emitter
 - V_{CE} might be a few volts
 - device resembles two back-to-back diodes – but has very different characteristics
 - with the base open-circuit negligible current flows from the collector to the emitter




- If the base is made more positive than the emitter
 - This forward biases the base-emitter junction
 - The base region is lightly doped and very thin
 - Because it is lightly doped, the current produced is mainly electrons flowing from the emitter to the base
 - Because the base region is thin, most of the electrons entering the base get swept across the base-collector junction (by E field there) into the collector
 - This produces a collector current (I in opposite direction of electron motion) that is much larger than the base current – this gives **current amplification**

NPN \Rightarrow **Not Pointing iN**
Negative-Positive-Negative = on

- **Transistor action**

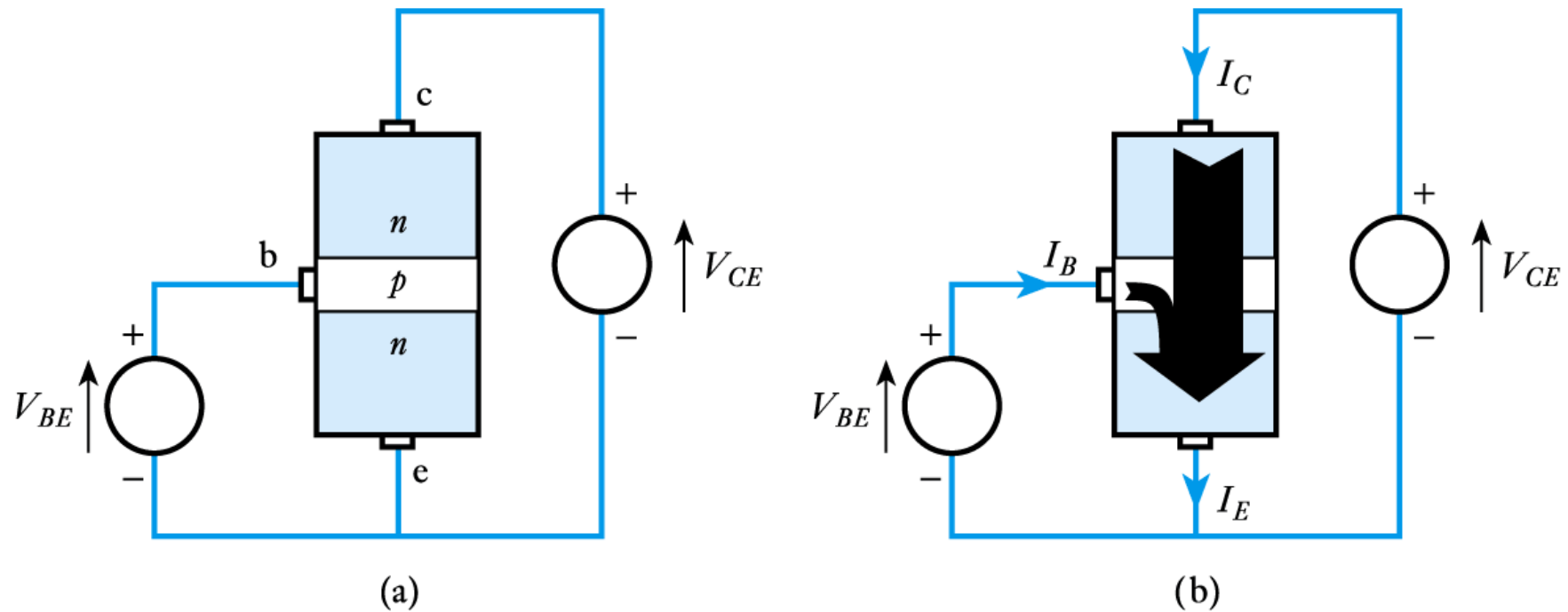


Set the way-back machine, Sherman

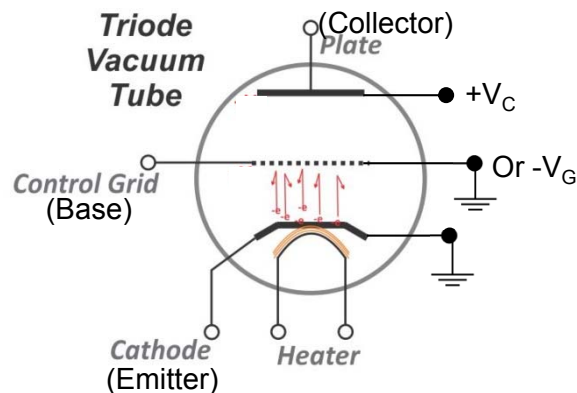

- A NPN transistor!

- Off state,

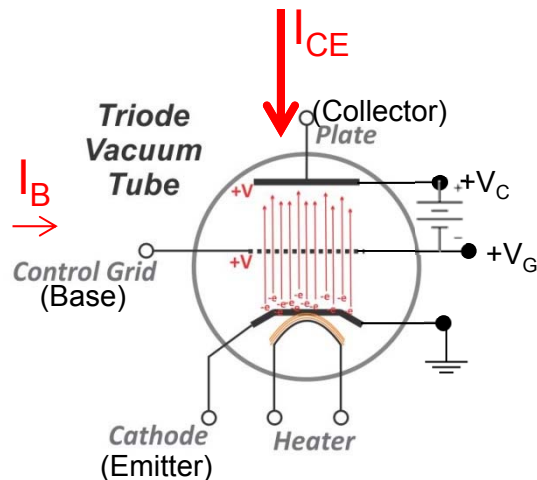- Electrons emitted but shielded from $+V_C$ by grid that is at ground or slightly negative $-V_G$
- Only a few make it to collector



- On state

- Emitted electrons accelerate towards grid at $+V_G$
- Most pass through the grid (a few electrons collected)
- Remainder see $+V_C (>V_G)$, and accelerate towards it
- Large number of electrons collected at collector.
- Small Base current, large Collector→Emitter current

18.10


NPN transistor in “on” bias state

Current attracts
electrons in
collector material

Collector

Base

Emitter

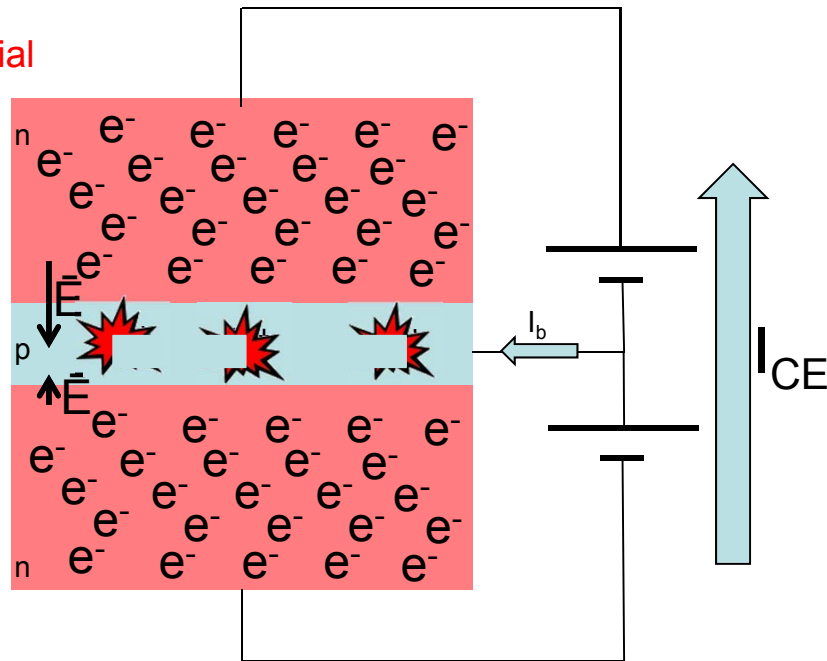

Current repels
electrons in emitter
material

- Bias creates current flow from emitter to collector
- Electrons in collector recombine with holes from battery
- Electrons in emitter get repelled and pushed into base by electrons from battery
- Very few recombine in base. The few that do, create the small base current
- Most get pushed into the depletion region of the base-collector
- There they accelerate through the electric field into the collector
- Get large, continuous I_{CE} current


18.11

Is it a current or voltage device? Answer: Yes

- How do I increase I_B ?
- Increase the forward bias ($I_B = I_{BS} \cdot e^{40 \cdot V_{BE}}$)
 - Where I_{BS} is a constant for the device
 - This lowers the base-emitter pn-barrier
 - This also makes the depletion region smaller
- More electrons are pushed through barrier
- I_C increases proportionately with I_B


- Behaviour can be described by the **current gain, h_{fe}** or by the **transconductance, g_m** of the device

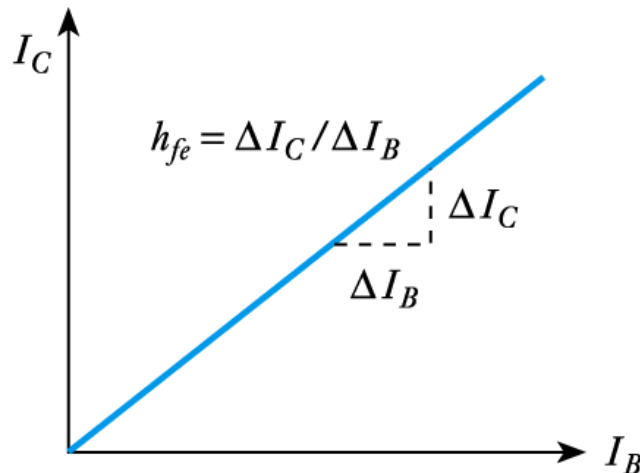The AC gain of the device
 $i_c = h_{fe} \cdot i_b$ ($I \Rightarrow DC, i \Rightarrow AC, \text{ or } \Delta I$)



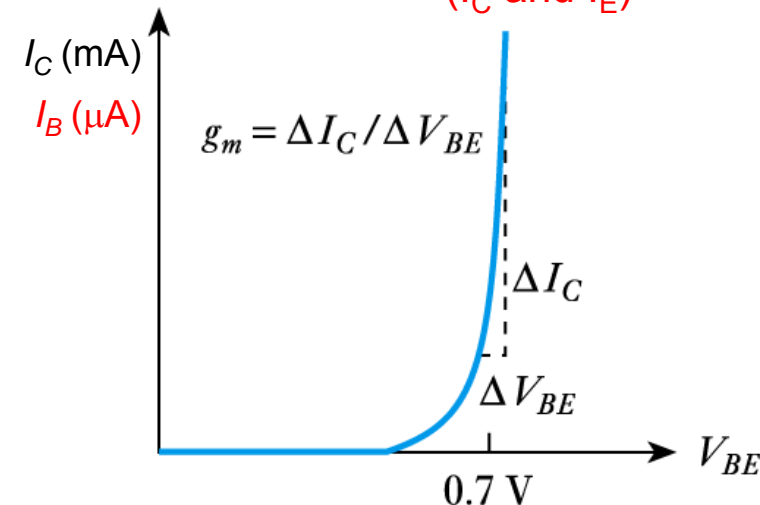(a) Relationship between output current and input current

Looks like a diode since I_C is \approx linear with I_B !
 Note g_m depends on where device is operated (I_C and I_E)



(b) Relationship between output current and input voltage




Video 19A



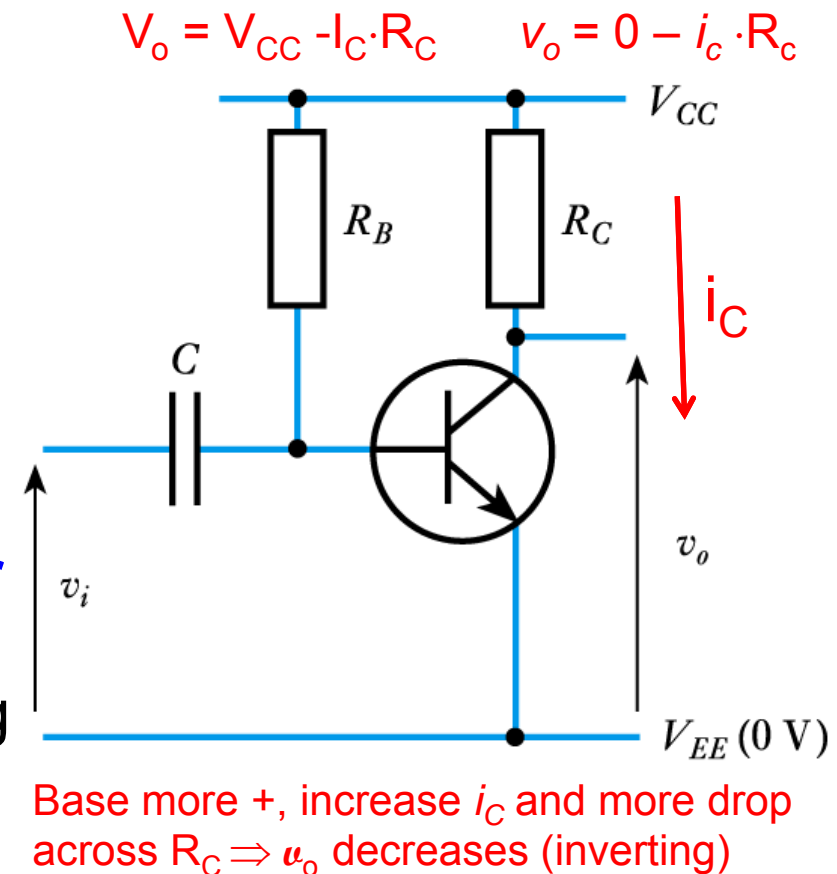19.4

A simple amplifier ($\pm v_i$)

- The circuit shows a simple amplifier
 - R_B is used to ‘**bias**’ the transistor by injecting an appropriate base current
 - **Forward biases B-E**
 - C is a **coupling capacitor** and is used to couple the AC signal while preventing external circuits from affecting the bias
 - This is an **AC-coupled amplifier**




18.14

Bipolar transistor characteristics


■ Transistor configurations

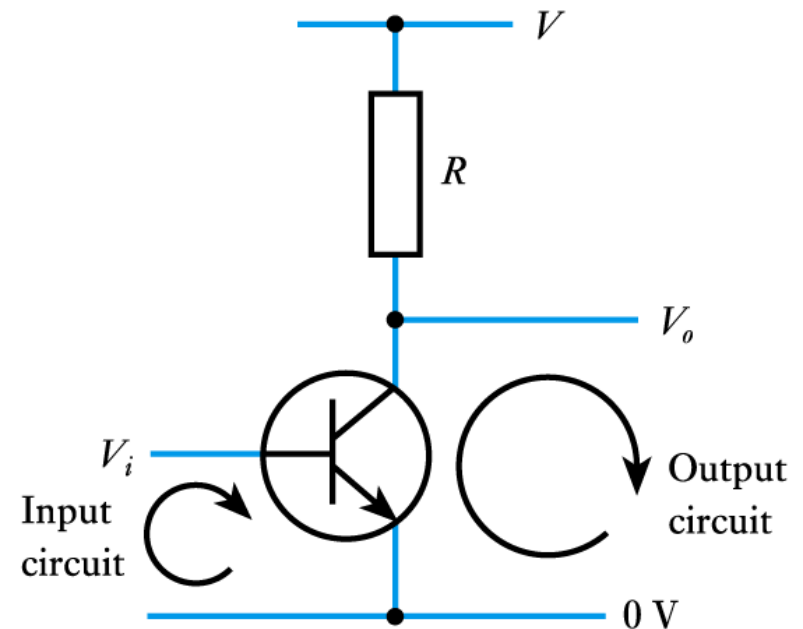- Transistors can be used in a number of configurations
- Most common is as shown
- *Emitter* terminal is common to input and output circuits
- This is a **common-emitter** configuration
- We will look at the characteristics of the device in this configuration



■ Input characteristics

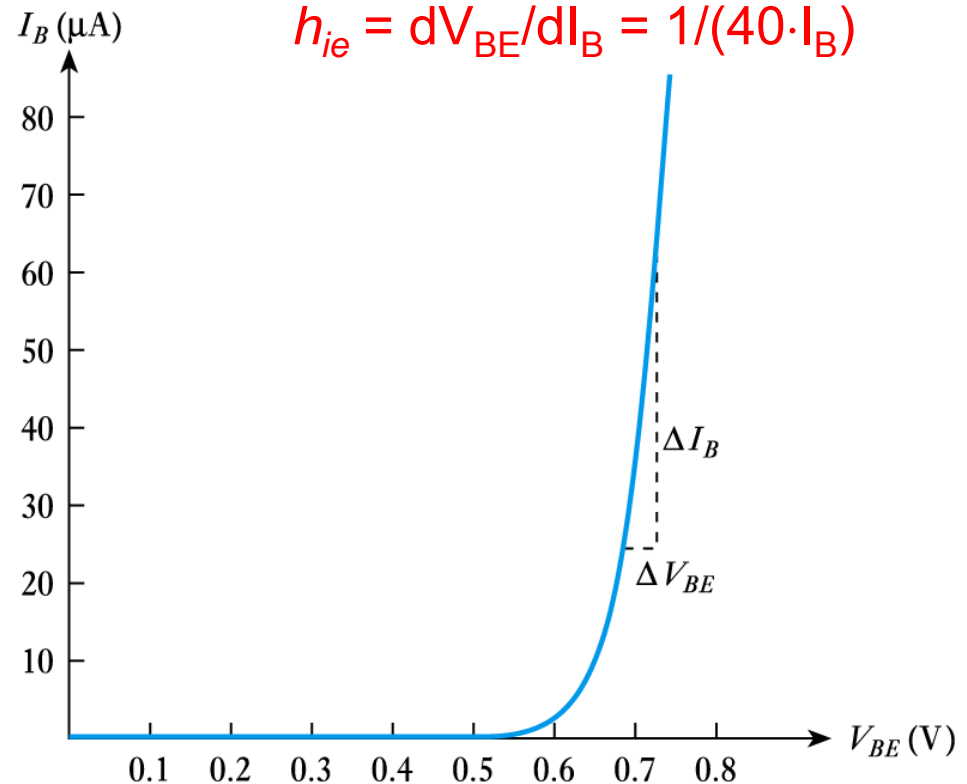- The input takes the form of a forward-biased *pn* junction
- The input characteristics are therefore similar to those of a semiconductor diode




$$I_B \approx \text{Constant} \cdot e^{40 V_{BE}}$$


\therefore input resistance:

$$h_{ie} = dV_{BE}/dI_B = 1/(40 \cdot I_B)$$

■ Output characteristics

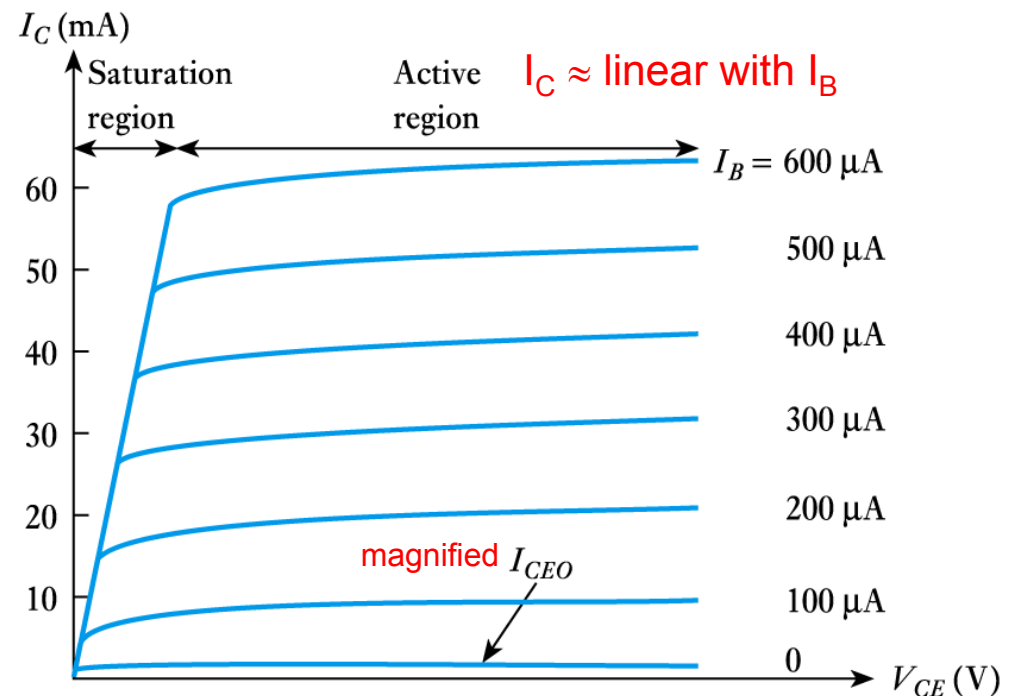
- region near to the origin is the **saturation region**
- this is normally avoided in linear circuits
- slope of lines represents the **output resistance** (r_o)



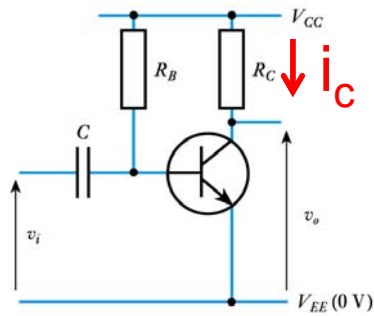

$$V_o = V_{CC} - I_C \cdot R_C \quad v_o = 0 - i_c \cdot R_C$$

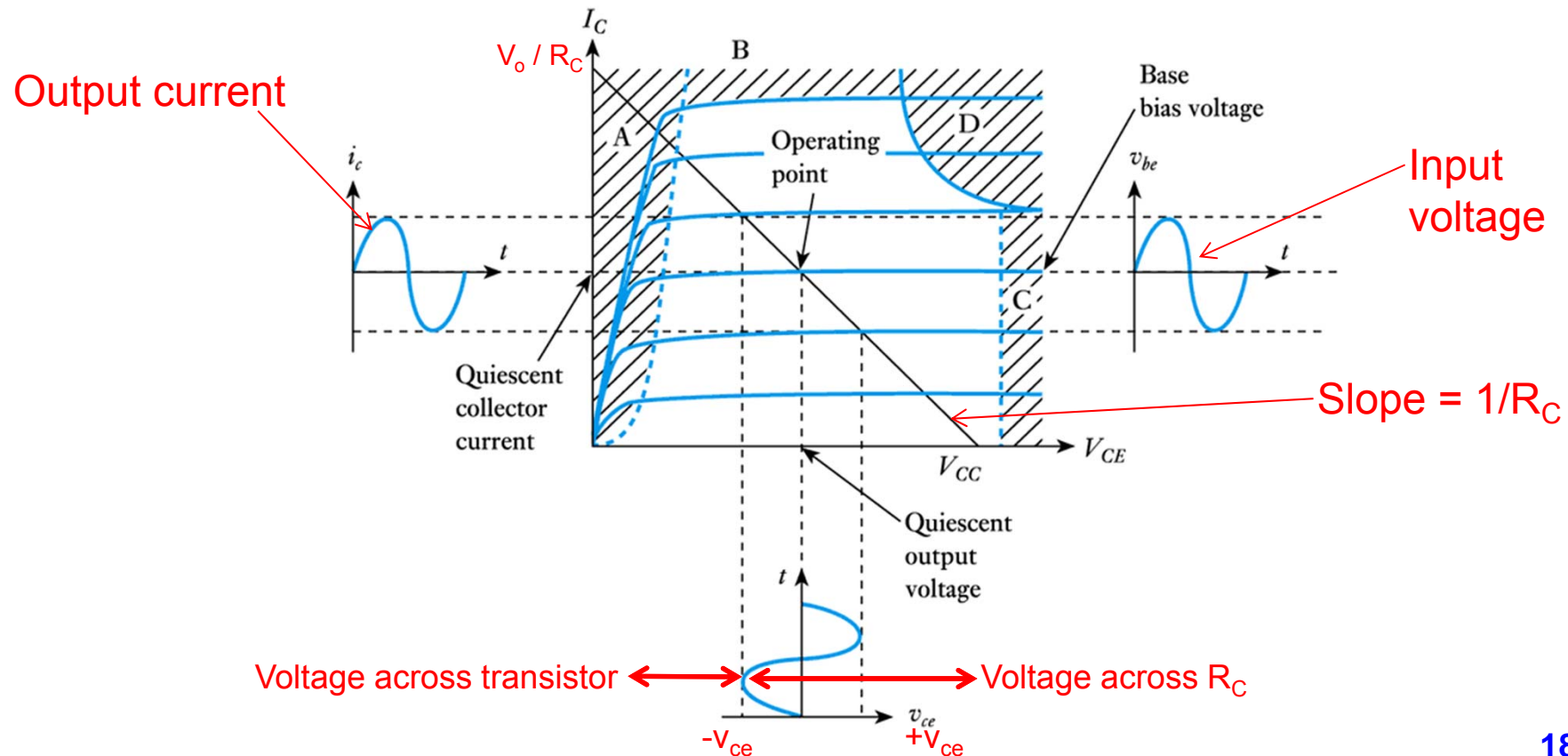■ Choice of operating point in a simple amplifier



■ Transfer characteristics


- can be described by either the current gain or by the transconductance
- DC current gain h_{FE} or β is given by I_C / I_B
- AC current gain h_{fe} is given by i_c / i_b
- transconductance g_m ($=dI_C/dV_{BE}$) is given approximately by
$$g_m \approx 40 \cdot I_C \approx 40 \cdot I_E \text{ siemens}$$

(Since $I_C \approx \text{Constant} \cdot e^{40V_{BE}}$)


-
- the units of g_m are those of admittance
 - therefore $1/g_m$ has the units of resistance
 - the quantity $1/g_m$ is termed the **emitter resistance r_e**
 - therefore
$$r_e = \frac{1}{g_m} \approx \frac{1}{40I_C} \approx \frac{1}{40I_E} \Omega$$

■ Simple equivalent circuits for a bipolar transistor

Base current control

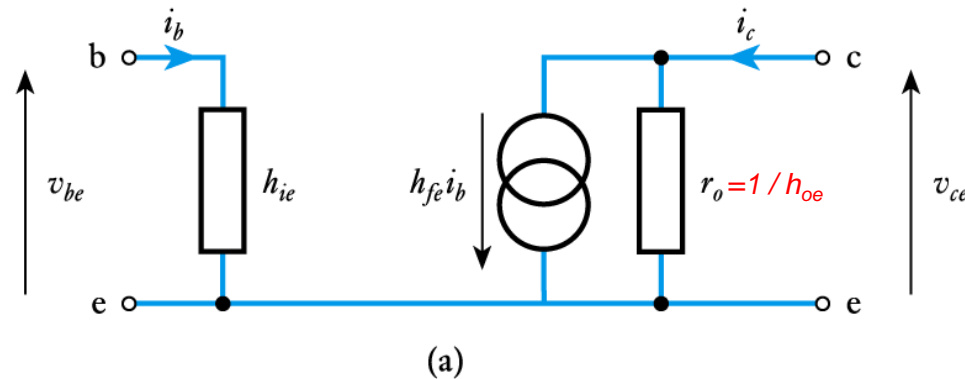

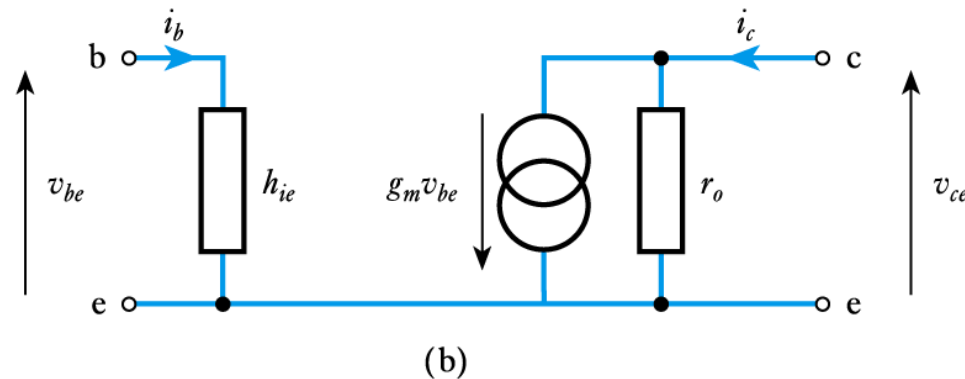
Base voltage producing
a base current control




V_{CE} affects the base bias
Called the Early effect

■ Limitations of the simple models

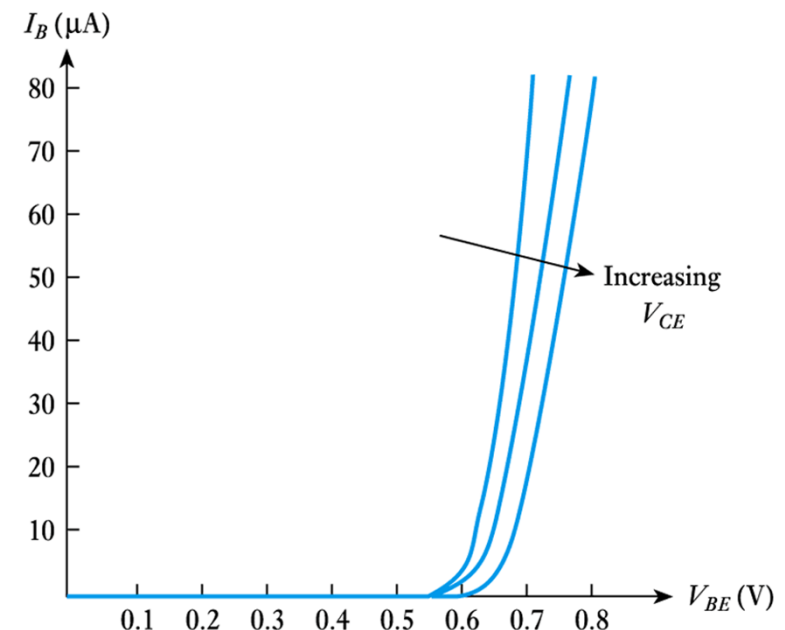- While the simple models shown above give a reasonable representation of the behaviour of devices they do not show the effects of the output voltage on the input (as shown here)
- This can be modelled by the reverse transfer ratio h_{re}




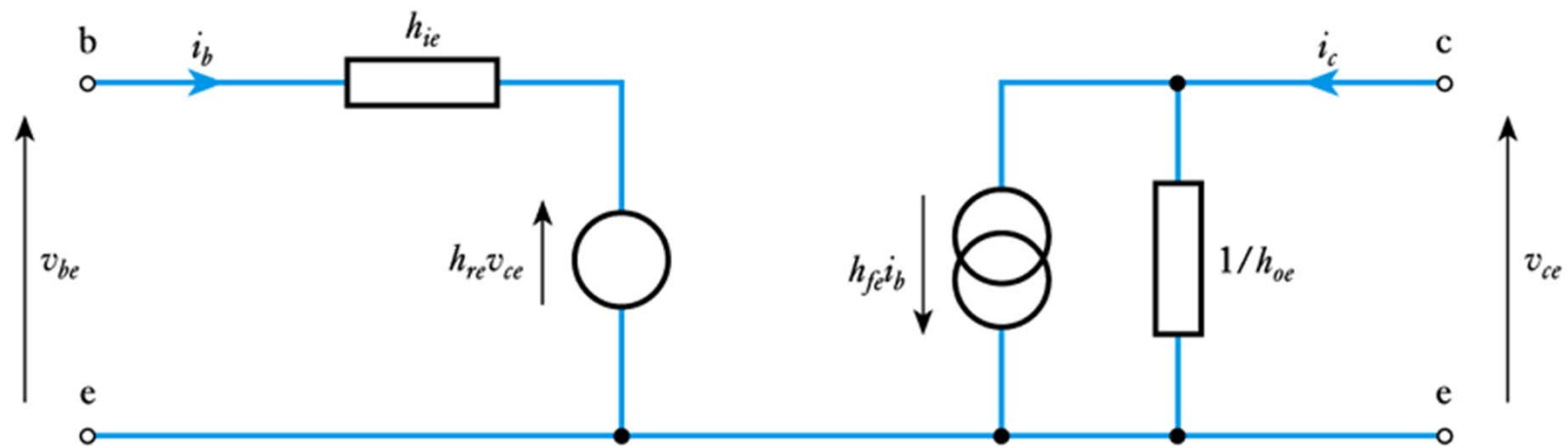- The hybrid-parameter model
(accounting for Early effect)




■ The hybrid- π model

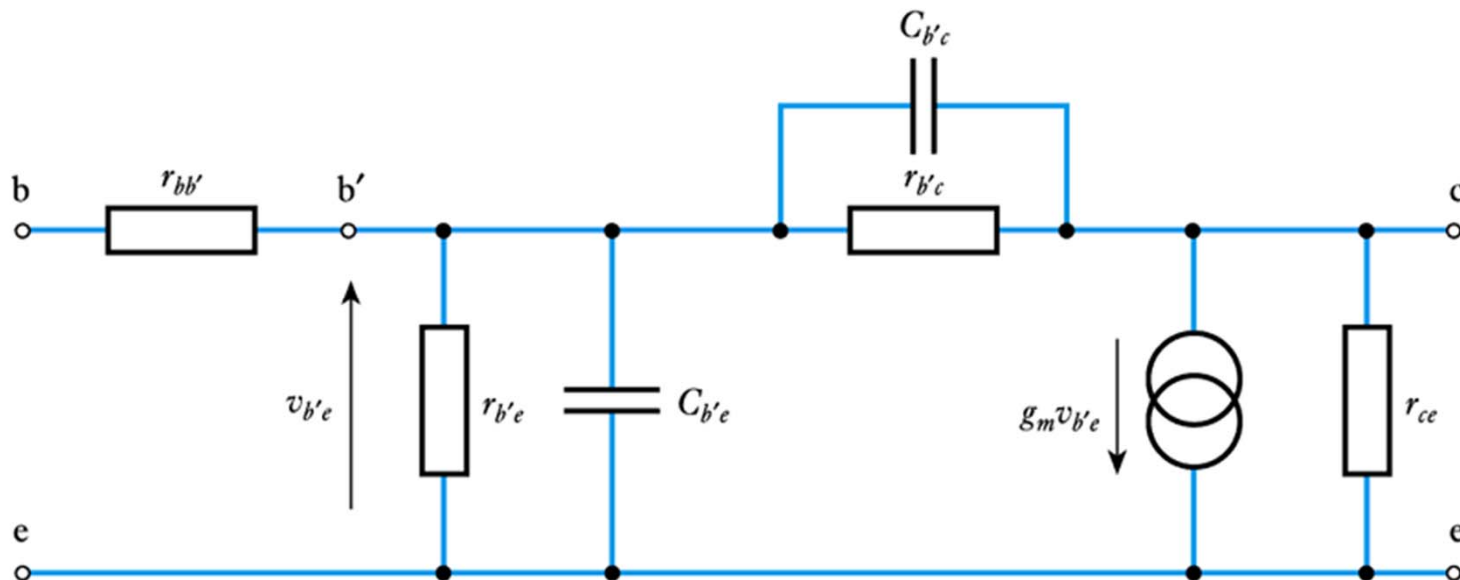- gives a better representation at high frequencies
- High $f \Rightarrow$ base, emitter and collector coupled capacitively



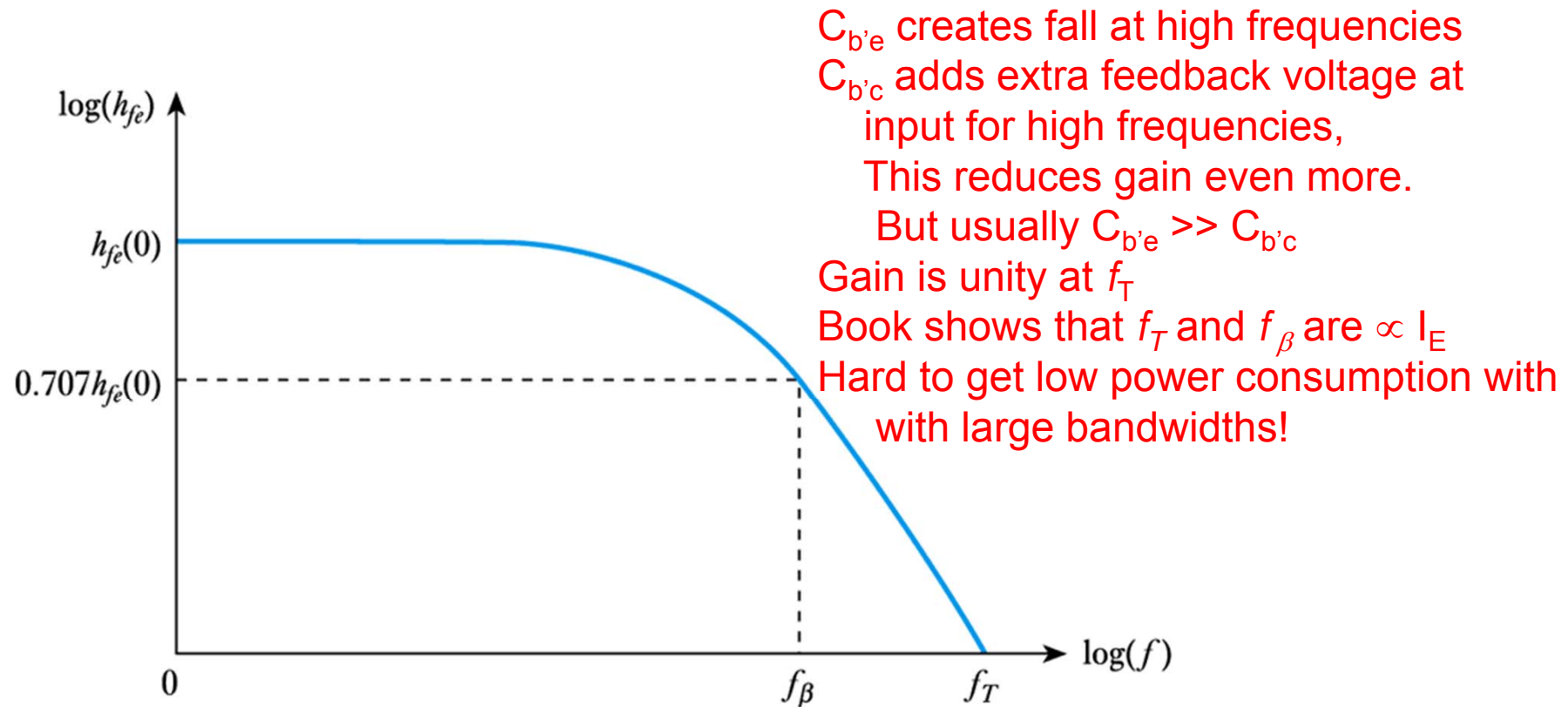■ Bipolar transistors at high frequencies



BJT parameters for common emitter configuration (subscript _e)

■ Input_i Output_o Forward_f Reverse_r

h_{FE}	DC gain	I_C / I_B	
h_{fe}	AC gain	i_c / i_b	$h_{FE} \approx h_{fe}$ (mostly)
g_m	Transconductance	$\Delta I_C / \Delta V_{BE} = i_c / v_{be}$	$\sim 40 \cdot I_C \approx 40 \cdot I_E$
h_{ie}	Small signal input resistance	$\Delta V_{BE} / \Delta I_B = v_{be} / i_b$	$\sim 1 / (40 \cdot I_B) \Omega \approx h_{fe} / (40 \cdot I_C)$
h_{oe}	Output admittance ($1/r_o$) where r_o = Slope in the active region	$\Delta I_C / \Delta V_{CE} = i_c / v_{ce}$	
r_e	Emitter resistance	$\Delta V_{BE} / \Delta I_C = v_{be} / i_c = 1/g_m$	$\approx v_{be} / i_e$ that is, $h_{ie} = h_{fe} \cdot r_e$
h_{re}	Early effect (V_{CE} affects bias V_{BE})	$\Delta V_{CE} / \Delta V_{BE}$	

$h_{FE} = \frac{I_C}{I_B}$ $I_E = I_C + I_B = (h_{FE} + 1) \cdot I_B$ <p>but because $h_{FE} \gg 1$,</p> $I_E \approx h_{FE} \cdot I_B = I_C$	$I_B = I_{BS} \cdot e^{40 \cdot V_{BE}} \quad \text{where } I_{BS} \text{ is constant}$ $I_C = h_{FE} \cdot I_B = h_{FE} \cdot I_{BS} \cdot e^{40 \cdot V_{BE}}$ $g_m = \frac{\Delta I_C}{\Delta V_{BE}} = \frac{dI_C}{dV_{BE}} = 40 \cdot h_{FE} \cdot I_{BS} \cdot e^{40 \cdot V_{BE}}$ $g_m = \quad \quad \quad = 40 \cdot I_C \approx 40 \cdot I_E$
--	---

18.26

BJT parameters for common emitter configuration (subscript _e)

Input

h_{FE}	D
h_{fe}	A
g_m	T
h_{ie}	S
h_{oe}	C
r_e	E
h_{re}	E

$$h_{FE} = \frac{I_C}{I_B}$$

$$I_E = I_C + I_B$$

but $I_E \approx I_C$



We will only use these to derive results
Just Remember the results!

Reverse

	ly)
	$\approx h_{fe} / (40 \cdot I_C)$
	is, $h_{ie} = h_{fe} \cdot r_e$

constant

$$I_{CQ} \cdot e^{40 \cdot V_{BE}}$$

$$\frac{0 \cdot I_E}{I_E}$$


18.27

Key points

- Bipolar transistors are widely used in both analogue and digital circuits
- They can be considered as either voltage-controlled or current-controlled devices
- Their characteristics may be described by their current gain or by their transconductance
- Many amplifier circuits use transistors in a common-emitter configuration where the input is applied to the base and the output is taken from the collector

Next time: Bipolar junction transistors

- Introduction
- An overview of bipolar transistors
- Bipolar transistor operation
- A simple amplifier
- Bipolar transistor characteristics
- **Bipolar amplifier circuits**

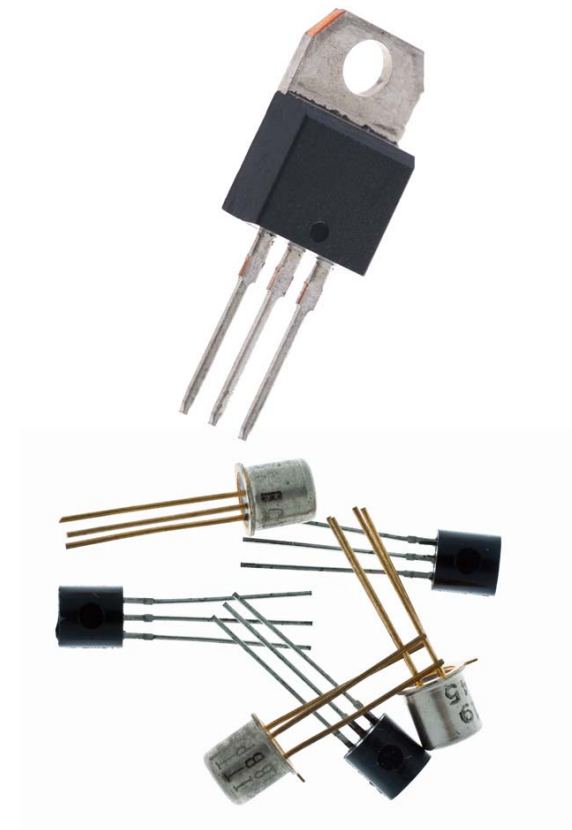



Video 19A




19.6

Bipolar amplifier circuits

■ Analysis of a simple amplifier

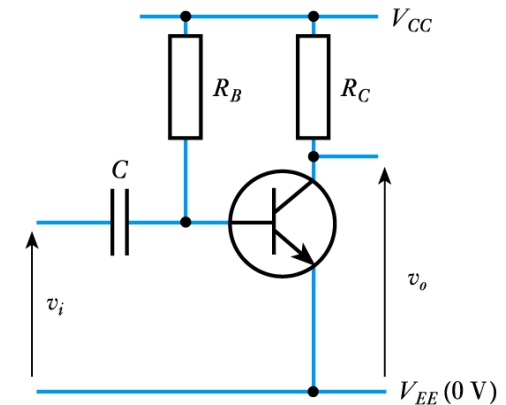- Earlier we looked at a simple amplifier
- This is an AC-coupled amplifier
- It is convenient to look at its **DC (or quiescent)** behaviour separately from its **AC (or small signal)** behaviour




19.30

DC analysis of a simple amplifier

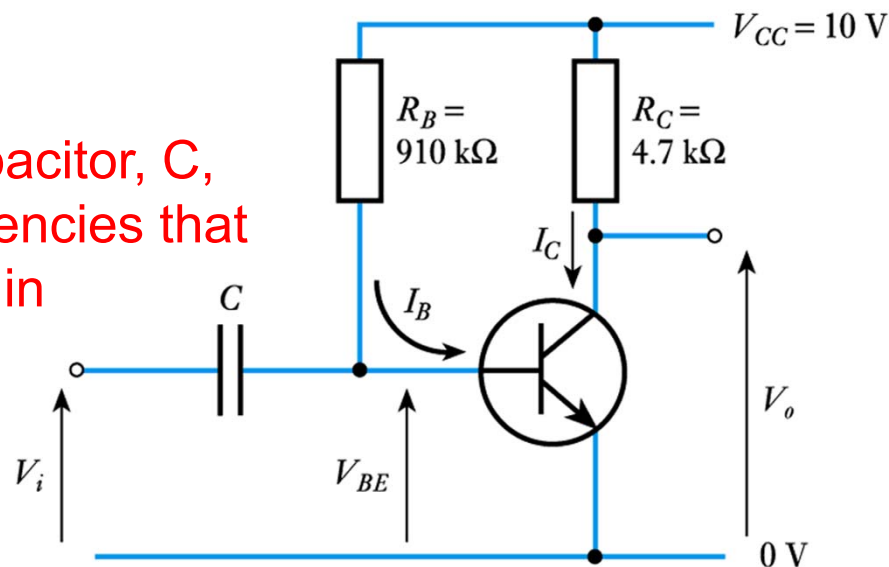- **Example** — see **Example 19.1** from course text

Determine the quiescent collector current and the quiescent output voltage of the following circuit, given that the h_{FE} of the transistor is 100

Note AC coupling capacitor, C , will remove low frequencies that we are not interested in



■ Example (continued)

- The base-to-emitter voltage V_{BE} is approximately 0.7 V.
- Therefore


$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{10 - 0.7 \text{ V}}{910 \text{ k}\Omega} = 10.2 \mu\text{A}$$

- Therefore

$$I_C = h_{FE} I_B = 100 \times 10.2 \mu\text{A} = 1.02 \text{ mA}$$


- and
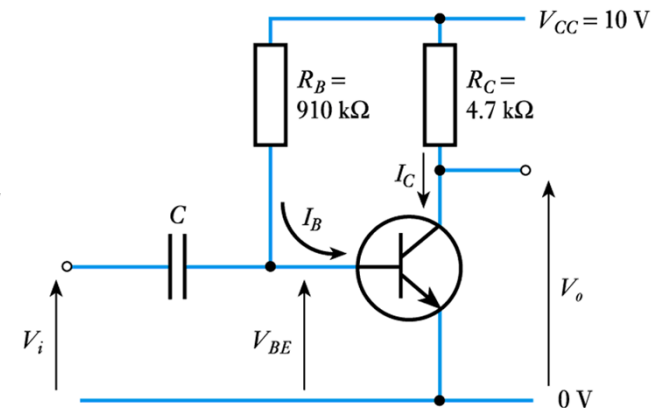
$$V_o = V_{CC} - I_C R_C = 10 - 1.02 \times 10^{-3} \times 4.7 \times 10^3 \approx 5.2 \text{ V}$$



Small signal analysis of an amplifier

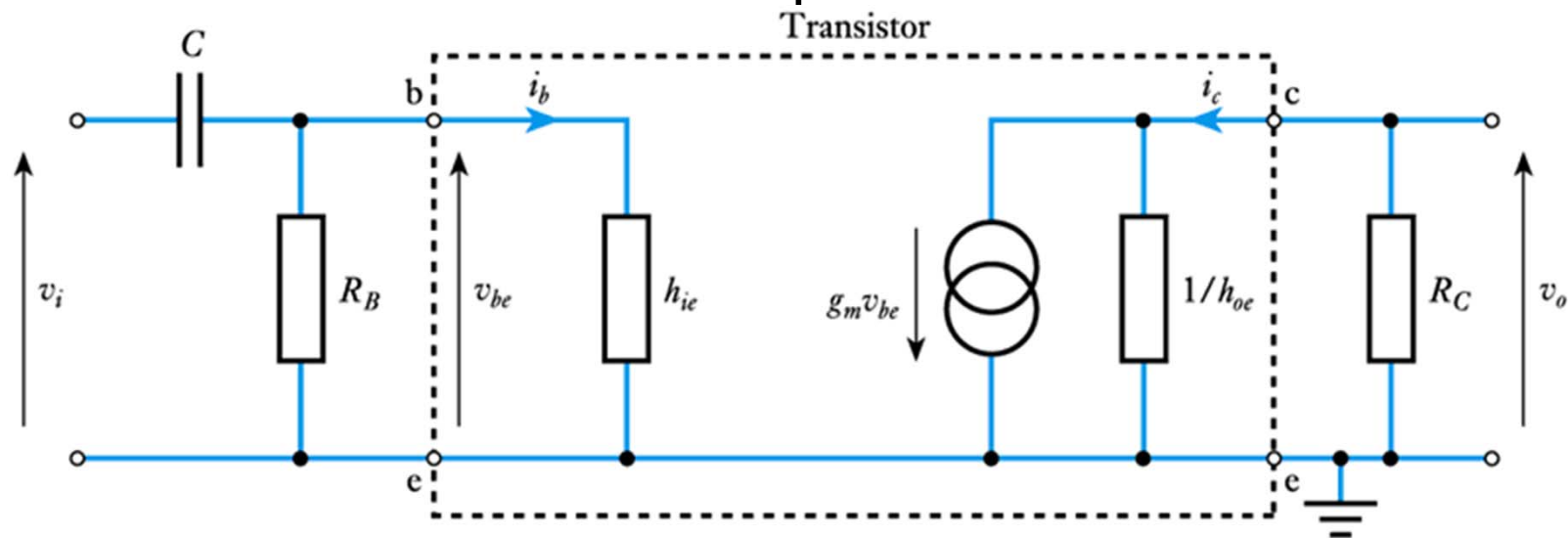- To determine the small-signal behaviour of the circuit, we first construct a small-signal equivalent circuit
 - We start with our model of the transistor
 - Then add the other components



19.33

- From the equivalent circuit,

$$V_{be} = V_i$$


and therefore

$$V_o = -g_m V_{be} \left(\frac{1}{h_{oe}} \parallel R_C \right) = -g_m V_i \left(\frac{1}{h_{oe}} \parallel R_C \right)$$

so

$$\text{voltage gain} = \frac{V_o}{V_i} = -g_m \left(\frac{1}{h_{oe}} \parallel R_C \right) = -g_m \frac{R_C}{h_{oe} R_C + 1}$$

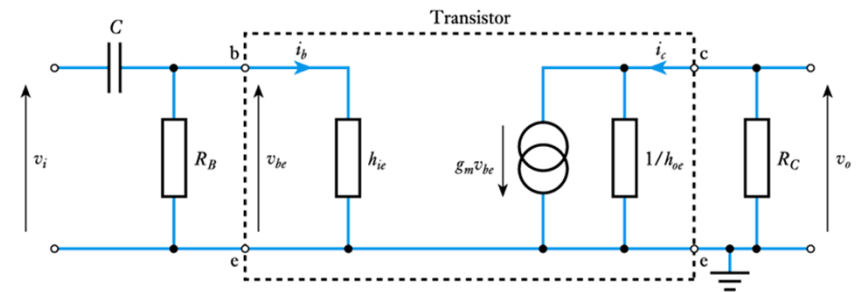Usually, $1/h_{oe} \gg R_C$, so $\text{voltage gain} = \frac{V_o}{V_i} = -g_m R_C = -\frac{R_C}{r_e}$




$$\text{voltage gain} = \frac{v_o}{v_i} = -g_m R_C = -\frac{R_C}{r_e}$$

Had $h_{FE} = 100$ and $h_{oe} = 100 \mu\text{S}$, calculated $I_E \approx I_C = 1.02 \text{ mA}$, $I_B = 10.2 \mu\text{A}$
 So we need to get g_m for the gain, and h_{ie} , for the input resistance


- **Same Example** — see **Example 19.2** from course text

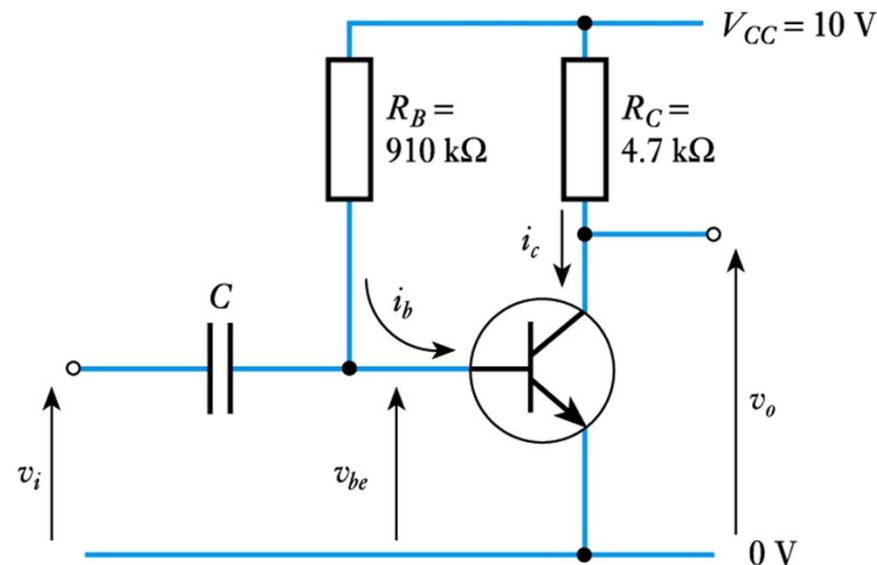Determine the small signal voltage gain, input resistance and output resistance of the following circuit, given that $h_{fe} = 100$ and $h_{oe} = 100 \mu\text{S}$



■ Example (continued)

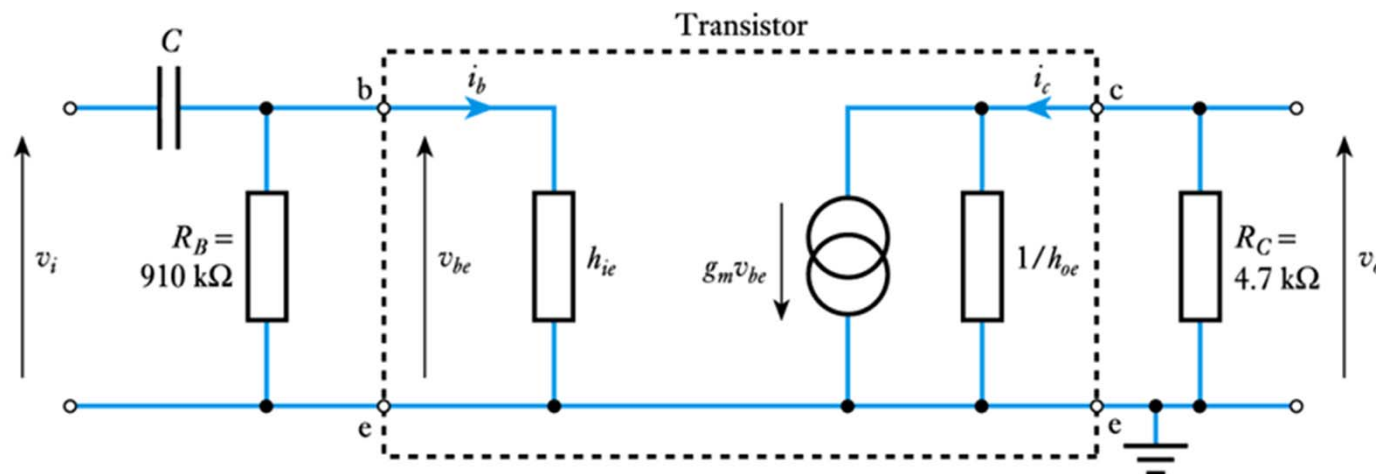The small signal equivalent circuit
and we want g_m and h_{ie}



Definitions :

$$g_m = \frac{i_c}{v_{be}} \Rightarrow i_c = g_m \cdot v_{be}$$

$$h_{fe} = \frac{i_c}{i_b} \Rightarrow i_c = h_{fe} \cdot i_b$$

$$\text{then } i_b \cdot h_{fe} = g_m \cdot v_{be}$$

$$h_{ie} = \frac{v_{be}}{i_b} \Rightarrow i_b = \frac{v_{be}}{h_{ie}}$$

$$\text{so } \frac{v_{be}}{h_{ie}} \cdot h_{fe} = g_m \cdot v_{be}$$

$$\text{or } h_{ie} = \frac{h_{fe}}{g_m}$$

19.36

Remember :

$$I_B = I_{BS} \cdot e^{40 \cdot V_{BE}}$$

$$g_m = \frac{i_c}{v_{be}} = \frac{\Delta I_C}{\Delta V_{BE}} = \frac{\partial (h_{FE} \cdot I_B)}{\partial V_{BE}} = 40 \cdot I_C$$

And :

$$h_{ie} = \frac{h_{fe}}{g_m}$$

- We first need to establish g_m and h_{ie} . From the earlier example $I_E \approx I_C = 1.02$ mA
Therefore

$$g_m = \frac{dI_C}{dV_{BE}} \approx 40 \cdot I_C \approx 40 \cdot I_E \approx 40.8 \text{ mS}$$


- **Voltage gain**

$$\text{voltage gain} = -g_m \frac{R_C}{h_{oe}R_C + 1} = -40.8 \times 10^{-3} \frac{4700}{10 \times 10^{-6} \times 4700 + 1} \approx -183$$

or, using the approximation

$$\text{voltage gain} \approx -g_m R_C = -40.8 \times 10^{-3} 4700 \approx -192$$

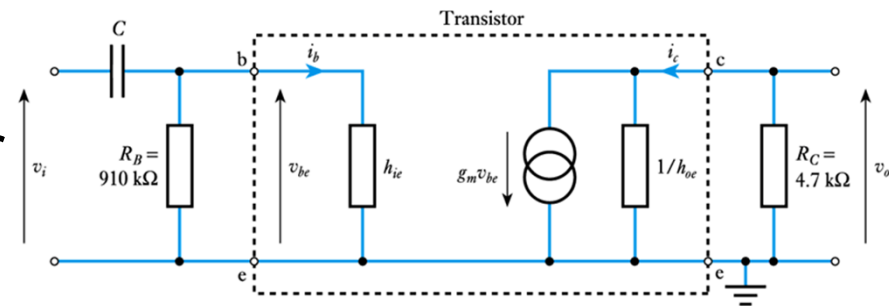Given all the \approx , this seems a reasonable approximation



$$h_{ie} \approx \frac{h_{fe}}{40 I_E} \approx \frac{100}{40 \times 1.02 \times 10^{-3}} \approx 2.45 \text{ k}\Omega$$

■ Input resistance

- from the equivalent circuit the input resistance is simply $R_B // h_{ie}$
- Since $R_B \gg h_{ie}$


$$r_i = R_B // h_{ie} \approx h_{ie} \approx 2.4 \text{ k}\Omega$$

■ Output resistance


- from the equivalent circuit the output resistance is $R_C // (1/h_{oe})$

$$r_o = R_C // (1/h_{oe}) \approx 4700 // 100,000 \approx 4.5 \text{ k}\Omega$$

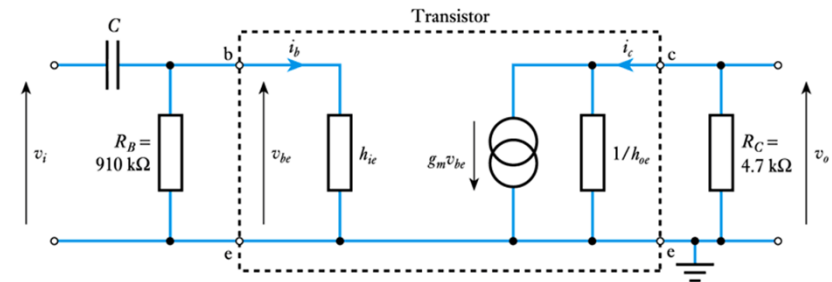- Since $R_C \ll 1/h_{oe}$ then $R_C // (1/h_{oe}) \approx R_C$ and therefore $r_o \approx R_C$



Summary: bipolar transistor-no feedback

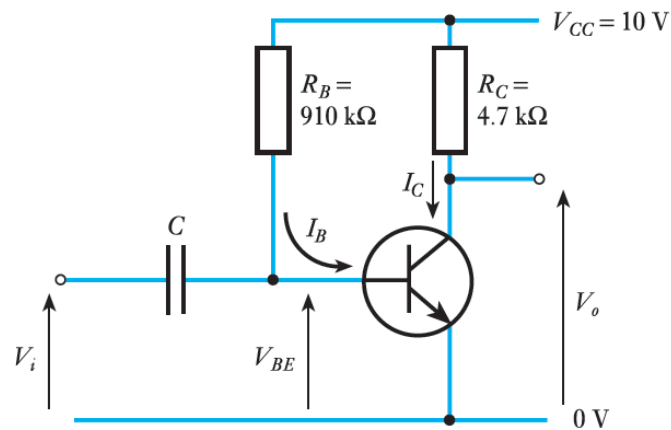


DC-large signal

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} :$$

$$I_C = h_{FE} I_B$$

$$V_o = V_{CC} - I_C R_C$$

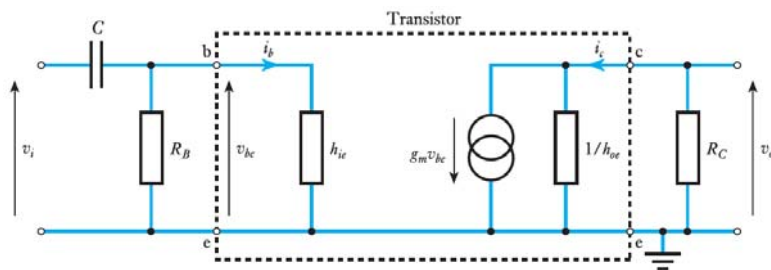

AC-small signal

$$\frac{v_o}{v_i} = -g_m \cdot \frac{R_C}{h_{oe} \cdot R_C + 1}$$

$$r_i = \frac{h_{ie}}{\frac{h_{ie}}{R_B} + 1}$$


$$r_o = \frac{R_C}{h_{oe} \cdot R_C + 1}$$

$$R_C \ll \frac{1}{h_{oe}} \Rightarrow \frac{v_o}{v_i} \approx -g_m \cdot R_C$$

$$R_B \gg h_{ie} \Rightarrow r_i \approx h_{ie}$$

$$R_C \ll \frac{1}{h_{oe}} \Rightarrow r_o = R_C$$

Problems with this circuit

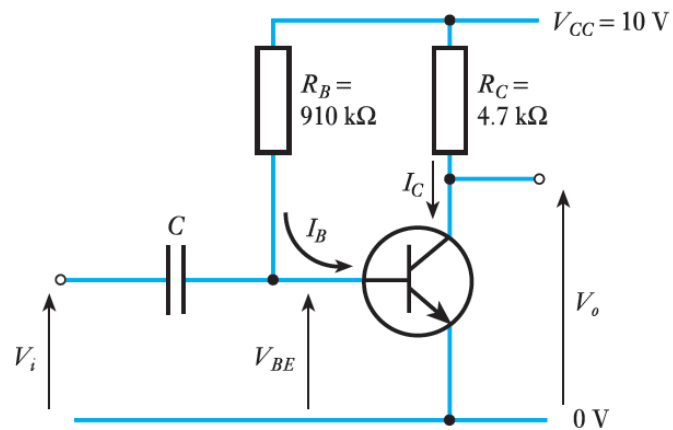

AC gains depend on:


Properties of transistor

And since $g_m \approx 40 \cdot I_C$,

$v_o/v_i \approx -40 \cdot V_{RC}$

the signal gain changes with DC operating point

R_L interacts with R_C to change gain

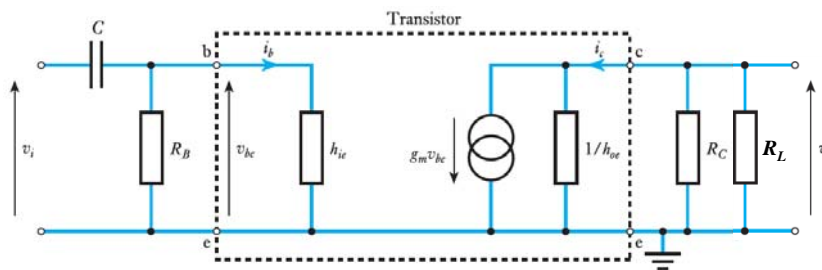

AC-small signal

$$\frac{v_o}{v_i} = -g_m \cdot \frac{R_C}{h_{oe} \cdot R_C + 1}$$

$$R_C \ll \frac{1}{h_{oe}} \Rightarrow \frac{v_o}{v_i} \approx -g_m \cdot R_C$$

$$r_i = \frac{h_{ie}}{\frac{h_{ie}}{R_B} + 1}$$


$$R_B \gg h_{ie} \Rightarrow r_i \approx h_{ie}$$

$$r_o = \frac{R_C}{h_{oe} \cdot R_C + 1}$$

$$R_C \ll \frac{1}{h_{oe}} \Rightarrow r_o = R_C$$

19.40

Problems with this circuit

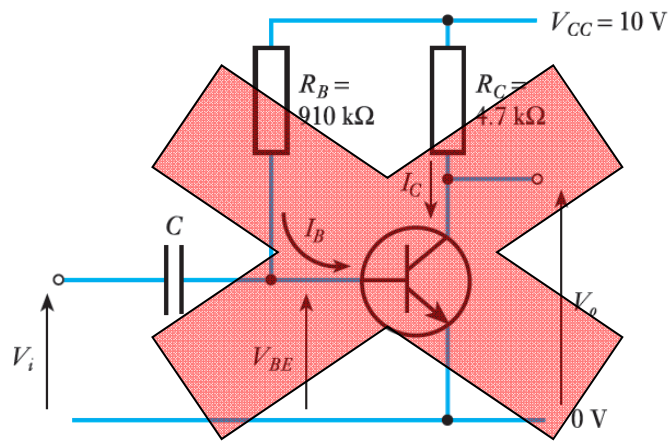

AC gains depend on:


Properties of transistor

And since $g_m \approx 40 \cdot I_C$,

$v_o/v_i \approx -40 \cdot V_{RC}$

the signal gain changes with DC operating point

R_L interacts with R_C to change gain

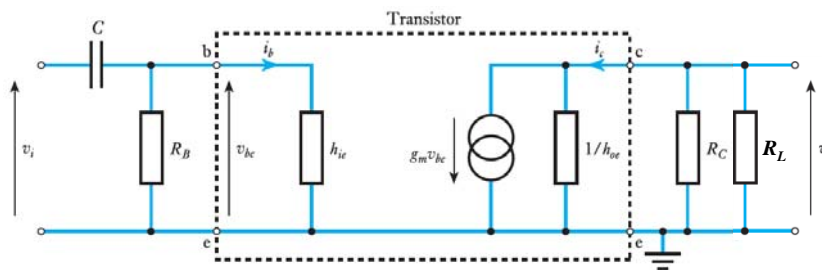

AC-small signal

$$\frac{v_o}{v_i} = -g_m \cdot \frac{R_C}{h_{oe} \cdot R_C + 1}$$

$$R_C \ll \frac{1}{h_{oe}} \Rightarrow \frac{v_o}{v_i} \approx -g_m \cdot R_C$$

$$r_i = \frac{h_{ie}}{\frac{h_{ie}}{R_B} + 1}$$

$$R_B \gg h_{ie} \Rightarrow r_i \approx h_{ie}$$

$$r_o = \frac{R_C}{h_{oe} \cdot R_C + 1}$$

$$R_C \ll \frac{1}{h_{oe}} \Rightarrow r_o = R_C$$



19.41



Video 19C

The use of feedback

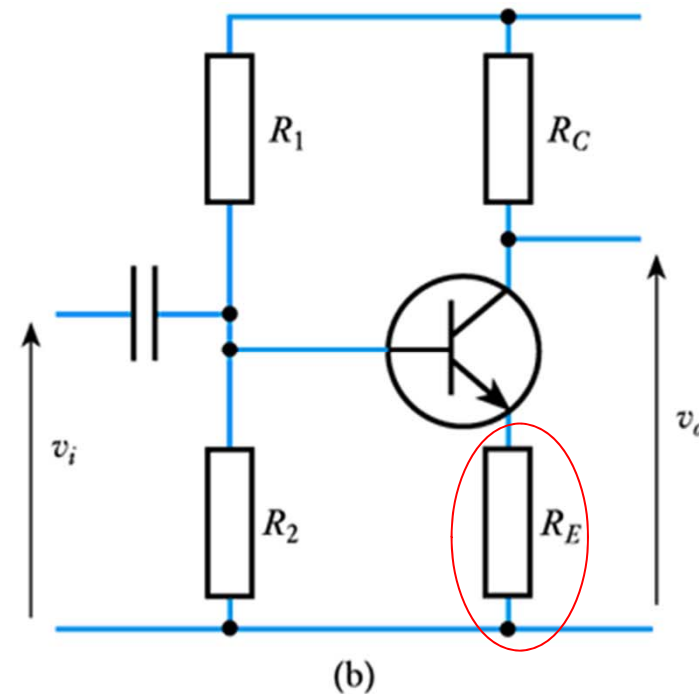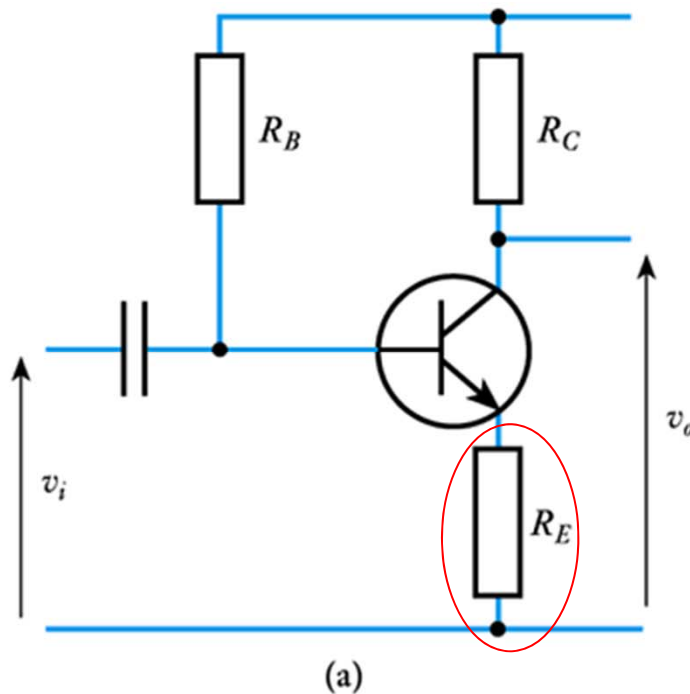
- Feedback can be used to overcome the effects of device variability. Consider the following circuits



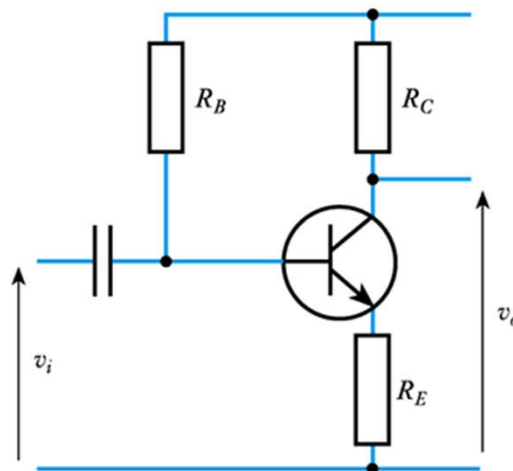
19.42

How does this work?

- As $v_i \approx v_b$ rises, v_{be} forward bias increases and more i_b flows
- This causes more current, i_c , to flow
- This increases the voltage at the top of R_E (*catches up to v_i*)
- And this reduces the v_{be} forward bias
- Voltage at the top of R_E tracks $v_b \approx v_i$, and reduces gain




(a)

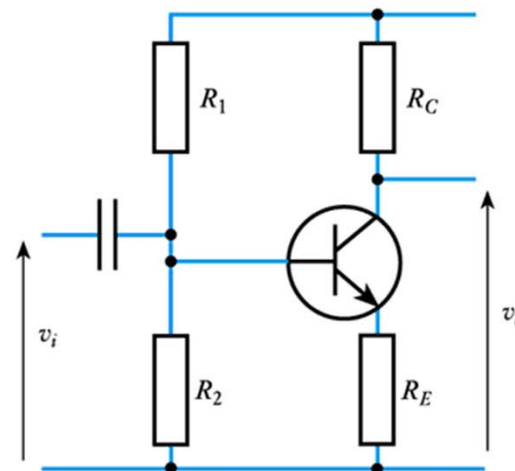

(b)

Analysis of amplifier with feedback

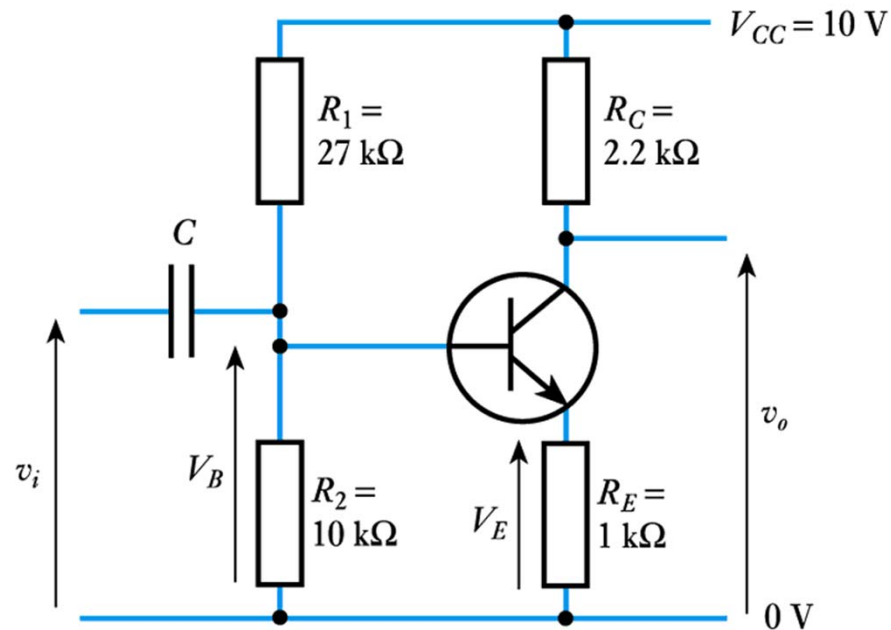
- See **Example 19.3** from course text
Determine the quiescent voltages and currents in the following circuit
- See **Example 19.4** from course text
Determine the small-signal behaviour of the following circuit



19.44

Results: Bipolar transistor-with feedback

DC-large signal

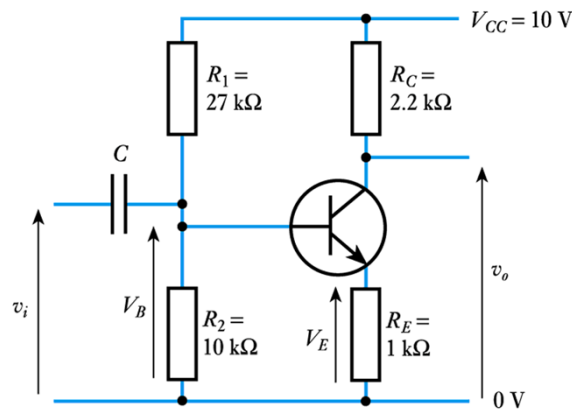

$$V_B \approx V_{CC} \frac{R_2}{R_1 + R_2}$$

$$V_E = V_B - V_{BE}$$

$$V_{BE} \approx \text{constant} \approx 0.7\text{V}$$

$$I_B \ll I_C \approx I_E$$

$$I_E \approx I_C = \frac{V_E}{R_E}$$

$$V_o = V_{CC} - I_C R_C$$

Gain, r_i and r_o only depend on passive components

AC-small signal

$$\frac{v_o}{v_i} = - \frac{R_C}{R_E + \frac{1}{g_m}}$$

$$R_E \gg \frac{1}{g_m}$$

$$\Rightarrow \frac{v_o}{v_i} \approx - \frac{R_C}{R_E}$$

$$r_b = h_{ie} + (h_{fe} + 1) R_E \quad h_{fe} \cdot R_E \gg h_{ie} \gg 1 \Rightarrow r_b \approx h_{fe} \cdot R_E$$


$$r_i = R_1 \parallel R_2 \parallel r_b$$

$$r_b \gg R_1 \approx R_2 \Rightarrow r_i \approx \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$r_o = R_C \parallel \left(\frac{1}{h_{oe}} + R_E \right)$$

$$R_C \ll \frac{1}{h_{oe}} + R_E \Rightarrow r_o \approx R_C$$


19.45

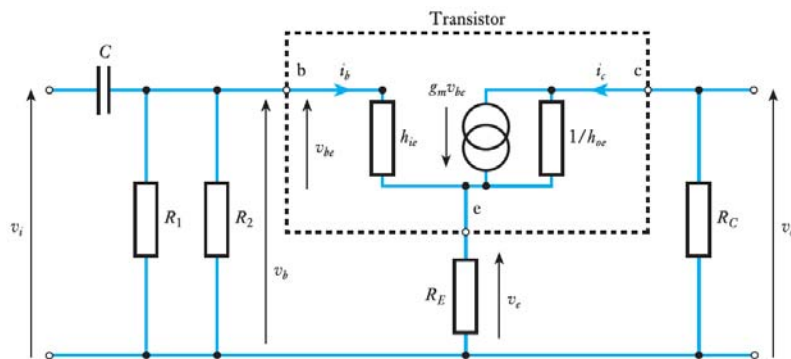


Reduces the amount of AC negative feedback while maintaining DC feedback.
This increases the small-signal gain of the circuit but does not affect the DC feedback,
This provides stability to the bias conditions of the circuit

Use of a decoupling capacitor

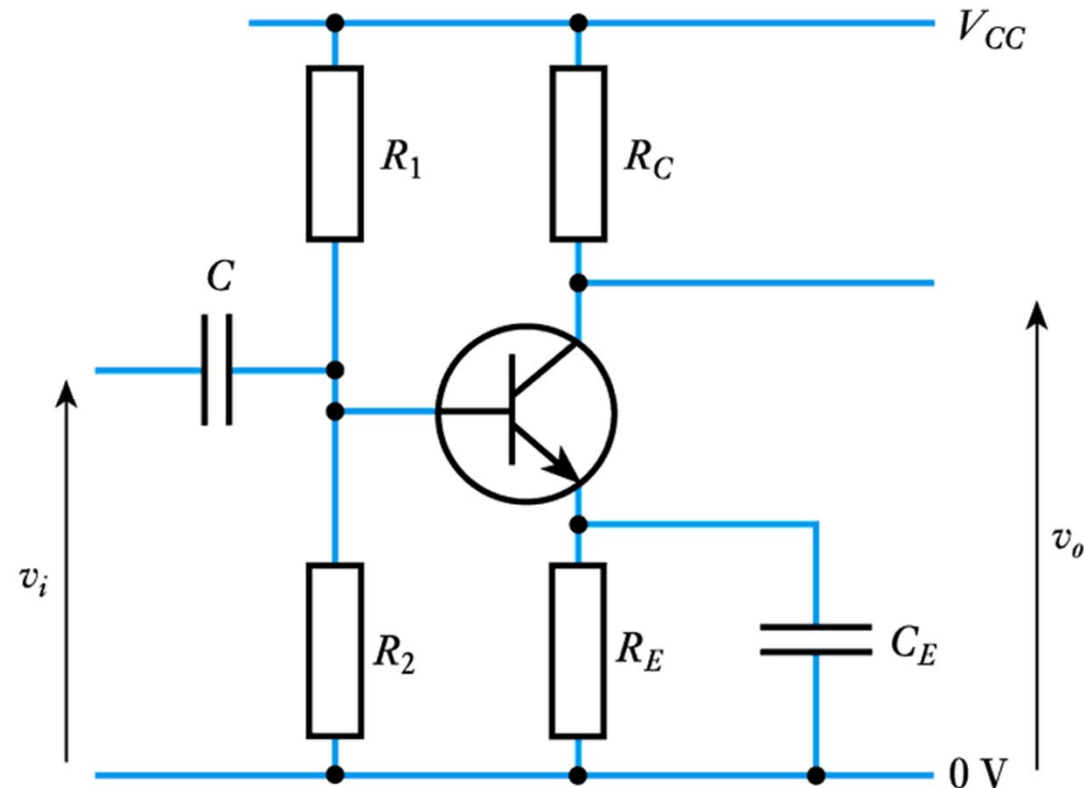
- A decoupling capacitor removes small-signal feedback



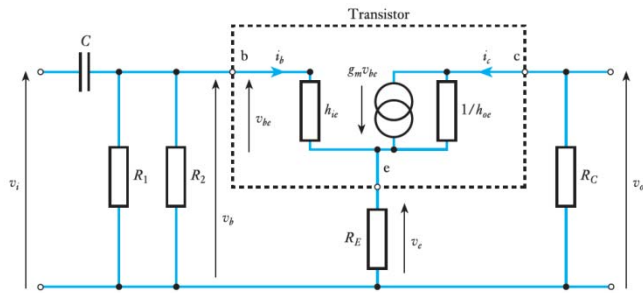

Small signal equivalent circuit without coupling capacitor

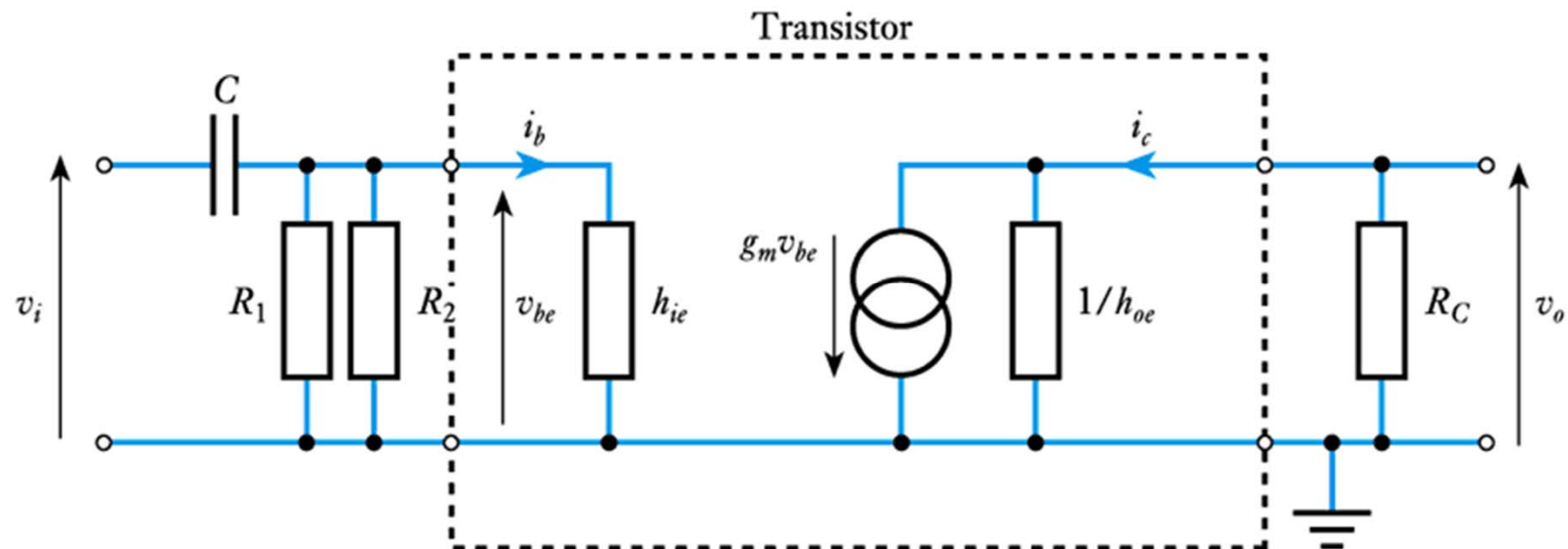- Small-signal equivalent circuit of an amplifier using a decoupling capacitor (Shorts out R_E in signal band)




Remember $r_e = 1/g_m$ and gain was $g_m \cdot R_c$

- A comparison of the frequency responses of various amplifiers

- for simplicity, the figure shows the responses of amplifiers that are *not* fitted with coupling capacitors

With an ac coupling capacitor

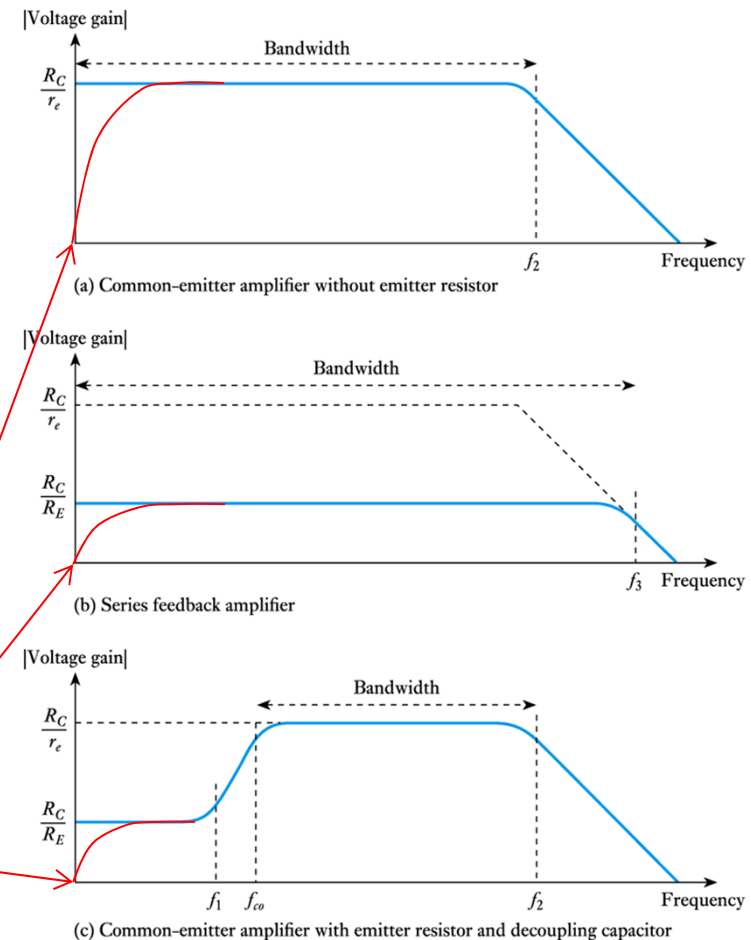

Summary

- DC and small-signal (AC) gains no feedback
 - Gain depends on characteristics of specific transistor
- DC and small-signal gains with negative feedback
 - Small-gain but depends on stable passive resistors
- Decoupling capacitor
 - Claw back some of the lost gain within the signal band