

## Frequency Characteristics of AC Circuits




Chapter 8

- Introduction
- Two-port Networks
- The Decibel (dB)
- Frequency Response
- A High-Pass RC Network
- A Low-Pass RC Network
- A Low-Pass RL Network
- A High-Pass RL Network
- A Comparison of RC and RL Networks
- Bode Diagrams
- Combining the Effects of Several Stages
- RLC Circuits and Resonance
- Filters
- Stray Capacitance and Inductance

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

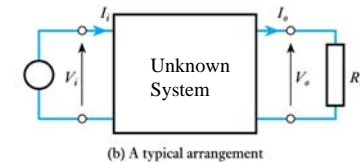8.1

- We then define voltages and currents at the input and output



- Then

$$\text{voltage gain } (A_v) = \frac{V_o}{V_i}$$

$$\text{current gain } (A_i) = \frac{I_o}{I_i}$$

$$\text{power gain } (A_p) = \frac{P_o}{P_i}$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.2

## The Decibel (dB)



8.3

- The power gain of amplifiers is often given in **decibels**, that allows gains of individual stages to be added
- The decibel is a dimensionless figure for power gain

$$\text{Power gain (dB)} = 10 \log_{10} \frac{P_{out}}{P_{input}}$$

- In terms of voltage gain, the power gain is given as:

$$\text{Power gain (dB)} = 10 \log_{10} \left( \frac{V_{out}^2}{V_{in}^2} \cdot \frac{R_{in}}{R_{out}} \right) \approx 20 \log_{10} \frac{V_2}{V_1}$$

$$\text{Power gain (dB)} = 20 \log_{10} (\text{Voltage gain})$$

- Generally used even when  $R_{out} \neq R_{in}$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.3

## Frequency response




8.4

- The way in which the gain of a circuit changes with frequency is termed its **frequency response** or **transfer function**
- These variations take the form of variations in the **magnitude** of the gain and in the **phase response**

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.4

### A High-Pass RC Network

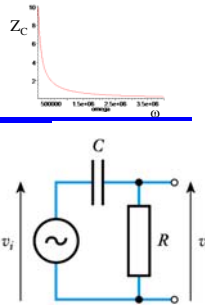

- The transfer function is

$$\frac{V_o}{V_i} = \frac{Z_R}{Z_R + Z_C} = \frac{R}{R - j\frac{1}{\omega C}} = \frac{1}{1 - j\frac{1}{\omega CR}}$$

- the *magnitude* of the voltage gain is

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1^2 + \left(\frac{1}{\omega CR}\right)^2}}$$

- When  $1/(\omega CR) = 1$

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707 \quad \text{Power gain} = \frac{1}{2} = -3\text{dB}$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.5

- The half power point is the **cut-off frequency**
  - the angular frequency  $\omega_c$  at which this occurs is

$$\frac{1}{\omega_c CR} = 1$$

$$\omega_c = \frac{1}{CR} = \frac{1}{T} \text{ rad/s}$$

- where  $T$  is the time constant of the  $CR$  network. Also

$$f_c = \frac{\omega_c}{2\pi} = \frac{1}{2\pi CR} \text{ Hz} \quad \text{and} \quad \frac{V_o}{V_i} = \frac{1}{1 - j\frac{1}{\omega CR}} = \frac{1}{1 - j\frac{1}{(2\pi f)\left(\frac{1}{2\pi f_c}\right)}} = \frac{1}{1 - j\frac{f_c}{f}}$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.6

$$\frac{V_o}{V_i} = \frac{1}{1 - j\frac{f_c}{f}}$$

- Consider the behaviour of the circuit at different frequencies:

- When  $f \gg f_c$**

–  $f_c/f \ll 1$ , the voltage gain  $\approx 1$

- When  $f = f_c$**

$$\frac{V_o}{V_i} = \frac{1}{1 - j\frac{f_c}{f}} = \frac{1}{1 - j} = \frac{1 \times (1 + j)}{(1 - j) \times (1 + j)} = \frac{(1 + j)}{2} = 0.5 + 0.5j$$

Output leads input by 45°

- When  $f \ll f_c$**


$$\frac{V_o}{V_i} = \frac{1}{1 - j\frac{f_c}{f}} \approx \frac{1}{-j\frac{f_c}{f}} = j\frac{f}{f_c}$$

Output leads input by 90°

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

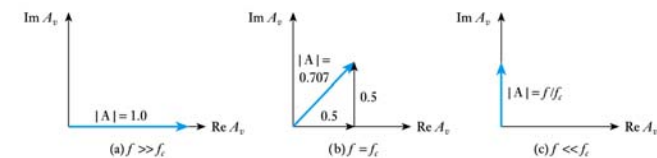8.7

- The behaviour in these three regions can be illustrated using phasor diagrams



- At *low* frequencies the gain is linearly related to frequency.  $\frac{1}{2}$  the frequency  $\Rightarrow \frac{1}{2}$  the voltage gain  
 $\frac{1}{2}$  the frequency  $\Rightarrow \frac{1}{4}$  the power gain  
 Power gain falls at -6dB/octave (-20dB/decade)


Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.8
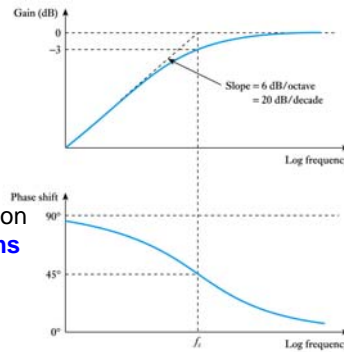
### A High-Pass RC Network (high frequencies passed to the output)

- Frequency response of the high-pass network
  - the gain response has two *asymptotes* that meet at the cut-off frequency
  - figures the transfer function are called **Blue diagrams**

Phase shifts important in control systems




8.9

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013
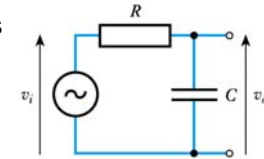
### A Low-Pass RC Network

- Transposing the  $C$  and  $R$  gives

$$\frac{V_o}{V_i} = \frac{Z_C}{Z_R + Z_C} = \frac{-j\frac{1}{\omega C}}{R - j\frac{1}{\omega C}} = \frac{1}{1 + j\omega CR}$$



- At high frequencies
  - $\omega$  is large, voltage gain  $\rightarrow 0$   
(capacitor looks like a wire  $\Rightarrow$  nearly all the voltage drops across resistor)
- At low frequencies
  - $\omega$  is small, voltage gain  $\approx 1$   
(capacitor looks like a huge resistor  $\Rightarrow$  hardly any voltage drop across resistor)

8.10

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


- A similar analysis to before gives

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1 + (\omega CR)^2}}$$

- Therefore when, when  $\omega CR = 1$

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$$

- Which is the cut-off frequency

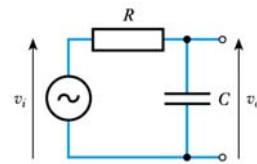

8.11

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

- Therefore
  - the angular frequency  $\omega_c$  at which this occurs is given by

$$\omega_c CR = 1$$

$$\omega_c = \frac{1}{CR} = \frac{1}{T} \text{ rad/s}$$

- where  $T$  is the time constant of the  $CR$  network, and as before

$$f_c = \frac{\omega_c}{2\pi} = \frac{1}{2\pi CR} \text{ Hz}$$

8.12

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

- Substituting  $\omega = 2\pi f$  and  $CR = 1/2\pi f_c$  in the earlier equation gives

$$\frac{V_o}{V_i} = \frac{1}{1 + j\omega CR} = \frac{1}{1 + j\frac{\omega}{\omega_c}} = \frac{1}{1 + j\frac{f}{f_c}}$$

- This is similar, but not the same, as the transfer function for the high-pass network (+j instead of -j)

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.13

- Consider the behaviour of this circuit at different frequencies:

- When  $f \ll f_c$**

–  $f/f_c \ll 1$ , the voltage gain  $\approx 1$

- When  $f = f_c$**

$$\frac{V_o}{V_i} = \frac{1}{1 + j\frac{f}{f_c}} = \frac{(1-j)(1+j)}{(1+j)(1+j)} = \frac{(1-j)}{2} = 0.5 - 0.5j$$


- When  $f \gg f_c$**

$$\frac{V_o}{V_i} = \frac{1}{1 + j\frac{f}{f_c}} \approx \frac{1}{j\frac{f}{f_c}} = -j\frac{f_c}{f}$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

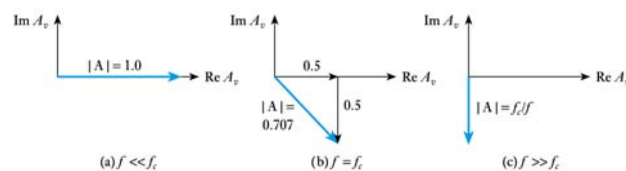8.14

- The output voltage lags the input voltage



- At *high* frequencies the gain is linearly related to frequency.
- Power gain falls at 6dB/octave (20dB/decade)

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


8.15

### A Low-Pass RC Network (low frequencies passed to the output)

- Frequency response of the low-pass network


- the gain response has two *asymptotes* that meet at the cut-off frequency

- you might like to compare this with the Bode Diagram for a high-pass network

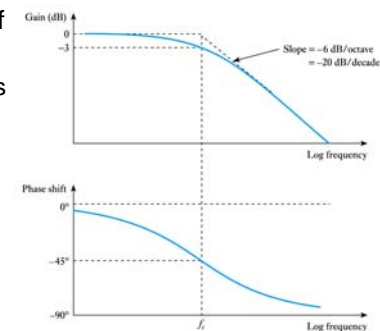Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.16

### A Low-Pass RL Network

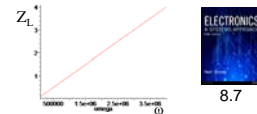

- Low-pass networks can also be produced using RL circuits
  - these behave similarly to the corresponding CR circuit
  - the voltage gain is

$$\frac{V_o}{V_i} = \frac{Z_R}{Z_R + Z_L} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega \frac{L}{R}}$$

- the cut-off frequency is


$$\omega_c = \frac{R}{L} = \frac{1}{T} \text{ rad/s} \quad f_c = \frac{\omega_c}{2\pi} = \frac{R}{2\pi L} \text{ Hz}$$

At Low frequencies  
L looks like a wire  
At High frequencies  
L looks like a big resistor

8.17

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

### A High-Pass RL Network

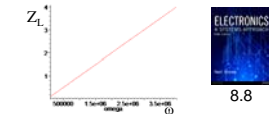

- High-pass networks can also be produced using RL circuits
  - these behave similarly to the corresponding CR circuit
  - the voltage gain is

$$\frac{V_o}{V_i} = \frac{Z_L}{Z_R + Z_L} = \frac{j\omega L}{R + j\omega L} = \frac{1}{1 + \frac{R}{j\omega L}} = \frac{1}{1 - j\frac{R}{\omega L}}$$

- the cut-off frequency is


$$\omega_c = \frac{R}{L} = \frac{1}{T} \text{ rad/s} \quad f_c = \frac{\omega_c}{2\pi} = \frac{R}{2\pi L} \text{ Hz}$$

8.18

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013
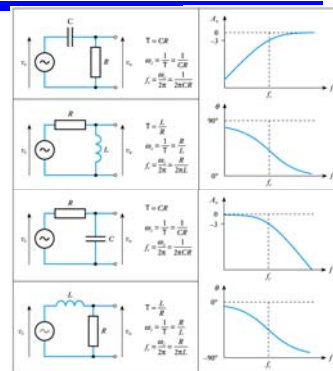
### A Comparison of RC and RL Networks

- Circuits using RC and RL techniques have similar characteristics
  - see **Figure 8.12** in the course text



8.19

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

### Bode Diagrams




Video 8A



8.10


- Straight-line approximations

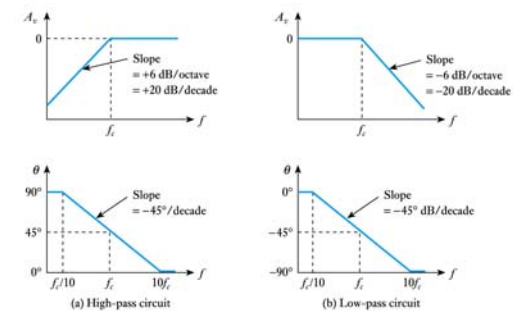

8.20

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

- Creating more detailed Bode diagrams

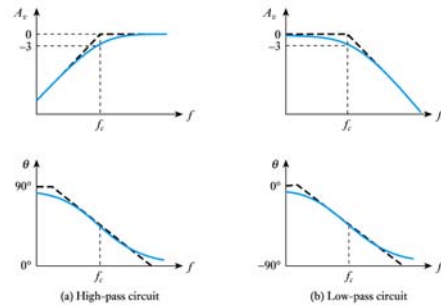


Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.21
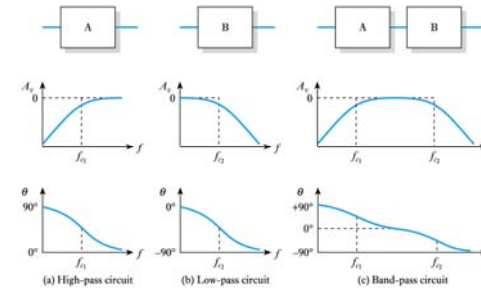
## Combining the Effects of Several Stages

ELECTRONICS  
8.11


- The effects of several stages 'add' in bode diagrams



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

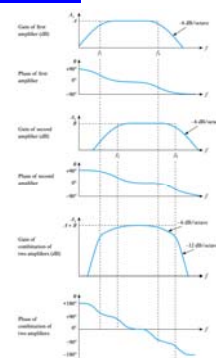8.22


- Multiple high- and low-pass elements may also be combined – this is illustrated in **Figure 8.16** in the course text



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.23
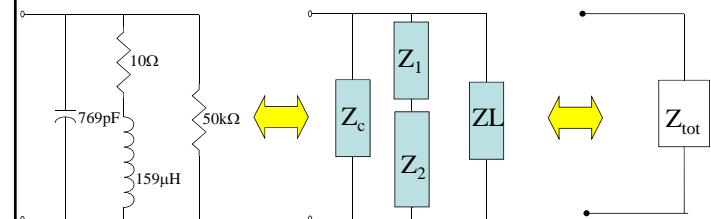
## Why did we say complex impedances made things easier?



$$\frac{1}{Z_{tot}} = \frac{1}{Z_c} + \frac{1}{(Z_1 + Z_2)} + \frac{1}{Z_L} \quad \text{Simple Arithmetic} \quad Z_{tot} = \frac{Z_L (Z_1 + Z_2) Z_c}{Z_c Z_1 + Z_c Z_2 + Z_L Z_1 + Z_L Z_2 + Z_L Z_c}$$


Substitute in complex, frequency dependent values, and let Maple solve it to get  
 $Z_{tot}(\omega) = Z_{re} + j \cdot Z_{im}$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.24
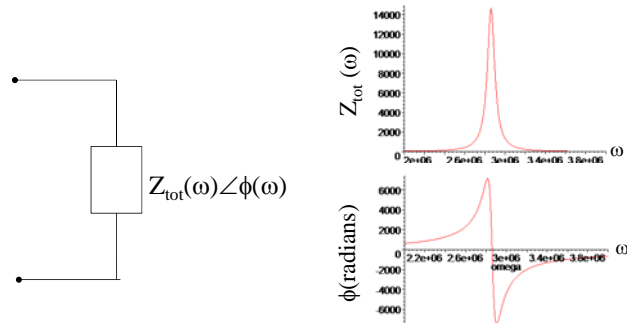
## Plot

How does the total impedance change with frequency?



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.25

## RLC Circuits and Resonance



8.12

### Series RLC circuits


- the impedance is given by

$$Z = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

- if the magnitude of the **reactance** of the inductor and capacitor are equal, the imaginary part is zero, and **the impedance is simply R**

- this occurs at frequency  $\omega_o$  when

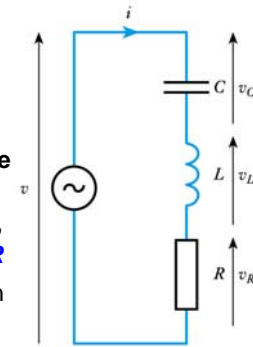
$$\omega_o L = \frac{1}{\omega_o C} \quad \omega_o^2 = \frac{1}{LC} \quad \omega_o = \frac{1}{\sqrt{LC}}$$



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.26
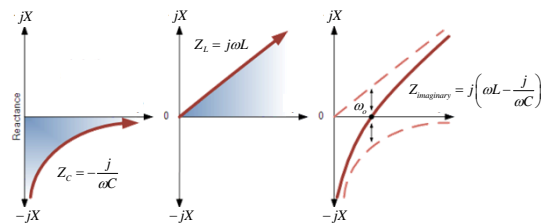
## How do the impedances change with frequency



- At one value of  $\omega$  the total reactive impedance is 0
  - As if the capacitor and inductor were replaced by a wire
- The impedance is a minimum value of R


Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.27
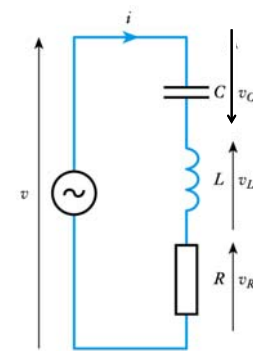
## At resonance, voltages in C and L 180° out of phase

- Resonance hits a sweet spot where the phasing between the voltage in the capacitor and the inductor are out of phase and cancel each other

- As a result, no net voltage drop across that part of the circuit (it looks like a wire), and the total resistance reduces to R, where  $v_R = V$



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


8.28

For  $R=50\text{k}\Omega$ ,  $C=769\text{ pF}$ ,  $L=159\mu\text{H}$ ,  
 $\omega_o=2.86\times 10^6\text{ rad/s} \Rightarrow f_o=455\text{ kHz}$

- This situation is referred to as **resonance**
  - the frequency at which it occurs is the **resonant frequency**

$$\omega_o = \frac{1}{\sqrt{LC}} \quad f_o = \frac{1}{2\pi\sqrt{LC}}$$

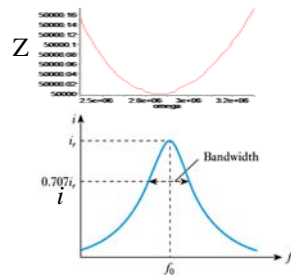- in the **series resonant circuit**, the *impedance* is at a **minimum** at resonance
- the *current* is at a maximum at resonance



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.29

- The resonant effect can be quantified by the **quality factor, Q**
  - this is the ratio of the **power stored** (in  $L$  or  $C$ ) to the **power dissipated** (in  $R$ ) in each cycle
  - it can be shown that

$$\text{Quality factor } Q = \frac{X_L}{R} = \frac{X_C}{R}$$

– and

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.30

- The series  $RLC$  circuit is an **acceptor circuit**
  - the narrowness of bandwidth is determined by the  $Q$

Not Proven  
Stole på oss!

$$\text{Quality factor } Q = \frac{\text{Resonant frequency } f_o}{\text{Bandwidth } B}$$


- combining this equation with the earlier one gives

$$B = \frac{R}{2\pi L} \text{ Hz}$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.31

### Parallel $RLC$ circuits

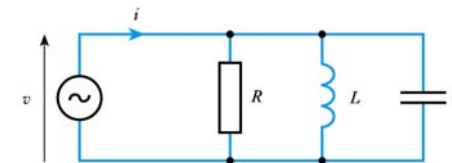

– as before

$$\frac{1}{Z_{tot}} = \frac{1}{R} + j\left(-\frac{1}{\omega L} + \omega C\right) \quad \omega_o = \frac{1}{\sqrt{LC}} \quad f_o = \frac{1}{2\pi\sqrt{LC}}$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.32




### Separate into real and imaginary parts

- $Z_{\text{tot}} = \frac{1}{\omega^2 L^2 + R^2 (\omega^2 CL - 1)} \left\{ R \omega^2 L^2 - j R^2 \omega L (\omega^2 CL - 1) \right\}$
- and when  $(\omega_0)^2 CL = 1$  we see
  - Reactive (Imaginary) part vanishes
  - Real part = R
- At resonance, impedance reaches a **maximum** and  $Z_{\text{tot}} = R$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.33
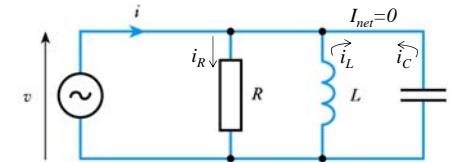
### At resonance the currents in the capacitor and inductor are 180° out of phase and cancel



- The reactive currents are flowing back and forth between the L and the C with a phase (tank circuit)
- At resonance, they are 180° out of phase and  $I_{\text{net}} = 0$
- Since there is no current flowing there, the L-C part of the circuit looks like an open circuit and  $i = i_R$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013



8.34

For  $R=50\text{k}\Omega$ ,  $C=769\text{ pF}$ ,  $L=159\mu\text{H}$ ,  
 $\omega_0=2.86 \times 10^6\text{ rad/s} \Rightarrow f_0 = 455\text{ kHz}$

- The parallel arrangement is a **rejector circuit**
  - in the **parallel resonant circuit**, the *impedance* is at a maximum at resonance
  - the *current* is at a minimum at resonance
  - in this circuit

$$Q = R \sqrt{\frac{C}{L}}$$

$$B = \frac{1}{2\pi RC} \text{ Hz}$$

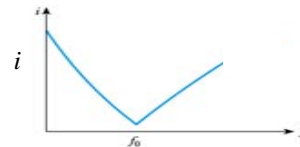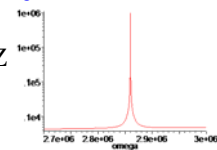Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.35

### Filters




8.13

- **RC and RL Filters**
- The RC and RL networks considered earlier are **first-order** or **single-pole** filters
  - these have a maximum roll-off of 6 dB/octave
  - they also produce a maximum of 90° phase shift
- Combining multiple stages can produce filters with a greater ultimate roll-off rates (12 dB, 18 dB, etc.) but such filters have a very soft 'knee'

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.36

- An ideal filter would have constant gain and zero phase shift for frequencies within its **pass band**, and zero gain for frequencies outside this range (its **stop band**)
- Real filters do not have these idealised characteristics

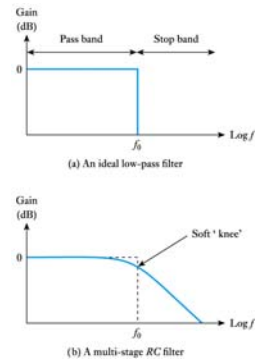
Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.37

### LC Filters

- Simple LC filters can be produced using series or parallel tuned circuits
  - these produce narrow-band filters with a centre frequency  $f_0$


$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

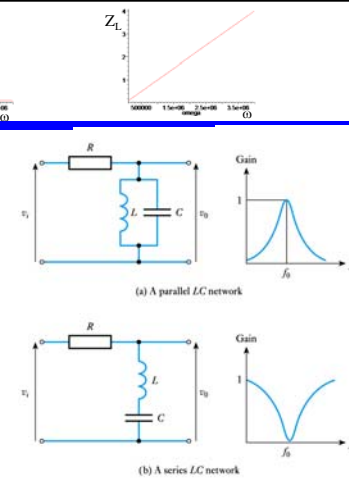Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.38

### Active filters


- combining an op-amp with suitable resistors and capacitors can produce a range of filter characteristics
- these are termed **active filters**

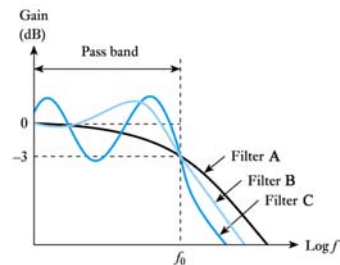Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.39

- Common forms include:

- **Butterworth**
    - optimised for a flat response
  - **Chebyshev**
    - optimised for a sharp 'knee'
  - **Bessel**
    - optimised for its phase response
- see **Section 8.13.3** of the course text for more information on these

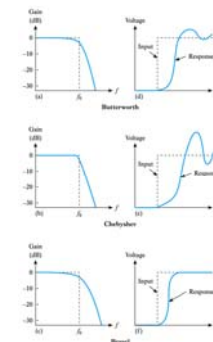Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


8.40

## Stray Capacitance and Inductance



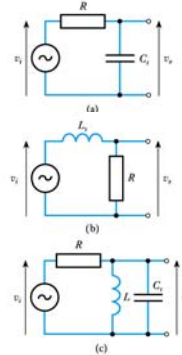8.14

- All circuits have stray capacitance and stray inductance
  - these unintended elements can dramatically affect circuit operation
  - for example:
    - (a)  $C_s$  adds an unintended low-pass filter
    - (b)  $L_s$  adds an unintended low-pass filter
    - (c)  $C_s$  produces an unintended resonant circuit and can produce instability



8.41

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

## Further Study



Video 8B Further Study

- The **Further Study** section at the end of Chapter 8 looks at the filter needed to select a single radio station from the multitude being transmitted.
- You are required to design a simply RLC filter to select a given station.
- When you have finished your design watch the video to see why this is not as simple as it perhaps appears.



8.42

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

## Key Points

- The reactance of capacitors and inductors is dependent on frequency
- Single  $RC$  or  $RL$  networks can produce an arrangement with a single upper or lower cut-off frequency
- In each case the angular cut-off frequency  $\omega_o$  is given by the reciprocal of the time constant  $T$
- For an  $RC$  circuit  $T = CR$ , for an  $RL$  circuit  $T = L/R$
- Resonance occurs when the reactance of the capacitive element cancels that of the inductive element
- Simple  $RC$  or  $RL$  networks represent single-pole filters
- Active filters produce high performance without inductors
- Stray capacitance and inductance are found in all circuits

8.43

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

## Transient Behaviour



Chapter 9

- Introduction
- Charging Capacitors and Energising Inductors
- Discharging Capacitors and De-energising Inductors
- Response of First-Order Systems
- Second-Order Systems
- Higher-Order Systems



8.44

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

## Introduction



9.1

- So far we have looked at the behaviour of systems in response to:
  - fixed DC signals
  - constant AC signals
- We now turn our attention to the operation of circuits before they reach steady-state conditions
  - this is referred to as the **transient response**
- We will begin by looking at simple *RC* and *RL* circuits

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.45

## Charging Capacitors and Energising Inductors



9.2

### Capacitor Charging

- Consider the circuit shown here
  - Applying Kirchhoff's voltage law


$$iR + v = V$$

- Now, in a capacitor

$$i = C \frac{dv}{dt}$$

- which substituting gives

$$CR \frac{dv}{dt} + v = V$$

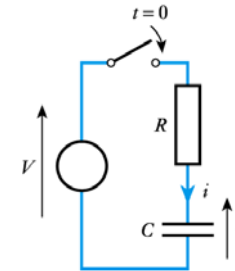Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.46

- The above is a first-order differential equation with constant coefficients
- Assuming  $V_C = 0$  at  $t = 0$ , this can be solved to give

$$v = V(1 - e^{-\frac{t}{CR}}) = V(1 - e^{-\frac{t}{T}})$$

- see **Section 9.2.1** of the course text for this analysis

- Since  $i = Cdv/dt$  this gives (assuming  $V_C = 0$  at  $t = 0$ )


$$i = Ie^{-\frac{t}{CR}} = Ie^{-\frac{t}{T}}$$

- where  $I = V/R$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.47

- Thus both the voltage and current have an exponential form

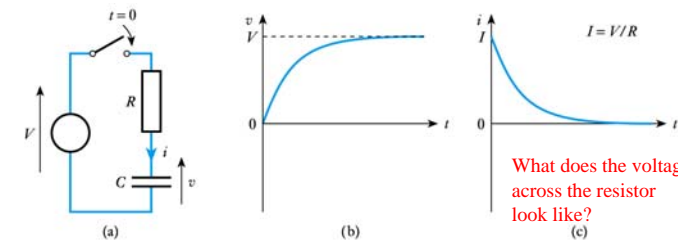Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.48

**Inductor energising** KVL  $\Rightarrow iR + v = V$ , and  $v = L(di/dt)$ 


- A similar analysis of this circuit gives

$$v = Ve^{-\frac{Rt}{L}} = Ve^{-\frac{t}{T}}$$

$$i = I(1 - e^{-\frac{Rt}{L}}) = I(1 - e^{-\frac{t}{T}})$$

where  $I = V/R$

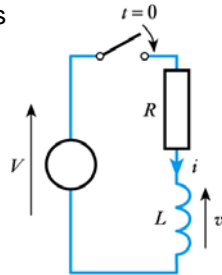
– see **Section 9.2.2** for this analysis



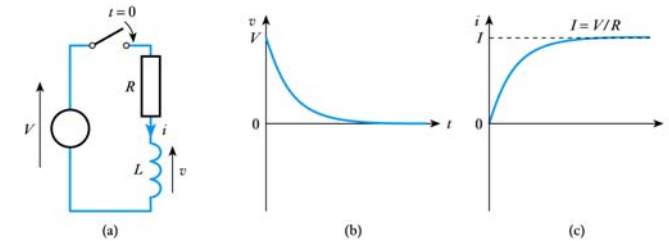8.49

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

- Thus, again, both the voltage and current have an exponential form



8.50


Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013**Discharging Capacitors and De-energising Inductors****Capacitor discharging**

- Consider this circuit for discharging a capacitor
  - At  $t = 0$ ,  $V_C = V$
  - From Kirchhoff's voltage law

$$iR + v = 0$$

– giving

$$CR \frac{dv}{dt} + v = 0$$

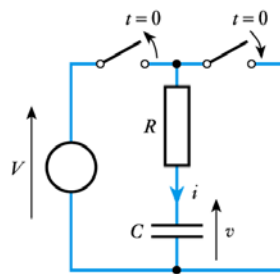

8.51

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

- Solving this as before gives

$$v = Ve^{-\frac{t}{CR}} = Ve^{-\frac{t}{T}}$$

$$i = -Ie^{-\frac{t}{CR}} = -Ie^{-\frac{t}{T}}$$


– where  $I = V/R$

– see **Section 9.3.1** for this analysis

8.52

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

- In this case, both the voltage and the current take the form of decaying exponentials

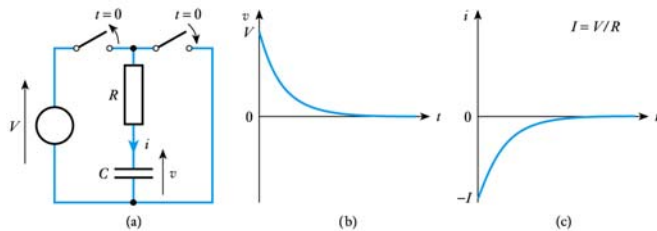Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.53

### Inductor de-energising


- A similar analysis of this circuit gives

$$v = -Ve^{-\frac{Rt}{L}} = -Ve^{-\frac{t}{T}}$$

$$i = Ie^{-\frac{Rt}{L}} = Ie^{-\frac{t}{T}}$$


– where  $I = V/R$

– see **Section 9.3.1** for this analysis

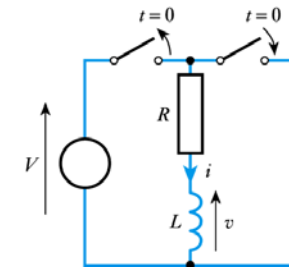Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


8.54

- And once again, both the voltage and the current take the form of decaying exponentials

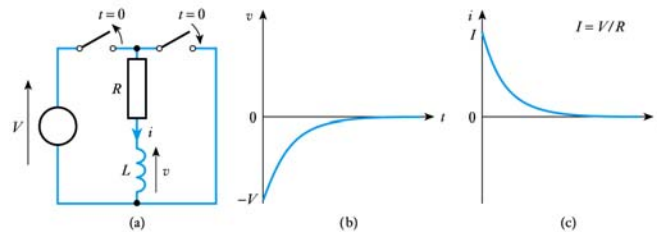Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.55

- A comparison of the four circuits

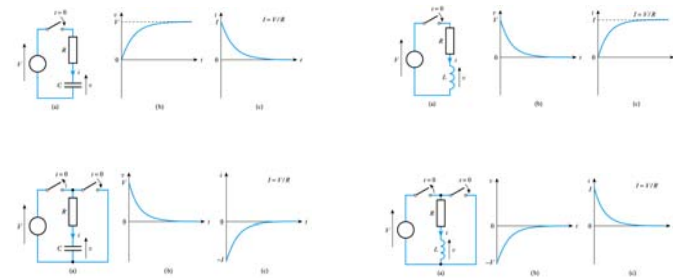Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.56

## Response of First-Order Systems



### Initial and final value formulae

- increasing or decreasing exponential waveforms (for either voltage or current) are given by:

$$v = V_f + (V_i - V_f)e^{-t/T}$$

$$i = I_f + (I_i - I_f)e^{-t/T}$$


- where  $V_i$  and  $I_i$  are the *initial* values of the voltage and current
- where  $V_f$  and  $I_f$  are the *final* values of the voltage and current
- the first term in each case is the **steady-state response**
- the second term represents the **transient response**
- the combination gives the **total response** of the arrangement

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.57
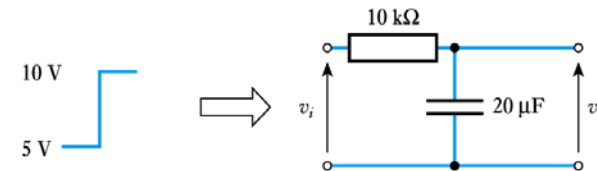
### Example – see Example 9.3 from course text

The input voltage to the following CR network undergoes a step change from 5 V to 10 V at time  $t = 0$ . Derive an expression for the resulting output voltage



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


8.58

Here the initial value is 5 V and the final value is 10 V. The time constant of the circuit equals  $CR = 10 \times 10^3 \times 20 \times 10^{-6} = 0.2$ s. Therefore, from above, for  $t \geq 0$

$$\begin{aligned} v &= V_f + (V_i - V_f)e^{-t/T} \\ &= 10 + (5 - 10)e^{-t/0.2} \\ &= 10 - 5e^{-t/0.2} \text{ volts} \end{aligned}$$

And the current?

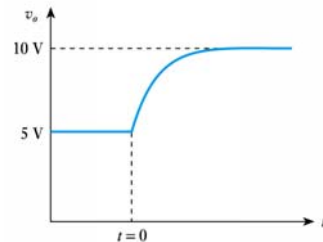
$$\begin{aligned} i &= C(dv/dt) \\ i &= (V_f - V_i)/R \cdot e^{-t/T} \\ I_i &= (V_f - V_i)/R, I_f = 0 \end{aligned}$$



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.59

### The nature of exponential curves

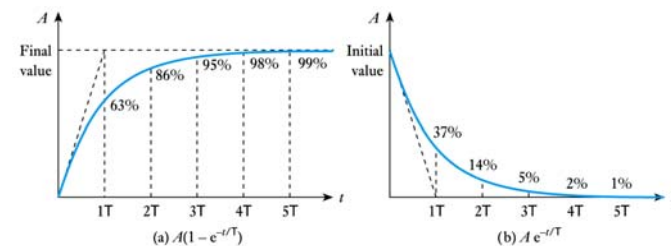


Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.60

### Response of first-order systems to a square waveform

– see **Section 9.4.3**

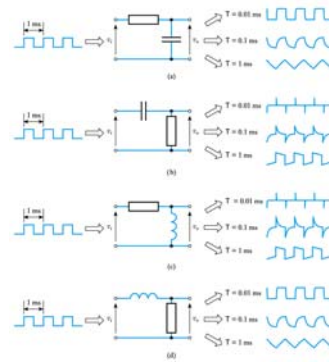


Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.61

### Response of first-order systems to a square waveform of different frequencies

– see **Section 9.4.3**

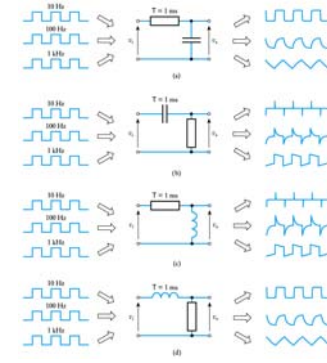

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.62


## Second-Order Systems

9.5

- Circuits containing both capacitance and inductance are normally described by second-order differential equations. These are termed **second-order systems** – for example, this circuit is described by the equation

$v_R + v_L + v_C = V$  and  $v_L = L(di/dt)$ , and  $v_R = iR$  but  $i = C(dv_C/dt)$ . So
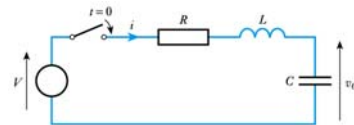
$$LC \frac{d^2 v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C = V$$



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.63

- When a step input is applied to a second-order system, the form of the resultant transient depends on the relative magnitudes of the coefficients of its differential equation. The general form of the response is

$$\frac{1}{\omega_n^2} \frac{d^2 y}{dt^2} + \frac{2\zeta}{\omega_n} \frac{dy}{dt} + y = x$$

- where  $\omega_n$  is the **undamped natural frequency** in rad/s and  $\zeta$  (Greek Zeta) is the **damping factor**


Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.64


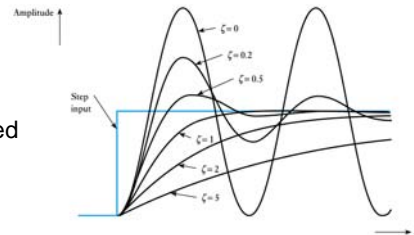
### Response of second-order systems

$\zeta = 0$  undamped  
 $\zeta < 1$  under damped  
 $\zeta = 1$  critically damped  
 $\zeta > 1$  over damped



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.65

### Higher-Order Systems



9.6

- Higher-order systems are those that are described by third-order or higher-order equations
- These often have a transient response similar to that of the second-order systems described earlier
- Because of the complexity of the mathematics involved, they will not be discussed further here

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.66

### Further Study



Video 9B Further Study

- The **Further Study** section at the end of Chapter 9 considers the problem of determining the time constant of a circuit, so that the initial and final value theorems can be applied.
- Two sample circuits are given so that you can test your understanding.
- Calculate the time constants of the circuits and then check your results by looking at the video.



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.67

### Key Points

- The charging or discharging of a capacitor, and the energising and de-energising of an inductor, are each associated with exponential voltage and current waveforms
- Circuits that contain resistance, and either capacitance or inductance, are termed first-order systems
- The increasing or decreasing exponential waveforms of first-order systems can be described by the initial and final value formulae
- Circuits that contain both capacitance and inductance are usually second-order systems. These are characterised by their undamped natural frequency and their damping factor

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

8.68