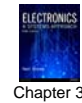


## Last time: Resistance and DC Circuits



Chapter 3

- Introduction
- Current and Charge
- Voltage Sources
- Current Sources
- Resistance and Ohm's Law
- Kirchhoff's Laws
- Resistors in Series and Parallel
- Thévenin's and Norton's Theorems
- Superposition
- Nodal Analysis
- Mesh Analysis
- Solving Simultaneous Circuit Equations
- Choice of Techniques

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.1

## Resistance and Ohm's Law



3.5

### Ohm's law

$$V \propto I$$

- constant of proportionality is the resistance  $R$
- hence

$$V = IR \quad I = \frac{V}{R} \quad R = \frac{V}{I}$$

- current through a resistor causes power dissipation

$$P = IV \quad P = \frac{V^2}{R} \quad P = I^2 R$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.2

## Kirchhoff's Laws



Video 3A



3.7

### Node

- a point in a circuit where two or more circuit components are joined

### Loop


- any closed path that passes through no node more than once

### Mesh

- a loop that contains no other loop
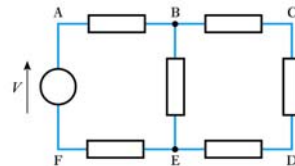
### Examples:

- A, B, C, D, E and F are *nodes*
- the paths ABEFA, BCDEB and ABCDEFA are *loops*
- ABEFA and BCDEB are *meshes*




3.3

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

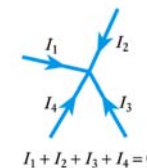
### Current Law

*At any instant, the algebraic sum of all the currents flowing into any node in a circuit is zero*

- if currents flowing *into* the node are positive, currents flowing *out* of the node are negative, then  $\sum I = 0$



$$I_1 + I_2 + I_3 + I_4 = 0$$

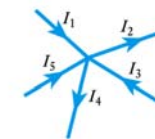

$$I_1 - I_2 + I_3 - I_4 + I_5 = 0$$


Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.4
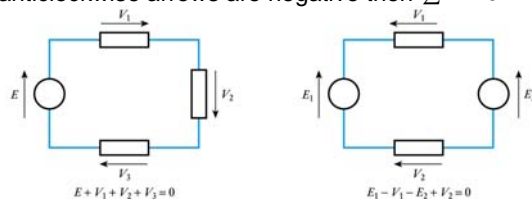
### Voltage Law

At any instant the algebraic sum of all the voltages around any loop in a circuit is zero

- if clockwise voltage arrows are positive and anticlockwise arrows are negative then  $\sum V = 0$



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.5

## Today: Resistance and DC Circuits



Chapter 3

- Introduction
- Current and Charge
- Voltage Sources
- Current Sources
- Resistance and Ohm's Law
- Kirchhoff's Laws
- Resistors in Series and Parallel
- Thévenin's and Norton's Theorems
- Superposition
- Nodal Analysis
- Mesh Analysis
- Solving Simultaneous Circuit Equations
- Choice of Techniques



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.6

## Thevenin's Theorem




3.8

- Any linear circuit with sources (dependent and/or independent) and resistors **can be replaced by an equivalent circuit containing a single voltage source and a single resistor.**
- Thevenin's theorem implies that we can replace arbitrarily complicated networks with simple networks for purposes of analysis.
- If we have a single "load" resistor which is subject to change, we simplify circuit to a simple Thevenin equivalent with a single resistor and can recalculate easily for many different loads

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.7

## A Realistic Source Model

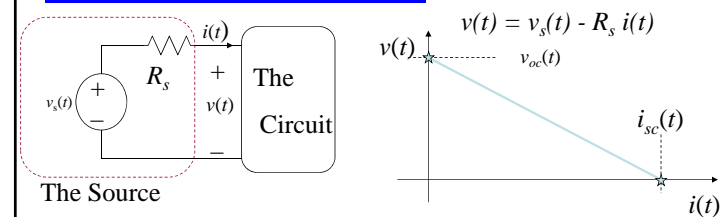

- Remove "The Circuit"  $\Rightarrow$  source supplies maximum voltage at 0 current
- Short out "The Circuit"  $\Rightarrow$  source supplies maximum current at 0 voltage
- Since the **open circuit voltage** and the **short circuit current** determine where the I-V line crosses both axes, they completely define the line.
- Any source circuit with the same I-V characteristics is equivalent.

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.8


## Norton's Theory 2

- Any Thevenin equivalent circuit is in turn equivalent to a current source in parallel with a resistor [source transformation].
- A current source in parallel with a resistor is called a Norton equivalent circuit.
- Finding a Norton equivalent circuit requires essentially the same process as finding a Thevenin equivalent circuit.

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

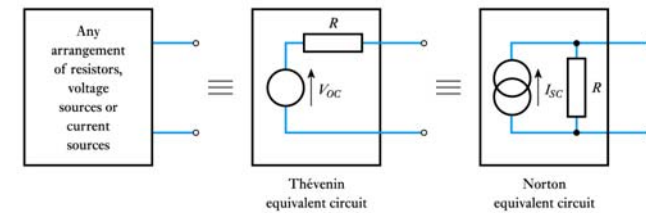3.9

An arbitrary, complicated circuit with independent sources  
Can be transformed to a Thévenin or Norton equivalent circuit:




- from the Thévenin equivalent circuit  $I_{SC} = \frac{V_{OC}}{R}$
- hence for *either* circuit  $R = \frac{V_{OC}}{I_{SC}}$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.10

- Example** – see **Example 3.3** from course text  
Determine Thévenin and Norton equivalent circuits of the following circuit

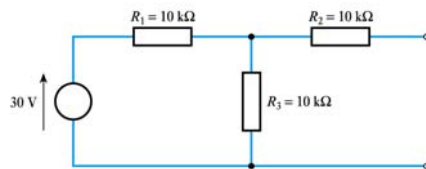Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.11

### Example (continued)

- if nothing is connected across the output no current will flow in  $R_2$  so there will be no voltage drop across it. Hence  $V_o$  is determined by the voltage source and the potential divider formed by  $R_1$  and  $R_3$ . Hence
- if the output is shorted to ground,  $R_2$  is in parallel with  $R_3$  and the current taken from the source is  $30V/15\text{ k}\Omega = 2\text{ mA}$ . This will divide equally between  $R_2$  and  $R_3$  so the output current, and so
- the resistance in the equivalent circuit is therefore given by

$$V_{OC} = \frac{30}{2} = 15\text{ V}$$

$$I_{SC} = 1\text{ mA}$$


$$R = \frac{V_{OC}}{I_{SC}} = \frac{15\text{ V}}{1\text{ mA}} = 15\text{ k}\Omega$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.12

**Example** (continued)


– hence equivalent circuits are:

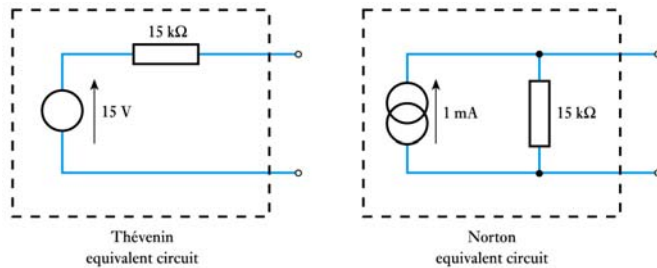

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.13
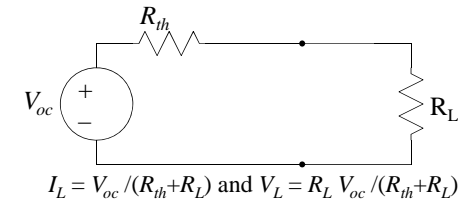
## Now compute the Thevenin equivalent circuit for calculations



Note, Power dissipated in the load is :


$$P_L = R_L I_L^2 = R_L [V_{oc} / (R_{th} + R_L)]^2$$

Differentiate with respect to  $R_L$  to find that the maximum energy transfer is when  $R_L = R_{th}$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.14

## Impedance Matched Circuit

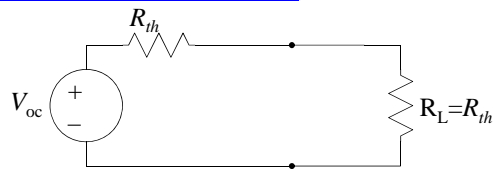

This circuit will dissipate the maximum energy in the load

E.g. audio circuit or heating circuit

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.15

## Circuit analysis techniques: Superposition



3.9

### Principle of superposition

*In any linear network of resistors, voltage sources and current sources, each voltage and current in the circuit is equal to the algebraic sum of the voltages or currents that would be present if each source were to be considered separately. When determining the effects of a single source the remaining sources are replaced by their internal resistance*

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.16


### How to Apply Superposition

- To find the contribution due to an individual independent source, zero out the other independent sources in the circuit.
  - Voltage source  $\Rightarrow$  short circuit.
  - Current source  $\Rightarrow$  open circuit.
- Solve the resulting circuit using your favorite technique(s).

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.17

### The Summing Circuit

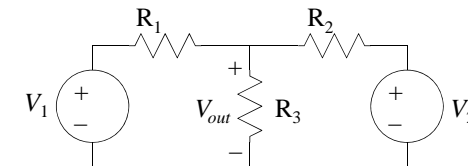


For a given  $V_1$  and  $V_2$ , what is the voltage  $V_{out}$  across  $R_3$ ?

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.18
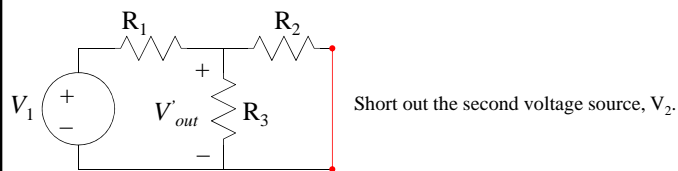
### Superposition-Solve for $V'_{out}$ from $V_1$ only



Short out the second voltage source,  $V_2$ .

$$I' = V_1 / (R_1 + R_{2//3})$$

$$V'_{out} = I' R_{2//3}$$

Where


$$R_{2//3} = R_2 R_3 / (R_2 + R_3)$$

Note  $R_{2//3} \Rightarrow R_2$  in parallel with  $R_3$ .  
 $R_{2//3} = (R_2 \cdot R_3) / (R_2 + R_3)$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.19
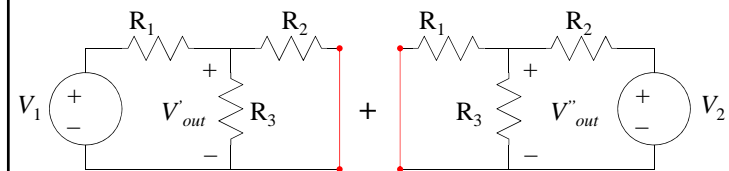
### Superposition-Then get $V''_{out}$ from $V_2$ only



$$I' = V_2 / (R_2 + R_{1//3})$$

$$V'_{out} = I' R_{2//3}$$

Where

$$R_{2//3} = R_2 R_3 / (R_2 + R_3)$$

$$I'' = V_2 / (R_2 + R_{1//3})$$

$$V''_{out} = I'' R_{1//3}$$

Where

$$R_{1//3} = R_1 R_3 / (R_1 + R_3)$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.20

### Use of Superposition

$$V_{out} = V'_{out} + V''_{out}$$

$$V'_{out} = \frac{V_1 \cdot R_2 \cdot R_3}{R_1 \cdot R_2 + R_1 \cdot R_3 + R_2 \cdot R_3} \quad V''_{out} = \frac{V_2 \cdot R_1 \cdot R_3}{R_1 \cdot R_2 + R_1 \cdot R_3 + R_2 \cdot R_3}$$

$$\text{If } R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$

then

$$V'_{out} = V_1 / 3$$

$$V''_{out} = V_2 / 3$$

$$V_{out} = V'_{out} + V''_{out} = V_1/3 + V_2/3$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.21


### Other circuit analysis techniques

- Brute force application of Ohm's law
- Nodal analysis
- Mesh analysis

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.22
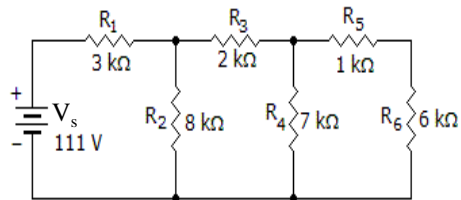
### Want to know the currents through $R_2$ , $R_4$ and $R_6$




Can be solved using:

- 1) Ohms law
- 2) Nodal analysis
- 3) Mesh analysis

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.23

### Ohms law solution:

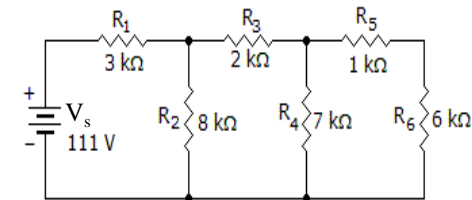

Total current is  $V_s$  across the total equivalent resistance

1) Equivalent resistance of  $R_3$  through  $R_6$ :


$$R_{eq1} = R_3 + R_4 / (R_5 + R_6) = 5500 \Omega$$

2) Total Equivalent Resistance  $R_1$  through  $R_6$ :

$$R_{eq} = R_1 + R_2 / R_{eq1} = 6259.26 \Omega$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


3.24

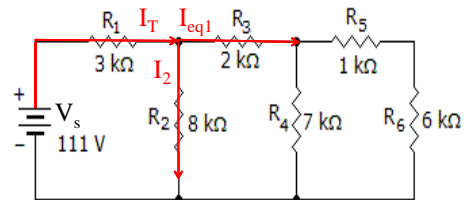**Ohms law solution:**

Total current is  $V_s$  across the total equivalent resistance  
 $I_T = V_s / R_{eq} = 111 \text{ V} / (6259.26 \Omega) = 17.73 \text{ mA}$   
 This current is split into  $I_2$  and  $I_{eq1}$  such that  $I_T = I_2 + I_{eq1}$   
 At the node,  $V_2 = V_{eq1}$ , and Ohms law says  $V = I \cdot R$ , so  
 $I_2 \cdot R_2 = I_{eq1} \cdot R_{eq1} \Rightarrow I_2 = I_T / (1 + R_2 / R_{eq1}) = 7.22 \text{ mA}$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


3.25

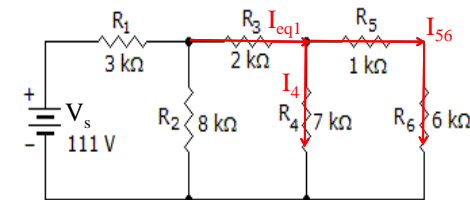**Ohms law solution:**

Similarly we can find that  $I_{eq1} = 10.5 \text{ mA}$   
 This current is split into  $I_4$  and  $I_{56}$  such that  $I_{eq1} = I_4 + I_{56}$   
 At the node,  $V_4 = V_{56}$ , and Ohms law says  $V = I \cdot R$ , so  
 $I_4 \cdot R_4 = I_{56} \cdot (R_5 + R_6) \Rightarrow I_4 = 5.25 \text{ mA}$ , &  $I_{56} = 5.25 \text{ mA}$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.26

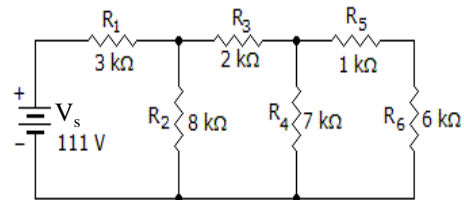**Want to know the currents through  $R_2$ ,  $R_4$  and  $R_6$** 

Can be solved using:

- 1) Ohms law ✓
- 2) Nodal analysis
- 3) Mesh analysis

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.27

**Nodal Analysis**

Video 3B




3.10

- Six steps:
  1. Chose one node as the reference node
  2. Label remaining nodes  $V_1$ ,  $V_2$ , etc.
  3. Label any known voltages
  4. Apply Kirchhoff's current law to each unknown node
  5. Solve simultaneous equations to determine voltages
  6. If necessary calculate required currents

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


3.28

### Want to know the currents through $R_2$ , $R_4$ and $R_6$

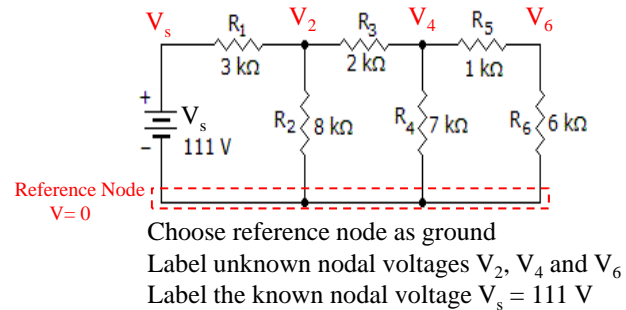Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


3.29

### Nodal Analysis

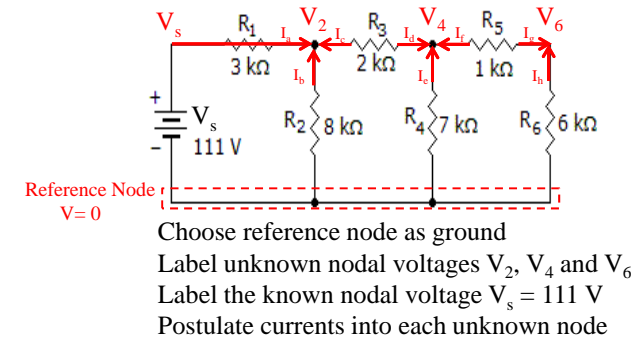Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


3.30

### Nodal Analysis - Apply KCL at each node

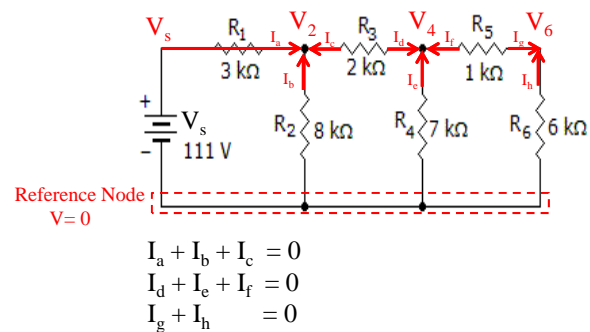Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.31


### Nodal Analysis -Apply Ohms law for each current

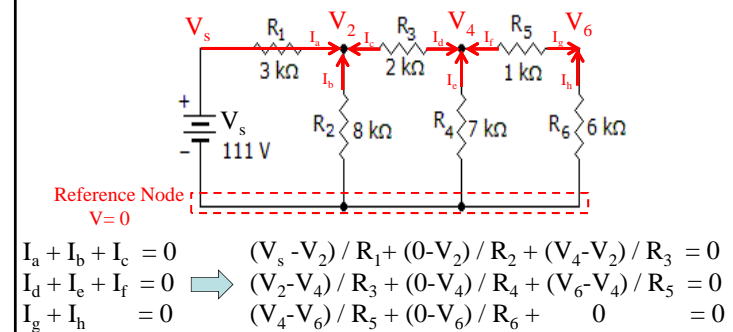Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.32


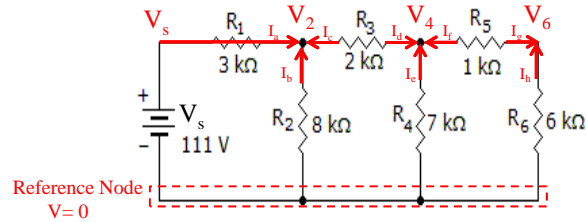
### Nodal Analysis –Gather terms for 3 unknown V's



$$\begin{aligned}
 V_2 \cdot (-1/R_1 - 1/R_2 - 1/R_3) + V_4 \cdot (1/R_3) + 0 &= V_s / R_1 \\
 V_2 \cdot (1/R_3) + V_4 \cdot (-1/R_3 - 1/R_4 - 1/R_5) + V_6 \cdot (1/R_5) &= 0 \\
 0 + V_4 \cdot (1/R_5) + V_6 \cdot (-1/R_5 - 1/R_6) &= 0
 \end{aligned}$$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.33

### Solving Simultaneous Circuit Equations

– these equations can be expressed as

$$\begin{bmatrix} -(1/R_1 + 1/R_2 + 1/R_3) & (1/R_3) & 0 \\ (1/R_3) & -(1/R_2 + 1/R_3 + 1/R_4) & (1/R_5) \\ 0 & (1/R_5) & -(1/R_5 + 1/R_6) \end{bmatrix} \begin{bmatrix} V_2 \\ V_4 \\ V_6 \end{bmatrix} = \begin{bmatrix} -111V_s/R_1 \\ 0 \\ 0 \end{bmatrix}$$

– This yields  $V_2 = 57.8 \text{ V}$ ,  $V_4 = 36.8 \text{ V}$  and  $V_6 = 31.5 \text{ V}$


– And Ohms law  $\Rightarrow I = V/R$

- Current through  $R_2 = V_2/R_2 = (57.8 \text{ V})/(8000 \Omega) = 7.22 \text{ mA}$
- Current through  $R_4 = V_4/R_4 = (36.8 \text{ V})/(7000 \Omega) = 5.25 \text{ mA}$
- Current through  $R_6 = V_6/R_6 = (31.5 \text{ V})/(6000 \Omega) = 5.25 \text{ mA}$

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.34
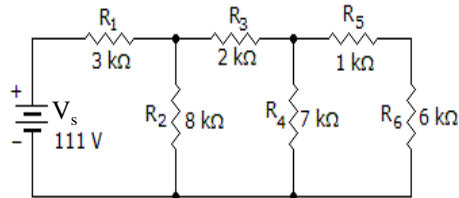
### Want to know the currents through $R_2$ , $R_4$ and $R_6$



Can be solved using:

- 1) Ohms law ✓
- 2) Nodal analysis ✓
- 3) Mesh analysis

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.35

### Mesh Analysis



Video 3C



3.11


▪ Five steps:

1. Identify the meshes and assign a clockwise-flowing current to each. Label these  $I_1$ ,  $I_2$ , etc.
2. Assign unknown voltages for each loop anti parallel to  $I_{\text{loop}}$
3. Apply Kirchhoff's voltage law to each mesh
4. Solve the simultaneous equations to determine the currents  $I_1$ ,  $I_2$ , etc.
5. Use these values to obtain voltages if required

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.36

### Mesh analysis

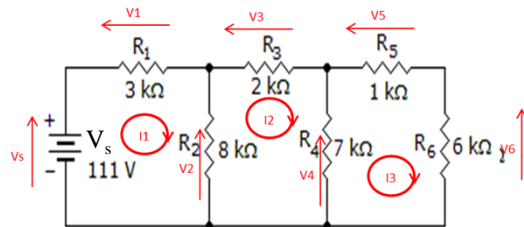

KVL around each mesh gives

$$V_S - V_1 - V_2 = 0$$

$$V_2 - V_3 - V_4 = 0$$

$$V_4 - V_5 - V_6 = 0$$

And want to apply  
Ohms law to each  
voltage drop

3.37

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

### Voltages from Mesh Currents



$$V_R = I_1 R$$

$$V_R = (I_1 - I_2) R$$

**Note Sign Convention:**  $I_1$  is anti-parallel to  $V_R \Rightarrow V_{R1} = I_1 \cdot R$

$I_2$  parallel to  $V_R \Rightarrow V_{R2} = -I_2 \cdot R$

total voltage is the sum  $V_R = (I_1 - I_2) \cdot R$


6.38

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

$$V_S - V_1 - V_2 = 0$$

$$V_2 - V_3 - V_4 = 0$$

$$V_4 - V_5 - V_6 = 0$$

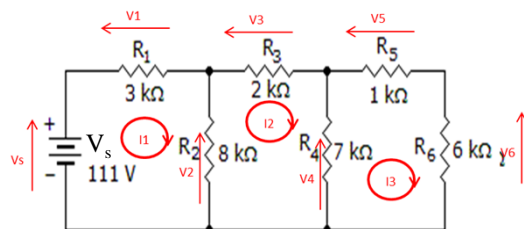

Using Ohms law gives

$$111V - R_1 \cdot I_1 - R_2 \cdot (I_1 - I_2) = 0$$

$$R_2 \cdot (I_1 - I_2) - R_3 \cdot I_2 - R_4 \cdot (I_2 - I_3) = 0$$

$$R_4 \cdot (I_2 - I_3) - R_5 \cdot I_3 - R_6 \cdot I_3 = 0$$


3.39

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

$$V_S - V_1 - V_2 = 0$$

$$V_2 - V_3 - V_4 = 0$$

$$V_4 - V_5 - V_6 = 0$$

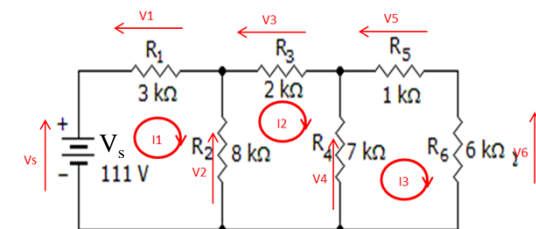

Using KVL gives

$$111V - R_1 \cdot I_1 - R_2 \cdot (I_1 - I_2) = 0$$


$$R_2 \cdot (I_1 - I_2) - R_3 \cdot I_2 - R_4 \cdot (I_2 - I_3) = 0$$

$$R_4 \cdot (I_2 - I_3) - R_5 \cdot I_3 - R_6 \cdot I_3 = 0$$

3.40

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

### Mesh Analysis

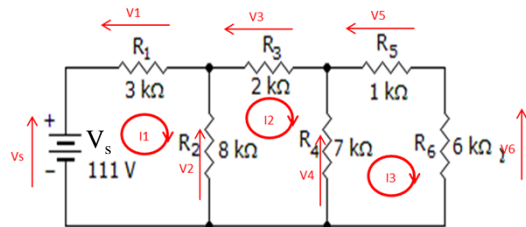

Using KVL gives

$$111\text{V} - R_1 \cdot I_1 - R_2 \cdot (I_1 - I_2) = 0$$


$$R_2 \cdot (I_1 - I_2) - R_3 \cdot I_2 - R_4 \cdot (I_2 - I_3) = 0$$

$$R_4 \cdot (I_2 - I_3) - R_5 \cdot I_3 - R_6 \cdot I_3 = 0$$

3.41

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

### Mesh Analysis

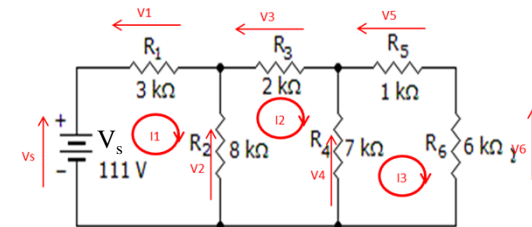

Expand to:

$$111\text{V} - (R_1 + R_2) \cdot I_1 + (R_2) \cdot I_2 + 0 \cdot I_3 = 0$$

$$(R_2) \cdot I_1 - (R_2 + R_3 + R_4) \cdot I_2 + (R_4) \cdot I_3 = 0$$

$$0 \cdot I_1 + (R_4) \cdot I_2 - (R_4 + R_5 + R_6) \cdot I_3 = 0$$

3.42

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

### Solving Simultaneous Circuit Equations

– these equations can be expressed as

$$\begin{bmatrix} -(R_1 + R_2) & R_2 & 0 \\ R_2 & -(R_2 + R_3 + R_4) & R_4 \\ 0 & R_4 & -(R_4 + R_5 + R_6) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -111\text{V} \\ 0 \\ 0 \end{bmatrix}$$

– This yields  $I_1 = 17.73\text{ mA}$ ,  $I_2 = 10.51\text{ mA}$  and  $I_3 = 5.25\text{ mA}$

– **But remember**

- Net Current through  $R_2 = I_1 - I_2 = 7.22\text{ mA}$
- Net Current through  $R_4 = I_2 - I_3 = 5.25\text{ mA}$
- Net Current through  $R_6 = I_3 = 5.25\text{ mA}$

3.43

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

### Advantages of Nodal Analysis

- Solves directly for node voltages.
- Current sources are easy.
- Voltage sources are either very easy or somewhat difficult.
- Works best for circuits with few nodes.
- Works for any circuit.

3.44

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

### Advantages of Loop Analysis

- Solves directly for some currents.
- Voltage sources are easy.
- Current sources are either very easy or somewhat difficult.
- Works best for circuits with few loops.

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.45

### Disadvantages of Loop Analysis

- Some currents must be computed from loop currents.
- Does not work with non-planar circuits.
- Choosing the right mesh may be difficult.
- FYI: PSpice uses a nodal analysis approach

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.46

### Choice of Techniques

- How do we choose the right technique?
  - nodal and mesh analysis will work in a wide range of situations but are not necessarily the simplest methods
  - no simple rules
  - often involves looking at the circuit and seeing which technique seems appropriate

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.47

### Further Study

- The [Further Study](#) section at the end of Chapter 3 investigates the choice of circuit analysis techniques.
- A circuit is presented which could be analysed in a number of ways.
- Have a look and see which you think is best, then watch the video.



Video 3D Further Study



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.48

### Key Points

- An electric current is a flow of charge
- A voltage source produces an e.m.f. which can cause a current to flow
- Current in a conductor is directly proportional to voltage
- At any instant the sum of the currents into a node is zero
- At any instant the sum of the voltages around a loop is zero
- Any two terminal network of resistors and energy sources can be replaced by a Thévenin or Norton equivalent circuit
- Nodal and mesh analysis provide systematic methods of applying Kirchhoff's laws

Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013


3.49
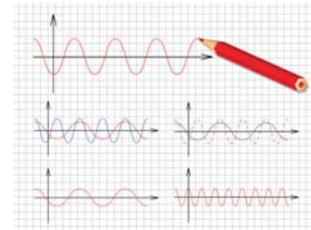
### Next time: Alternating Voltages and Currents



Chapter 6

- Introduction
- Voltage and Current
- Reactance of Inductors and Capacitors
- Phasor Diagrams
- Impedance
- Complex Notation



Neil Storey, *Electronics: A Systems Approach*, 5<sup>th</sup> Edition © Pearson Education Limited 2013

3.50