 


Last time: Semiconductors and diodes

- Introduction
- Electrical properties of solids
- Semiconductors
- *pn* Junctions
- Diodes
- Semiconductor diodes
- Special-purpose diodes (Zener diode most important)
- Diode circuits.
- Field effect transistors



Last time Diode circuits





Video 17A





17.8

- **Half-wave rectifier**

  

- **Full-wave rectifier**

  - reservoir capacitor typically used in both to produce a steadier output



17.2




Video 17B

■ Signal rectifier

Signal is the low frequency part
Carrier is the high frequency part

 - used to demodulate full amplitude modulated signals (**full-AM**)
- also known as an **envelope detector**
- found in a wide range of radio receivers from crystal sets to superheterodynes









17.3

■ Signal clamping

- a simple form of **signal conditioning**

      
- circuits limit the excursion of the voltage waveform
- can use a combination of signal and Zener diodes



Input to a device where
input voltage must be $< V_Z$

■ Catch diode

 - used when switching inductive loads
- the large back e.m.f. can cause problems such as arcing in switches
- **catch diodes** provide a low impedance path across the inductor to dissipate the stored energy
- the applied voltage reverse-biases the diode, which therefore has no effect
- when the voltage is removed the back e.m.f. forward biases the diode which then conducts





Video 17C Further Study

Further Study

- The Further Study section at the end of Chapter 17 is concerned with the design of a mains power supply.
- The supply is to drive an appliance that requires a fairly constant input of 12V and takes a current that varies from 100 to 200 mA.
- Design such a unit and then look at the video.



Key points

- Diodes allow current to flow in only one direction
- At low temperatures semiconductors act like insulators
- At higher temperatures they begin to conduct
- Doping of semiconductors leads to the production of p -type and n -type materials
- A junction between p -type and n -type semiconductors has the properties of a diode
- Silicon semiconductor diodes approximate the behaviour of ideal diodes but have a conduction voltage of about 0.7 V
- There are also a wide range of special purpose diodes
- Diodes are used in a range of applications

-
- Questions so far?

-
- A series of five MOSFETs of increasing size, arranged diagonally from bottom-left to top-right on a white background. The packages shown are TO-18, TO-18, TO-18, TO-18, and TO-247. Each MOSFET has three metal leads extending from its base. The TO-247 package is the largest, featuring a large circular hole in its top surface for heat dissipation.



18.1


Introduction

- **Field-effect transistors (FETs)** are probably the simplest form of transistor
 - widely used in both analogue and digital applications
 - they are characterized by a very high input resistance and small physical size, and they can be used to form circuits with a low power consumption
 - they are widely used in **very large-scale integration**
 - two basic forms:
 - **junction gate FETs**
 - **insulated gate FETs**

 18.10

Simple amplifiers

- Amplifiers can also be formed using a 'control device'
 - circuit is a potential divider with one resistor replaced with a variable resistor that controls I flowing through the resistors
 - If we could control (adjust) R_2 or the current from V to ground with the input voltage, then we have $V_o \propto V_i$ which is an amplifier




A potential divider

As R_2 decreases, V_o decreases
(or I through the system increases)
As $R_2 \rightarrow 0$, (I increases) and $V_o \rightarrow 0$

As R_2 increases, V_o increases
(or I through the system decreases)
When R_2 is $\gg R_1$, $R_2/(R_1+R_2) \rightarrow R_2/R_2 = 1$
And $V_o \rightarrow V$


Simple amplifiers

 - Amplifiers can also be formed using a 'control device'
 - circuit is similar to a potential divider with one resistor replaced with a variable resistor that controls I flowing through the resistors
 - 'control device' typically a **transistor**
 - $V_o = V \cdot I \cdot R_1$ so that if the device controls I , it controls V_o



A potential divider


 
V_i controls R of box
(or I thorough box)



A simple amplifier


An overview of field-effect transistors

  - Many forms, but basic operation is the same
 - a voltage on a control input produces an electric field that affects the current between two other terminals
 - when considering amplifiers we looked at a circuit using a ‘control device’
 - a FET is a suitable control device



■ Notation


 
- FETs are 3 terminal devices
 - drain (d)
 - source (s)
 - gate (g)
- the gate is the control input
- diagram illustrates the notation used for labelling voltages and currents



  18.14


Why does this work? What's in the box?

A diode—pn-junctions!
An n-type bar with 1 or 2 p-type inserts
Will get majority carriers diffusing
across the junction that leave
ionized dopants
Creates electric fields and
depletion regions




How do I adjust current with a control voltage?

 - With a source-drain voltage (gate at ground)-majority charges carriers flow in the n-material (electrons)




Current depends on V and the number of free charge carriers (enhanced in doped material)

- Does not matter the direction

 


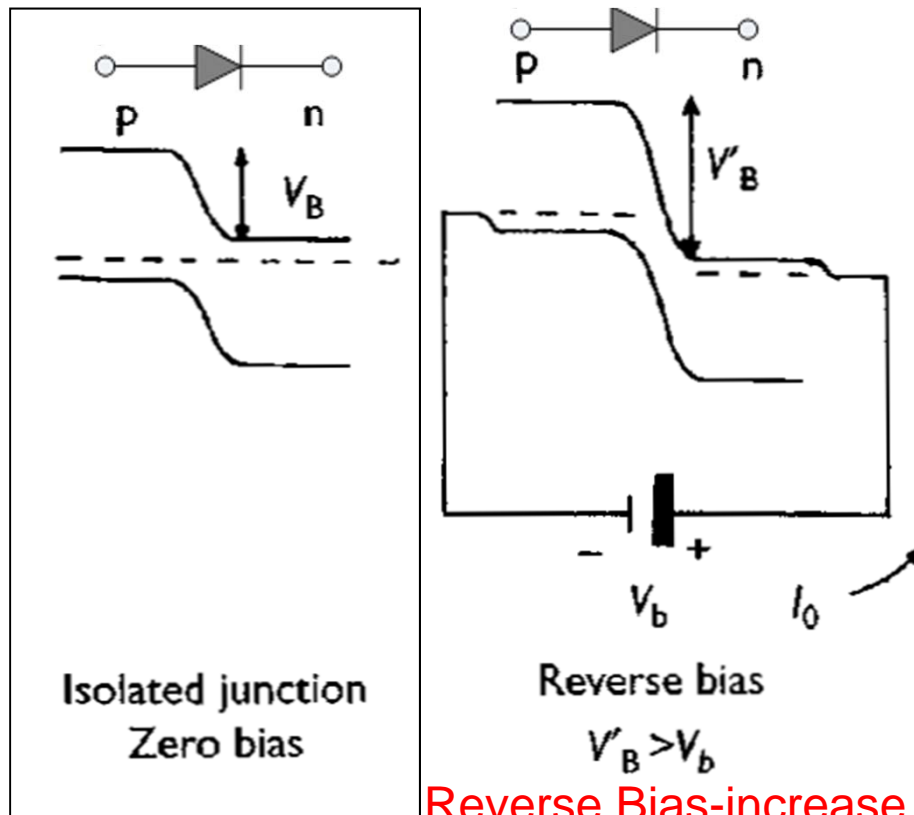Reverse bias gate-source (p-n) to change the width of the **depletion** region



Reverse Bias-increase V_B

$$V'_B = V_B + |V_b|$$

 


Reverse battery bias:

- attract majority carriers to battery terminal away from junction.
- **Depletion region thickness increases.**
- No sustained current flows
- Only random thermal events supply I_s

 18.17

Adjust gate-source voltage to adjust resistance



- Increasing the reverse bias on the pn-junction (a→d in figure)
- The wider the **depletion** region (white) becomes
- The thinner the conduction channel (green) becomes
- Fewer free charge carriers in depletion region to carry current
- Higher resistance (V_{bias} controls I between source & drain)

18.18



18.4

Junction-gate field-effect transistors


- Sometimes known as a **JUGFET**
- Here we will use another common name – the **JFET**
- Here the gate is a reverse-biased *pn* junction
- Since the gate junction is always reverse-biased no current flows into the gate and it acts as if it were insulated

18.19

JFET


- **Construction (1 insert)**

 – two polarities: *n*-channel and *p*-channel



JFET

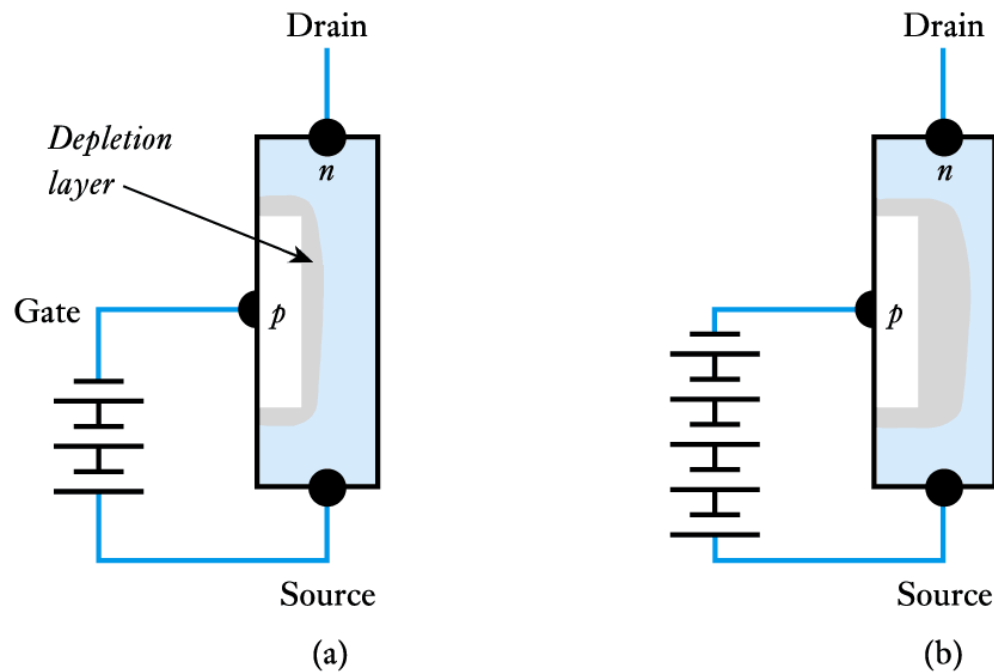- the effect of varying the gate voltage (n-channel device)



- The greater the reverse bias, the narrower the conduction channel and the lower the drain-source current

18.21



18.3

Insulated-gate field-effect transistors


- Such devices are sometimes called **IGFETs** (insulated-gate field-effect transistors) or sometimes **MOSFETs** (metal oxide semiconductor field-effect transistors)
- Digital circuits constructed using these devices are usually described as using **MOS technology**
- Here we will describe them as MOSFETs

18.22

DE-MOSFET

■ Construction

 – two polarities: n -channel and p -channel



DE-MOSFET


■ Operation

- Gate voltage controls the thickness of the channel.
- Consider an n -channel device
 - making the gate more *positive* attracts electrons to the gate and makes the electron (n) channel *thicker* – reducing the resistance of the channel. The channel is said to be **enhanced**
 - making the gate more *negative* repels electrons from the gate and makes the n-channel *thinner* – increasing the resistance of the channel. The channel is said to be **depleted**


DE-MOSFET

- The effect of varying the gate voltage


Un-biased

 

Enhanced
channel ($V_G > V_S$)

 


Depleted
channel ($V_G < V_S$)

 

-
- Devices as described are termed depletion-enhancement MOSFETs or simply **DE MOSFETs**
 - Some MOSFETs are constructed so that in the absence of any gate voltage there is no channel
 - Such devices can be operated in an enhancement mode, but not in a depletion mode (since there is no channel to deplete)
 - These are called **Enhancement MOSFETs**
 - Both forms of MOSFET are available as either *n*-channel or *p*-channel devices


An enhancement MOSFET

 - With no voltage on plate, just have MOS capacitor




- Charge plate positive, attract electrons from the p-type Si towards the oxide dielectric (just like a capacitor).
- This creates an enriched electron channel under the oxide
- This will also create a depletion region that isolates the enhanced channel from the bulk silicon substrate.

To get the voltage controlled current:

 


- Separate n-type materials are used for S and D and are embedded in the p-type material
- The separate pn-junctions allow diffusion of majority charge carriers, forming electric fields and isolated depletion regions
- Put the $+V_{GS}$ to create an enhanced electron channel between the two pn-junctions, allowing current to flow between them
- Resistance of channel depends on strength of the V_{GS} potential


■ MOSFET circuit symbols

 


n -channel
DE MOSFET

 

n -channel enhancement
MOSFET

 

p -channel
DE MOSFET

 

p -channel enhancement
MOSFET




18.5

FET characteristics


- While MOSFETs and JFETs operate in different ways, their characteristics are quite similar
- **Input characteristics**
 - in both MOSFETs and JFETs the gate is effectively insulated from the remainder of the device (no current in)
- **Output characteristics**
 - consider n -channel devices
 - usually the drain is more positive than the source
 - the drain voltage affects the thickness of the channel

 18.30

Effectively get a bias set up between the potential on the drain and the gate.
MOSFET $V_D > V_G \rightarrow$ depleted channel, $V_G > V_S \rightarrow$ enhanced channel
JFET $V_{GD} > V_{GS} \rightarrow$ larger reverse bias at drain end \rightarrow larger depletion region
Tapers the channel.





(a) MOSFET

 

(b) JFET


■ FET output characteristics

  

(a)

Here channel has resistance set by V_{GS}

 Above here the channel thickness is ≈ 0 at drain



(b)

Here $I_D \sim$ independent of the applied voltage & controlled by V_{GS}


18.32

Want to look at output versus input.


In saturation region, $V_{in} = V_{GS}$; output = I_D .

■ Transfer characteristics

 
- similar shape for all forms of FET – but with a different offset
- not a linear response (\approx parabolic), but over a small region might be considered to approximate a linear



(a) JFET

 


(b) DE MOSFET

 


(c) Enhancement MOSFET


■ Normal operating ranges for FETs

 

(a) JFET

 

(b) DE MOSFET

 

(c) Enhancement MOSFET

-
- When operating about its **operating point** we can describe the transfer characteristic by the *change* in output that is caused by a certain *change* in the input
 - This corresponds to the slope of the earlier curves
 - This quantity has units of current/voltage, which is the reciprocal of resistance (that is *conductance*)
 - Since this quantity describes the transfer characteristics it is called the **transconductance**, g_m (units $1/\Omega = \text{Siemens}$)

Note:

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

&

$$g_m \neq \frac{I_D}{V_{GS}}$$


Not a DC
transfer device!

18.35

Since output is a current, I_D , model as a Norton output
Current “downward” out of phase with input

- **Small-signal (AC) equivalent circuit of a FET**

 - models the behaviour of the device for small variations of the input about the operating point





What happened to the DC voltages?


Amplifying AC signals, so what happens at high frequencies
Basically the “pn-capacitors” act like capacitors

■ FETs at high frequencies

  - at high frequencies more sophisticated models are used



FET amplifiers

 


Video 18A




 
18.6

- Simple amplifiers can be formed using any kind of FET
 - Figure (a) shows a circuit using a **DE MOSFET**
 - Figure (b) uses an **enhancement MOSFET**
 - Figure (c) uses a **JFET**
 - Figure (d) is a generic circuit that could use any FET
 - These are **common source amplifiers**



18.38

Gain of device

  

So, the FET is the control device and


$$V_{\text{output}} = V_{DD} - I_D \cdot R_D$$

- When $V_i = V_{GS}$ increases, I_D increases
 - Almost as if the resistance of the control device gets smaller (it doesn't, $R_o = \text{constant}$)
- Then most of the voltage, V_{DD} , drops across R_D
 - Thus, V_o gets smaller
- Inverting amplifier
- V_{GS} decreases $\Rightarrow I_D$ decreases $\Rightarrow V_o$ increases



Video 18B

Equivalent circuit of a FET amplifier

 


- This circuit can represent any of the FET amplifiers above (by choosing an appropriate value of R_G)
 - This is a **small signal-equivalent circuit**
 - Note that R_D goes to *ground*, since the supply voltage V_{DD} is a virtual earth point for small signals

 18.40

Small-signal voltage gain

- From the equivalent circuit we can derive the small-signal voltage gain



$$V = I \cdot R \Rightarrow V_o = -g_m v_{gs} (r_d \parallel R_D)$$
$$= -g_m v_i (r_d \parallel R_D)$$

therefore


$$\frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$

- Also

$$r_i \approx R_G$$

$$r_o \approx r_d \parallel R_D$$

 - In many cases $r_d \gg R_D$ so r_d can often be ignored
- If this is the case



$$\text{voltage gain} = \frac{v_o}{v_i} \approx -g_m R_D$$

$$r_i \approx R_G$$

$$r_o \approx R_D$$

Biasing considerations

- The biasing arrangement determines the operation of the circuit
 - This is its **quiescent** state
- The quiescent output voltage $v_{o(quies)}$ is given by

$$V_{o(quies)} = V_{DD} - I_{D(quies)}R_D$$


- However, since the FET is not linear, determining the quiescent conditions is not straightforward


$$V_{\text{output}} = V_{DS} = V_{DD} - I_D \cdot R_D$$


When $I_D = 0 \Rightarrow V_{DS} = V_{DD}$


When $V_{DS} = 0 \Rightarrow V_{DD} = I_D \cdot R_D$


- One approach is to use a **load line**

 

 

 


 

 



Device variability

 - FETs, like all active devices, suffer from variability



- The effects of device variability on the quiescent conditions of a circuit can be tackled using feedback

  - for example, the use of **‘automatic’ bias**
- As we change V_{GS} we move along the $-1/R_S$ line when we have feedback
- Stable, but large loss in gain! (I_D does not change as much for a change in V_{GS})
- see **Examples 18.3 and 18.4** of the course text



I_D increases
 $V_{RS} = I_D \cdot R_S$ increases
 V_{GG} the same so
 V_{GS} more negative
 So I_D decreases

