

Last time Frequency Characteristics of AC Circuits



Chapter 8

- Introduction
- Two-port Networks
- The Decibel (dB)
- Frequency Response
- A High-Pass *RC* Network
- A Low-Pass *RC* Network
- A Low-Pass *RL* Network
- A High-Pass *RL* Network
- A Comparison of *RC* and *RL* Networks
- Bode Diagrams
- Combining the Effects of Several Stages
- *RLC* Circuits and Resonance
- Filters
- Stray Capacitance and Inductance

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.1

Key Points

- The reactance of capacitors and inductors is dependent on frequency
- Single *RC* or *RL* networks can produce an arrangement with a single upper or lower cut-off frequency
- In each case the angular cut-off frequency ω_o is given by the reciprocal of the time constant *T*
- For an *RC* circuit $T = CR$, for an *RL* circuit $T = L/R$
- Simple *RC* or *RL* networks represent single-pole filters

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013


9.2

A Comparison of *RC* and *RL* Networks



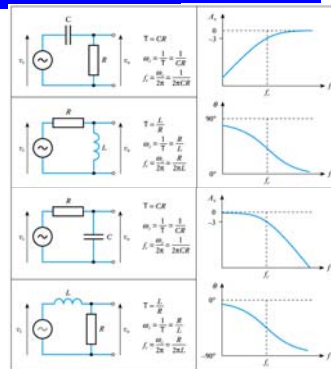8.9

- Circuits using *RC* and *RL* techniques have similar characteristics
 - see **Figure 8.12** in the course text



9.3

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

Filters




8.13

- ***RC* Filters**
- The *RC* networks considered earlier are **first-order** or **single-pole** filters
 - these have a maximum roll-off of 6 dB/octave
 - they also produce a maximum of 90° phase shift
- Combining multiple stages can produce filters with a greater ultimate roll-off rates (12 dB, 18 dB, etc.) but such filters have a very soft 'knee'

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.4

RLC Circuits and Resonance

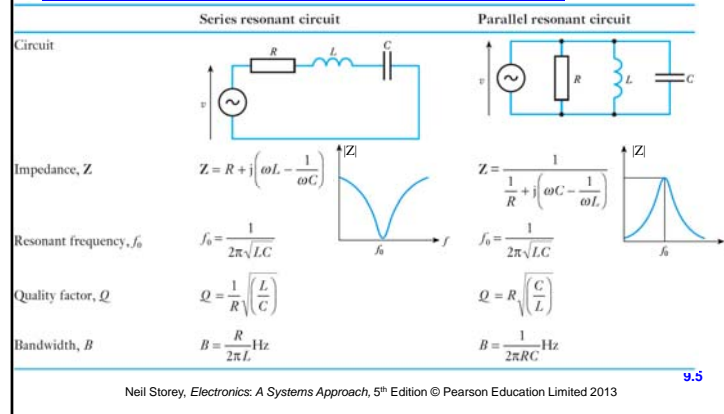

Key Points

- The reactance of capacitors and inductors is dependent on frequency
- Single RC or RL networks can produce an arrangement with a single upper or lower cut-off frequency
- In each case the angular cut-off frequency ω_0 is given by the reciprocal of the time constant T
- For an RC circuit $T = CR$, for an RL circuit $T = L/R$
- Simple RC or RL networks represent single-pole filters
- Resonance occurs when the reactance of the capacitive element cancels that of the inductive element
- RLC circuits in resonance will have maximum impedance, R, in a parallel configuration and minimum impedance, R, when in series
- 2nd order circuits (RLC) can produce sharper filters
- Active filters produce high performance without inductors
- Stray capacitance and inductance are found in all circuits

9.6

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

Transient Behaviour



Chapter 9

- Introduction
- Charging Capacitors and Energising Inductors
- Discharging Capacitors and De-energising Inductors
- Response of First-Order Systems
- Second-Order Systems
- Higher-Order Systems



9.7

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

Introduction



9.1

- So far we have looked at the behaviour of systems in response to:
 - fixed DC signals
 - constant AC signals
- We now turn our attention to the operation of circuits before they reach steady-state conditions
 - this is referred to as the **transient response**
- We will begin by looking at simple RC and RL circuits

9.8

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

Charging Capacitors and Energising Inductors



Capacitor Charging

- Consider the circuit shown here
 - Applying Kirchhoff's voltage law


$$iR + v = V$$

- Now, in a capacitor

$$i = C \frac{dv}{dt}$$

- which substituting gives

$$CR \frac{dv}{dt} + v = V$$

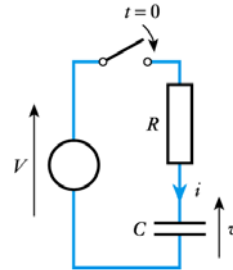

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.9

- The above is a first-order differential equation with constant coefficients
- Assuming $V_C = 0$ at $t = 0$, this can be solved to give

$$v = V(1 - e^{-\frac{t}{CR}}) = V(1 - e^{-\frac{t}{T}})$$

- see **Section 9.2.1** of the course text for this analysis
- Since $i = Cdv/dt$ this gives (assuming $V_C = 0$ at $t = 0$)


$$i = Ie^{-\frac{t}{CR}} = Ie^{-\frac{t}{T}}$$

- where $I = V/R$

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

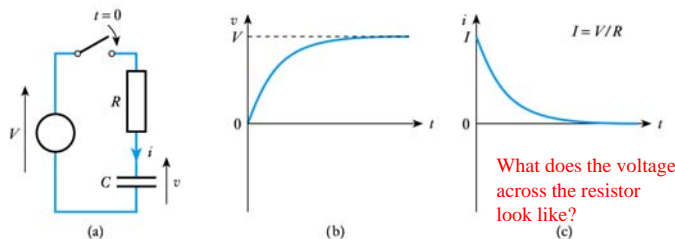9.10

- Thus both the voltage and current have an exponential form



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.11

Inductor energising KVL $\Rightarrow iR + v = V$, and $v = L(di/dt)$

- A similar analysis of this circuit gives


$$iR + L \frac{di}{dt} = V$$

$$i = I(1 - e^{-\frac{Rt}{L}}) = I(1 - e^{-\frac{t}{T}})$$

$$v = Ve^{-\frac{Rt}{L}} = Ve^{-\frac{t}{T}}$$

where $I = V/R$

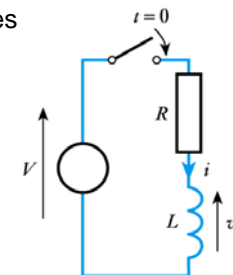
- see **Section 9.2.2** for this analysis



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.12

- Thus, again, both the voltage and current have an exponential form

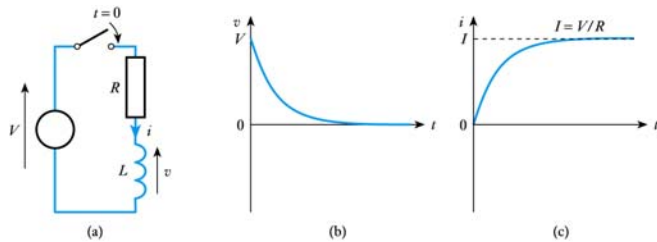Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.13

Discharging Capacitors and De-energising Inductors




Capacitor discharging

- Consider this circuit for discharging a capacitor
 - At $t = 0$, $V_C = V$
 - From Kirchhoff's voltage law

$$iR + v = 0$$
 - giving

$$CR \frac{dv}{dt} + v = 0$$

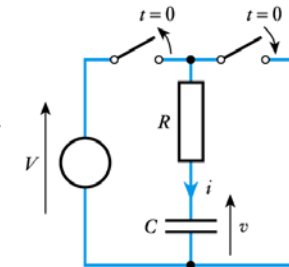Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.14

- Solving this as before gives

$$v = Ve^{-\frac{t}{CR}} = Ve^{-\frac{t}{T}}$$


$$i = -Ie^{-\frac{t}{CR}} = -Ie^{-\frac{t}{T}}$$

- where $I = V/R$
- see **Section 9.3.1** for this analysis

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.15

- In this case, both the voltage and the current take the form of decaying exponentials

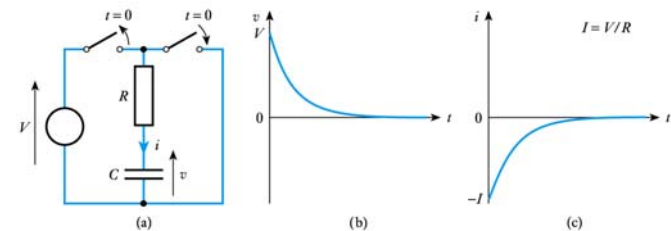Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.16

Inductor de-energising

- A similar analysis of this circuit gives

$$iR + L \frac{di}{dt} = 0$$

$$i = I e^{-\frac{Rt}{L}} = I e^{-\frac{t}{T}}$$


$$v = -V e^{-\frac{Rt}{L}} = -V e^{-\frac{t}{T}}$$

– where $I = V/R$


– see **Section 9.3.1** for this analysis

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.17

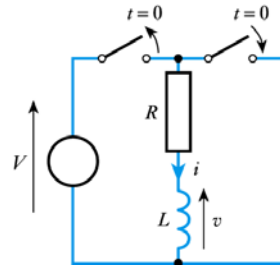

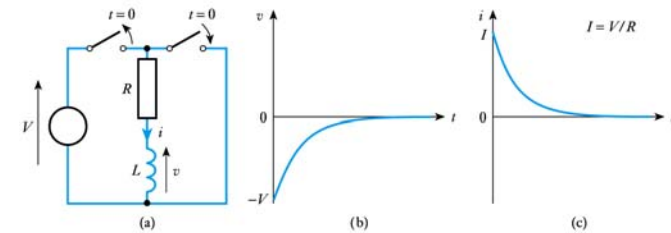
- And once again, both the voltage and the current take the form of decaying exponentials



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.18

- A comparison of the four circuits

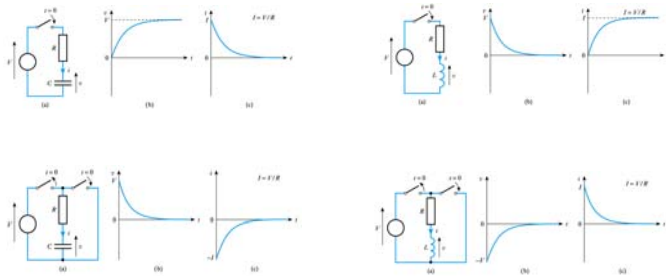

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.19

Response of First-Order Systems



9.4

- Initial and final value formulae**

- increasing or decreasing exponential waveforms (for either voltage or current) are given by:

$$v = V_f + (V_i - V_f)e^{-t/T}$$

$$i = I_f + (I_i - I_f)e^{-t/T}$$


- where V_i and I_i are the *initial* values of the voltage and current
- where V_f and I_f are the *final* values of the voltage and current
- the first term in each case is the **steady-state response**
- the second term represents the **transient response**
- the combination gives the **total response** of the arrangement

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.20

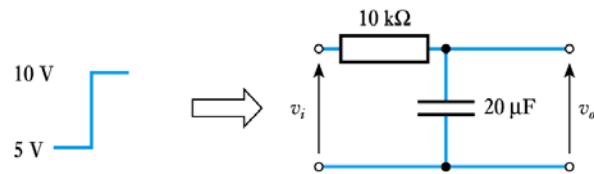Example – see **Example 9.3** from course text

The input voltage to the following CR network undergoes a step change from 5 V to 10 V at time $t = 0$. Derive an expression for the resulting output voltage



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013


9.21

Here the initial value is 5 V and the final value is 10 V. The time constant of the circuit equals $CR = 10 \times 10^3 \times 20 \times 10^{-6} = 0.2$ s. Therefore, from above, for $t \geq 0$

$$\begin{aligned} v &= V_f + (V_i - V_f)e^{-t/T} \\ &= 10 + (5 - 10)e^{-t/0.2} \\ &= 10 - 5e^{-t/0.2} \text{ volts} \end{aligned}$$

And the current?

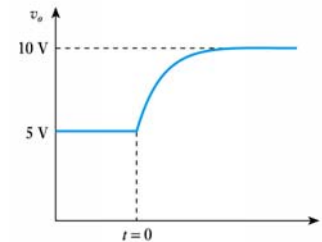
$$\begin{aligned} i &= C(dv/dt) \\ i &= (V_f - V_i)/R \cdot e^{-t/T} \\ I_i &= (V_f - V_i)/R, I_f = 0 \end{aligned}$$



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.22

The nature of exponential curves

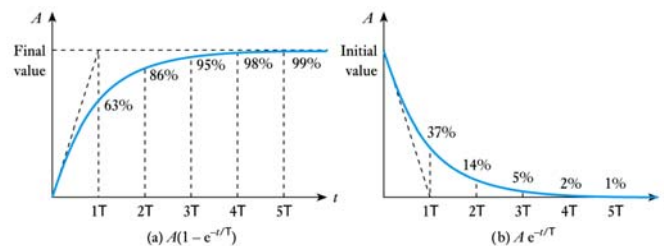


Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.23

Response of first-order systems to a square waveform

– see **Section 9.4.3**

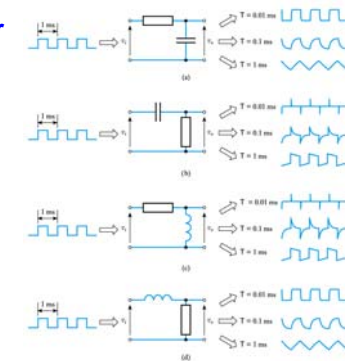


Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.24

Response of first-order systems to a square waveform of different frequencies

– see **Section 9.4.3**

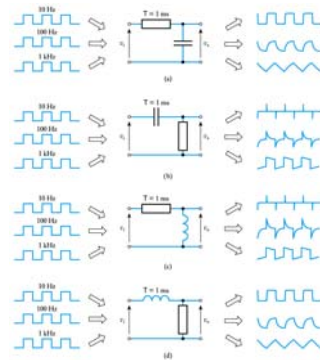

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.25

Second-Order Systems




9.5

- Circuits containing both capacitance and inductance are normally described by second-order differential equations. These are termed **second-order systems** – for example, this circuit is described by the equation

$v_R + v_L + v_C = V$ and $v_L = L(di/dt)$, and $v_R = iR$
but $i = C(dv_C/dt)$. So
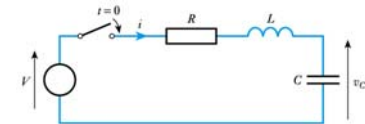
$$LC \frac{d^2 v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C = V$$



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.26

- When a step input is applied to a second-order system, the form of the resultant transient depends on the relative magnitudes of the coefficients of its differential equation. The general form of the response is

$$\frac{1}{\omega_n^2} \frac{d^2 y}{dt^2} + \frac{2\zeta}{\omega_n} \frac{dy}{dt} + y = x$$


– where ω_n is the **undamped natural frequency** in rad/s and ζ (Greek Zeta) is the **damping factor**

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

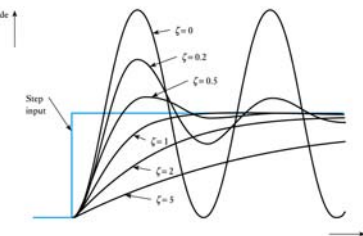9.27

Response of second-order systems

- $\zeta = 0$ undamped
- $\zeta < 1$ under damped
- $\zeta = 1$ critically damped
- $\zeta > 1$ over damped



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.28

Higher-Order Systems



9.6

- Higher-order systems are those that are described by third-order or higher-order equations
- These often have a transient response similar to that of the second-order systems described earlier
- Because of the complexity of the mathematics involved, they will not be discussed further here

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.29

Further Study



Video 9B Further Study

- The **Further Study** section at the end of Chapter 9 considers the problem of determining the time constant of a circuit, so that the initial and final value theorems can be applied.
- Two sample circuits are given so that you can test your understanding.
- Calculate the time constants of the circuits and then check your results by looking at the video.

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.30


Key Points

- The charging or discharging of a capacitor, and the energising and de-energising of an inductor, are each associated with exponential voltage and current waveforms
- Circuits that contain resistance, and either capacitance or inductance, are termed first-order systems
- The increasing or decreasing exponential waveforms of first-order systems can be described by the initial and final value formulae
- Circuits that contain both capacitance and inductance are usually second-order systems. These are characterised by their undamped natural frequency and their damping factor

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013


9.31

Today: Amplification

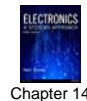

Chapter 14

- Introduction
- Electronic amplifiers
- Sources and loads
- Equivalent circuit of an amplifier
- Output power
- Power gain
- Frequency response and bandwidth
- Differential amplifiers
- Simple amplifiers

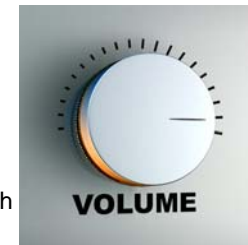Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.32

Introduction



14.1

- Amplification is one of the most common processing functions
- **Amplification** means making things bigger
- **Attenuation** means making things smaller
- There are many non-electronic forms of amplification

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013


9.33

Amplifiers

Non-electronic amplifiers

– Levers

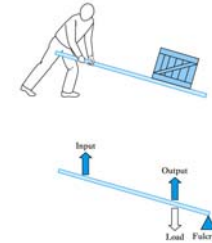- Example shown on the right is a force *amplifier*, but a displacement *attenuator*
- Reversing the position of the input and output would produce a force *attenuator* but a displacement *amplifier*
- This is an example of a **non-inverting amplifier** (since the input and output are in the same direction)



A lever arrangement


Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.34

Non-electronic amplifiers

– Pulleys

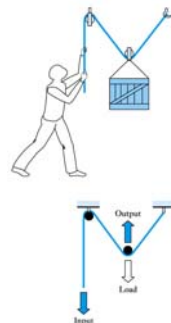- Example shown right is a force *amplifier*, but a displacement *attenuator*
- This is an example of an **inverting amplifier** (since the input and output are in opposite directions) but other pulley arrangements can be non-inverting



A pulley arrangement

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.35

Passive and active amplifiers


- Levers and pulleys are examples of **passive amplifiers** since they have no external energy source
 - In such amplifiers the power delivered at the output must be less than (or equal to) that absorbed at the input
- Some amplifiers are not passive but are **active amplifiers** in that they have an external source of power
 - In such amplifiers the output can deliver more power than is absorbed at the input

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

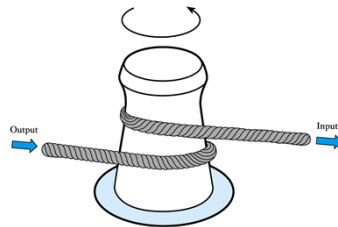9.36

Non-electronic active amplifiers

- an example is the torque amplifier shown here



Small force here
Increase friction and
proportionally get the
motor's power at output

Big motor turning the winch

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.37

Electronic amplifiers



14.2


- Can be passive (e.g. a transformer) but most are active
- We will concentrate on *active* electronic amplifiers
 - take power from a power supply
 - amplification described by gain

What
about
in dB?

$$\text{Voltage Gain } (A_v) = \frac{V_o}{V_i}$$

$$\text{Current Gain } (A_i) = \frac{I_o}{I_i}$$
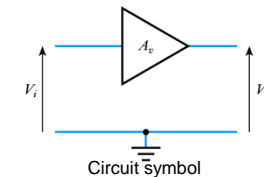
$$\text{Power Gain } (A_p) = \frac{P_o}{P_i}$$




Circuit symbol

9.38

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

Electronic amplifiers

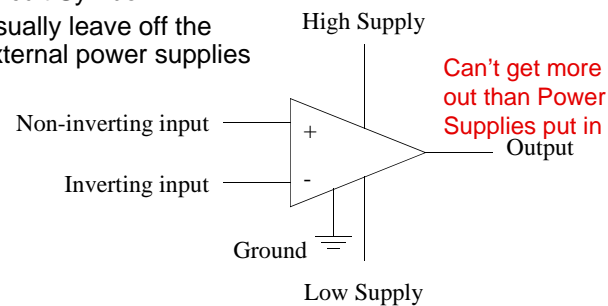- Circuit Symbol
- Usually leave off the external power supplies




Neil Storey, *Electr*

Sources and loads



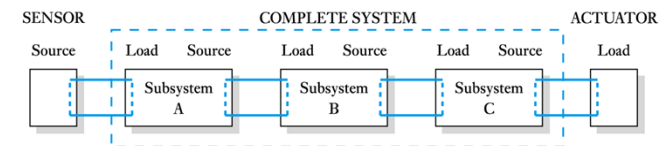14.3

- An *ideal* voltage amplifier would produce an output determined only by the input voltage and its gain.
 - irrespective of the nature of the source and the load
 - in real amplifiers this is not the case
 - the output voltage is affected by **loading**




9.40

Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

Modelling sources and loads

Modelling the input of an amplifier

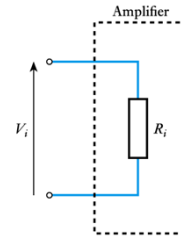- the input can often be adequately modelled by a simple resistor
- the **input resistance**




Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

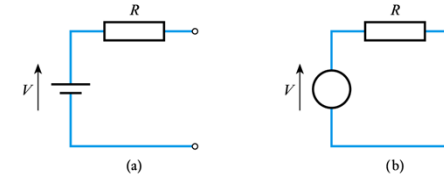9.41

Modelling the output of a circuit

- all real voltage sources have an output resistance
- for example, a battery can be represented by an ideal voltage source and a series resistance representing its **output resistance**




Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

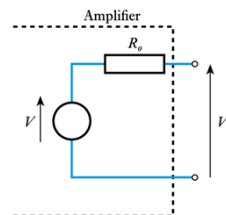9.42

Modelling the output of an amplifier

- Similarly, the output of an amplifier can be modelled by an ideal voltage source and an output resistance.
- This is an example of a **Thévenin equivalent circuit**




Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

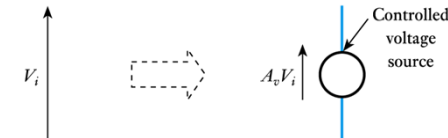9.43

Modelling the gain of an amplifier

- can be modelled by a controlled voltage source
- the voltage produced by the source is determined by the input voltage to the circuit



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.44

Equivalent circuit of an amplifier




Video 14A



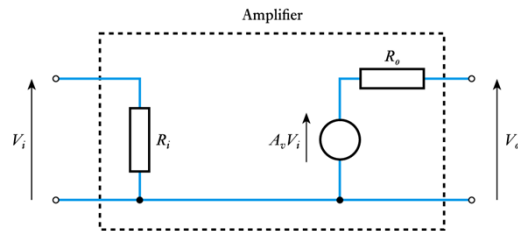14.4

- Having modelled the input, the output and the gain, we can now model the entire amplifier



Neil Storey, *Electronics: A Systems Approach*, 5th Edition © Pearson Education Limited 2013

9.45